



Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Network Theory

Time: 3 hrs.


Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1


- 1 a. Using source transformation technique find the current through 5Ω resistor for the circuit shown in Fig.Q.1(a) (06 Marks)

Fig.Q.1(a)

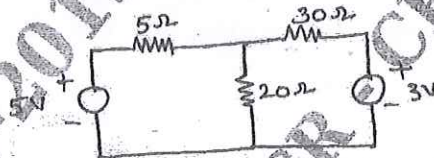


- b. Use Mesh Analysis to determine the Mesh currents i_1 , i_2 and i_3 for the network shown in Fig.Q.1(b). (06 Marks)

Fig.Q.1(b)

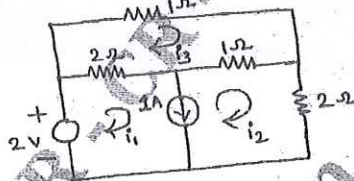

- c. Find the power delivered by 1A current source using nodal analysis for the circuit shown in Fig.Q.1(c). (08 Marks)


Fig.Q.1(c)

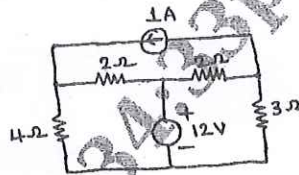

OR


- 2 a. Three Impedances are connected in delta, obtain the star equivalent of the network. (06 Marks)
- b. Use Mesh Analysis to find the power delivered by the dependent voltage source in the circuit shown in Fig.Q.2(b). (06 Marks)

Fig.Q.2(b)

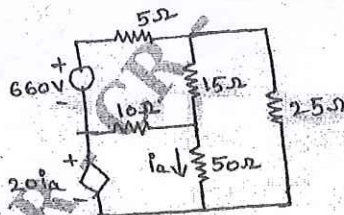

- c. Determine all the node voltages for the circuit shown in Fig.Q.2(c) using nodal analysis. (08 Marks)

Fig.Q.2(c)

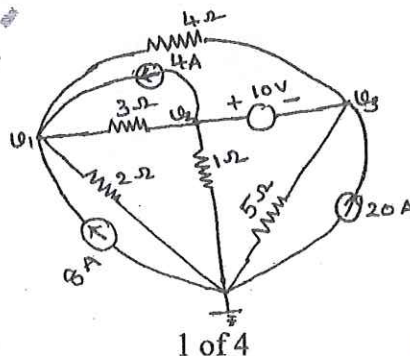

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. State and explain superposition theorem (06 Marks)
 b. Use Millman's Theorem to find the current flowing through $(2 + j3)\Omega$ impedance for the circuit shown in Fig.Q.3(b). (08 Marks)

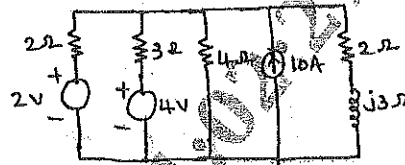


Fig.Q.3(b)

- c. State and prove Norton's theorem. (06 Marks)

OR

- 4 a. Find the Thevenin's equivalent for the circuit shown in Fig.Q.4(a) with respect to terminals X-Y. (08 Marks)

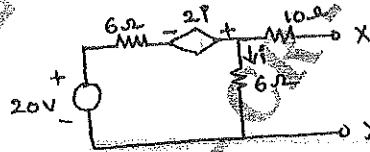


Fig.Q.4(a)

- b. Find the condition for maximum power transfer in the AC circuit, where both R_L and X_L are varying. (06 Marks)
 c. Determine the current through the load resistance using Norton's Theorem for the circuit shown in Fig.Q.4(c). (06 Marks)

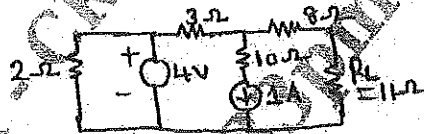


Fig.Q.4(c)

Module-3

- 5 a. Explain the behavior of R, L, C elements at the time of switching at $t = 0$, at $t = 0^+$ and $t = \infty$. (07 Marks)
 b. In the network shown in Fig.Q.5(b). Find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. Assume that the capacitor is initially uncharged. (07 Marks)

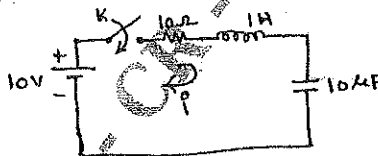


Fig.Q.5(b)

- c. In the network shown in Fig.Q.5(c) find, i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. The switch k is closed at $t = 0$ with zero current in the inductor. (06 Marks)

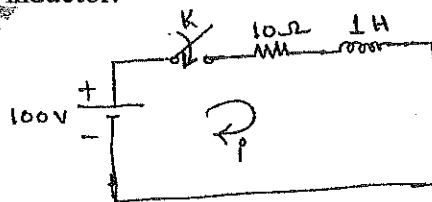


Fig.Q.5(c)

OR

- 6 a. In the network shown in Fig.Q.6(a). The switch k is changed from position a to b at $t = 0$, the steady state is reached at position a. Find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. Assume that the capacitor is initially uncharged. (10 Marks)

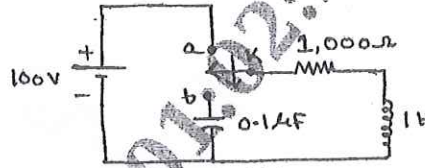


Fig.Q.6(a)

- b. For the network shown in Fig.Q.6(b). The network is in steady state with switch k is closed. At $t = 0$, the switch is opened. Determine the voltage across the switch V_k and $\frac{d}{dt}V_k$ at $t = 0^+$. (10 Marks)

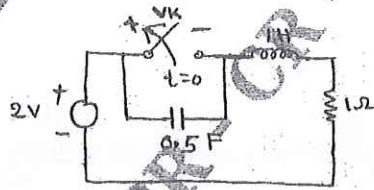


Fig.Q.6(b)

Module-4

- 7 a. Obtain Laplace transform of
 i) Step function
 ii) Ramp function
 iii) Impulse function. (09 Marks)
- b. Find the Laplace transform of the periodic signal $x(t)$ as shown in Fig.Q.7(b). (11 Marks)

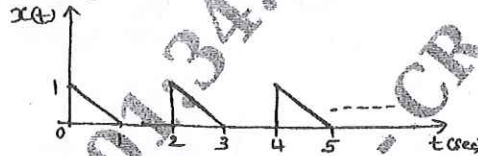


Fig.Q.7(b)

OR

- 8 a. In the series RL circuit shown in Fig.Q.8(a), the source voltage is $v(t) = 50 \sin 250t$ V. Using Laplace transform determine, the current when switch K is closed at $t = 0$. (10 Marks)

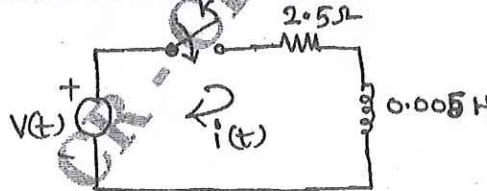


Fig.Q.8(a)

- b. Find the Laplace transform of the non-sinusoidal periodic waveform shown in Fig.Q.8(b)

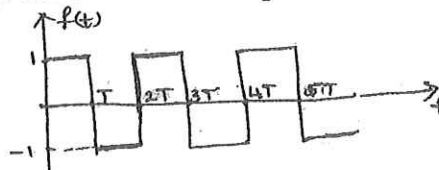


Fig.Q.8(b)

(10 Marks)

Module-5

- 9 a. Define Z parameters. Determine Z parameters in terms of Y parameters. (06 Marks)
- b. Determine h parameters of the circuit shown in Fig.Q.9(b) (07 Marks)

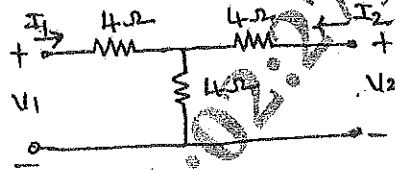


Fig.Q.9(b)

- c. For the network shown in Fig.Q.9(c) Find the transmission parameters. (07 Marks)

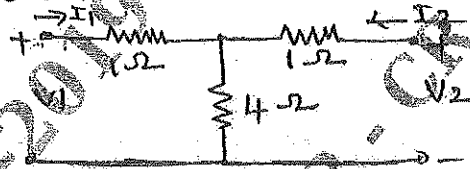


Fig.Q.9(c)

OR

- 10 a. Define Q-factor, selectivity and Band width. (03 Marks)
- b. A series RLC circuit has a resistance of 10Ω , an inductance of 0.3H and a capacitance of $100\mu\text{F}$. The applied voltage is 230V . Find: i) The resonant frequency ii) lower and upper cut off frequencies iii) current at resonance iv) currents at f_1 and f_2 v) Voltage across the inductance at resonance. (07 Marks)
- c. Derive the expression for the resonant frequency of the circuit shown in Fig.Q.10(c). Also show that the circuit will resonate at all frequency if $R_L = R_C = \sqrt{\frac{L}{C}}$. (10 Marks)

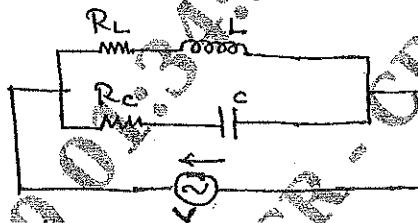


Fig.Q.10(c)


* * * * *

Solution and Scheme for 18EC32, Dec 2019/
Jan 2020, Prepared and Submitted by

Prof. Nikhil Kulkarni
ECE Dept, KISS; VDIIT, Talajal



Nikhil Kulkarni

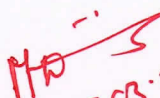
15.03.2022
Head of the Department
ECE Dept & Communication Engg
VLSI (AI), TALAJAL (VIT)


Q. No

Prepared by: Prof. Nikhil A. Kulkarni, E&C Dept, KLS, VJIT.



Module - 1

1a)

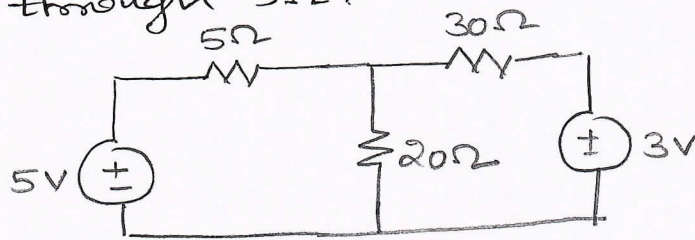Using Source Transformation, find the current through 5Ω .



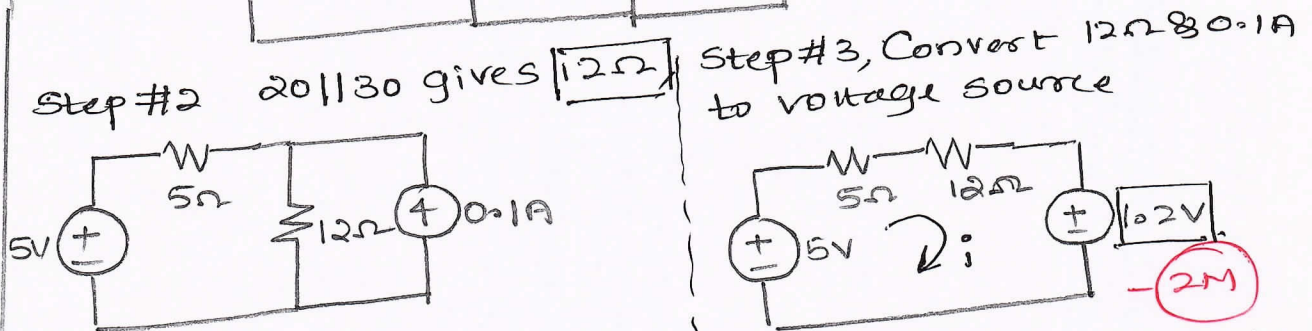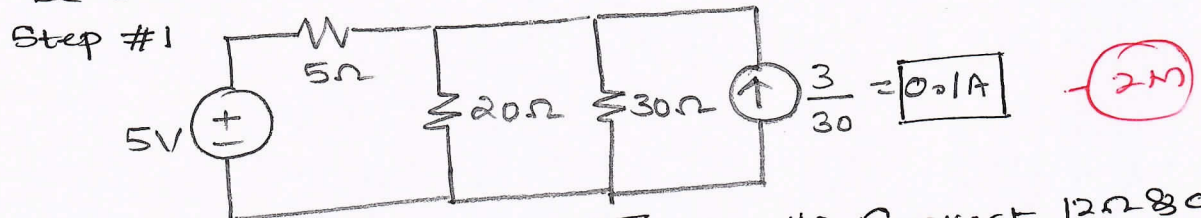Solⁿ: As current through 5Ω is required, by using source transformation, $5V, 5\Omega$ should not be considered for transformation, hence $3V, 30\Omega$ can be converted into eq. current source.




As, we have single loop in Step #3, same current will flow through $5\Omega, 12\Omega$, \therefore by KVL.

$$-5 + 5i + 12i + 1.2 = 0, \therefore i = \frac{3.8}{17} = 0.22A, \therefore$$

$i_{5\Omega} = 0.22A$ (2M)

1b)

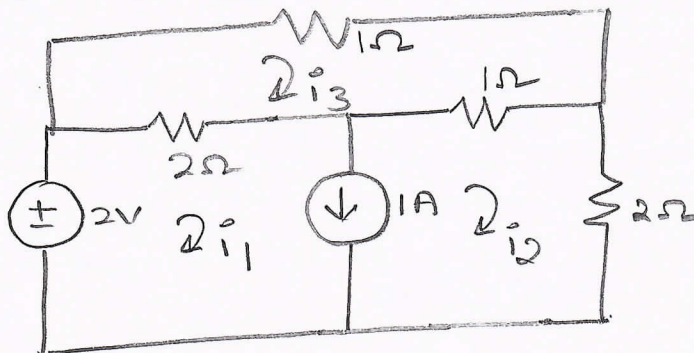Determine the 3 mesh currents i_1, i_2 and i_3



Q. No

1b

Continued

There are 3 mesh M_1, M_2 and M_3 , with 3 current i_1, i_2 and i_3 .

As, we can observe, A supermesh is formed b/w M_1 and M_2 ,

\therefore Constraint-eqⁿ: $i_1 - i_2 = 1A$ - (1) (1M)

KVL to supermesh gives

$-2 + 2i_1 + 3i_2 - 3i_3 = 0$, $2i_1 + 3i_2 - 3i_3 = 2$ - (2) (2M)

KVL to Normal Mesh [i.e mesh 3]


$-2i_1 - i_2 + 4i_3 = 0$ - (3) (1M)

Solving eqⁿ (1), (2) and (3), we get-

$i_1 = 1.54A$, $i_2 = 0.54A$, $i_3 = 0.90A$ (2M)

1c

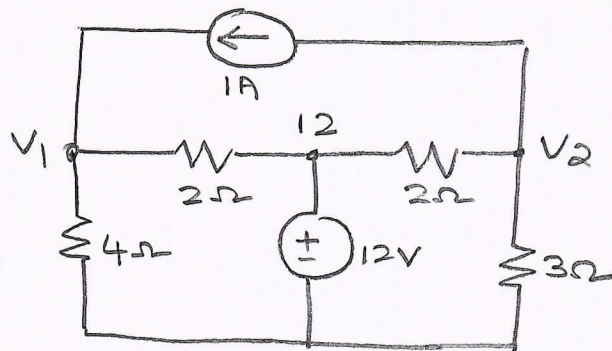Using Nodal Analysis, Find the power delivered by 1A current-source



Let the two node voltages be V_1 and V_2

KCL to node V_1 gives

$\frac{V_1}{4} + \frac{V_1 - 12}{2} = 1$, $\Rightarrow V_1 \left[\frac{1}{4} + \frac{1}{2} \right] = 7$

$\therefore V_1 = 9.33$ volts (2M)

KCL to node V_2 gives

$\frac{V_2}{3} + \frac{V_2 - 12}{2} + 1 = 0$, $V_2 \left[\frac{1}{3} + \frac{1}{2} \right] = 5$

$V_2 = 6.02$ volts (2M)

\therefore Power delivered by 1A source is

$P = VI = (V_2 - V_1)(1A) = -3.31$ Watts (4M)



OK

Q.No

2a)

Three impedances are connected in Delta, Obtain the Star equivalent of the network.

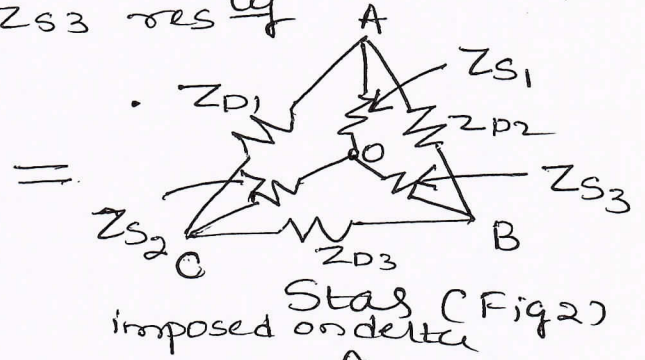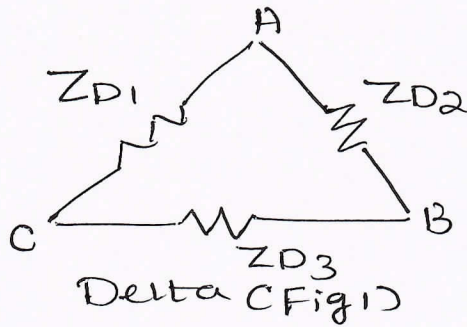Solⁿ Let, the three impedance of delta networks are Z_{D1}, Z_{D2}, Z_{D3} , Let the eq. Star impedance as Z_{S1}, Z_{S2}, Z_{S3} res by



Proof:

#1] Comparing Fig 1 and 3

#2] Resistance b/w node A & C is

→ In Delta

$$= Z_{D1} \parallel (Z_{D2} + Z_{D3})$$

$$= \frac{Z_{D1} [Z_{D2} + Z_{D3}]}{Z_{D1} + Z_{D2} + Z_{D3}} \quad \text{--- (1)}$$

#3] Resistance b/w node A & C in Star

$$= Z_{S1} + Z_{S2} \quad \text{--- (2)}$$

#4] Equating (1) and (2)

$$\frac{Z_{D1} [Z_{D2} + Z_{D3}]}{Z_{D1} + Z_{D2} + Z_{D3}} = Z_{S1} + Z_{S2} \quad \text{--- (3)}$$

#5] Resistance between C and B of Δ and Y are equalled as it was done in eqⁿ (1) & (2) we get

$$\frac{Z_{D3} [Z_{D1} + Z_{D2}]}{Z_{D1} + Z_{D2} + Z_{D3}} = Z_{S2} + Z_{S3} \quad \text{--- (4)}$$

3M

AK

Q. No

2a)
Continued

#6] Res b/w A and B terminals of Δ and equaling them gives us

$$\frac{Z_{D2} [Z_{D1} + Z_{D3}]}{Z_{D1} + Z_{D2} + Z_{D3}} = Z_{S1} + Z_{S3} \quad - (5)$$

#7] Adding three eqⁿs (3), (4) and (5) gives,

$$2 [Z_{S1} + Z_{S2} + Z_{S3}] = \frac{2 [Z_{D1} - Z_{D3} + Z_{D3} Z_{D2} + Z_{D2} Z_{D1}]}{Z_{D1} + Z_{D2} + Z_{D3}} \quad - (6)$$

eqⁿ (6) - (3) gives.

$$Z_{S3} = \frac{Z_{D2} \times Z_{D3}}{Z_{D1} + Z_{D2} + Z_{D3}} \quad - (7)$$

3M

eqⁿ (6) - (4) gives


$$Z_{S1} = \frac{Z_{D1} \times Z_{D2}}{Z_{D1} + Z_{D2} + Z_{D3}} \quad - (8)$$

eqⁿ (6) - (5) gives.

$$Z_{S2} = \frac{Z_{D1} \times Z_{D3}}{Z_{D1} + Z_{D2} + Z_{D3}} \quad - (9)$$

2b)

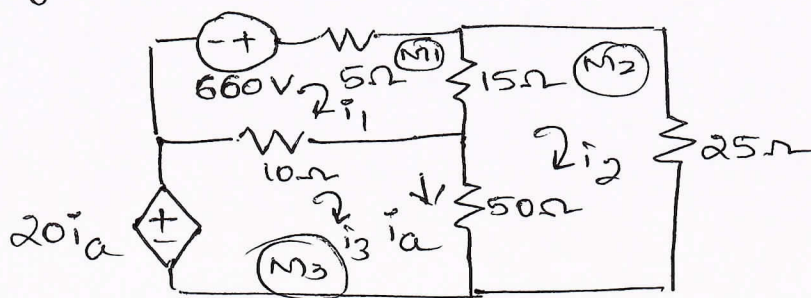Using Mesh Analysis, find the power delivered by the dependent source.



Q.No

2b
Continued

From Fig $i_a = i_3 - i_2$

KVL M1

$$30i_1 - 15i_2 - 10i_3 = 660 \quad \text{--- (1)}$$

(1M)

KVL M2

$$-15i_1 + 40i_2 + 50i_2 - 50i_3 = 0$$

$$-15i_1 + 90i_2 - 50i_3 = 0 \quad \text{--- (2)}$$

(1M)

KVL M3

$$-20i_a + 60i_3 - 10i_1 - 50i_2 = 0$$

$$-20i_3 + 20i_2 + 60i_3 - 10i_1 - 50i_2 = 0$$

$$-10i_1 - 30i_2 + 40i_3 = 0 \quad \text{--- (3)}$$

(2M)

$$i_1 = 42A, \quad i_2 = 22A, \quad i_3 = 27A$$

$$P_{20i_a} = 20i_a \times (-i_3)$$

$$= 20(i_3 - i_2) \times (-i_3)$$


$$P_{20i_a} = -2700 \text{ Watts}$$

(2M)

OK

Q.No

2c)

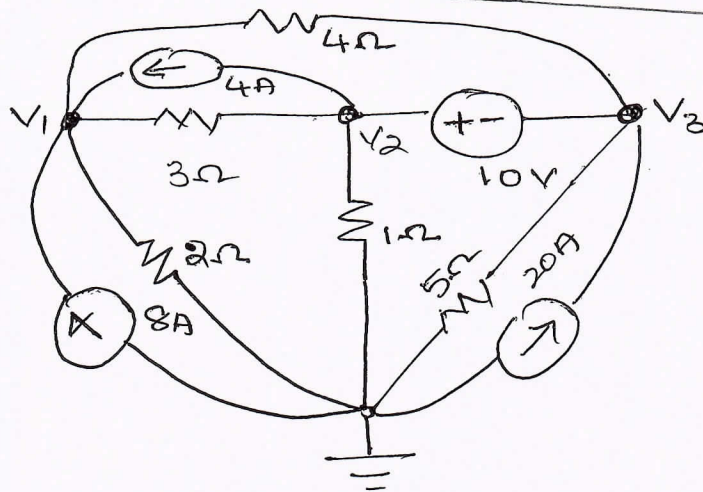


KCL at V_1

$$\frac{V_1}{2} + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{4} = 12; V_1[1.08] - V_2[0.33] - V_3[0.25] = 12$$

KCL at V_2 and V_3 cannot be applied directly, as it is forming supernode,

∴ Constraint eqn gives $V_2 - V_3 = 10$ — (2) — (4M)

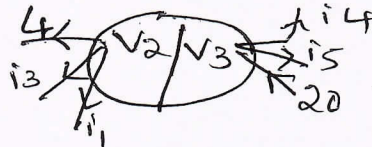Combining node (2) and (3) and applying KCL,



$$V_2 + \frac{V_2 - V_1}{3} + 4 + \frac{V_3 - V_1}{4} + \frac{V_3}{5} + (-20) = 0$$

$$V_1[-0.58] + V_2[1.33] + V_3[0.45] = 16$$
 — (3) — (4M)

Solving eqn (1), (2) and (3) we get

$$V_1 = 18.15 \text{ V}, V_2 = 17.43 \text{ V} \text{ and } V_3 = 7.43 \text{ V}$$

Module-2

3a)

State and Explain Superposition theorem.

Statement: In any linear circuit, containing multiple sources, the response in any branch of the network is the algebraic sum of the responses obtained by considering each source as acting separately, during which, all other sources are disabled except any dependent sources.

— (1M)


AK

Q.No

3a
Continued


Explanation: Consider the following ckt,

SM

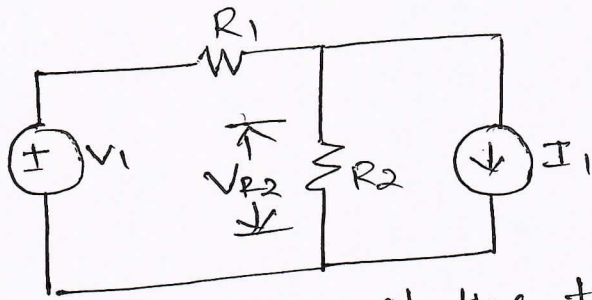


Let us assume that voltage across R_2 is required,

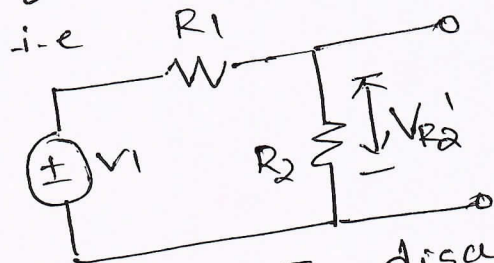Step 1] Keep one of the two sources active, Let V_1 be active, I_1 is disabled (open ckt), and find voltage across R_2 , call it as V_{R2}^I



$$V_{R2}^I = \frac{V_1 \times R_2}{R_1 + R_2} \quad \text{--- (1)}$$

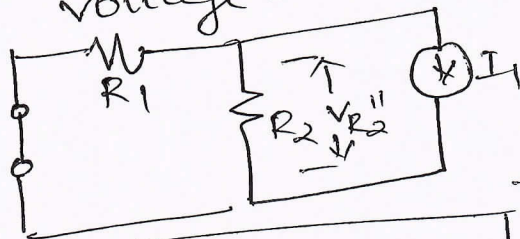Step 2] Enable I_1 , disable V_1 (short ckt), find voltage across R_2 , call it as V_{R2}^{II}



If current through R_2 is I_2


$$I_2 = \frac{I_1 \times R_1}{R_1 + R_2}$$

$$\therefore V_{R2}^{II} = I_2 \times R_2 \quad \text{--- (2)}$$

$$\therefore \boxed{V_{R2} = V_{R2}^I + V_{R2}^{II}}$$

3b)

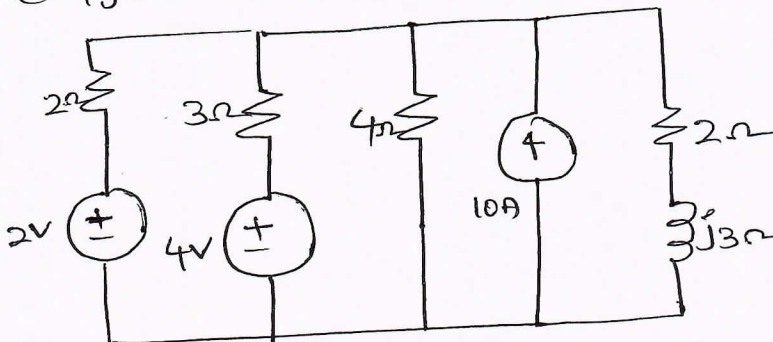Using Millman's theorem, find current through 3Ω




AK

Q.No

3b
Continued

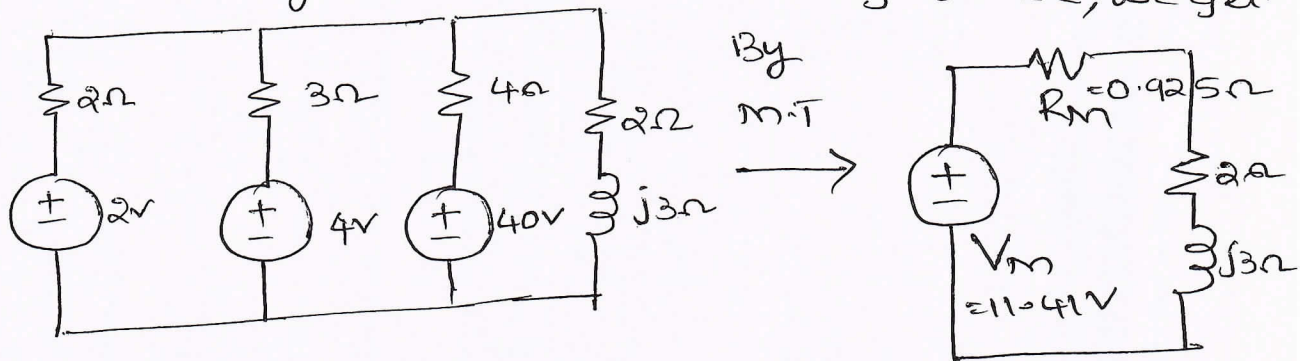Transforming 4Ω and $1A$ to voltage source, we get



where

$$V_m = (2) \times \frac{1}{2} + 4 \times \frac{1}{3} + 40 \times \frac{1}{4} = 11.41V$$

$$\frac{1}{2} + \frac{1}{3} + \frac{1}{4}$$

$$R_m = \frac{1}{\frac{1}{2} + \frac{1}{3} + \frac{1}{4}} = 0.925\Omega$$

∴ Current through $(2+j3)\Omega$ = $2.71 \angle -45^\circ A$

3C)

Statement and Proof of Norton's Theorem:

Sol D:

Statement: Any combination of linear bilateral circuit elements and active sources, regardless of the connection or complexity, connected to a given load Z_L , can be replaced by a simple two terminal network, consisting of a single current source of I_N amperes and a single impedance Z_N in parallel with it, across the two terminals of the load Z_L .


Proof: Consider the following circuit diagram, here let us understand the method followed to find current through 3Ω , using conventional method and other by Norton's Theorem

Handwritten signature

Q. No

3C) continued


Consider the following circ-

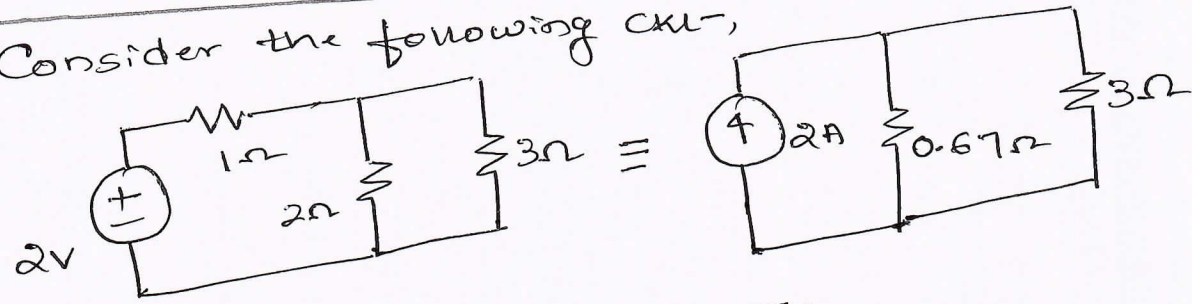

$$\therefore I_{3\Omega} = \frac{2 \times 0.67}{3.67} \approx 0.365 \text{ A}$$


Now by, Norton's theorem

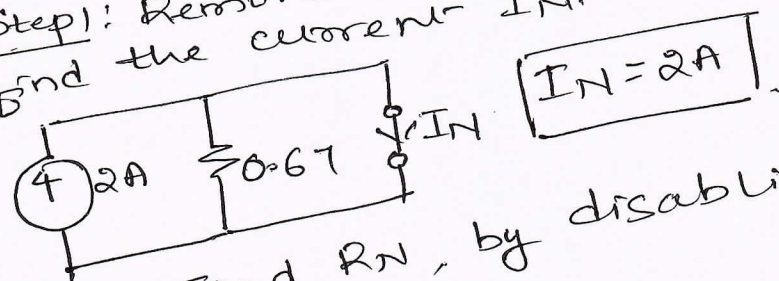Step 1: Remove 3Ω , replace it by short-circuit, and find the current I_N .




4M

Step 2: Find R_N , by disabling source

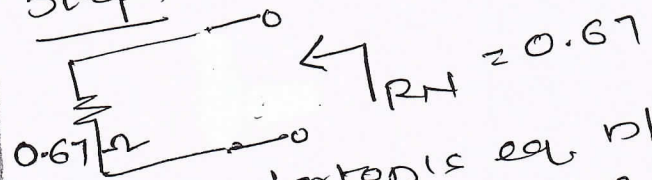

Step 3: Norton's eq. plus is

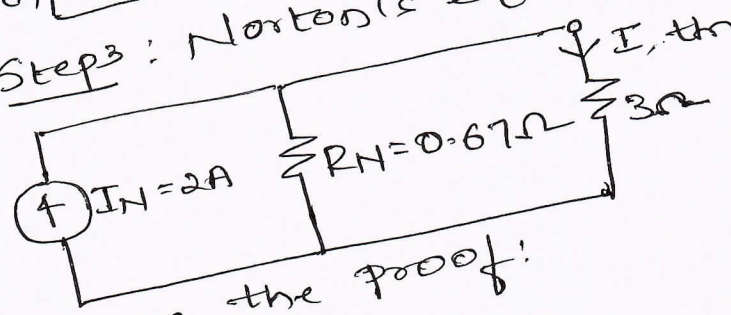


$$I_3 = \frac{0.67 \times 2}{2.67} = 0.365 \text{ A}$$

hence the proof!

4a)

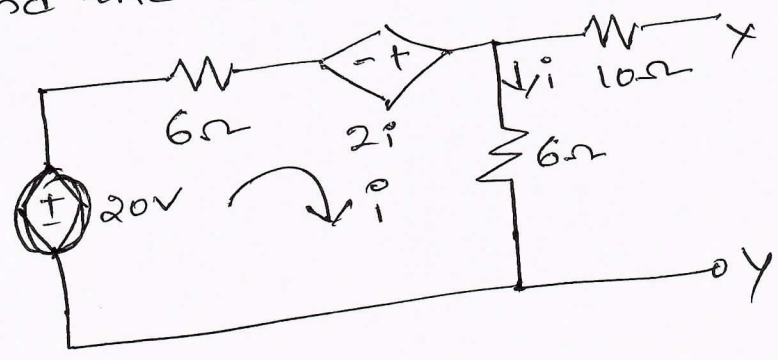Find the Thevenin's equivalent w.r.t. points X-Y



Q.No

4a)
Continued

To obtain V_{th} , as we have dependent source we need open circuit voltage across, $x-y$.
KVL to left side mesh, we get

$$-20 + 6i - 2i + 6i = 0, \therefore \boxed{i = 2A}$$

As, no current flows through 10Ω ,
 \therefore KVL to outer path of right side gives

$$-6i + 0 \times 10 + V_{oc} = 0$$

$$\therefore V_{oc} = 6i \Rightarrow \boxed{V_{oc} = 6 \times 2 = 12V}$$


$$\therefore \boxed{V_{th} = 12V}$$

4M

To find R_{th} , we need I_{sc} through $x-y$, \therefore

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

Shorting $x-y$, terminals we get

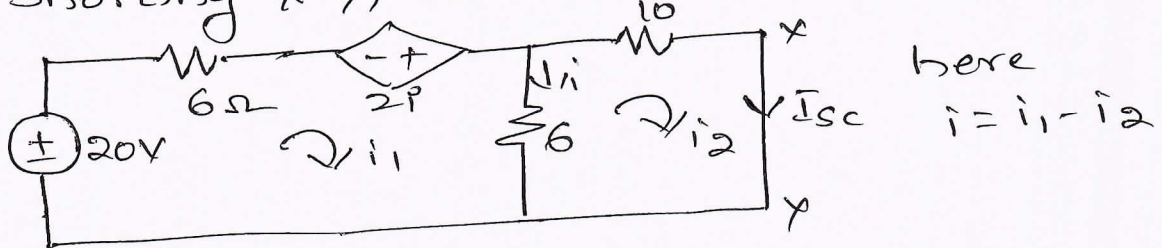

KVL to M_1

$$-20 + 6i_1 - 2i_1 + 2i_2 + 6i_1 - 6i_2 = 0$$

$$\therefore \boxed{10i_1 - 4i_2 = 20} \quad \text{--- (1)}$$


KVL to M_2

$$\boxed{-6i_1 + 16i_2 = 0} \quad \text{--- (2)}$$

$$i_2 = I_{sc} = \frac{120}{136}$$

$$\therefore R_{th} = \frac{12}{\frac{120}{136}} = 13.6\Omega$$

4M

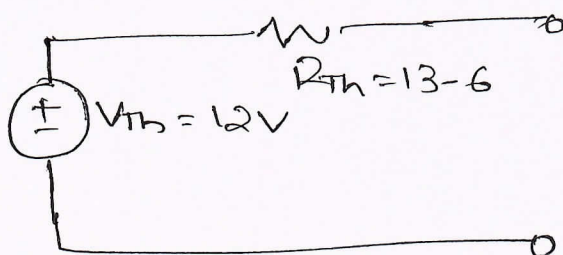


OK

Q.No

4b) Find the condition for maximum power transfer in AC circuit, where both R_L and X_L are variable.

Sol: Consider the following circuit -

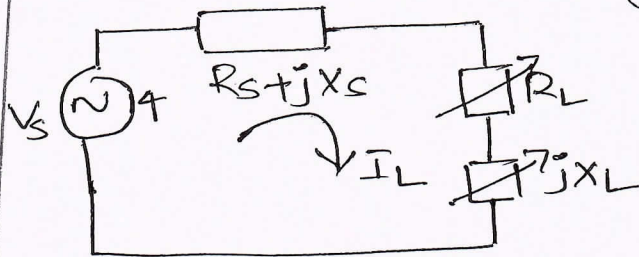

From above circuit,

$$I_L = \frac{V_s}{(R_s + jX_s) + (R_L + jX_L)} = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$\therefore |I_L| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$\therefore P = |I_L|^2 \times R_L$$

$$= \frac{V_s^2}{(R_s + R_L)^2 + (X_s + X_L)^2} \times R_L$$

$$= \frac{V_s^2 \times R_L}{(R_s + R_L)^2}$$

- (3M)

If, R_L varies, then, $\frac{dP}{dR_L}$ will give us, maximum power as

$$\frac{dP}{dR_L} = \frac{V_s^2 \times (R_s + R_L)^2 \times 1 - 2(R_s + R_L)}{(R_s + R_L)^2} = 0$$

$$\therefore (R_s + R_L)^2 - 2(R_s + R_L) = 0$$

$$\therefore \boxed{R_L = R_s}$$

- (3M)


$$\therefore Z_L = (R_s - jX_s) \text{ i.e. } Z_L = Z_s^*$$

OK
Pr...

Q. No.



4CJ

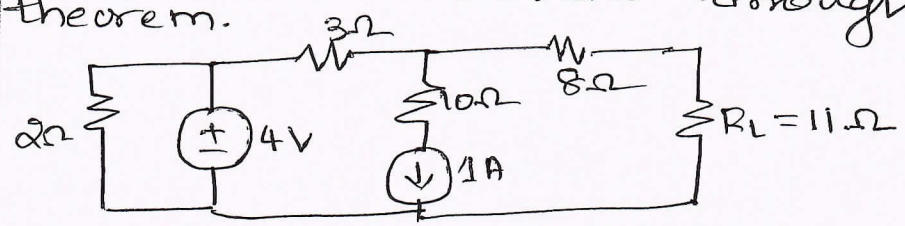Determine the current through R_L , using Norton theorem.




Soln: As, it is required to find current through R_L by N/T, let us reduce the circuit complexity by source transformation.

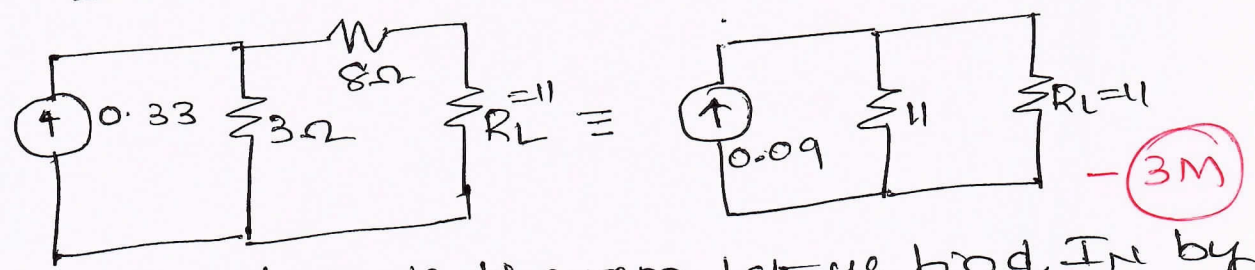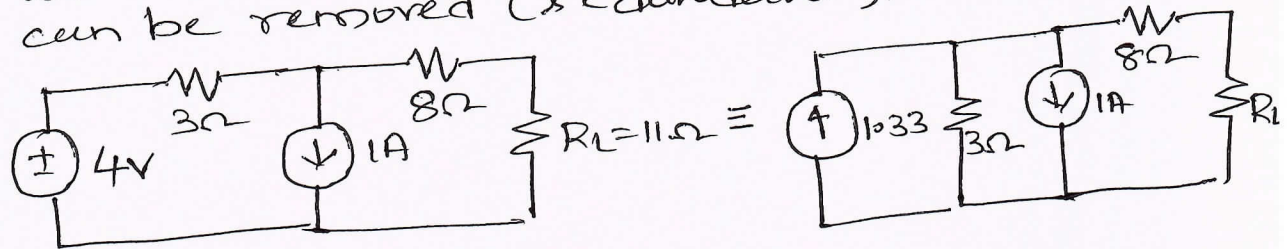
Step 1: as 2Ω and $4V$ are parallel to each other, 2Ω can be removed (redundant), \therefore Converting $4V$, 3Ω to current source we get, and also 10Ω is in series with $1A$ current source, 10Ω can be removed (redundant).



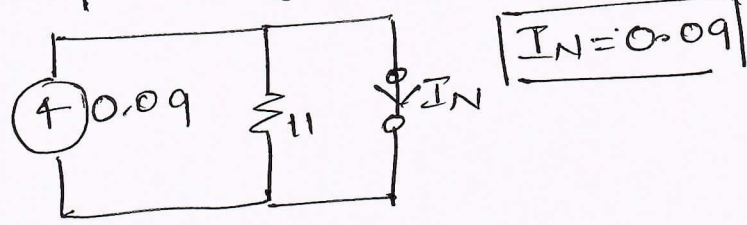
Step 2: By Norton's theorem, let us find I_N by replacing R_L by S/C, \therefore



$I_N = 0.09$

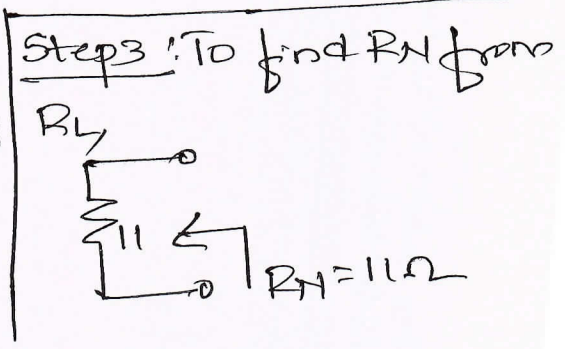

\therefore Norton's eq. n/w is

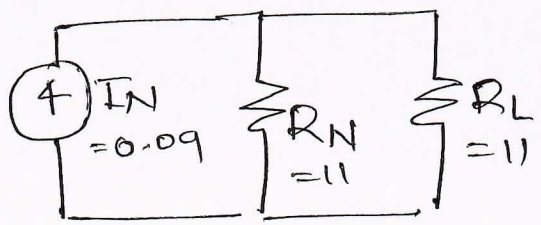

$I_{RL} = \frac{0.09 \times 11}{11 + 11}$
 $I_{RL} = 0.045 \text{ A}$


OK

Q.No

5a)

Explain the behaviour of R, L, C elements at the time of switching at $t=0$, $t=0+$ and $t=\infty$

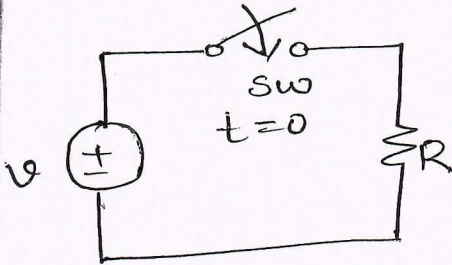i] For Resistor (R) Time SW $i(t)$ $v(t)$
 0 closing $i(0) = \frac{V(0)}{R}$ $V(0) = i(0)R$
 $0+$ } Remains closed $i(0+) = \frac{V(0)}{R}$ $V(0+) = i(0+)R$
 $\&$
 $\&$
 ∞ } $i(\infty) = \frac{V(\infty)}{R}$ $V(\infty) = i(\infty)R$




Current through resistor and voltage across resistor changes instantly (1M)


ii] $v(t)$ $i(t)$
 $\frac{1}{L} \int v_L(t) \cdot dt$
 $\therefore i_L(t) = \frac{1}{L} \int_{-\infty}^{0^-} v \cdot dt + \frac{1}{L} \int_{0^-}^t v \cdot dt$

$i_L(t) = i_L(0^-) + \left\{ \frac{1}{L} \int_{0^-}^{0^+} v \cdot dt \right\} \rightarrow 0$ (3M)

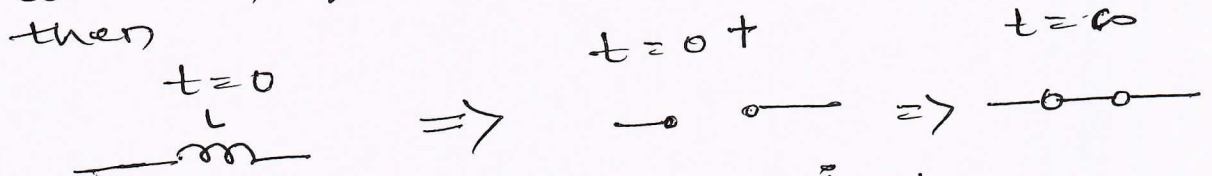\therefore at $t=0+$
 $i_L(0+) = i_L(0^-)$ indicates current through inductor cannot change instantly, \therefore For inductor at $t=0$, if inductor has zero initial current then



if it carries initial current I_0 then

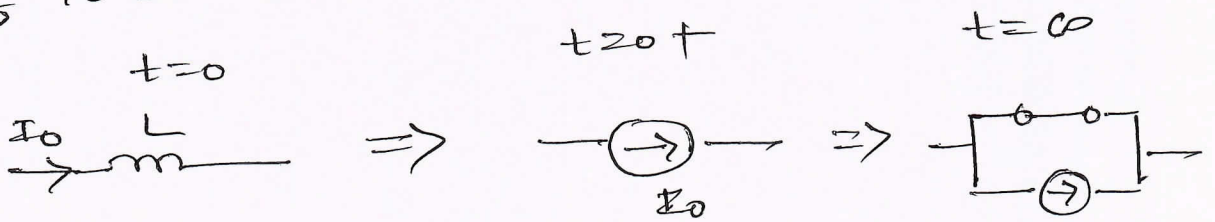


~~(3M)~~

Q.No

5a)
Continued

For Capacitor

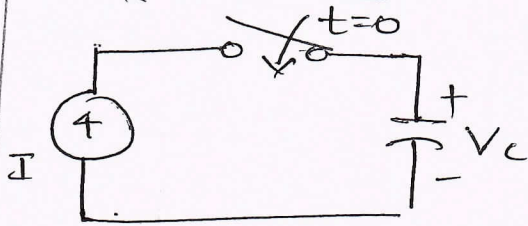

WKT

$$V_c = \frac{1}{C} \int_{-\infty}^t i(t) dz$$

$$\therefore V_c(t) = \frac{1}{C} \int_{-\infty}^{0^-} i(t) dz + \frac{1}{C} \int_{0^-}^t i(t) dz$$

$$\therefore V_c(t) = V_c(0^-) + \frac{1}{C} \int_{0^-}^t i(t) dz$$


For $t=0+$

$$V_c(0+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0+} i(t) dz \rightarrow 0$$


$\therefore \boxed{V_c(0+) = V_c(0^-)} \Rightarrow$ Voltage across capacitor cannot change instantaneously.

3M

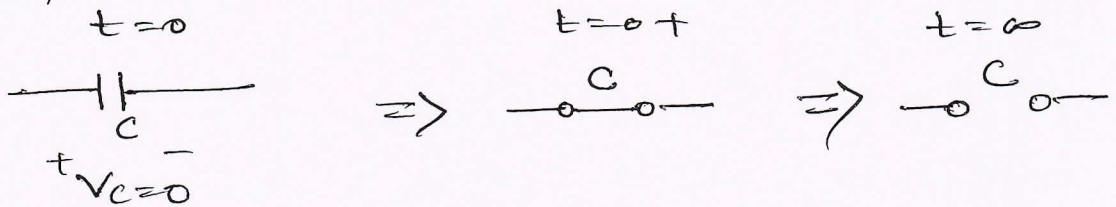Case (i): If capacitor is initially not having voltage then




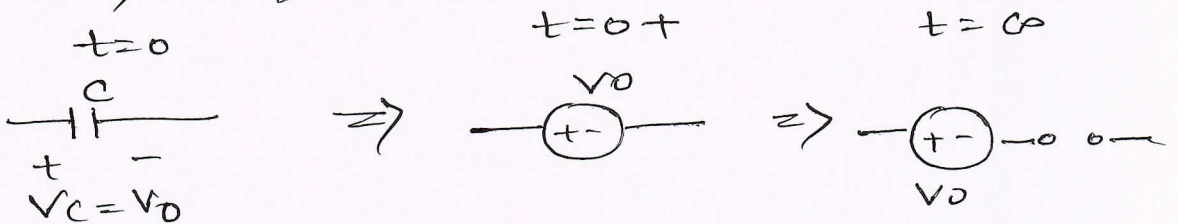Case (ii): If capacitor is having some initial voltage across it, then



5b]

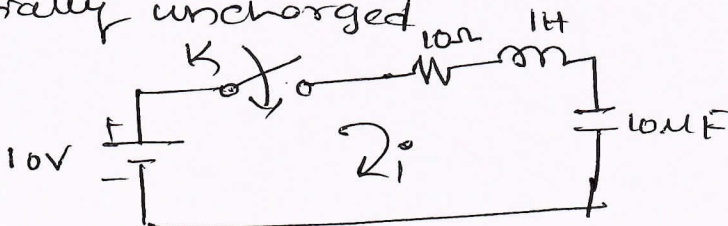
Find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0+$, assume capacitor is initially uncharged.





AE

5b] Continued

At $t=0^-$ (sw is open), \therefore

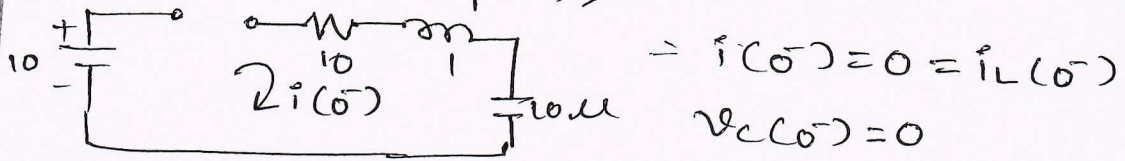

At $t=0^+$ (sw is closed)

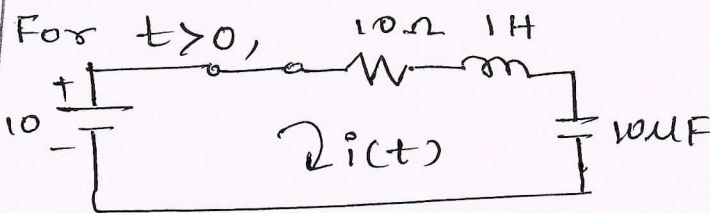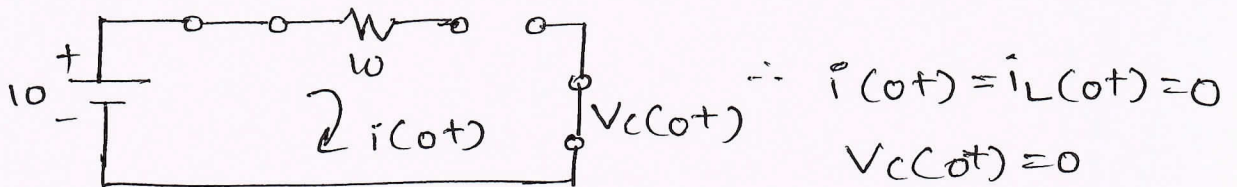

By KVL

(4M)

$$-10 + 10i(t) + 1 \frac{di(t)}{dt} + \frac{1}{10 \times 10^{-6}} \int_0^t i(t) dt = 0 \quad \text{--- (1)}$$

For $t=0^+$

$$-10 + 10i(0^+) + \frac{di(0^+)}{dt} + 0 = 0$$

$$\therefore \boxed{\frac{di(0^+)}{dt} = 10 \text{ A/s}} \quad \text{--- (2)}$$

Diff eq (1),


$$0 + 10 \frac{di(0^+)}{dt} + \frac{d^2i(0^+)}{dt^2} + \frac{1}{10^{-5}} i(0^+) = 0$$

$$\boxed{\frac{d^2i(0^+)}{dt^2} = -10 \times 10 = -100 \text{ A/s}^2} \quad \text{--- (2)}$$

(3M)

5c]

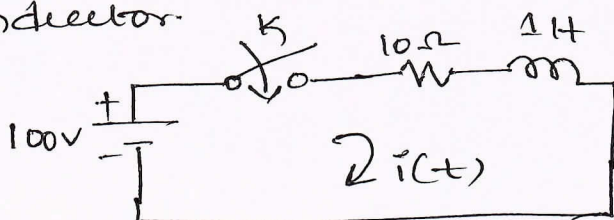Find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$, sw is closed at $t=0$, assume zero initial current through inductor.




at


Q.No

5c)
Continued

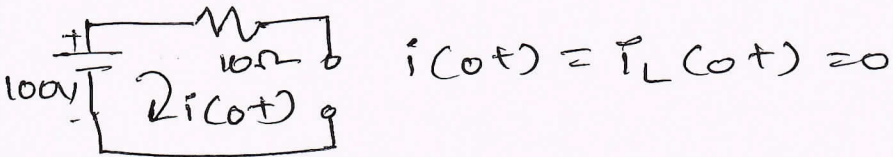At, $t=0^-$, Sw is open, $\therefore i_L(0^-) = 0 = i_L(0^+)$
 At, $t=0^+$, Sw is closed ($\therefore L \leftarrow 0/c$)



For $t > 0$

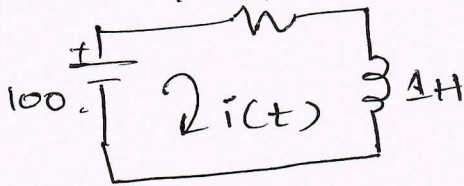

By KVL

$$-100 + 100i(t) + L \frac{di(t)}{dt} = 0 \quad \text{--- (1)}$$

$$100i(t) + \frac{di(t)}{dt} = 100 \quad \text{--- (2)}$$

\therefore at $t=0^+$, $\frac{di(0^+)}{dt} = 100 - 100i(0^+) = 100 \text{ A/s}$


Diff eqn (2), and solving at $t=0^+$ 3M

$$10 \frac{di(0^+)}{dt} + \frac{d^2i(0^+)}{dt^2} = 0, \therefore$$

$$\frac{d^2i(0^+)}{dt^2} = -10 \times 100 = -1000 \text{ A/s}^2 \quad \text{--- (3M)}$$

6a)

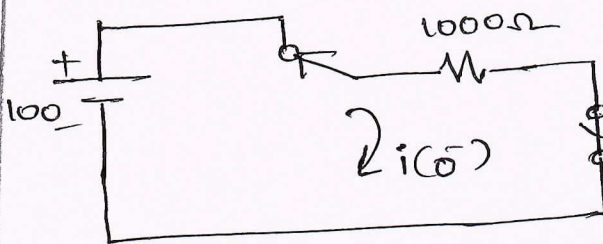For $t=0^-$, (Sw $\leftarrow a$, S.S. is reached), \therefore




$$V_L(0^-) = 0$$

$$i(0^-) = i_L(0^-) = \frac{100}{1000} = 0.1 \text{ A}$$

$$\therefore i_L(0^+) = i_L(0^-) = 0.1 \text{ A}$$

For $t=0^+$ (Sw $\leftarrow b$,

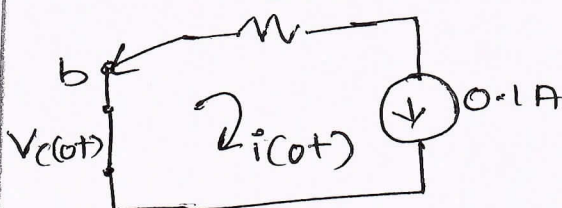


$$i(0^+) = i_L(0^+) = 0.1 \text{ A}$$

$$V_L(0^+) = 0 \quad \text{--- (5M)}$$

Q.No

6a
Continued

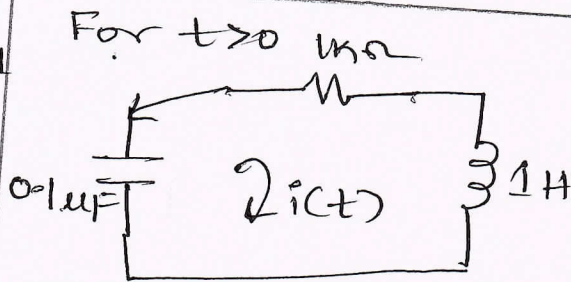

By KVL

$$\frac{1}{0.1 \mu\text{F}} \int_0^t i(t) dt + 1000 i(t) + \frac{1}{1} \frac{d i(t)}{dt} = 0 \quad \text{--- (1)}$$

For $t = 0^+$,

First term in eqn (1) is $V_C(0^+) = 0$, $\therefore i(0^+) = 0.1$

$$\therefore \frac{d i(0^+)}{dt} = -1000 \times 0.1 = -100 \text{ A/s} //$$

Diff eqn (1) again,

$$\frac{1}{10^{-7}} i(t) + 1000 \frac{d i(t)}{dt} + \frac{d^2 i(t)}{dt^2} = 0$$

At $t = 0^+$,

$$10^7 i(0^+) + 1000(-100) + \frac{d^2 i(0^+)}{dt^2} = 0$$


$$\therefore \frac{d^2 i(0^+)}{dt^2} = -9 \times 10^5 \text{ A/s}^2$$

(SM)

6b.


At $t = 0^-$, (switch ~~opens~~ ^{closed}), $\therefore V_C(0^-) = V_K(0^-) = 0$
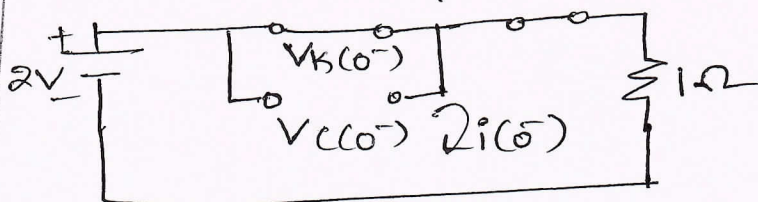
$$i(0^-) = i_L(0^-) = \frac{2}{1} = 2 \text{ A}$$



At $t = 0^+$, C \leftarrow S/C, L \leftarrow 2A, \therefore

(SM)

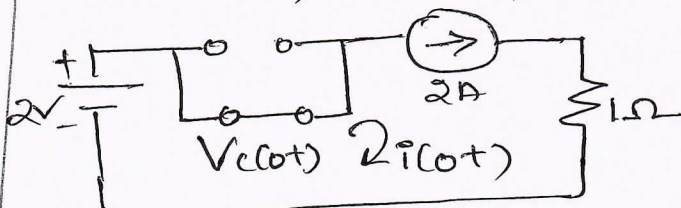

$$i(0^+) = i_L(0^+) = 2 \text{ A}$$

$$V_C(0^+) = 0, V_K(0^+) = 0$$

here, $V_K = \frac{1}{C} \int i(t) dt \Rightarrow \frac{dV_K(t)}{dt} = \frac{i(t)}{C}$, For $t > 0^+$

$$\frac{dV_K(0^+)}{dt} = \frac{i(0^+)}{C} = \frac{2}{0.5} = 4 \text{ A/s} //$$

(SM)

OK

Q.No

Module - 4


7a)

i] Laplace Transform of a unit step function:

It is defined mathematically as

$$u(t) = 1 \text{ for } t \geq 0$$

$$= 0 \text{ for } t < 0$$

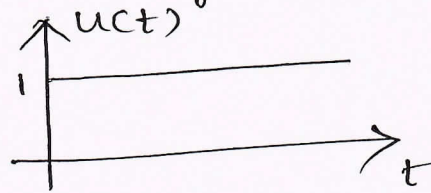

$$\therefore L\{u(t)\} = \int_0^{\infty} u(t) \cdot e^{-st} \cdot dt$$

$$= \int_0^{\infty} 1 \cdot e^{-st} \cdot dt$$

$$= \left[\frac{e^{-st}}{-s} \right]_0^{\infty} = \left[\frac{e^{-\infty}}{-s} - \frac{e^0}{-s} \right]$$

$$\boxed{L\{u(t)\} = \frac{1}{s}}$$


3M

ii] Ramp function $f(t) = r(t) = \tau(t)$

It is given by

$$r(t) = t \text{ for } t \geq 0$$

$$= 0 \text{ for } t < 0$$

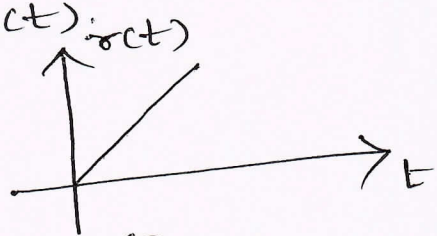

$$L\{r(t)\} = \int_0^{\infty} r(t) \cdot e^{-st} \cdot dt = \int_0^{\infty} t \cdot e^{-st} \cdot dt$$

$$= \left[\frac{t \cdot e^{-st}}{-s} \right]_0^{\infty} - \int_0^{\infty} \frac{e^{-st}}{-s} \cdot 1 \cdot dt$$

$$= [0 - 0] + \frac{1}{s} \int_0^{\infty} e^{-st} \cdot dt$$

$$= \frac{1}{s} \left[\frac{e^{-st}}{-s} \right]_0^{\infty} = \frac{1}{s} \left[0 - \frac{1}{-s} \right]$$


$$\boxed{L\{r(t)\} = \frac{1}{s^2}}$$

3M

Q. No

7a)
Continued

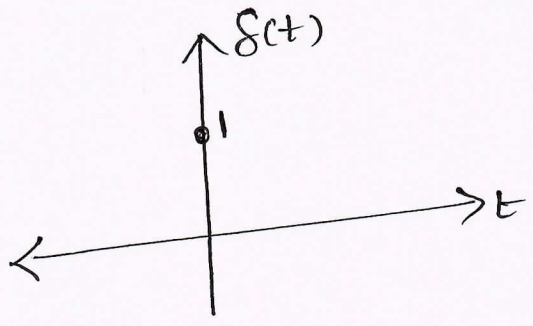impulse function $\delta(t)$.
It is defined as $\delta(t) = 1$ for $t=0$
 $= 0$ for $t \neq 0$.




$$\delta(t) = \frac{d}{dt} u(t) = \mathcal{L}\{u(t)\} - u(t) \Big|_{t=0^-} = s \cdot \frac{1}{s} - 0$$


$$\boxed{\mathcal{L}\{\delta(t)\} = 1} \quad (3M)$$

7b)

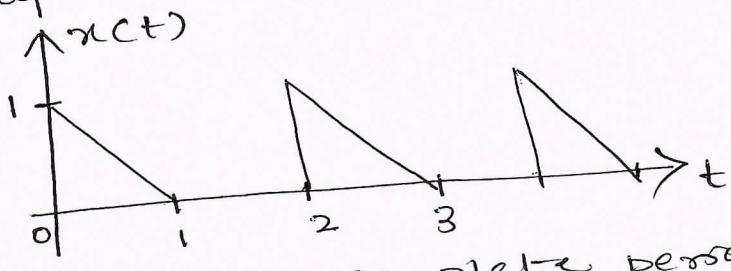Laplace transform of periodic signal $x(t)$.



Consider one complete period T

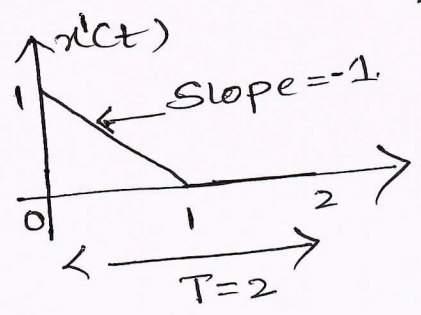


$$x'(t) = u(t) - \tau(t) + \tau(t-1) \quad \therefore X'(s) = \frac{1}{s} - \frac{1}{s^2} + \frac{1}{s^2} e^{-s} \quad (8M)$$

$$\therefore X(s) = \frac{X'(s)}{1 - e^{-Ts}} = \frac{\frac{1}{s} - \frac{1}{s^2} + \frac{1}{s^2} e^{-s}}{1 - e^{-2s}} \quad (3M)$$

Q.No

8a

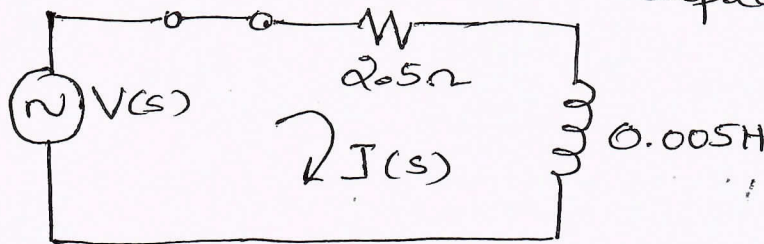Converting the circuit into Laplace domain we get



$$\begin{aligned}
 I(s) &= \frac{12,500}{(2.5 + 0.005s)(s^2 + (250)^2)} \\
 &= \frac{12500}{0.005 [s + 500] [s^2 + 250^2]} \\
 &= \frac{2.5 \times 10^6}{(s + 500)(s^2 + 250^2)}
 \end{aligned}$$

(SM)

$$I(s) = \frac{A}{s + 500} + \frac{Bs + C}{s^2 + 250^2}$$

By P.F, we get

$$\begin{aligned}
 &= \frac{A(s^2 + 62500) + (s + 500)(Bs + C)}{(s + 500)(s^2 + 250^2)} \\
 &=
 \end{aligned}$$

equating co-efficient on b/s of s

$$A + B = 0 \text{ --- (1)}, \quad 500B + C = 0, \quad 62500A + 500C = 2.5 \times 10^6$$

$$\text{Solving } A = 8, \quad B = -8, \quad C = 4000,$$

$$\therefore I(s) = \frac{8}{s + 500} - \frac{8s}{s^2 + 250^2} + \frac{4000}{250} \times \frac{250}{s^2 + 250^2}$$


$$\therefore i(t) = 8e^{-500t} - 8 \cos(250t) + 16 \sin(250t) \text{ A} //$$

(SM)

Q. No


8b)

Given waveform is

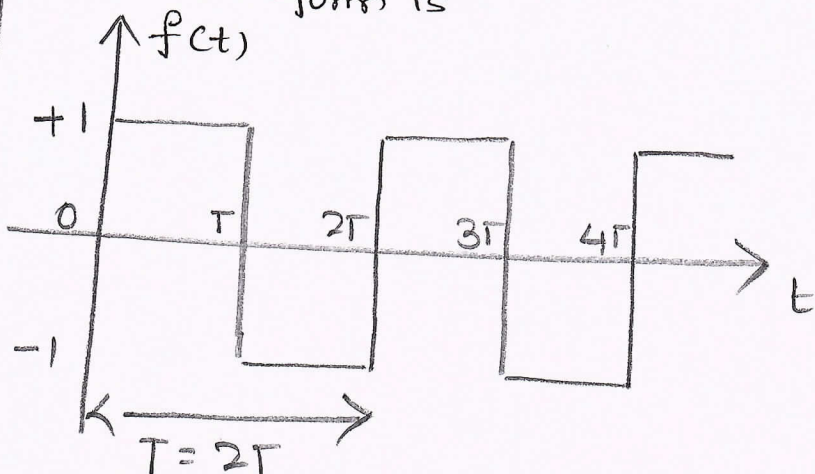

(5M)

Considering one complete cycle, we get

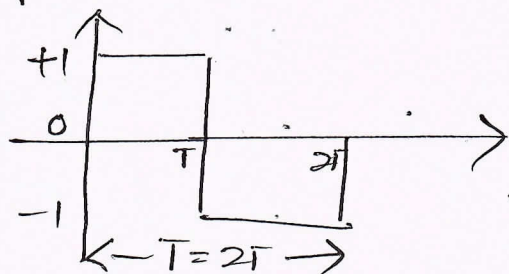

$$f'(t) = u(t) - u(t-T) - u(t-2T) + u(t-2T)$$

$$f'(t) = u(t) - 2u(t-T) + u(t-2T)$$

$$\therefore F'(s) = \frac{1}{s} - \frac{2}{s} e^{-Ts} + \frac{1}{s} e^{-2Ts}$$

(5M)

$$\therefore F(s) = \frac{F'(s)}{1 - e^{-Ts}} = \frac{\frac{1}{s} [1 - 2e^{-Ts} + e^{-2Ts}]}{1 - e^{-2Ts}}$$

Module-5

9a)

Z-Parameter: The Z-parameters of a two-port network is expressed by two port voltages V_1, V_2 as a function of two port-current I_1, I_2 . i.e.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Z-terms of Y parameter

$$\text{whr } I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

(2M)

~~11~~

Q. No

9a)
Continue

By crammers rule

$$V_1 = \frac{\begin{vmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{vmatrix}}{\begin{vmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{vmatrix}} = \frac{Y_{22} I_1 - Y_{12} I_2}{\Delta Y}$$

$$\therefore V_2 = \frac{\begin{vmatrix} Y_{11} & I_1 \\ Y_{21} & I_2 \end{vmatrix}}{\Delta Y} = \frac{Y_{11} I_2 - Y_{21} I_1}{\Delta Y}$$


$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix}$$

- (2M)

- (2M)

9b)

h-parameters.

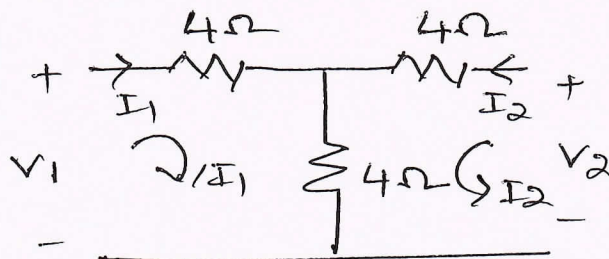

KVL to i/p side gives

$$-V_1 + 8I_1 + 4I_2 = 0$$

$$\boxed{V_1 = 8I_1 + 4I_2} \quad \text{--- (1)}$$

KVL to o/p side

$$\boxed{V_2 = 4I_1 + 8I_2} \quad \text{--- (2)}$$

(4M)

From (2), $\boxed{I_2 = \frac{1}{8} V_2 - \frac{1}{2} I_1}$

$$\therefore I_2 = -\frac{1}{2} I_1 + \frac{1}{8} V_2 \Rightarrow \boxed{h_{21} = -\frac{1}{2}}, \quad \boxed{h_{22} = \frac{1}{8}}$$

Using I_2 in V_1 , we get-

$$V_1 = 8I_1 + (-4/2)I_1 + \frac{1}{2} V_2$$


$$V_1 = 6I_1 + \frac{1}{2} V_2 \Rightarrow \boxed{h_{11} = 6}, \quad \boxed{h_{12} = \frac{1}{2}}$$

(3M)

~~AT~~

Q.No

9c)

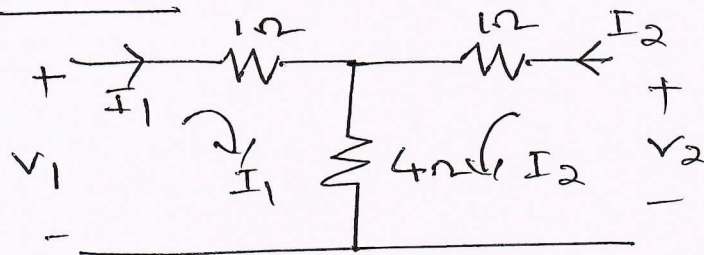Given

$$\text{KVL M1: } v_1 = 5I_1 + 4I_2 \quad \text{--- (1)} \quad \text{(1M)}$$

$$\text{KVL M2: } v_2 = 4I_1 + 5I_2 \quad \text{--- (2)} \quad \text{(1M)}$$

$$\text{Solving } I_1 \text{ from (2), } I_1 = \frac{1}{4}v_2 - \frac{5}{4}I_2 \quad \text{--- (3)} \quad \text{(3M)}$$

$$\therefore \boxed{C = \frac{1}{4}} \quad \boxed{D = \frac{5}{4}} \quad \text{(3M)}$$

Using (3) in (1)

$$v_1 = \frac{5}{4}v_2 - \frac{25}{4}I_2 + 4I_2; \quad v_1 = \frac{5}{4}v_2 - \frac{9}{4}I_2$$

$$\boxed{A = \frac{5}{4}} \quad \boxed{B = \frac{9}{4}} \quad \text{(3M)}$$

10c) i) Quality factor: $Q = \frac{\omega_0 L}{R}$ but $\omega_0 = 2\pi f_0$.

$$\therefore Q = 2\pi f_0 \frac{L}{R} \quad \text{(1M)}$$

Energy stored in Inductor at resonance is $\frac{1}{2} L I_0^2$, x and \div by $\frac{1}{2} I_0^2$, we get-

$$Q = 2\pi f_0 \frac{L}{R} = 2\pi f_0 \left[\frac{\frac{1}{2} L I_0^2}{\frac{1}{2} R I_0^2} \right]$$

$$Q = 2\pi \left[\frac{\text{max energy stored in } L}{\text{Total energy w.r.t time}} \right]$$


AK

Q.No

10a
continued

ii) Selectivity: $S = \frac{f_0}{f_2 - f_1} = \frac{f_0}{BW} = \frac{f_0}{\frac{R}{2\pi L}}$ (1M)

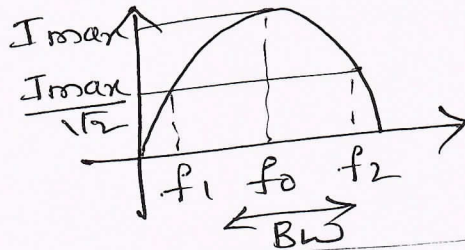iii) Band width: $BW = f_2 - f_1$, it gives the range of operatable frequency for getting resonance condⁿ at f_0 , by varying L and C



(1M)

10b) Given: $R = 10\Omega$, $L = 0.3H$, $C = 100\mu F$, $V_{in} = 230V$.
 $f_0 = ?$, f_1 and $f_2 = ?$, $I_0 = ?$, I at f_1 and $f_2 = ?$.

$V_L = ?$

i) $f_0 = \frac{1}{2\pi\sqrt{LC}} \approx 29.05 \text{ Hz}$ (1M)

ii) $\Delta f = \frac{R}{4\pi L} = 2.65$, $\therefore f_1 = f_0 - \Delta f = 26.4 \text{ Hz}$ (2M)

$f_2 = f_0 + \Delta f = 31.7 \text{ Hz}$


iii) $I_0 = \frac{V}{R} = \frac{230}{10} = 23 \text{ A}$ (1M)

iv) Current at f_1 and f_2
 I at f_1 and $f_2 = 0.707 \times I_0 = 16.26 \text{ A}$ (2M)

v) $V_L = jQ_0 V = j\left(\frac{1}{R}\sqrt{\frac{L}{C}}\right) \cdot V = 1259 \angle 90^\circ \text{ V}$ (1M)

10c)

Show that all resonates at all frequency

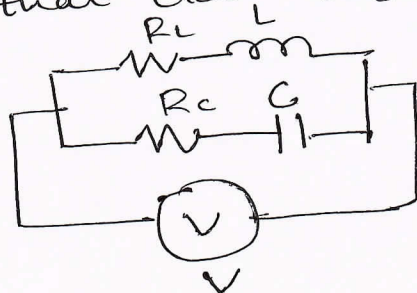

Q.No

IOC
Continued

Taking admittance of each branch

$$Y = \left(\frac{1}{R_L + jX_L} \right) + \left(\frac{1}{R_C - jX_C} \right)$$

- 2M

$$= \frac{R_C - jX_C + R_L + jX_L}{(R_L + jX_L)(R_C - jX_C)}$$

but $X_L \cdot X_C = \frac{L}{C}$

$$= \frac{(R_L + R_C) + j(X_L - X_C)}{R_L R_C + X_L X_C + j(R_C X_L - R_L X_C)}$$

- 2M

if we put $R_L = R_C = \sqrt{\frac{L}{C}}$ then

$$Y = \frac{(\sqrt{L/C} + \sqrt{L/C}) + j(X_L - X_C)}{\sqrt{L/C} \sqrt{L/C} + \frac{L}{C} + j(\sqrt{L/C})(X_L - X_C)}$$

- 2M

$$= \frac{2\sqrt{L/C} + j(X_L - X_C)}{2\sqrt{L/C} + j(\sqrt{L/C})(X_L - X_C)}$$

- 2M

$$= \frac{2\sqrt{L/C} + j(X_L - X_C)}{\sqrt{L/C} [2\sqrt{L/C} + j(X_L - X_C)]}$$

- 2M

$$= \frac{1}{\sqrt{L/C}} = \frac{1}{R} = \sqrt{\frac{C}{L}}$$