



CBCS SCHEME

18CS33

Third Semester B.E. Degree Examination, Aug./Sept.2020 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With a neat diagram, explain the working principle of photocoupler. (08 Marks)
b. List the different types of BJT biasing. Derive the expression for collector emitter voltage (V_{CE}) for fixed bias circuit. (08 Marks)
c. Write a note on light emitting diode. (04 Marks)

OR

- 2 a. Explain with neat diagram, the construction, working principle and characteristics equation of photodiode. (08 Marks)
b. With a neat waveform and circuit diagram, explain the working of monostable multivibrator. (06 Marks)
c. Explain with neat diagram R-2R ladder type DAC and derive the expression for V_0 . (06 Marks)

Module-2

- 3 a. Minimize the following function for SOP using K-map and implement it using basic gates:
 $f(a,b,c,d) = \prod M(5, 7, 13, 14, 15) + d(1, 2, 3, 9)$ (06 Marks)
b. Design the function EX-OR using (i) NAND gates only (ii) NOR gates only (06 Marks)
c. A switching circuit has two control inputs (C_1 and C_2), two data inputs (X_1 and X_2) and one output Z . The circuit performs one of the logic functions such as OR, XOR, AND, EQU for control inputs combination C_1, C_2 as 00, 01, 10, 11 respectively:
(i) Derive the truth table for Z
(ii) Use a K-map to find minimum AND-OR gate circuit to realize Z . (04 Marks)

OR

- 4 a. Minimize the following function for POS using Kmap and realize it by using basic gates:
 $f(a,b,c,d) = \prod M(0, 1, 6, 8, 11, 12) + d(3, 7, 4, 15)$ (06 Marks)
b. Plot the following function on a K-map (Do not expand to minterm before plotting):
 $F(A,B,C,D) = \overline{A} \overline{B} + \overline{C} \overline{D} + ABC + \overline{A} \overline{B} \overline{C} \overline{D} + ABC\overline{D}$, find the minimum sum of products. (06 Marks)
c. A digital system is to be designed in which the month of the year is given as I/P is four bit form. The month January is represented as '0000', February as '0001' and so on. The output of the system should be '1' corresponding to the input of the month containing 31 days or otherwise it is '0'. Consider the excess number in the I/P beyond '1011' as don't care condition:
(i) Write truth table, SOP Σm and POS ΠM form
(ii) Simplify for SOP using K-map
(iii) Realize using basic gates (08 Marks)

Module-3

- 5 a. Explain with neat diagram static hazard 0 and its recover method. (06 Marks)
- Implement the following function using $3 \times 4 \times 2$ PLA:
- b. $A(x, y, z) = \sum m(0, 1, 3, 4); B(x, y, z) = \sum m(1, 2, 3, 4, 5)$ (08 Marks)
- Using EVM method simplify the following function and implement it by using 8:1 MUX
- c. $F(a, b, c, d) = \sum m(0, 1, 2, 4, 5, 6, 9, 10, 12, 13, 14, 15)$ (06 Marks)

OR

- 6 a. With a neat diagram, explain 3 to 8 line decoder. (04 Marks)
- b. Construct 32:1 MUX using 8:1 MUX and 2:4 decoder. (08 Marks)
- c. Design 7 segment decoder and realize using PLA. (08 Marks)

Module-4

- 7 a. Explain with a neat diagram, VHDL program structure. (06 Marks)
- b. Construct SR gates latch using NAND gates and derive the characteristics equation for the same. (08 Marks)
- c. Explain T-flipflop with characteristics equation. (06 Marks)

OR

- 8 a. Explain with neat diagram, working of JK flipflop and derive its characteristic equation. (08 Marks)
- b. Write VHDL code for 4 bit adder. (06 Marks)
- c. Explain the application of SR latch in switch debouncing technique. (06 Marks)

Module-5

- 9 a. With neat diagram, explain 4 bit parallel adder with accumulator. (08 Marks)
- b. With diagram explain 4 bit SISO register. (08 Marks)
- c. Write a note on Johnson tail counter. (04 Marks)

OR

- 10 a. Design Mod 5 counter using JK flipflops. (10 Marks)
- b. Explain 4 bit PIPO shift register with block diagram. (06 Marks)
- c. Write a note on ring counter. (04 Marks)

* * * *



Third Semester B.E Degree Examination,

Aug - Sept, 2020.


18CS33.

Analog and Digital Electronics M.marks: 10

Module 01.

Ques.

 - 1a. With a neat diagram, explain the working principle of photo coupler? 08m
al



working principle of photo coupler.

When the light from LED hits the photodiode, this sets up a reverse current in the output circuit.


The reverse current produces a voltage ~~across~~ at the op-amp resistor. When the input voltage is varying, the amount of light is fluctuating. This means the output voltage is varying in step with the input voltage. The combination of an LED & a photodiode is called an opto coupler.

- 1b. List the different types of BJT Biasing. Derive the expression for Collector-Emitter Voltage for fixed bias current. 08 marks

There are mainly 3 types, ¹ i.e., Biasing a transistor

- a) Base bias or fixed bias
- b) collector to ^{base} \uparrow Bias
- c) voltage divider Bias.

- a) Base Bias or fixed bias

 

Base resistors R_B is used between V_{CC} & Base to establish this base current I_B .

As V_{CC} & R_B are fixed quantity it remains fixed hence called fixed or Base Bias.

Applying KVL for base circuit

$$V_{CC} - I_B R_B - V_{BE} = 0.$$

$$I_B R_B = V_{CC} - V_{BE}.$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Applying KVL for collector circuit.

$$V_{CC} - I_C R_C - V_{CE} = 0.$$

$$\boxed{V_{CE} = V_{CC} - I_C R_C.}$$

Q: Write a note on light emitting diode? Okmali


LED is a PN junction diode which emits light when an electric current passes through the forward direction.

The energy converted during recombination at the junction is dissipated in the form of heat within the structure & the emitted light.

When the device is forward biased, electrons from the P-N junction from the n-type material recombine with holes in the p-type material.

Example / Applications - TV Remote, Calculator, Watches & Traffic Signals.

 Q2. Explain with neat diagram, the construction, working principle & characteristic equation of Photodiode. Q8m



Photodiode is a light detection semi-conductor device that converts light energy into electric current on voltage which depends upon the mode of operation.



Construction.

→ The surface of a layer of n-type is bombarded with p-type silicon ions to produce a p-type layer about 1μm thick.

During the formation of the diode, electrons from

the p-type material & holes from the p-type are attracted into the n-type layer, resulting in the removal of free charge carriers close to the PN junction, so creating a depletion region.

  The top of the diode is protected by a layer of silicon dioxide in which there is a window for light to shine on the semiconductor. Beneath the n-type layer is a more heavily doped n+ layer to provide a low resistance connection to the cathode.




V-I characteristics of photodiode.

When pn junction of photodiode is exposed to light, the reverse current increases with increase in light intensity. The reverse-biased current is produced by thermally generated electron-hole pairs in the depletion region.


Q.b: with a neat waveform and circuit diagram, explain the working of monostable multivibrator? Or

monostable multivibrator is circuit which contains one stable state.

Circuit diagram.

 

waveform.

 

$$T_{ON} = T_2 - T_1$$


Working: Initially the SR flip flop is set ($Q=1$). Transistor T is driven into saturation & capacitor is by-passed by the transistor.

$V_C=0$ and O/P V_g is also zero. When we pulses applied to trigger input of comparator then comparator

output goes high & SR flipflop is reset & Q goes high.

Then, $t_{ON} = 1.7 R_{AC}$.

 Q.C.: Explain the with neat diagram R-2R ladder type DAC & derive the expression for V_o ? [06 marks]



DAC is a circuit which converts digital signals into analog signals. It has n -electronic switches as shown in the figure, which are connected to resistor $2R$ & R . If binary input is high, then switch connects to resistance path. Similarly for binary input low it disconnects.

Mathematically,

for ON switch, current $I_1 = \frac{VR}{2R}$.

for OFF switch, current $I_1 = 0$

Similarly for $I_2 = \frac{VR/2}{2R} = \frac{VR}{4R}$.

$I_3 = \frac{VR/4}{2R} = \frac{VR}{8R}$.

$$I_m = \frac{VR}{2R} \int \sin^2 \omega t$$

W.K.T $v_o = -I_f R_f$

$$v_o = -R_f \left[\frac{VR}{2R} b_1 + \frac{VR}{4R} b_2 + \frac{VR}{8R} b_3 + \dots + \frac{VR}{2^n R} b_n \right]$$

$$v_o = -\frac{R_f}{R} VR \left[b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots + b_n 2^{-n} \right].$$

When $R_f = R$,

$$v_o = -VR \left[b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots + b_n 2^{-n} \right].$$

=

Module 02.

3a. Minimize the following function for SOP using K-map and implement it using basic gates. normally

$$f(a,b,c,d) = \pi m(5,7,13,14,15) + d(1,2,3,9)$$

Given $f(a,b,c,d) = \pi m(5,7,13,14,15) + d(1,2,3,9)$

Converting into minterm form for SOP.

$$f(a,b,c,d) = \sum m(4,6,8,10,11,12) + d(1,2,3,9)$$

		cd	00	01	11	10
		ab	00	01	11	10
	00	0	X	X	X	X
	01	1	0	0	0	1
	11	1	0	0	0	0
	10	1	X	1	1	0


SOP expression

$$= b\bar{c}\bar{d} + \bar{a}\bar{b} + \bar{a}c\bar{d}$$

SOP expression

$$Y = b\bar{c}\bar{d} + \bar{a}b + \bar{a}c\bar{d}$$

Realize the circuit using basic gates.

 


3b) Design the function XOR using. i) NAND gates only. ii) NOR gates only. Q 0 marks

 
i) NAND gates only.

Required

$$\text{XOR} - A \oplus B = \overline{AB} + A\overline{B}$$



Available.
NAND.

 

$$\overline{AB} + A\overline{B} = \overline{AB} \parallel \overline{B} \text{ Derr (or)}$$

ii) XOR gate using NOR gate.

$$F = A\bar{B} + \bar{A}B$$


$$F = (A+B)(\bar{A}+\bar{B})$$

$$F = (A+B)(A\bar{B}) \quad \text{by De Morgan law.}$$

$$\bar{F} = (\bar{A}+\bar{B}) + (\bar{A}\bar{B})$$

$$F = \bar{\bar{F}} = \overline{AB + (\bar{A}\bar{B})}$$

$\times \quad Y$

 

$$F = \overline{AB + (A \bar{T} B)}$$

$$\begin{aligned} &= \overline{AB} \cdot (\overline{A \bar{T} B}) = (\bar{A} + \bar{B})(A \bar{T} B) \\ &= \bar{A}B + A\bar{B} \end{aligned}$$

=====

3c

A switching circuit has two control inputs (C_1 and C_2) and two data inputs (x_1 and x_2) and one output Z . The circuit performs one of the logic functions such as OR, XOR, AND, EQU for control inputs combination C_1, C_2 as 00, 01, 10, 11 respectively. 04 marks.

i) Derive the truth table for Z .


ii) use a K-map to find minimum AND-OR gate

i) Truth table for Z.

x_1	x_2	c_1	c_2	Z.
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	1	1	1
<hr/>				y OR.
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	1	1	0
<hr/>				y XOR.
0	0	0	0	0
0	1	0	1	0
1	0	1	0	0
1	1	1	0	1
<hr/>				y AND.
0	0	1	1	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1
<hr/>				y equ.


Truth table:-

x_1	x_2	c_1	c_2	Z.
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	1	0	1
1	0	1	1	0
1	0	0	0	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

 


$$Y = \bar{a}\bar{b}c\bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}cd + abc + b\bar{c}\bar{d} + \bar{a}\bar{b}\bar{c}$$

Realize the given expression.

 

 
- 4a) Minimize the following function for POS using K-map. and realize it by using basic gates.
- $f(a,b,c,d) = \text{TIM}(0,1,6,8,11,12) + d(3,7,14,15)$



$$Y = (c+d)(\bar{c}+\bar{d})(a+b+c) \\ (a+b+d)$$

Realize the expression Y .

a b c d.

 

4b)

plot the following function on K-map (do not expand to minterm before plotting):

$$F(A,B,C,D) = \bar{A}\bar{B} + C\bar{D} + AB\bar{C} + \bar{A}\bar{B}C\bar{D} + ABC$$

find minimum sum of products. **06marks**

$$F(A,B,C,D) = m_3 + m_2 + m_1 + m_0 + m_4 + m_6 + m_5$$

AB/CD	00	01	11	10
00	1	1	1	1
01	0	0	0	1
10	0	0	1	1
11	0	0	0	1

$$Y = \underline{\overline{AB}} + \overline{CD} + \overline{ABC}$$

4c. A digital system is to be designed in which the month of the year is given as I/p is four bit form. The month January is represented as '0000'. February as '0001' and so on. The output of the system should be '1' corresponding to the input of the month containing 31 days or otherwise it is '0'. Consider the excess number in the I/p beyond '1011' as don't care condition.

i) Write truth table, SOP Σm and POS ΠM for

ii) Simplify for SOP using K-map. Q8mark

iii) Realize using basic gates.

i) Truth table:

month	A	B	C	D	Output
Jan	0	0	0	0	1
Feb	0	0	0	1	0
March	0	0	1	0	1
April	0	0	1	1	0
May	0	1	0	0	1
June	0	1	0	1	0
July	0	1	1	0	1
Aug	0	1	1	1	1
Sep.	1	0	0	0	0
	1	0	0	1	1
Oct	1	0	1	0	0
Nov	1	0	1	1	1
Dec.	1	1	0	0	X
	1	1	0	1	X
	1	1	1	0	X
	1	1	1	1	X

SOP form —

$$Y = \Sigma m(0, 2, 4, 6, 7, 9) + \Sigma d(12, 13, 14, 15)$$

POS form —


$$Y = \Pi M(1, 3, 5, 8, 10) + \Pi D(12, 13, 14, 15)$$

iii) SOP using K-map.

AB \ C	00	01	11	10
00	1	0	0	1
01	1	0	1	0
11	X	X	X	X
10	0	1	1	0

$$Y = AD + BC + \bar{A}\bar{D}$$

iii) Realize the expression.

 


Module 03.

5a. Explain with neat diagram Static hazard & its recover method? 06marks

Static 0 hazard — This type of hazard occurs for product of sum expression.

 
It occurs for the situation $Y = A \cdot A'$.



Example: $y = f(a,b,c) = \text{sum}(0,1,3,4)$.

a	b\c	00	01	11	10
0	0	0	0	1	
1	0	1	1	1	1

$$y = (b+c)(a+c)$$

 

Case 1: If $b=0, a=0, c=1$.

Due to not gate delay c' produces o/p at 1 and changes only after τ time.

$$\begin{aligned} bc &= 0 \cdot 1 = 0 \\ ac' &= 0 \cdot 1 = 0 \quad \{ y = 0 \} \end{aligned}$$

Case 2: If $b=0, a=0, c=0, y=0$.

Hazard Covel:

Hazard Covel is adding extra minterms to the logic expression.

a	b\c	00	01	11	10
0	0	0	0	1	
1	0	1	1	1	1

$$y = (b+c)(a+c)(a+b)$$

$(a+b)$ term is independent of c.

5.b. Implement the following function using $3 \times 4 \times 2$ PLA

$$A(x,y,z) = \sum m(0,1,3,4); B(x,y,z) = \sum m(1,2,3,4,5).$$

Osmalke

$$A(x,y,z) = \sum m(0,1,3,4)$$

	00	01	11	10
0	1	1	1	0
1	1	0	0	0

$$A = \bar{x}z + \bar{y}\bar{z}$$


$$B(x,y,z) = \sum m(1,2,3,4,5)$$

	00	01	11	10
0	0	1	0	1
1	1	1	0	0

$$B = \bar{x}\bar{y} + \bar{x}z + \bar{x}\bar{y}z$$

PLA Table.

Product Terms.	X	Y	Z	A	B
$\bar{x}z$	0	-	1	1	-
$\bar{y}\bar{z}$	-	0	0	1	-
$x\bar{y}$	1	0	-	-	1
$\bar{x}y$	0	1	-	-	1

 

5c. Using EXM method Simplify the following function
and implement it by using 8:1 mux. osmarks

$$F(a,b,c,d) = \sum(0,1,2,4,5,6,9,10,12,13,14,15)$$


Truth table.

A	B	C	D	y.
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	0	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


Assume \emptyset as MEX
EXM table

A	B	C	y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

8:1 mux

 


 6a) With a neat diagram, explain 3 to 8 line decoder output



a	b	c	Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 6b) Construct 32:1 mux using 8:1 mux and 2:1 dec
output




6c) Design 7-Segment decoder and realize using PLA. 08marks.

Truth table for 7-Segment decoder.

Digit	A	B	C	D	\bar{a}	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	0	0	0	0
3	0	0	1	1	1	1	0	1	1	0	1
4	0	1	0	0	1	1	1	1	0	0	1
5	0	1	0	1	0	1	1	0	0	1	1
6	0	1	1	0	1	0	1	1	0	1	1
7	0	1	1	1	1	0	1	1	1	1	1
8	1	0	0	0	1	1	1	1	0	0	0
9	1	0	0	1	1	1	1	1	0	1	1


K-map Simplification

For a.

 

$$a = A + C + BD + \bar{B}\bar{D}$$

For b

 

$$b = \bar{B} + \bar{C}\bar{D} + CD$$

for C

AB\CD	00	01	11	10
00	1	1	1	0
01	1	1	1	1
11	x	x	x	y
10	1	x	x	x

$$C = B + \bar{C} + D.$$

for D

AB\CD	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	x	x	x	x
10	1	1	x	x

$$d = \bar{B}\bar{D} + \bar{C}\bar{D} + B\bar{C}D + \bar{B}C + A$$

for E

AB\CD	00	01	11	10
00	1	0	0	1
01	0	0	0	1
11	x	x	x	x
10	0	x	x	x

$$E = \bar{B}\bar{D} + \bar{C}\bar{D}$$

for F


AB\CD	00	01	11	10
00	0	0	1	1
01	1	1	0	1
11	x	x	x	x
10	1	1	x	x

$$F = A + B\bar{C} + \bar{B}C + \bar{C}\bar{D}$$

For F.

AB	CD	00	01	11	10
00		0	0	0	0
01		1	0	X	X
11		X	X	X	X
10		1	X	X	X


$$F = A + \bar{C}\bar{D} + B\bar{C} + B\bar{D}$$

 

Module 04.

7a) Explain with a neat diagram, VHDL program structure. 06marks

VHDL Program Structure.

 

When we describe a system in VHDL, we must specify an entity and an architecture at the top level and also specify an architecture for each component modules that are the part of the systems.

A VHDL module must have all inputs & output described in entity declaration & specifying the internal operation of the module using architecture declaration.

General format of entity declaration.

entity entity-name is

[part (interface - signal)-declaration);].

end [entity] [entity name];

General format for architecture
 architecture architecture-name of entityname is.
 [declarations]


begin

architecture body.

end

[architecture] [architecture-name];

7b) Construct SR gates latch using NAND gates and
 derive the characteristics equation for the same?
osmally

 

Case 1: $S=1, R=0, Q=0, \bar{Q}=1$

$S=1, R=1, Q=0, \bar{Q}=1$ memory,

Case 2: $S=0, R=1, Q=1, \bar{Q}=0$

$S=1, R=1, Q=1, \bar{Q}=0$ memory,

Case 3: $S=0, R=0, Q=1, \bar{Q}=1$ not used

$S=1, R=1, Q=1, \bar{Q}=0$.

S	R	Q	\bar{Q}
0	0	Not used	
0	1	1	0
1	0	0	1
1	1	memory	

Characteristic table

S	R	Q_n	Q_{n+1}
0	0	0	X
0	0	1	X
0	1	0	X
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Characteristic Eqn

S	Q_n	00	01	10	11
0	(X)	X	1	1	1
1	0	0	1	0	.


$$Q_{n+1} = \bar{S} + R_n$$

T.C

Explain T-flip-flop with characteristics equation?

Offmally

 - * T flip-flop is also known as 'Toggle flip'
- * T flipflop is a modification of the JK flipflop
- * It is obtained by connecting both inputs of JK together.



Truth table for T-flip flop.

CLK	T	Q_{n+1}
0	X	Q_n
1	0	memory
1	1	\bar{Q}_n


Characteristic Table.

Q_n	T	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0.

Characteristic Equation

$$Q_{n+1} = Q_n \oplus T$$

 8a. Explain with neat diagram, working of JK flip flop and derive its characteristic equation? [8marks]



$CLK = 0$, memory

$CLK = 1, J = 1, K = 0, Q = 1, \bar{Q} = 0$.

$CLK = 1, J = 0, K = 1, Q = 0, \bar{Q} = 1$.

$CLK = 1, J = 1, K = 1, Q = 0, 1, 0, 1 \dots \bar{Q} = 1, 0, 1, 0 \dots$

Assume $Q = 0, \bar{Q} = 1$.

Truth table

CLK	$J \backslash K$	Q_{n+1}
0	xx	Q_n
1	00	Q_n
01		0
10		1
11		toggle(\bar{Q}_n)

Characteristic table

$Q_n \backslash J \backslash K$	000	001	010	011	100	101	110	111
0	0	0	1	1	0	0	1	1
1	1	1	0	0	1	1	0	0

Characteristic eqn

$Q_n \backslash JK$	00	01	10	11
0	0	0	1	1
1	1	1	0	0

$$Q_{n+1} = \bar{Q}_n J + Q_n \bar{K}$$

8b. write VHDL code for 4 bit adder? ~~of marks~~

```
entity Adder4 is
port (A,B : in bit_vector(3 downto 0);
      Ci : in bit;
      S : out bit_vector(3 downto 0);
      Co : out bit);
end Adder4;
```

architecture Structure of Adder4 is

component FullAdder

```
- port (x,y,Cin : in bit;
       Cout, Sum : out bit)
```

end component;

Signal C : bit_vector(3 downto 1),

begin

FA0 : FullAdder port map (A(0), B(0), Ci, C(0), SC0)

FA1 : FullAdder port map (A(1), B(1), C(0), C(1), SC1)

FA2 : FullAdder port map (A(2), B(2), C(1), C(2), SC2)



FA3 : FullAdder port map (A(3), B(3), C(2), C(3), SC3)

end Structure;

  c) Explain the application of SR latch in switch debouncing technique. (6marks).

* useful application of the SR latch is for debouncing switches. When a mechanical switch is opened or closed, the switch contacts tend to vibrate or bounce open & closed several times before settling down to their final position. This produces a noisy transition, and this noise can interfere with the proper operation of a logic circuit.

The input of the switch in fig. below is connected to a logic 1 (+V). The pull down resistors connected to contacts a & b assure that when the switch is between a & b the latch inputs S & R will always be at logic 0, and the latch output will not change state.




Module -05

Q.a with neat diagram, explain 4 bit parallel adder with accumulator. 08marks.

In computer circuits, it is frequently desirable to store one number in a register of flip-flops and add a second number to it, leaving the result stored in the accumulator.

One way to build a parallel adder with an accumulator is as shown in fig. below.

 
Suppose that the number $x = x_n \dots x_2 x_1$ is stored in the accumulator. Then the number $y = y_n \dots y_2 y_1$ is applied to the full adder inputs and after the carry has propagated through the adders, the sum of $x & y$ appears at the adder outputs.



qb. with neat diagram explain 4 bit SISO register

SISO Register? (8marks)

Serial Input

 

Serial Data
output

→ This register has four flip-flops (D) connected serially where data is made input on one side and output appears on other side serially.

- The Q output of each flip flop is connected to D input of next flip flop.
- The control input i.e., the clock input of each flip flop is connected together to a common synchronizing signal called clock.
- Thus, on the trailing edge of the clock signal, the contents of each flip flop is shifted one position to the right.

The output from the shift register occurs at the right most flip flop on the serial data outline.

Q6) write a note on Johnson Rail counter? ok make

The Johnson Ring counter is another shift register with feedback exactly the same as a ring counter except here the inverted output \bar{Q} of the last flip-flop is now connected back to the input D of the first flip-flop.

The main advantage of this type of ring counter is that it only needs half the number of flip-flops compared to the standard ring counter then its number is halved. So a n-stage Johnson counter will circulate a single data bit giving sequence of 2^n different states.

It can be considered as "mod- 2^n counter"

10a. Design Mod 5 counter using JK flipflops. 1 or 2

State table.

C	B	A	Ctrl	Bt1	At1	J _C	K _C	J _B	K _B	J _A	K _A
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	Y
0	1	1	1	0	0	0	1	X	1	X	1
1	0	0	0	0	0	0	X	0	X	0	X

K-map:

		B\A	00	01	11	10
		C	1	X	X	1
J _A	0	0	0	X	X	X
	1	1	X	X	X	X

T_n - T

		B\A	00	01	11	10
		C	X	1	1	X
K _A	0	0	X	X	X	X
	1	1	X	X	X	X

1 - 0 = 1

		<u>J_B</u>	<u>K_B</u>		
		00	01	11	10
$C \setminus BA$	00	0	1	X	X
	01	X	X	X	X

$$J_B = A$$

		<u>J_B</u>	<u>K_B</u>		
		00	01	11	10
$C \setminus BA$	00	X	(X)	1	0
	01	X	X	X	X


$$K_B = A \cdot$$

		<u>J_C</u>	<u>K_C</u>		
		00	01	11	10
$C \setminus BA$	00	0	0	1	0
	01	X	X	X	X

$$J_C = A \cdot B$$


		<u>J_C</u>	<u>K_C</u>		
		00	01	11	10
$C \setminus BA$	00	X	X	X	X
	01	1	X	X	X

$$K_C = J$$

 

 
b) Explain 4 bit PIPD shift register with block diagram? **Osmarks**

In parallel in parallel out there is simultaneous entry of all data bits and the bits appear on parallel outputs.



- Inputs are applied simultaneously at I_3, I_2, I_1 & I_0
- When inputs are loaded into flipflops it is reflected back in outputs Q_3, Q_2, Q_1, Q_0 at the same time.
- Clock pulse is applied to each flip-flop to make it positive or negative or edge triggering.

 ~~Ques~~) Write a note on Ring Counter? our marks.



- Here @the Q of each flip-flop is connected to the D input of the next flip-flop & the output of the last flip-flop is feedfed back to the input of first flip-flop.


The CTR & PRE pins make the output of first flip flop to '1' and remaining QP as zero.
 i.e. Q_A is 1 and Q_B, Q_C & Q_D are '0'.

Truth table

Clock pulse

	Q_A	Q_B	Q_C	Q_D
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3.	0	0	0	1

Waveforms

 

Sandeep P. Patel & R.



P. Patel
S. Patel