

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--	--	--

18EE32

Third Semester B.E. Degree Examination, Aug./Sept.2020 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Determine voltage V_3 for the circuit shown in Fig.Q1(a), using Mesh analysis method.

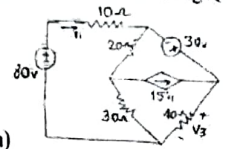


Fig.Q1(a)

(08 Marks)

- b. Apply node analysis method to find node voltages V_1, V_2, V_3 for the circuit shown in Fig.Q1(b).

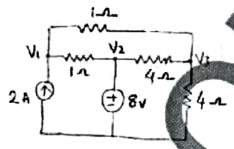


Fig.Q1(b)

(07 Marks)

- c. Determine the equivalent resistance between the terminals AB for circuit shown in Fig.Q1(c).



Fig.Q1(c)

(05 Marks)

OR

- 2 a. Apply loop analysis method to find voltage V , such that current through $(2 + j3) \Omega$ resistor is zero. For the circuit shown in Fig.Q2(a).

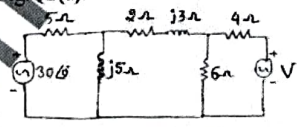


Fig.Q2(a)

(07 Marks)

- b. Determine the voltage V_x in the circuit shown in Fig.Q2(b) using Nodal analysis method.

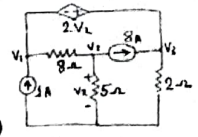


Fig.Q2(b)

(07 Marks)

- c. Apply source transformation and shifting method to reduce the circuit shown in Fig.Q2(c) to a single voltage source in series with resistance.

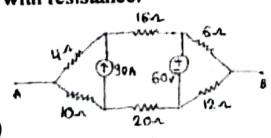


Fig.Q2(c)

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8=50, will be treated as malpractice.

18EE32

Module-2

- 3 a. In the circuit shown in Fig.Q3(a), determine current I_x using super position theorem.

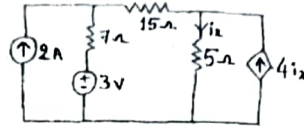


Fig.Q3(a)

- b. Determine Thevenin's equivalent of the circuit in Fig.Q3(b).

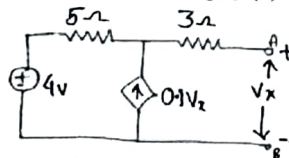


Fig.Q3(b)

- c. Use Millman's theorem to find current I , for the circuit shown in Fig.Q3(c).

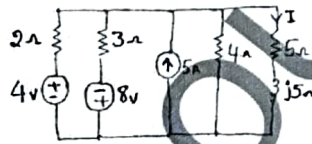


Fig.Q3(c)

- 4 a. Determine current through 1Ω resistor. Using Norton's theorem for the circuit shown in Fig.Q4(a).

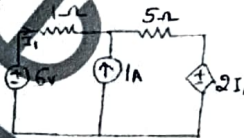


Fig.Q4(a)

- b. Determine the load resistance R_L to receive maximum power from the source. Also find maximum power delivered to the load in the circuit shown in Fig.Q4(b).

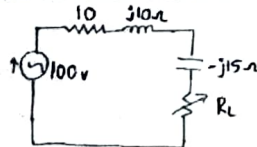


Fig.Q4(b)

- c. State and verify reciprocity theorem for the circuit shown in Fig.Q4(c).

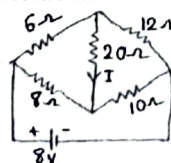


Fig.Q4(c)

18EE32

Module-3

- 5 a. Derive an expression for the resonance frequency of a resonant circuit consisting of R_L, X_L in parallel with RC, X_C . (07 Marks)
- b. An impedance coil having a resistance of 4Ω and an inductance of $1mH$ connected in series with $10\mu F$ capacitor. Determine resonant frequency, impedance at resonance, half power frequencies, Q of the circuit and bandwidth. (08 Marks)
- c. For the circuit shown in Fig.Q5(C), the switch is moved from position 1 to 2 at $t=0$. The steady state has been reached before switching. Determine : $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t=0$.

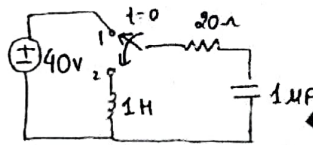


Fig.Q5(c)

(05 Marks)

OR

- 6 a. In circuit shown in Fig.Q6(a), the switch K is closed at $t=0$. Calculate $\frac{di_1(0^+)}{dt}$ and $\frac{di_2(0^+)}{dt}$. Assume that the circuit was not activated before $t=0$.

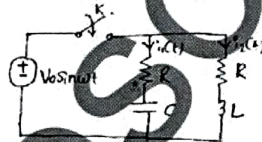


Fig.Q6(a)

(10 Marks)

- b. Determine R_L and R_C for which the circuit shown in Fig.Q6(b), resonances at all frequencies.

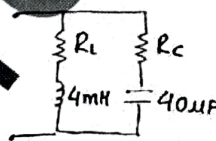


Fig.Q6(b)

(04 Marks)

- c. Show that in series RLC circuit, the resonant frequency $f_0 = \sqrt{f_1 f_2}$. (06 Marks)

Module-4

- 7 a. State and prove initial and final value theorem in Laplace transformation. (08 Marks)
- b. Find Laplace transform of the signal shown in Fig.Q7(b).

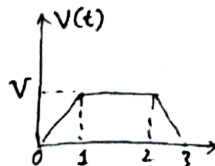


Fig.Q7(b)

(08 Marks)

- c. Find Laplace transform of unit step function. (04 Marks)

OR

181132

8. a. State and prove shifting theorem.
 b. Verify initial value theorem, given $f(t) = 10e^{-t}$
 c. Find Laplace-transform of the signal in Fig.Q8(c)

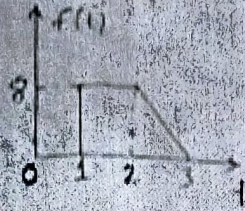


Fig.Q8(c)

(05 Marks)
 (05 Marks)

(10 Marks)

Module-5

9. a. Three impedances $Z_1 = 20 \angle 30^\circ \Omega$, $Z_2 = 40 \angle 60^\circ \Omega$ and $Z_3 = 10 \angle 90^\circ \Omega$ are delta connected to a 400V, 3 phase system as show in Fig.Q9(a). Determine the
 i) Phase currents ii) Line currents



Fig.Q9(a)

(06 Marks)

- b. Determine Y parameters for the circuit shown in Fig.Q9(b).

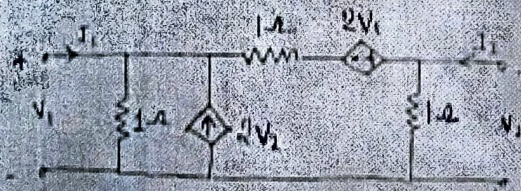


Fig.9(b)

(06 Marks)

- c. Express Y-parameters in terms of Z-parameters.

(06 Marks)

OR

10. a. An unbalanced four-wire, star connected load has a balanced voltage of 400V, the loads are $Z_1 = (4 - j8)\Omega$, $Z_2 = (3 + j4)\Omega$, $Z_3 = (15 + j20)\Omega$. Calculate the i) line currents ii) current in the neutral wire. (06 Marks)
 b. Find Z-parameters and T-parameters for the circuit shown in Fig.Q10(b).

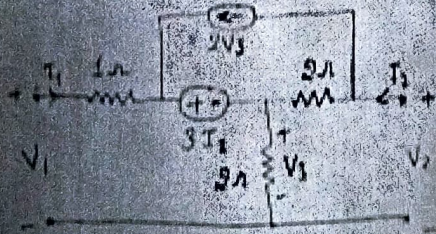


Fig.Q10(b)

(10 Marks)

- c. Define H-parameters with necessary equations.

(04 Marks)

Aug/Sep - 2020


MODULE - 1

1
a. Determine Voltage V_3 for the circuits shown in fig using Mesh analysis method.

→ applying KVL to loop 1

$$-10(I_1) - 20(I_1 - I_2) - 30(I_1 - I_3) = +30V - 30V$$
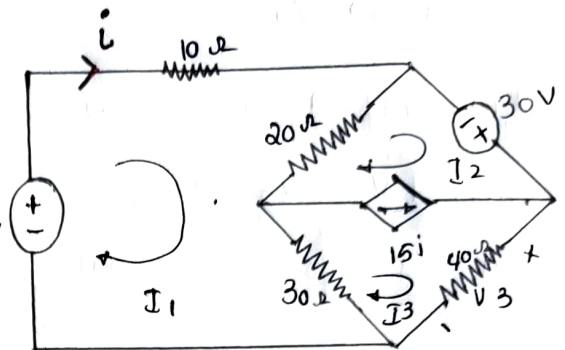
$$60I_1 + 20I_2 + 30I_3 = -30 \quad \text{--- (1)}$$



applying KVL to loop 2 & 3

$$-20(I_2 - I_1) + 30 - 40I_3 - 30(I_3 - I_1) = 0$$

$$50I_1 - 20I_2 - 70I_3 = -30 \quad \text{--- (2)}$$

eqⁿ for 15i

$$I_3 - I_2 = 15i$$

$$\text{but } i = I_1$$

$$I_3 - I_2 = +15I_1$$

$$-15I_1 - I_2 + I_3 = 0 \quad \text{--- (3)}$$

solving (1) (2) & (3)

$$I_1 = 10.24A$$

$$I_2 = -11.0A$$

$$I_3 = 4.3A$$

$$\text{Voltage for } V_3 = I_3 \cdot 40$$

$$= 40 \times 4.34$$

$$V_3 = \underline{\underline{173.6V}}$$

B. Apply node analysis method to find node voltages V_1, V_2, V_3 for circuit shown in fig.

Solⁿ

Apply KCL to V_1

$$2 - 1(V_1 - V_2) - 1(V_1 - V_3) = 0$$

$$2 - 2V_1 + V_2 + V_3 = 0$$

$$2V_1 - V_2 - V_3 = 2 \quad \text{--- (1)}$$

Apply KCL to V_3

$$\frac{1}{4}(V_3 - 0) - \frac{1}{4}(V_3 - V_2) - 1(V_3 - V_1) = 0$$

$$0.25V_3 - 0.25V_3 + 0.25V_2 - 1V_3 + V_1 = 0$$

$$V_1 - V_3 + 0.25V_2 = 0$$

$$V_1 + 0.25V_2 - V_3 = 0 \quad \text{--- (2)}$$

eqⁿ for 8V source

$$V_B - 0 = 8$$

$$V_B = 8 \quad \text{--- (3)}$$


Solving eqⁿ (1) (2) & (3)

$$V_1 = 12V$$


7, 8, 8.5

$$V_2 = 8V$$


$$V_3 = 14V \quad //$$

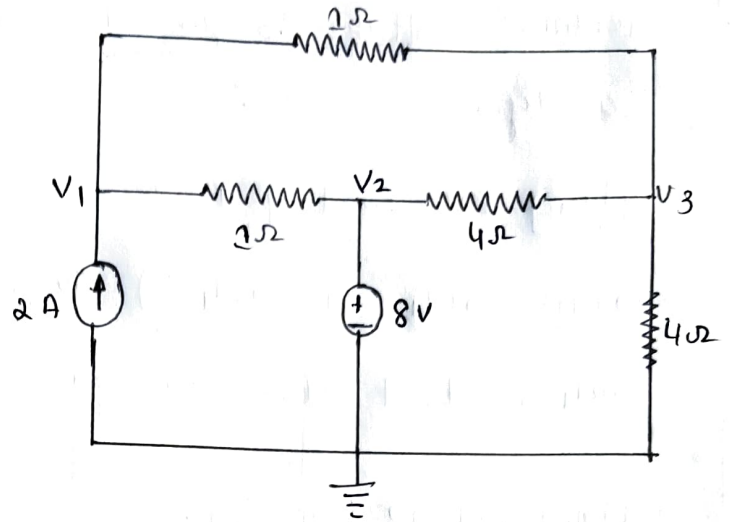

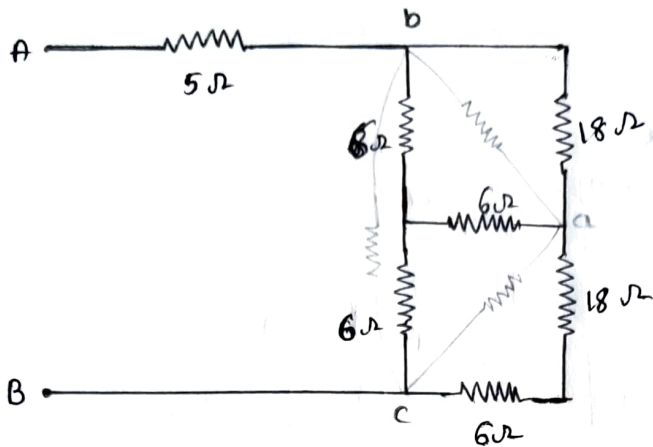C. Determine the equivalent resistance between the terminals AB for circuit shown.




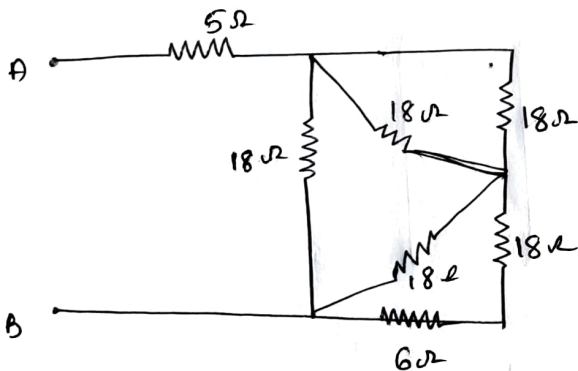Soln Converting star to delta :- $R_{ab} = \frac{6 \times 6 + 6 \times 6 + 6 \times 6}{6} = 18 \Omega$




$18 \parallel 18 \Omega$, $18 \parallel (18 + 6 \Omega)$

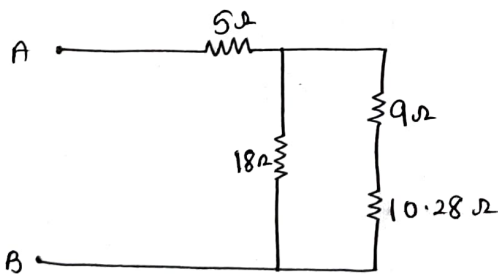
~~$9 \parallel 10.28$~~
 $9 \parallel 10.28$



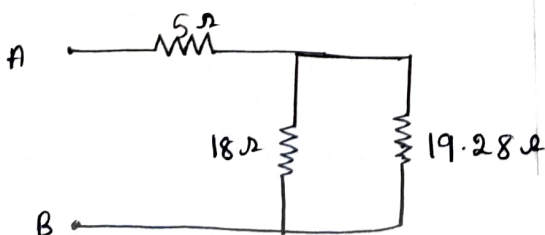9Ω is series with 10.28
 hence $R_{eq} = R_1 + R_2 = 19.28$




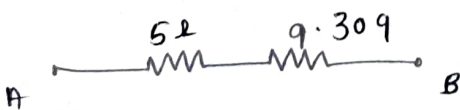$19.28 \parallel 18 \Omega = 9.309 \Omega$



\equiv $5 \Omega + 9.309 \Omega = 14.309 \Omega$

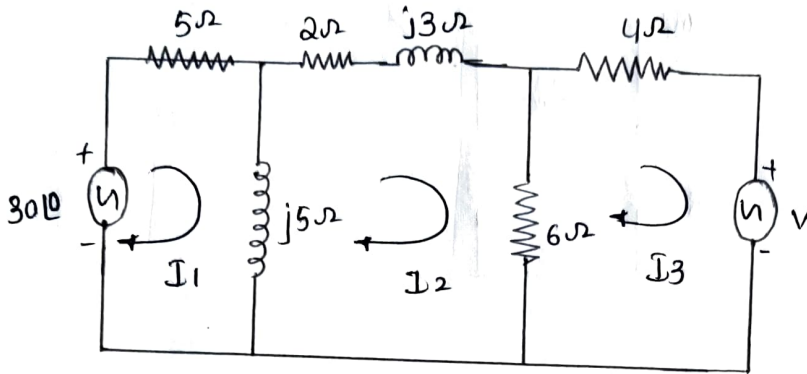2.a. Apply loop a mesh analysis method to find voltage V . Such that current through $(2+j3)\Omega$ resistor is zero for circuit shown in fig.



$$[\bar{Z}] [\bar{I}] = [\bar{V}]$$

$$\begin{bmatrix} (5+j5) & (-j5) & 0 \\ (-j5) & (8+j8) & (-6) \\ 0 & (-6) & (10) \end{bmatrix} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \\ \bar{I}_3 \end{bmatrix} = \begin{bmatrix} 30\angle 0 \\ 0 \\ -V \end{bmatrix}$$

$$\bar{I}_2 = \left| \begin{array}{ccc|c} (5+j5) & (30\angle 0) & (0) & \\ (-j5) & 0 & (-6) & \\ 0 & (-V) & (10) & \end{array} \right|$$

$$\left| \begin{array}{ccc|c} (5+j5) & (-j5) & 0 & \\ (-j5) & (8+j8) & (-6) & \\ 0 & (-6) & (10) & \end{array} \right|$$

$$\frac{(5+j5)(6V_2) - (30\angle 0^\circ)[(10)(-j5)]}{(5+j5)[(8+j8)(10) - 36] - (10j5)[(-j5)(10)]} = 0$$

$$(5+j5)(6V_2) = (30\angle 0^\circ)[(-j5)(10)]$$

$$V_2 = \frac{(30\angle 0^\circ)(-j5)(10)}{6(5+j5)}$$

$$V_2 = \frac{-j250}{5+j5} = -25 - 25i$$

b. Determine the Voltage V_x in the circuit shown in fig.

Soln

KCL for V_1 & V_3

$$1 - 0.125(V_1 - V_2) - 0.5V_3 + 8 = 0$$

$$0.125V_1 - 0.125V_2 - 0.5V_3 = -9 \quad \text{--- (1)}$$

KCL for V_2

$$-8 - 0.2V_2 - 0.125(V_2 - V_1) = 0$$


$$0.125V_1 - 0.325V_2 = 8 \quad \text{--- (2)}$$

Eqⁿ for $2V_x$

$$V_1 - V_3 = 2V_x$$

$$\text{but } V_x = V_2$$
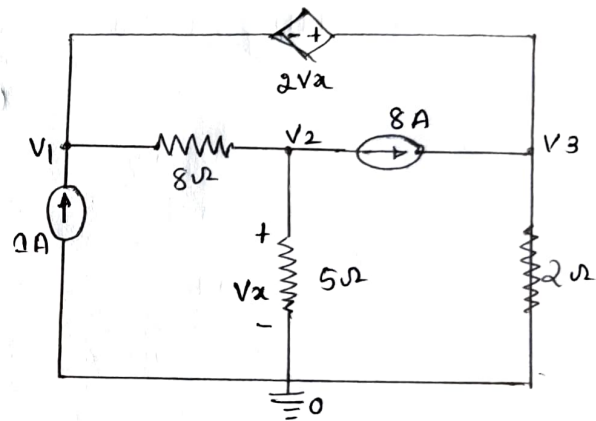
$$V_1 - 2V_2 - V_3 = 0 \quad \text{--- (3)}$$




Solving (1) (2) & (3)

$$V_1 = 42.9V \quad V_2 = 8.1V$$

$$V_3 = 26.7V$$



$$V_x = V_2 = 8.1V$$

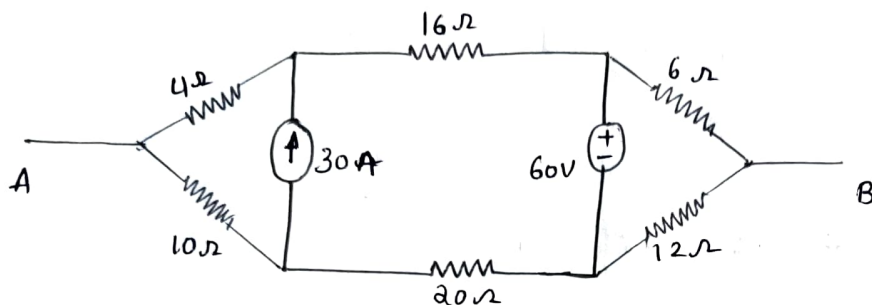c. Apply source transformation and shifting method to reduce the circuit shown in fig to single voltage source in series with resistance.







Solⁿ

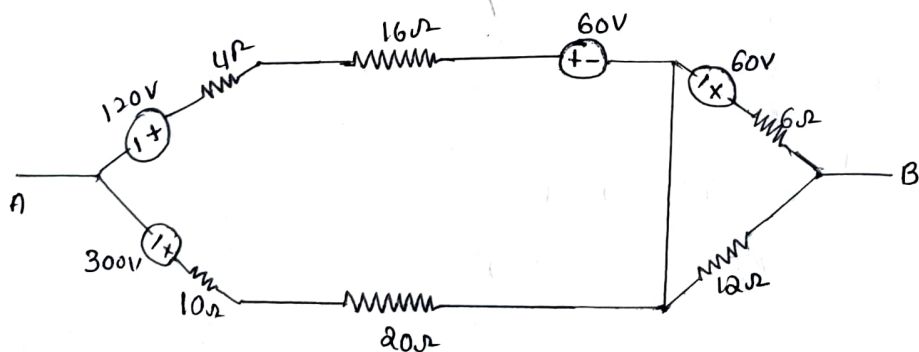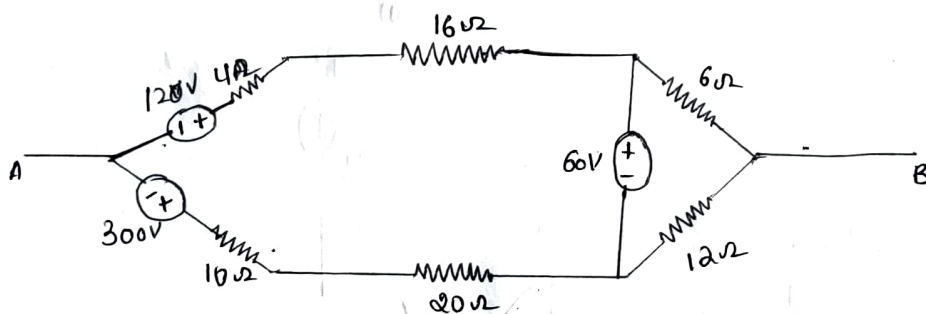converting ideal current source to ideal voltage source.




4Ω series with 16Ω & 20Ω series with 10Ω

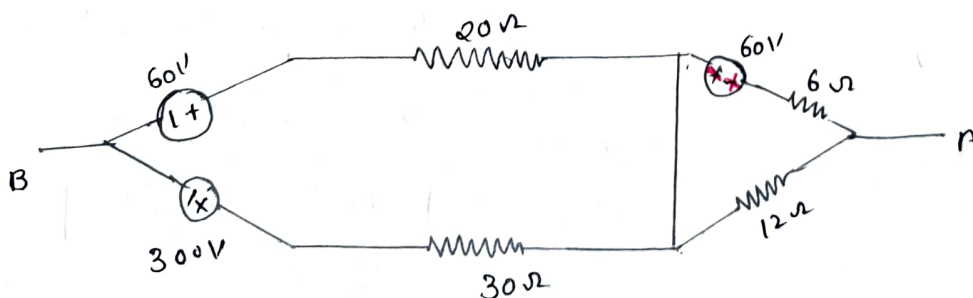

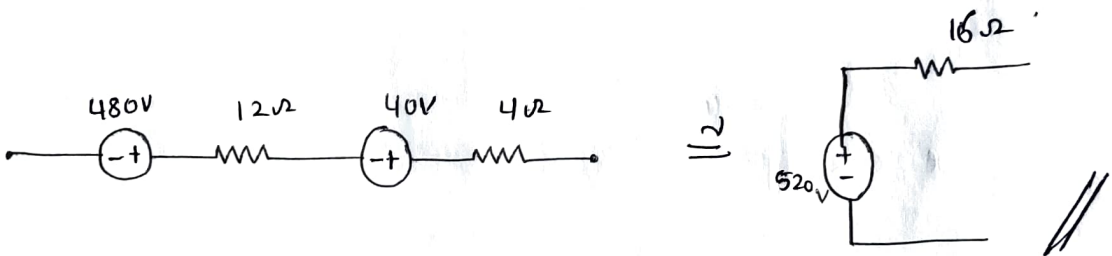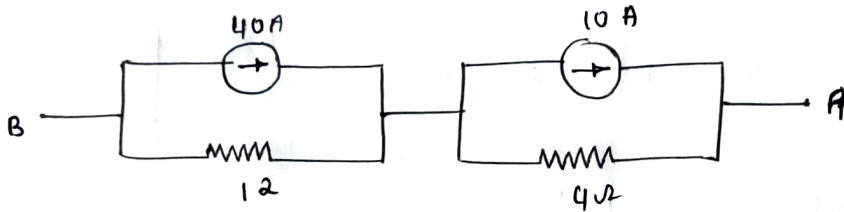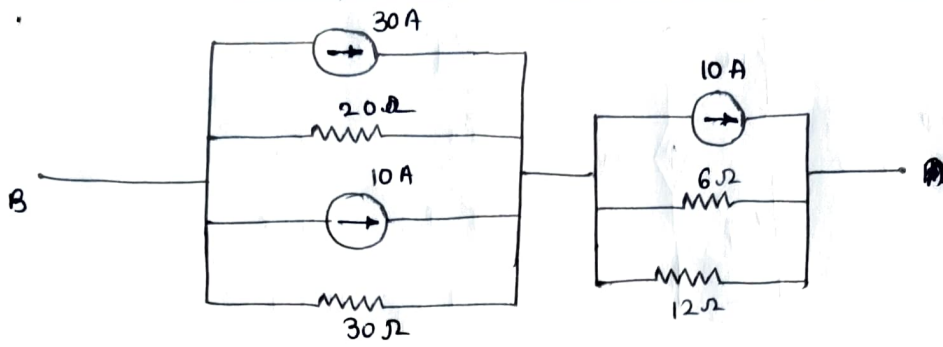

MODULE - 2

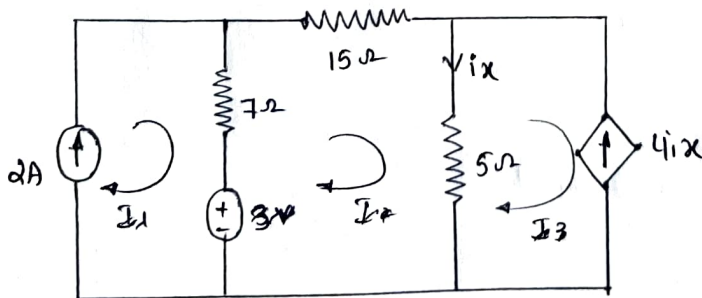3.a. In the circuit shown in fig determine current I_x using Super position theorem.




Soln I_x through 2A source

$$I_1 = 2A$$

$$\text{KVL to } I_2 : -15I_2 - 5(I_2 - I_3) - 7(I_2 - I_1) = 0$$

$$7I_1 - 27I_2 + 5I_3 = 0$$

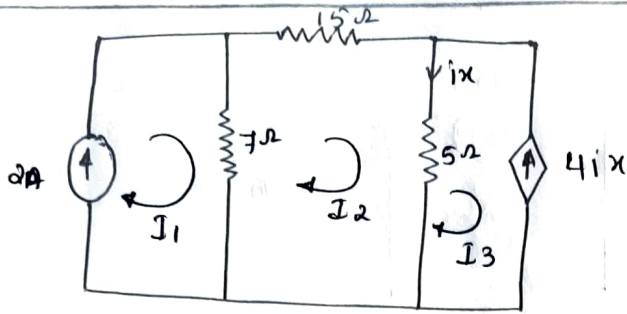

eqⁿ for $4i_x$

$$i_x = I_2 - I_3$$

$$I_3 = -4i_x$$

$$I_3 = -4(I_2 - I_3)$$

$$I_3 = -4I_2 + 4I_3$$

$$-4I_2 + 3I_3 = 0$$

Solving ① ② & ③

$$I_1 = 2A \quad I_2 = 0.59A \quad I_3 = 0.39A.$$

$$I_x = I_2 - I_3$$

$$I_x = 0.2A$$

⑥ I_x through 3V source

KVL to I_1

$$3 - 7I_1 - 15I_1 - 5(I_1 - I_2) = 0$$

$$-27I_1 + 5I_2 + 3 = 0$$

$$3 = 27I_1 - 5I_2 \quad \text{--- ①}$$

eqⁿ for $4i_x$

$$I_2 = -4i_x \quad \text{but } i_x = I_1 - I_2$$


$$I_2 = -4I_1 + 4I_2$$

$$4I_1 - 4I_2 + I_2 = 0$$

$$4I_1 - 3I_2 = 0 \quad \text{--- ②}$$

$$I_1 = 0.147A$$

$$I_2 = 0.196A.$$

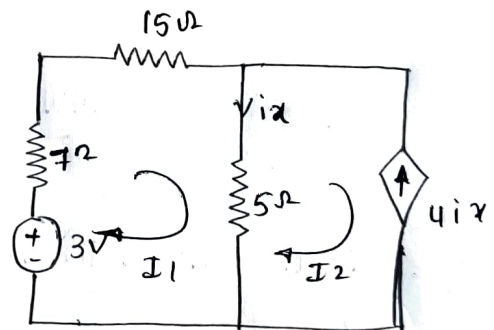


$$\underline{I_x = -0.049A}$$

$$I_x |_{2A + 3V} = I_x |_{2A} + I_x |_{3V}$$

$$0.2 - 0.049$$

$$\boxed{I_x = 0.151A}$$

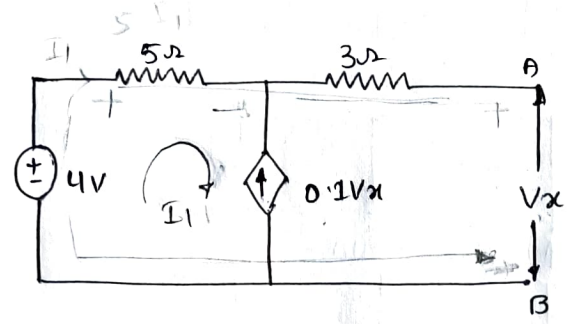B. Determine Thevenin's equivalent of the circuit



solⁿ at finding V_{TH} .

$$I_1 = -0.1V_x \quad \text{--- (1)}$$

$$V_x + 5I_1 - 4 = 0$$

$$V_x + 5(-0.1V_x) - 4 = 0$$

$$0.5V_x = 4$$

$$\boxed{V_x = V_{TH} = 8V}$$


finding R_{TH}

KVL to super mesh

$$-5I_1 - 3I_2 + 4 = 0$$

$$5I_1 + 3I_2 = 4 \quad \text{--- (1)}$$

eqⁿ for current source

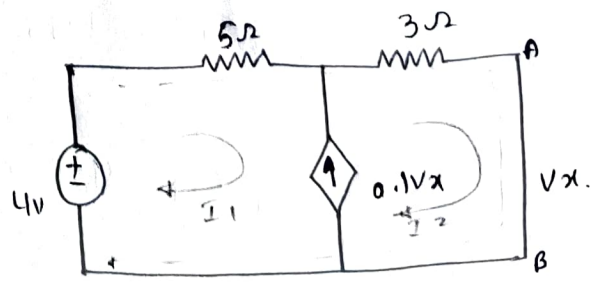


$$I_1 = 0.5 \text{ A}$$


$$I_2 = 0.5 \text{ A}$$

$$I_{NOR} = 0.5 \text{ A}$$
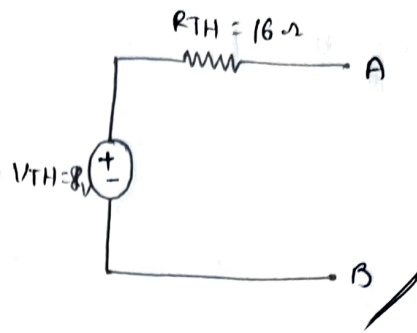
$$R_{TH} = \frac{V_{TH}}{I_{NOR}} = \frac{8}{0.5} = 16 \Omega$$




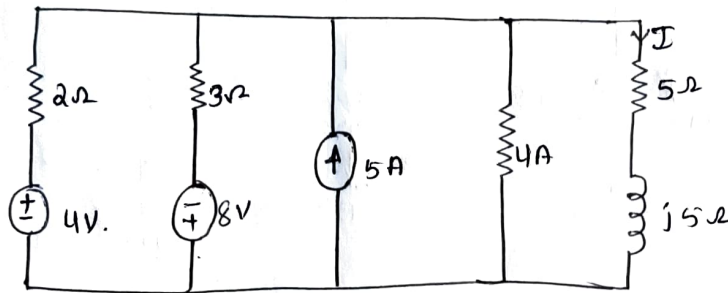c. Use Milliman's theorem to find current I for the circuit shown in fig



Solⁿ:-

Convert PCS to PVS

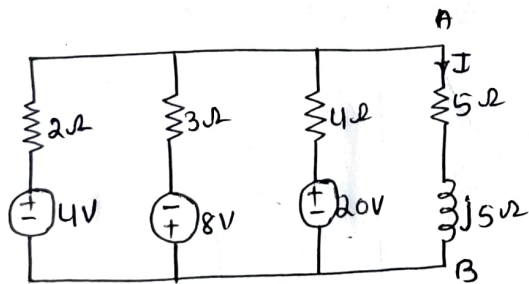


$$V_{eq} = \frac{V_1 G_1 - V_2 G_2 + V_3 G_3}{G_1 + G_2 + G_3}$$

$$= \frac{(4 \times 0.5) - (8 \times 0.33) + (20 \times 0.25)}{0.5 + 0.33 + 0.25}$$

$$V_{eq} = 4.03 \text{ Volts}$$


$$R_{eq} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{0.5 + 0.33 + 0.25}$$

$$R_{eq} = 0.925 \Omega$$

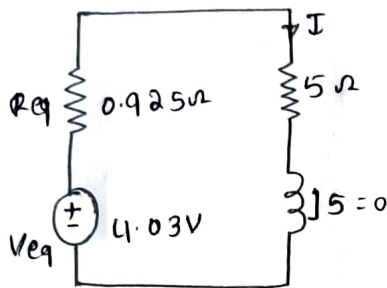

It is DC circuit hence effect of inductance is zero


$$\text{Hence } I_5 = 0$$

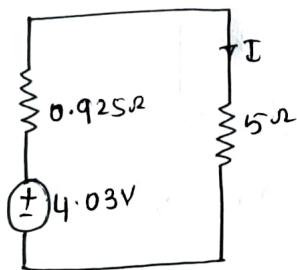

$$I = \frac{4.03}{(0.925 + 5)}$$

$$I = \underline{\underline{0.68 \text{ Amps}}}$$

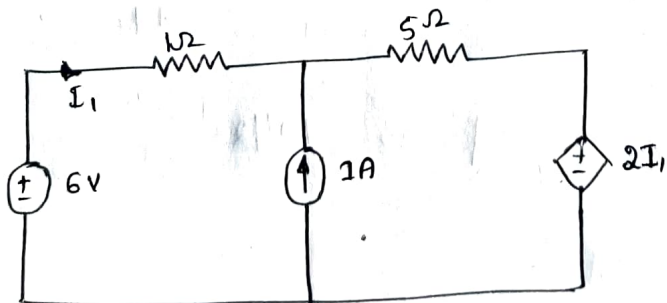447 Determine Current through 1Ω resistor. Using Norton's theorem for circuit shown.




finding I_{NOR}

KVL to supermesh

$$2I_1 + 5I_b - 6 = 0$$

$$\text{but } I_1 = I_a$$

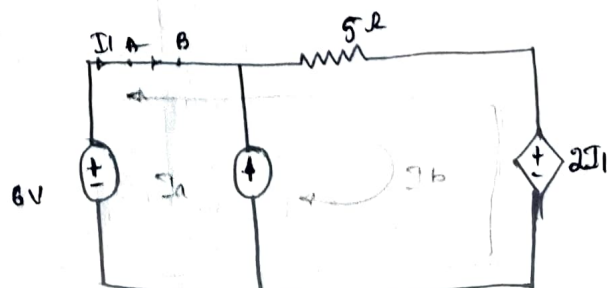

$$2I_a + 5I_b = 6 = 0$$


$$5I_b = 6 \quad \text{--- (1)}$$

$$I_b - I_a = 1$$

$$I_a = 0.142 \quad I_b = 1.143 \text{ A}$$

$$I_{NOR} = 0.142$$

b) (b) finding R_{NOR}

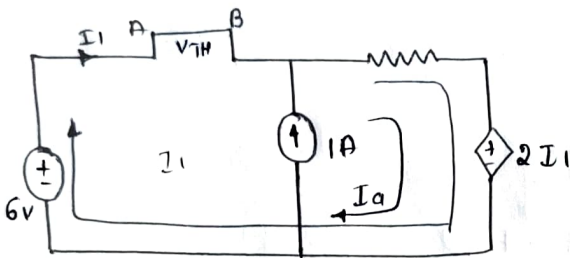

$$I_a = 1 \text{ A}$$

KVL to supermesh


$$-5I_a - 2I_1 + 6 - V_{TH} = 0$$

$$V_{TH} = 5I_a - 2I_1 - 6$$

$$V_{TH} = 1 \text{ V}$$

Current through 1Ω resistor is

I_1 becomes zero because of o.c

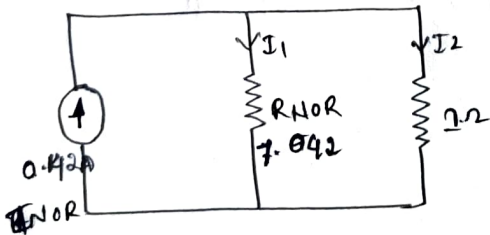

$$R_{NOR} = \frac{V_{TH}}{I_{NOR}} = \frac{1}{0.142}$$


$$R_{NOR} = 7.042 \Omega$$

by current dividing rule

$$I_2 = \frac{R_{NOR}}{1 + R_{NOR}} \times I_{NOR} = \frac{7.042}{8.042} \times 0.142$$

current through 1Ω resistor is 0.12 A

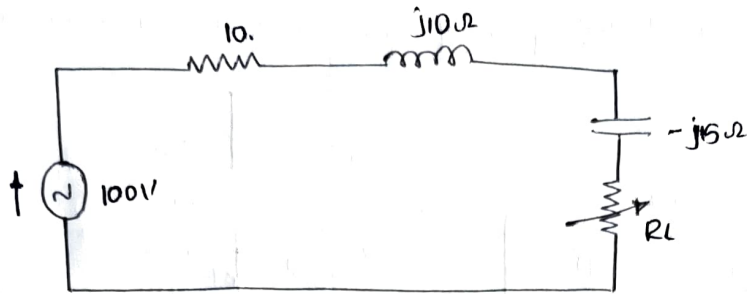
b. Determine the load resistance R_L to receive maximum power from Source. Also find maximum power delivered to the load in the circuit



i. $Z_{TH} = 10 - j5$

$|Z_{TH}| = \sqrt{10^2 + 5^2} = \sqrt{125}$


$R_L = 11.18 \Omega$

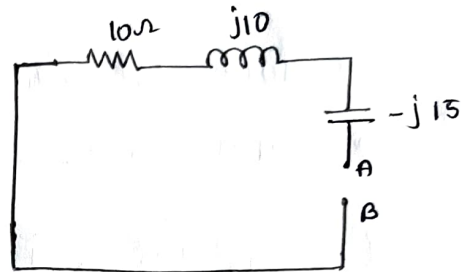

ii. $\bar{I} = \frac{V}{Z} = \frac{100 \angle 0}{21.18 - j5} = 4.47 + 1.05j$


$|I| = \sqrt{4.47^2 + 1.05^2}$

$|I| = 4.598 A$

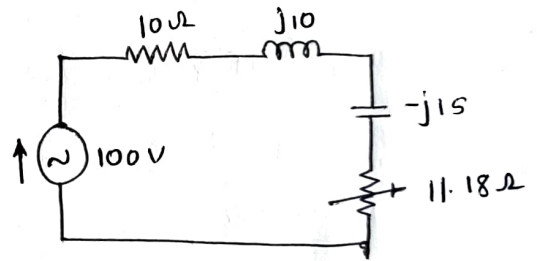

$P = |I|^2 R_L = 236.4 W. \approx 236.36 W.$

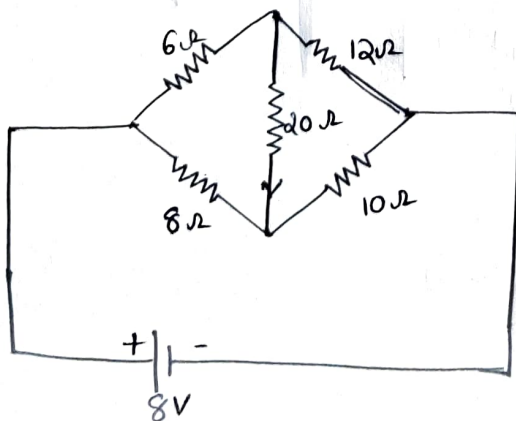c) state and verify reciprocity theorem for the circuit shown fig.



Solⁿ: Statement :- The theorem states that In any linear bilater
 -al n/w the ratio of Excitation to response remains unalter
 if the position of excitation & response are interchange

KVL to I_1, I_2 & I_3

$$-6I_1 - 20(I_1 - I_2) - 8(I_1 - I_3) = 0$$

$$-34I_1 + 20I_2 + 8I_3 = 0 \quad \text{--- (1)}$$

$$-12I_2 - 10(I_2 - I_3) - 20(I_2 - I_1) = 0$$

$$20I_1 - 40I_2 + 10I_3 = 0 \quad \text{--- (2)}$$

$$-8(I_3 - I_1) - 10(I_3 - I_2) + 8 = 0$$

$$8I_1 + 10I_2 - 18I_3 = -8$$

Solving I_1 & I_2 & I_3

$$I = I_1 - I_2$$

$$I = 0.03A$$

By interchanging the excitation

$$-6I_1 - 20(I_1 - I_2) + 8 - 8(I_1 - I_3) = 0$$



$$-34I_1 + 20I_2 + 8I_3 = -8 \quad \text{--- (1)}$$

$$-12I_2 - 10(I_2 - I_3) - 8 - 20(I_2 - I_1) = 0$$

$$20I_1 - 42I_2 + 10I_3 = 8 \quad \text{--- (2)}$$

$$-8(I_3 - I_1) - 10(I_3 - I_2) = 0$$
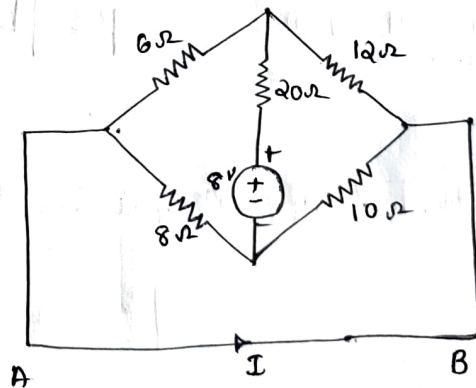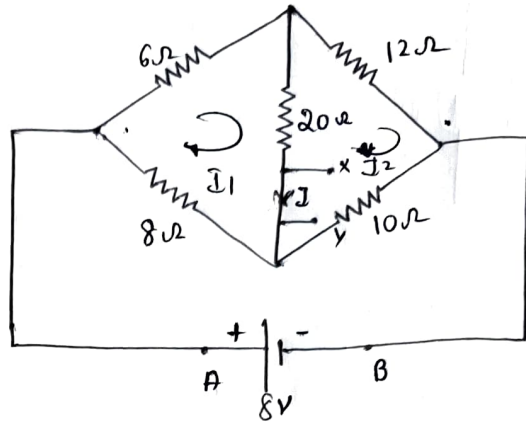
$$8I_1 + 10I_2 - 18I_3 = 0 \quad \text{--- (3)}$$



$$I_1 = 0.1875A$$

$$I_2 = -0.09375A$$

$$I_3 = 0.03125A$$

$$I = 0.031A$$


Hence reciprocity theorem is proved.

MODULE - 3

5a. Derive an expression for the resonance frequency of a resonant circuit consisting of R_L, X_L in parallel with R_C, X_C .

→ Input impedance $Y = Y_1 + Y_2$
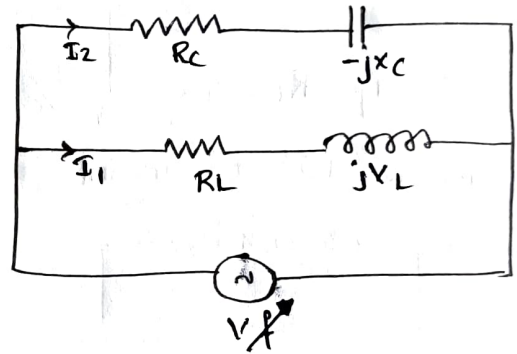
$$Y_1 = \frac{1}{R_L + jX_L} \times \frac{R_L - jX_L}{R_L - jX_L} = \frac{R_L}{R_L^2 + X_L^2} - \frac{jX_L}{R_L^2 + X_L^2}$$



$$Y_2 = \frac{1}{R_C - jX_C} \times \frac{R_C + jX_C}{R_C + jX_C} = \frac{R_C}{R_C^2 + X_C^2} + \frac{jX_C}{R_C^2 + X_C^2}$$

$$Y = \left(\frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} \right) + j \left(\frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} \right)$$

Equating imaginary part to zero.

$$\frac{X_C}{R_C^2 + X_C^2} = \frac{X_L}{R_L^2 + X_L^2}$$

$$\frac{1/\omega C}{R_C^2 + \left(\frac{1}{\omega C}\right)^2} = \frac{\omega L}{R_L^2 + (\omega L)^2}$$

$$R_L^2 + \omega^2 L^2$$

$$R_L^2 \frac{1}{\omega C} + \frac{\omega L^2}{C} = R_C^2 \omega L + \frac{L}{\omega C^2}$$

$$\frac{R_L^2 + \omega^2 L^2}{\omega C} = \frac{R_C^2 \omega^2 L C^2 + L}{\omega C^2}$$

$$R_L^2 C + \omega^2 L^2 C = R_C^2 \omega^2 L C^2 + L$$


$$\omega = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L - \frac{L}{C}}{R_C - \frac{L}{C}}}$$

If $R_L = R_C = \sqrt{\frac{L}{C}}$ then resonant frequency of the circuit is resonant for all the frequency at resonance I become minimum.

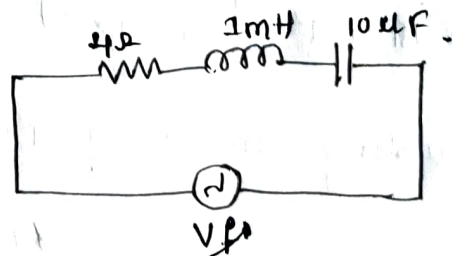- b. An impedance coil having a resistance of 4Ω & an inductance of 1mH connected in series with $10\mu\text{F}$ capacitor. Determine resonant frequency, impedance at resonance, half power frequency, Q of the circuit and bandwidth.

→ Resonant frequency $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\omega_0 = \frac{1}{\sqrt{1 \times 10^{-6}}} = 316.2 \text{ rad/sec.}$$



$$\omega_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = \frac{-4}{2 \times 1} + \sqrt{\left(\frac{4}{2 \times 1}\right)^2 + \frac{1}{1 \times 10^{-6}}}$$

$$= -2 + 316.2$$

$$\omega_1 = 314.2 \text{ rad/sec.}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = \frac{4}{2 \times 1} + \sqrt{\left(\frac{4}{2 \times 1}\right)^2 + \frac{1}{1 \times 10 \mu}} = 318.2 \text{ rad/sec}$$

$$\text{Bandwidth} = \frac{R}{L} = \frac{4}{1} = 4$$



$$\text{Q.F.} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{4} \sqrt{\frac{1}{10 \mu}} = 316.4 \text{ rad/sec.}$$

c. For circuit shown in fig. the switch is moved from position 1 to 2 at $t=0$. The steady state has been reached before switching.

Determine ; i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0$.


→ When $t < 0$

at $t(0^-)$

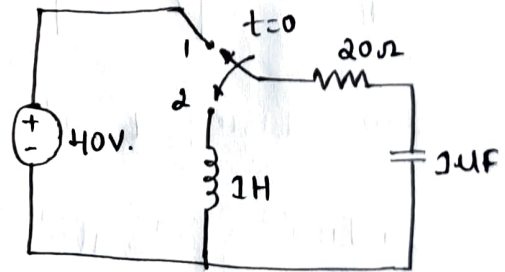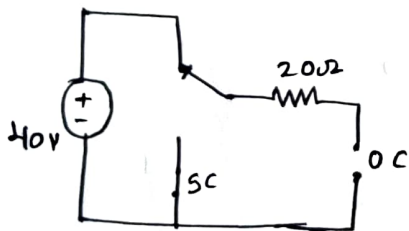


$$i_L(0^-) = 0 \text{ Amps.}$$

at $t(0^+)$

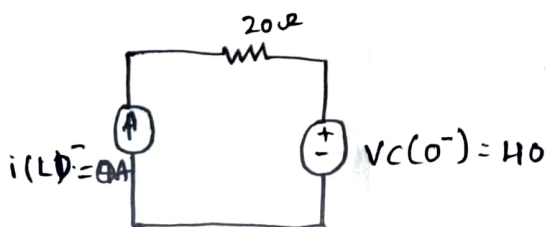


|||

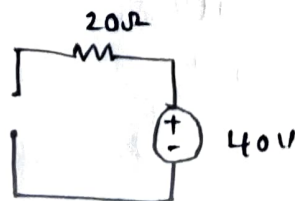

$$i(0^+) = 0 \text{ Amps.}$$

at $t > 0$

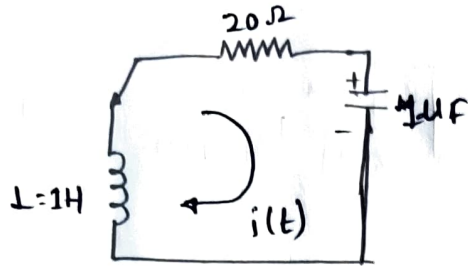

KVL eqⁿ 1.

$$-20i(t) - \left[\frac{1}{C} \int_0^t i(t) dt + V_C(0^-) \right] + L \frac{di(t)}{dt} = 0$$

→ ①

Substitute $t = 0^+$

$$-20i(0^+) - [40] + 1 \frac{di}{dt}(0^+) = 0$$

$$0 - 40 + 1 \frac{di(0^+)}{dt} = 0$$

$$\frac{di(0^+)}{dt} = 40 \text{ Amp/sec.}$$

Differentiate eqⁿ ① again.

$$-20 \frac{di(t)}{dt} - \left[\frac{1}{C} i(t) \right] + L \frac{d^2i(t)}{dt^2} = 0$$


Substituting $t = 0^+$

$$-20 \frac{di(0^+)}{dt} - \left[\frac{1}{1\mu} i(0^+) \right] + 1 \frac{d^2i(0^+)}{dt^2} = 0$$

$$-20(40) + 1 \frac{d^2i(0^+)}{dt^2} = 0$$

$$\frac{d^2i(0^+)}{dt^2} = 800 \text{ Amp/sec}^2$$

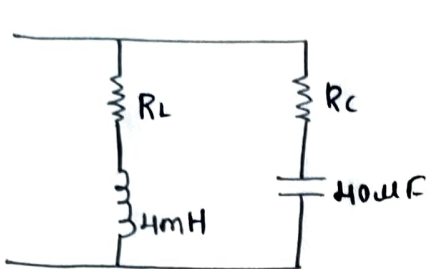
6. Determine R_L and R_C for which the circuit shown in fig resonates at all frequencies.



$$R_L = R_C = \sqrt{\frac{L}{C}} = \sqrt{\frac{4 \times 10^{-3}}{40 \times 10^{-6}}}$$

$$R_L = R_C = 10$$

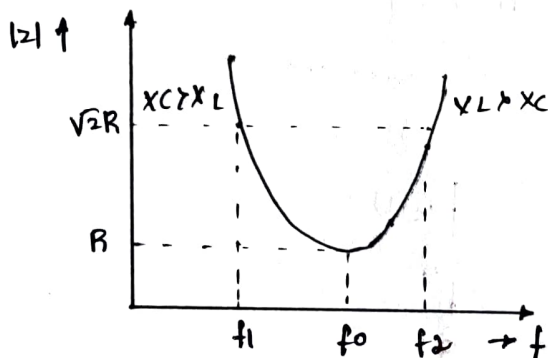- b. Show that in series RLC circuit, the resonant frequency $f_0 = \sqrt{f_1 f_2}$.



at half power frequencies $|Z_1| = |Z_2|$

$$\sqrt{R^2 + (X_{C1} - X_{L1})^2} = \sqrt{R^2 + (X_{L2} - X_{C2})^2}$$

$$X_{C1} - X_{L1} = X_{L2} - X_{C2}$$

$$\frac{1}{\omega_1 C} - \omega_1 L = \omega_2 L - \frac{1}{\omega_2 C}$$

$$\frac{1}{\omega_1 C} + \frac{1}{\omega_2 C} = \omega_2 L + \omega_1 L$$

$$\frac{1}{C} \left[\frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right] = L (\omega_1 + \omega_2)$$

$$\omega_1 \omega_2 = \frac{1}{LC}$$


$$\omega_1 \omega_2 = \omega_0^2$$

$$2\pi f_1 \times 2\pi f_2 = 2\pi f_0^2$$

$$f_0^2 = f_1 f_2$$


$$f_0 = \sqrt{f_1 \times f_2} //$$

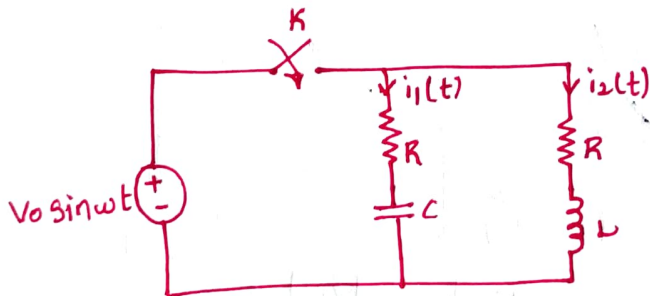6a In circuit shown in fig the switch K is closed at $t=0$
 Calculate $\frac{di_1(0^+)}{dt}$ and $\frac{di_2(0^+)}{dt}$




→ draw circuit at $t=0^-$ $V_C(0^-) = 0V$ $I_L(0^-) = 0A$


Circuit at $t=0^+$

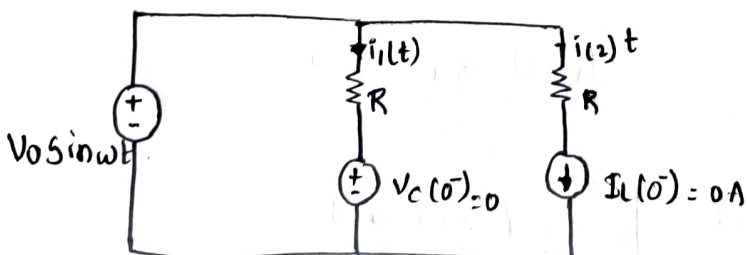

22

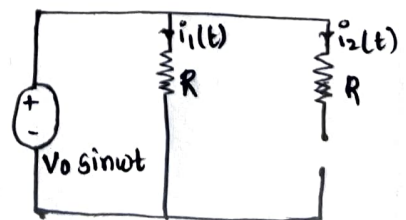
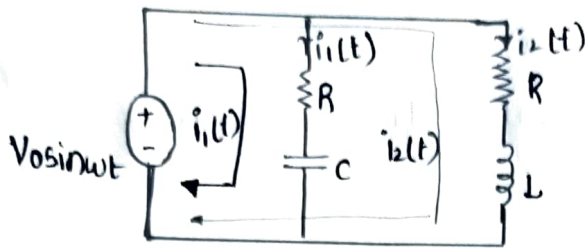
$$i_2(0^+) = 0A \quad i_1(0^+) = \frac{V_0 \sin \omega t}{R}$$



KVL to $i_1(t)$

$$R i_1(t) + \frac{1}{C} \int_{0^-}^t i_1(t) dt + V(0^-) = V_0 \sin \omega t$$

Differentiating.

$$R \frac{d i_1(t)}{dt} + \frac{1}{C} i_1(t) = V_0 \cos \omega t$$

KVL to $i_2(t)$

$$-R i_2(t) - L \frac{d i_2}{dt} + V_0 \sin \omega t = 0$$

Substitute 0^+

$$L \frac{d i_2(t)}{dt} = V_0 \sin \omega t$$

$$\boxed{\frac{d i_2(t)}{dt} = \frac{V_0 \sin \omega t}{L}}$$

77
a. State and Prove initial and final Value theorem in Laplace Transform.

→ Initial Value Theorem :- states that the initial value of the function $f(t)$ can be found as $f(0) = \lim_{s \rightarrow \infty} sF(s)$

Proof :- W.K.T $\text{LT} \left[\frac{df(t)}{dt} \right] = sF(s) - f(0)$

$$sF(s) = \int_0^{\infty} \frac{df(t)}{dt} e^{-st} dt + f(0)$$

$$\lim_{s \rightarrow \infty} sF(s) = \int_0^{\infty} \frac{df(t)}{dt} dt$$

$$\boxed{f(0) = \lim_{s \rightarrow \infty} sF(s)}$$

Final Value Theorem :- states that the final value of the function $f(t)$ can be found as $f(\infty) = \lim_{s \rightarrow 0} sF(s)$

Proof! $sF(s) = \int_0^{\infty} \frac{df(t)}{dt} dt + f(0)$

$$= f(t) \Big|_0^{\infty} + f(0)$$

$$= f(\infty) - f(0) + f(0)$$


$$= f(\infty)$$

$$\boxed{f(\infty) = \lim_{s \rightarrow 0} sF(s)}$$

b) Find the Laplace Transform of Unit step function.

→ for $t < 0$ $u(t) = 0$

for $t > 0$ $u(t) = 1$

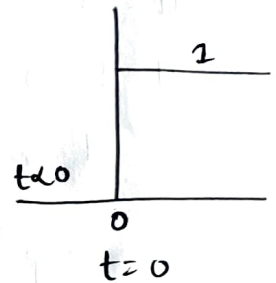

$$F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

$$= \int_0^{\infty} u(t) e^{-st} dt$$

WKT $u(t) = 1$ for $t=0$ to ∞

$$= \int_0^{\infty} 1 e^{-st} dt$$

$$= \left[\frac{e^{-st}}{-s} \right]_0^{\infty}$$

$$= -\frac{1}{s} [e^{-\infty} - e^0]$$

$$= -\frac{1}{s} [0 - 1]$$

$$= \frac{1}{s}$$

Hence Laplace Transform of unit step function is $\frac{1}{s}$.

8)

a. State and Prove shifting theorem.

→ Statement: - If $F(s)$ is LT of $f(t)$ then $\mathcal{L}\{f(t-t_0)\} = e^{-st_0} F(s)$

Change

Proof: - $\mathcal{L}\{f(t-t_0)\} = \int_0^{\infty} f(t-t_0) e^{-st} dt$

change the variable

$$\text{let } t-t_0 = z \quad \text{Then } t = z+t_0$$

$$dt = dz$$

$$\text{at } t=0 \quad z = -t_0$$

$$t = \infty \quad z = \infty$$

$$= \int_{-t_0}^{\infty} f(z) e^{-s(z+t_0)} dz$$

$$= \int_{-t_0}^0 f(z) e^{-s(z+t_0)} dz + \int_0^{\infty} f(z) e^{-s(z+t_0)} dz$$

$$\mathcal{L}\{f(t-t_0)\} = e^{-st_0} \int_0^{\infty} f(z) e^{-zs} dz$$

$$\underline{\underline{\mathcal{L}\{f(t-t_0)\} = e^{-st_0} F(s)}}$$

Proved.

b) Verify initial value theorem, given $f(t) = 10e^{5t}$

$$f(t) = 10e^{5t}$$

$$f(0) = 10e^{5 \times 0} = 10e^0 = 10$$

Verifying $f(0) = \lim_{s \rightarrow \infty} sF(s)$


$$F(s) = 10 \frac{1}{s-5}$$

$$sF(s) = \frac{10s}{s-5} = \frac{10s}{s(1-5/s)} = \frac{10}{1-5/s} \quad s \rightarrow \infty$$

$$f(0) = \lim_{s \rightarrow \infty} sF(s)$$

$$\boxed{f(0) = 10} \quad \text{Verified.}$$

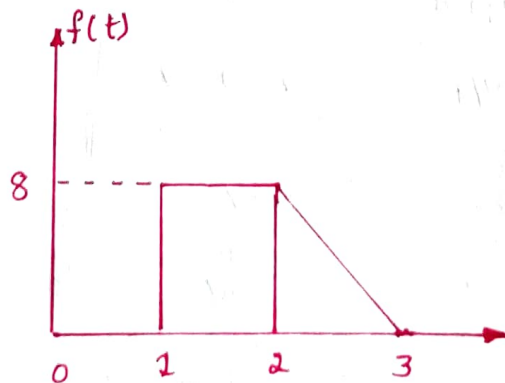c) Find the Laplace transform of the fig shown.



$$f_1(t) = +8u(t-1)$$

$$f_2(t) = -16r(t-2)$$

$$f_3(t) = 8r(t+3)$$


$$f(t) = f_1(t) + f_2(t) + f_3(t) = 8u(t-1) - 16r(t-2) + 8r(t+3)$$

taking Laplace Transform of $f(t)$

$$\mathcal{L}\{f(t)\} = \frac{8e^{-s}}{s} - \frac{16e^{-2s}}{s^2} + \frac{8e^{2s}}{s^2}$$

7c)

Find the Laplace Transform of fig show.

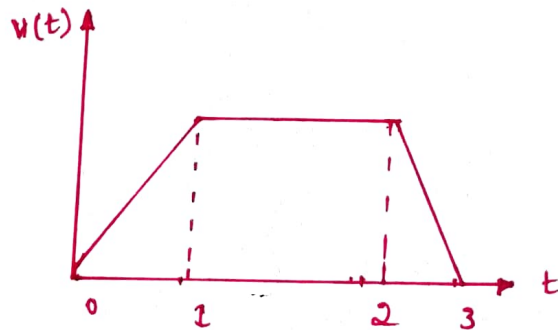

	slope before	slope after	change	
0	0	$V/1$	$V - 0 = V$	$Vr(t)$
1	$V/1$	0	$0 - V = -V$	$-Vr(t-1)$
2	0	$-V$	$-V$	$-Vr(t-2)$
3	$-V$	0	$0 - (-V) = V$	$Vr(t-3)$

$$V(t) = Vr(t) - Vr(t-1) - Vr(t-2) + Vr(t-3)$$

Taking Laplace transform.

$$LT[V(t)] = \frac{V}{s^2} - \frac{V e^{-s}}{s^2} - \frac{V e^{-2s}}{s^2} + \frac{e^{-3s}}{s^2}$$

MODULE - 5


9] a) Three impedances $Z_1 = 20 \angle 30^\circ \Omega$, $Z_2 = 40 \angle 60^\circ \Omega$ and $Z_3 = 10 \angle -90^\circ \Omega$ are delta connected to 400V, 3 phase systems as shown in fig. Determine the i) Phase current ii) Line current.

→ Phase current

$$\bar{V}_{RY} = 400 \angle 0^\circ \text{ V}$$

$$\bar{V}_{YB} = 400 \angle -120^\circ \text{ V}$$
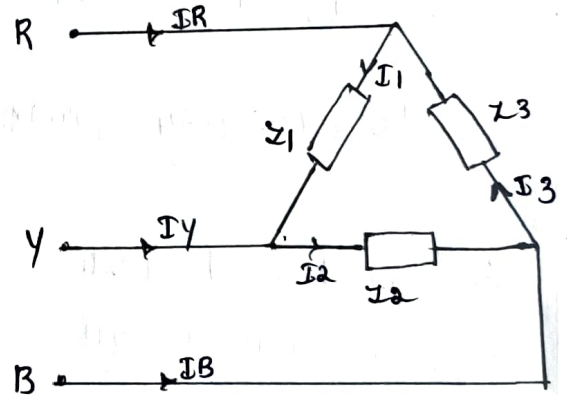
$$\bar{V}_{BR} = 400 \angle -240^\circ \text{ V}$$



$$\bar{I}_1 = \frac{\bar{V}_{RY}}{Z_1} = \frac{(400 \angle 0^\circ)}{(20 \angle 30^\circ)} = 20 \angle -30^\circ \text{ or } 17.32 - j10 \text{ A}$$

$$\bar{I}_2 = \frac{\bar{V}_{YB}}{Z_2} = \frac{(400 \angle -120^\circ)}{(40 \angle 60^\circ)} = -10 + j0 \text{ A}$$

$$\bar{I}_3 = \frac{\bar{V}_{BR}}{Z_3} = \frac{(400 \angle -240^\circ)}{(10 \angle -90^\circ)} = -34.64 - j20 \text{ A}$$

Line current :-

KCL

$$I_R - I_1 + I_3 = 0$$

$$I_R = I_1 - I_3 = (17.32 - j10) - (-34.64 - j20)$$

$$I_R = (51.96 - j10) \text{ A}$$

$$I_Y + I_1 - I_2 = 0$$

$$I_Y = I_2 - I_1 = (-10 + j0) - (17.32 - j10)$$

$$I_Y = (-17.32 + j10) \text{ A}$$

$$I_B + I_2 - I_3 = 0$$

$$I_B = I_3 - I_2 = (-34.64 - j20) - (-10 + j0)$$

$$I_B = (-24.64 - j20) \text{ A}$$

100)

An Unbalanced 4 wire star connected, star connected load has a balanced voltage of 400V the loads are

$$Z_1 = (4 + j8) \Omega$$

$$Z_2 = (3 + j4) \Omega$$

$$Z_3 = (15 + j20) \Omega \text{ calculate}$$


the line & Neutral current.

→

$$V_{RN} = \frac{400}{\sqrt{3}} = 230.9 \text{ V}$$

$$V_{BN} = 230.9 \angle -120^\circ \text{ V}$$
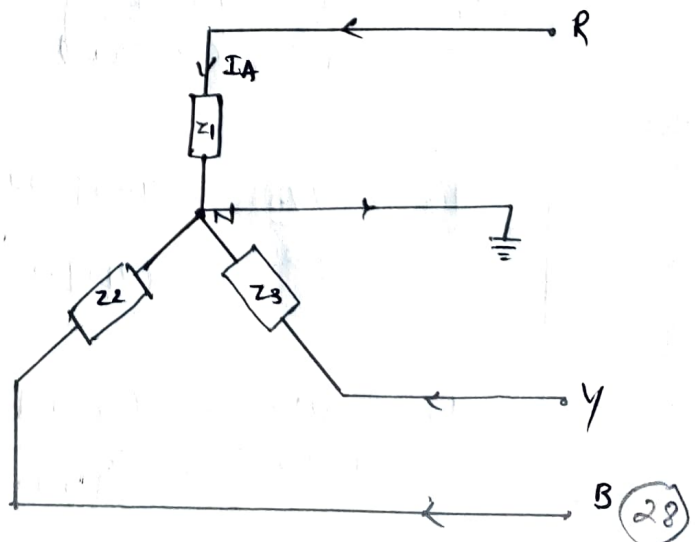
$$V_{YN} = 230.9 \angle -240^\circ \text{ V}$$



$$V_{RY} = 400 \angle 30$$

$$V_{YB} = 400 \angle -90$$

$$V_{BR} = 400 \angle -240$$

Line current

$$I_A = \frac{V_{AN}}{Z_1} = \frac{(230 \cdot 9 \angle 0)}{(4 + j8)} = (11.5 - j23.09) \text{ A}$$

$$I_B = \frac{V_{YN}}{Z_2} = \frac{(230 \cdot 9 \angle -120)}{(3 + j4)} = (-45.85 - j5.52) \text{ A}$$

$$I_C = \frac{V_{BN}}{Z_3} = \frac{(230 \cdot 9 \angle -240)}{(15 + j20)} = (3.63 + j8.49) \text{ A}$$

10 c) Define H parameter with necessary equation:

→ Parameter relating H variable called H Parameter. The term hybrid was chosen because of the mixture for variable V & I in each equation.

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$


$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$


$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

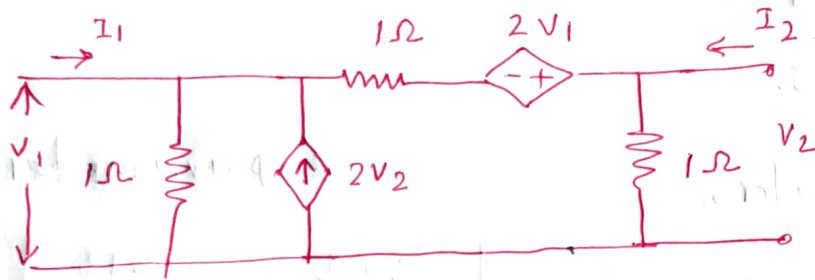9b. Determine Y-Parameters for the circuit shown.




Solⁿ: A. Finding Y_{11} & Y_{21} .
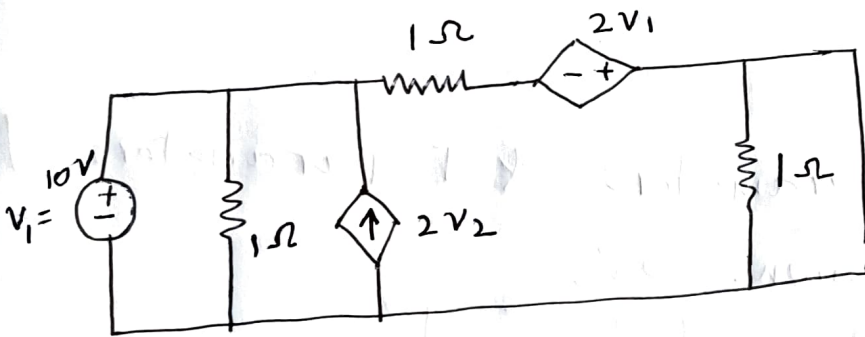
$$Y_{11} = \frac{I_1}{V_1}, \quad Y_{21} = \frac{I_2}{V_1} \quad \text{with } V_2 = 0.$$



$$\therefore Y_{11} = \frac{+40}{10} = +4 \text{ S} \quad Y_{12} = \frac{-30}{10} = -3 \text{ S}$$

B. Finding Y_{12} & Y_{22} .

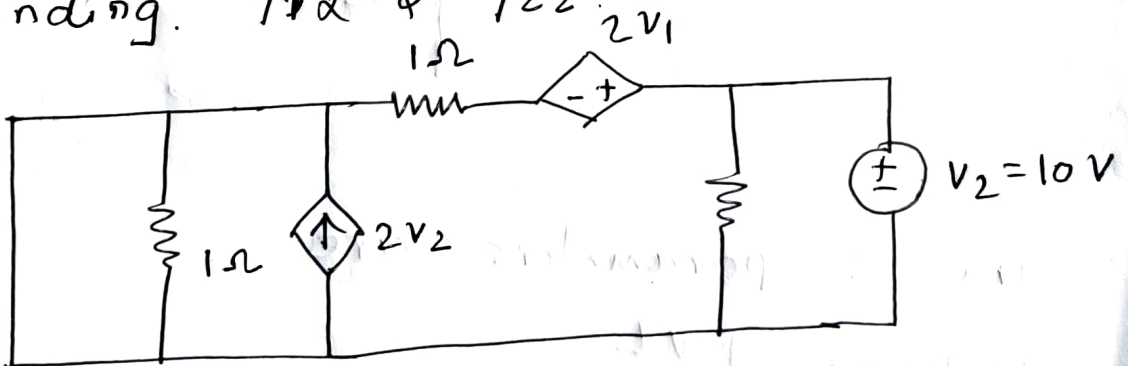

$$Y_{12} = \frac{I_1}{V_2} = \frac{30}{10} = 3 \text{ S} \quad Y_{22} = \frac{20}{10} = 2 \text{ S}$$

9c Express Y parameters in terms of Z parameters.


Solⁿ

Y parameters

Z parameters

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & -\frac{Z_{12}}{\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix}$$

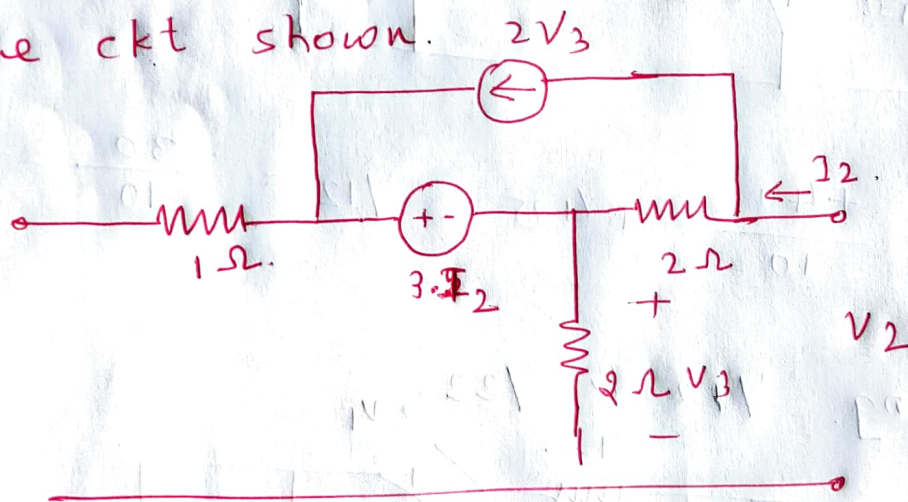10b. Find Z -parameters & T parameters for the ckt shown.



Solⁿ

The Z -parameters are

Applying KVL

$$V_1 = (I_1 + 2V_3) \times 1 + 2(I_1 + I_2) \quad \text{--- (1)}$$

$$V_2 = (I_2 - 2V_3) \times 3 + 2(I_1 + I_2) \quad \text{--- (2)}$$

$$V_3 = 2(I_1 + I_2) \quad \text{---}$$

Putting values of V_3 in (1) & (2)

$$V_1 = I_1 + 4I_1 + 4I_2 + 2I_1 + 2I_2$$

$$V_1 = 7I_1 + 6I_2$$

$$V_2 = (I_2 - 4I_1 - 9I_2) \times 3 + 2I_1 + 2I_2$$

$$V_2 = -12I_1 - 9I_2 + 2I_1 + 2I_2$$

$$V_2 = -10I_1 - 7I_2$$

$$\therefore z_{11} = 7, \quad z_{12} = 6 \Omega, \quad z_{21} = -10, \quad z_{22} = -7.$$

$$\therefore A = \frac{z_{11}}{z_{21}} = \frac{7}{-10} = -0.7$$

$$B = \frac{|z_{12}|}{z_{21}} = 0.6$$

$$C = \frac{1}{z_{21}} = \frac{1}{-10} = -0.1$$

$$D = \frac{z_{22}}{z_{11}} = \frac{-7}{7} = -1.$$

Uttam

~~Uttam~~

Dean, Academics.

Dr. Uttam
Satpute