

Model Question Paper-I/II with effect from 2022-23 (CBCS Scheme)

USN

--	--	--	--	--	--	--

First/Second Semester B.E. Degree Examination
Introduction to Electronics Engineering

TIME: 03 Hours**Max. Marks: 100**

Note: 01. Answer any **FIVE** full questions, choosing at least **ONE** question from each **MODULE**.

Module -1			*Bloom's Taxonomy Level	Marks
Q.01	a	What is a regulated power supply? With neat block diagram Summarize the working of DC power supply. Also mention the principal components used in each block.		L2 6M
	b	Discuss the need of filter circuit. With circuit diagram and waveforms brief out the operation of smoothing filter for full wave rectifiers.	L2 7M	
	c	With neat diagram Summarize working principle of the voltage divider bias CE amplifier with feedback.	L2 7M	
OR				
Q.02	a	A 5V zener diode has a maximum rated power dissipation of 500 mW. If the diode is to be used in a simple regulator circuit to supply a regulated 5V to a load having a resistance of $500\ \Omega$, determine a suitable value of series resistor for operation in conjunction with a supply of 9V.	L3 7M	
	b	What is voltage multiplier and mention its applications? With circuit diagram brief out the operation of voltage Tripler circuit.	L2 7M	
	c	Illustrate how BJT is used as a switch.	L4 6M	
Module-2				
Q. 03	a	Sketch the circuits of each of the following based on use of Operational Amplifier a) Differentiator. b) Integrator .	L1 6M	
	b	Write a note on Ideal characteristics of Op-Amp	L1 7M	
	c	Explain the operation of Single stage Astable Oscillator with its circuit diagram.	L2 7M	
OR				
Q.04	a	Mention the condition of sustained oscillations. Determine the frequency of oscillations of a three stage ladder network in which $C=10nF$ and $R=10K\Omega$.	L2 6M	
	b	With a neat circuit diagram and Waveforms, describe the operation of Crystal controlled Oscillator.	L2 7M	
	c	With a neat circuit diagram explain single stage Multivibrators.	L2 7M	
Module-3				
Q. 05	a	With the help of truth table explain the operation of Full Adder with its circuit diagram and reduce the expression for Sum and carry.	L2 7M	
	b	Mention the different theorems and Postulates of Boolean Algebra and Prove each of them with truth table.	L1 7M	
	c	Subtract using (r-1)'s compliment method a) $4456_{(10)} - 34234_{(10)}$ Subtract using r's compliment method a) $1010100_{(2)} - 1000100_{(2)}$	L3 6M	
OR				
Q. 06	a	Convert the following a) $3A6.C58D_{(16)} = ?_{(8)}$ b) $0.6875_{(10)} = ?_{(2)}$	L3 8M	




	c) Compute the 9's compliment of $25.639_{(10)}$ d) Compute the 1's compliment of $11101.0110_{(2)}$		37
b	State and prove De-morgan's Theorem with its truth table.	L1	5M
c	Minimize the following function a) $F(x,y,z) = xy + x'z + yz$ Find the compliment of the function F1 and F2 $F1(x,y,z) = x'y'z' + x'y'z$ $F2(x,y,z) = x(y'z' + yz')$	L3	7M
Module-4			
Q. 07	a) Compare Embedded Systems and General Computing Systems, also provide the applications of Embedded systems.	L2	5M
	b) Write a note on core of an Embedded systems with its block diagram.	L2	8M
	c) Write a note on Transducers? Explain one type of Sensor and Actuator with its operation.	L2	7M
OR			
Q. 08	a) Explain how 7 seg Display can be used to Display the data and write a brief note on operation of LED.	L2	7M
	b) What is an Embedded system and brief about the different elements of an Embedded systems.	L2	8M
	c) Write a note on classification of Embedded systems.	L2	6M
Module-5			
Q. 09	a) Write a note on different types of modulations and briefly describe each in detail.	L2	8M
	b) Brief about Modern Communication System with its block diagram.	L2	7M
	c) List out the advantages of Digital Communication over Analog Communications.	L2	5M
OR			
Q. 10	a) Explain with a neat diagram the concept of Radio wave Propagation and its different types.	L2	7M
	b) Consider the following binary data and sketch the ASK, FSK & PSK modulated waveforms. 	L2	6M
	c) Describe about Radio signal transmission and Multiple access techniques.	L2	7M

Figure 10.b

* Bloom's Taxonomy Level: Indicate as L1, L2, L3, L4, etc. It is also desirable to indicate the COs and POs to be attained by every bit of questions.

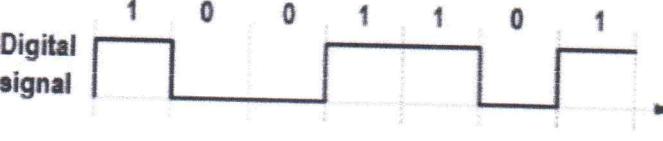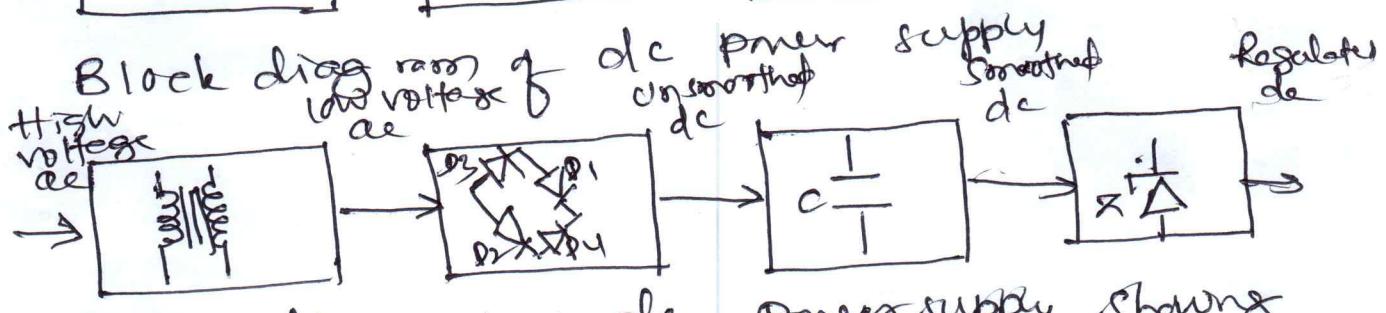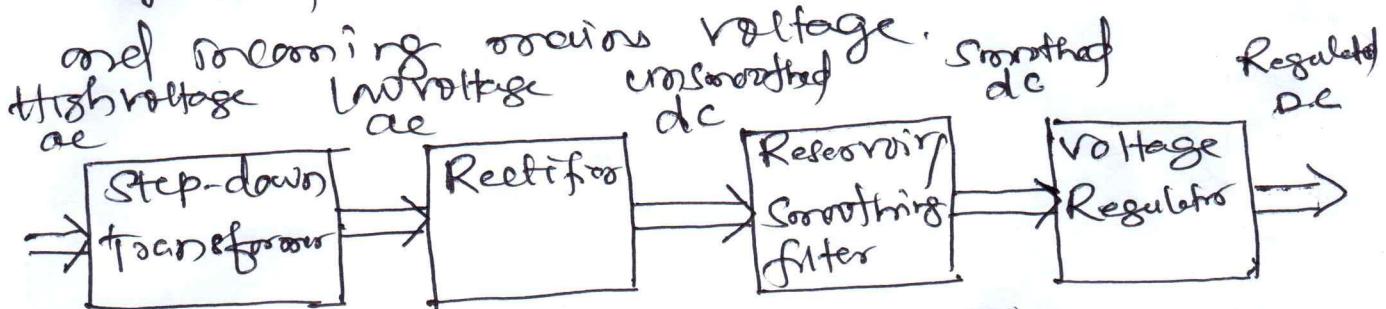
Q19. Regulated power supply is an electronic device that can provide stable dc power to the load, which will stabilize the output voltage so that it remains relatively constant inspite of variations in both load current and incoming mains voltage.



Block diagram of dc power supply showing principle components.

The main input is fed of relatively high voltage a step down transformer with appropriate turns ratio is used to convert this low voltage, ac output is then rectified using diode to produce an unsmoothed (pulsating) output. Then this is smoothed and filtered using connecting the capacitors across the load, which will be regulated by connecting zener diode. The output remains constant inspite of variation of load and input voltage.

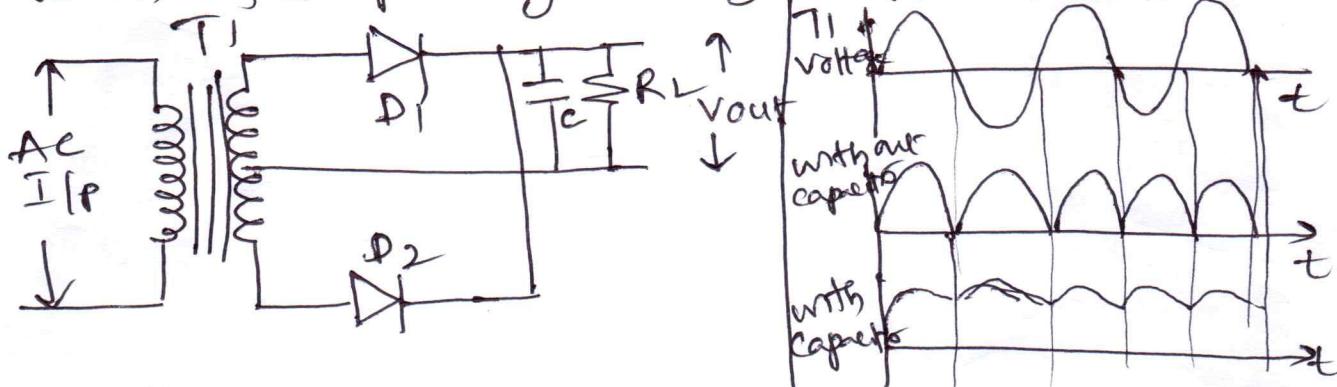
1 b The filter circuit provides considerable ³⁷ improvement (Smoothing) in the conversion of AC-DC. The capacitor has been added to ensure that the output voltage remains at or near the peak voltage even when the diode is not conducting when the primary voltage applied to the T₁.



A better rectifier arrangement make use of both positive and negative half cycles. Positive half cycle diode D₁ allows conduction while D₂ will not allow the conduction. During negative half cycle D₂ will allow the conduction while D₁ will not allow the conduction.

The reservoir (filter) C can be added to ensure the output voltage remains at or near the peak voltage. It charges approximately at the peak of positive half cycle and holds the voltage at this level when the diodes are in their non-conducting states. Hence C charges very rapidly as soon as either D₁ or D₂ starts conducting. The time required for C to discharge is in contrast very much greater. The discharge contrast is determined by capacitor value.

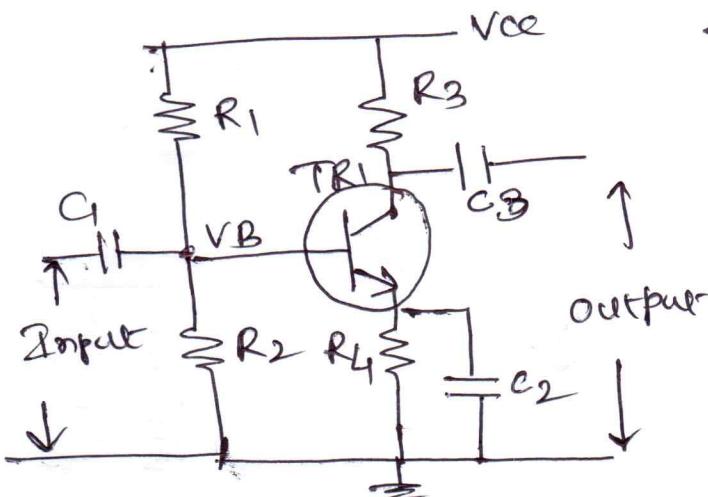IC CE amplifier with feedback. The voltage divider
 35
 CE amplifier with negative feedback provides effective bias stabilization.



The negative feedback path provides feedback ac signal component of dc bias. As a result of slight reduction of signal gain. The

Signal gain can be increased by removing the ac signal component from the feed back path so that only the dc component is present. In the circuit R_1 & R_2 forms a potential divider that determines dc base potential V_B . The base emitter voltage is the difference between potential present at base V_B and emitter V_E . The potential at emitter is governed by the emitter current I_E as the emitter voltage V_E will increase consequently V_{BE} will fall and produce reduction in the emitter current. The increase in bias results in an increase in emitter current compensating for the original change.

$$V_B = \frac{R_2 \cdot V_{CE}}{R_1 + R_2}$$

2a Power dissipation - $500mW = P_{Z\max}$ 33

diode regulated 5V

Load resistance $500\Omega = R_L$

$R_s\min = ?$ $R_s\max = ?$ R_s

$$\therefore R_{s\max} = R_L \left(\frac{V_{IN}}{V_Z} - 1 \right) = 500 \left(\frac{9}{5} - 1 \right) = 500 \times (1.8 - 1)$$


$$R_{s\min} = 500 \times 0.8 = 400\Omega$$

$$\& R_{s\min} = \frac{V_{IN} \cdot V_2 - V_Z^2}{P_{Z\max}} = \frac{9 \times 5 - 5^2}{0.5} = \frac{45 - 25}{0.5} = 40\Omega$$


R_s would be midway between two extremes

$$R_s = 180\Omega$$

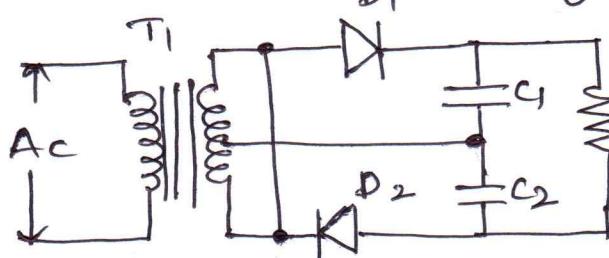2b Voltage multiplier produce the higher voltage using the cascade arrangement and it can increase the output stage by stage



Voltage doubler

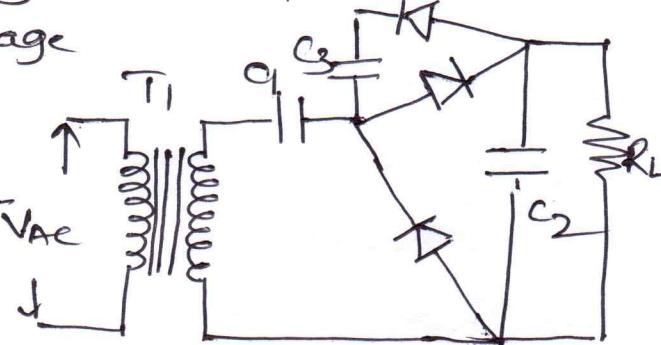

Voltage Tripler



Voltage doubler C_1 charges to the positive peak.

Secondary voltage C_2 will charge to the negative peak secondary voltage since the output is taken from C_1 & C_2 connected in series the resulting output voltage

will twice that produced by one diode alone. It can be extended to provide higher voltage but the efficiency of the circuit becomes increasingly impaired. and high order voltage multipliers provide relatively small currents.



2c BJT is used as switch.

31

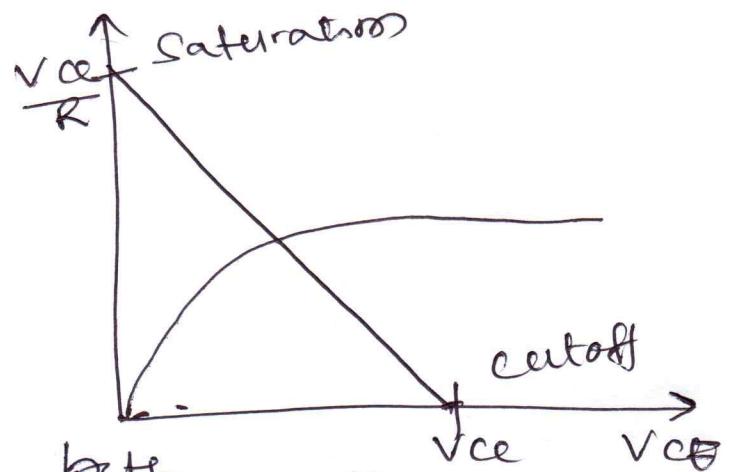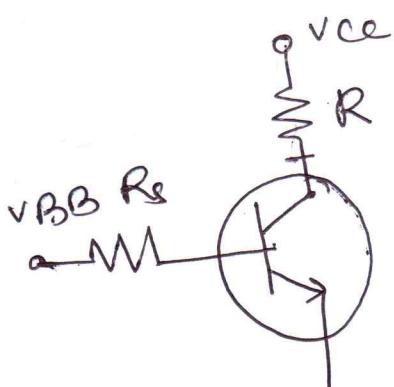

In cutoff region both emitters to base and base to collector junctions is reverse biased and no current flows through transistor acts as open switch.

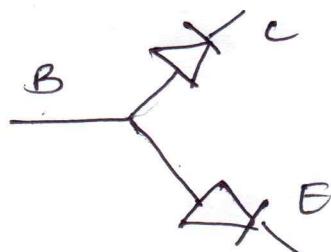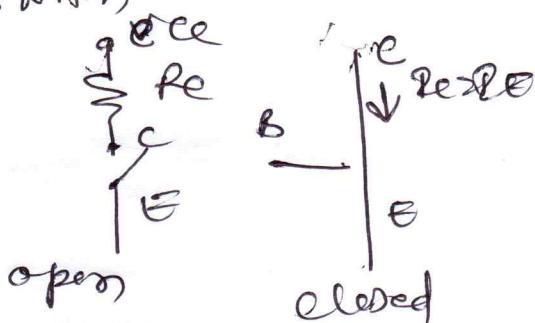In saturation region both junctions are forward biased and transistor acts as closed switch.




Active region - Emitter to base junction is forward biased and base collector junction is reverse biased. In active region transistor acts as an amplifier.

In active region Collector Current β times of the base current


BJT \rightarrow amplifiers, filters, Rectifiers, oscillators or even as a switch.

8a Q Differentiator :

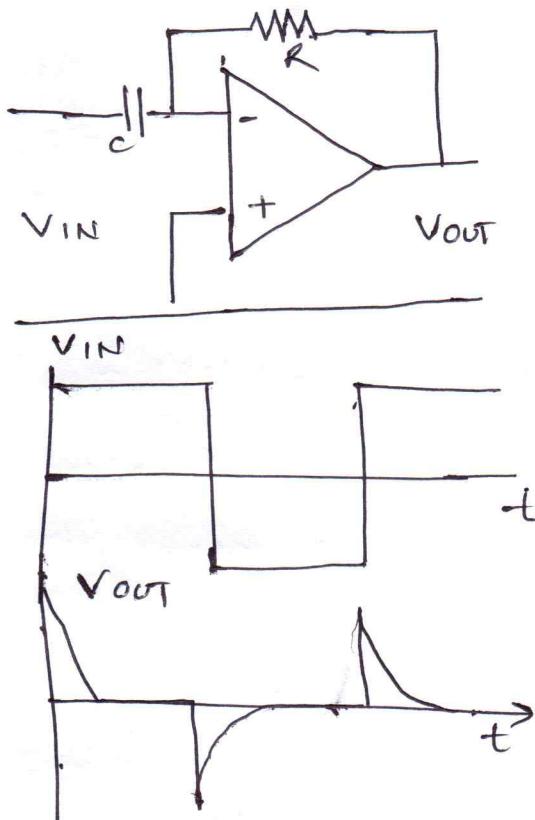

Differentiator produced ²⁹ the output voltage equivalent to the rate of change of its input. If the input voltage remains constant the output voltage remains constant. Faster the input voltage changes the greater will the output be. The input output waveforms are shown in fig. Output is inverted because signal applied to inverting input of the operational amplifier.

8b Q Integrator :

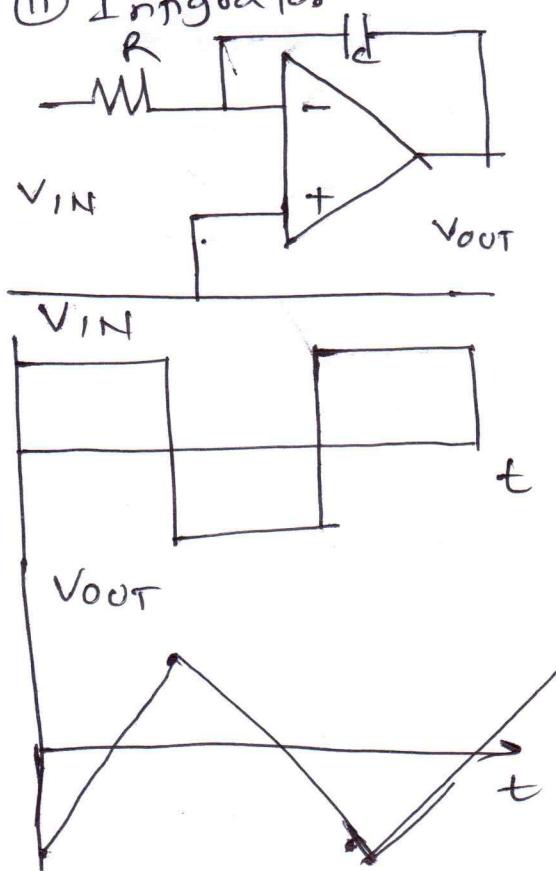

Integrator is operational amplifier circuit provides the opposite function of differentiator. The output voltage is equivalent to the area under the graph of input function rather than its rate of change. If the input voltage remains constant the output voltage will ramp up or down according to the polarity of the input. Notice that square wave input is converted to a wave that has triangular shape.


3b Ideal Characteristics of an op-amp 27

- ① The open loop voltage gain should be very high (Ideally Infinite)
- ② Input resistance of the opamp is very high (Ideally Infinite)
- ③ The output resistance should be very low (Ideally ≈ 0)
- ④ Full power bandwidth should be as wide as possible
- ⑤ Slew rate should be as large as possible
- ⑥ Input offset should be as small as possible

parameter	Ideal	Real
1. Voltage gain	Infinite	1,00,000
2. Input resistance	Infinite	100M Ω
3. Output resistance	Zero	2 Ω
4. Bandwidth	Infinite	2MHz
5. Slew rate	Infinite	10V/ μ s
6. Input offset	Zero	Less than 50mV

3c Single stage Astable oscillator

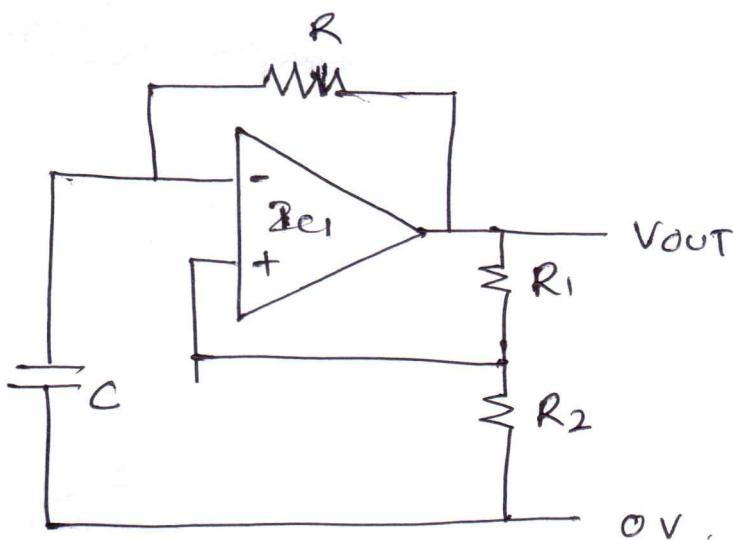A simple form of Astable oscillator that produces square wave output using one operational amplifier. The circuit employs positive feedback with the output fed back to the non inverting input via the potential divider formed by R_1 and R_2 . This circuit is shown in fig below.



Frequency can be made adjustable by varying in R . Assume C is initially uncharged & voltage at the inverting input is slightly less than the voltage at Non-inverting input, the output will rise rapidly to $+V_{CC}$ and voltage at inverting input begin to rise exponentially as capacitor C charges through R .

The voltage at inverting input will reach and exceed that present at the Non-inverting input and output voltage fall to $-V_{CC}$ and capacitor C charges in the other direction. The upper threshold the voltage max. at inverting is $V_{UT} = \frac{V_{CC} \times R_2}{R_1 + R_2}$

and The lower threshold maximum negative value for the voltage at inverting input

$$V_{LT} = -\frac{V_{CC} \times R_2}{R_1 + R_2}$$

complete one cycle output waveform

$$T = CR \left(\ln \left(1 + 2 \frac{R_2}{R_1} \right) \right)$$

4a. Conditions of sustained oscillation are 23


- ① The feed back must be positive & if the signal fed back must arrive back in phase with signal at input
- ② The overall loop gain must be greater than 1

The frequency of oscillation of three stage ladder network $C = 10\text{nF}$ and $R = 10\text{k}\Omega$

$$f = \frac{1}{2\pi\sqrt{LCR}} = \frac{1}{6.28 \times 2.45 \times 10^{-9} \times 10 \times 10^3}$$

$$= \frac{1}{6.28 \times 2.45 \times 10^{-4}} = \frac{10^4}{15.386} = 647 \text{ Hz}$$


4b Crystal Controlled oscillator - Accurately maintain an exact frequency of oscillation. The quartz crystal is used as the frequency determining element. Quartz crystal stabilize the frequency of oscillation of a circuit to within few parts in a million. Crystal manufactured for operation in fundamental mode 100kHz to well over 100MHz. Simple crystal oscillator circuit provides feedback from drain to the source of JFET.

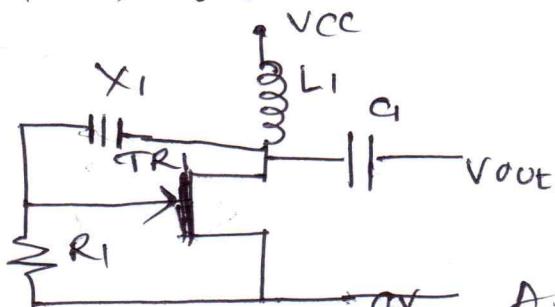

or A simple JFET oscillator

Ab Quartz Crystal Vibrator Whenever the potential difference is applied across its faces. (The phenomenon is known as piezoelectric effect) The frequency of oscillation is determined by the crystal cuts and physical size

Ac Single Stage multivibrator: multivibrators are family of oscillator circuits produces output waveforms consisting of one or more rectangular pulses; multivibrators are regenerative, the active device present within the oscillator being operated as a switcher alternatively cut off and driven into saturation mono stable multivibrator that produces the single off pulse referred as one shot; single stage produces square wave output using one operational amplifier. The circuit is shown as

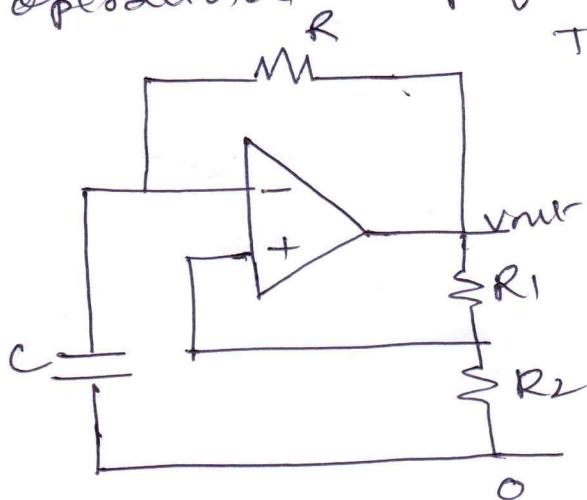

The circuit employs positive feedback with a p/f feed back to the non inverting i/p with potential divider formed by R_1 & R_2


The frequency can be made adjustable by varying R
Also C is mainly controlled at inverting input slightly less than the voltage at non inverting input. The off will rise to $+V_{cc}$

The voltage at non inverting will reached and exceed non inverting and output voltage fall to $-V_{cc}$

5a Full Adder. Full adder is a ¹⁹ combinational logic circuit that forms arithmetic sum of three input bits. It consists of three inputs and two outputs.

Two input variables x & y and third input variable z represents the Carry from previous lower significant position. The two output designated by S (S_{sum}) & C (C_{Carry})

x	y	z	C	S	Sum = S
0	0	0	0	0	$S = x'y'z + x'yz'$
0	0	1	0	1	$+ xy'z' + xyz$
0	1	0	0	1	Carry = C
0	1	1	1	0	$\therefore C = x'yz + xy'z$
1	0	0	0	1	$+ xy'z' + xyz$
1	0	1	1	0	$= xy + xz + yz$
1	1	0	1	0	
1	1	1	1	1	

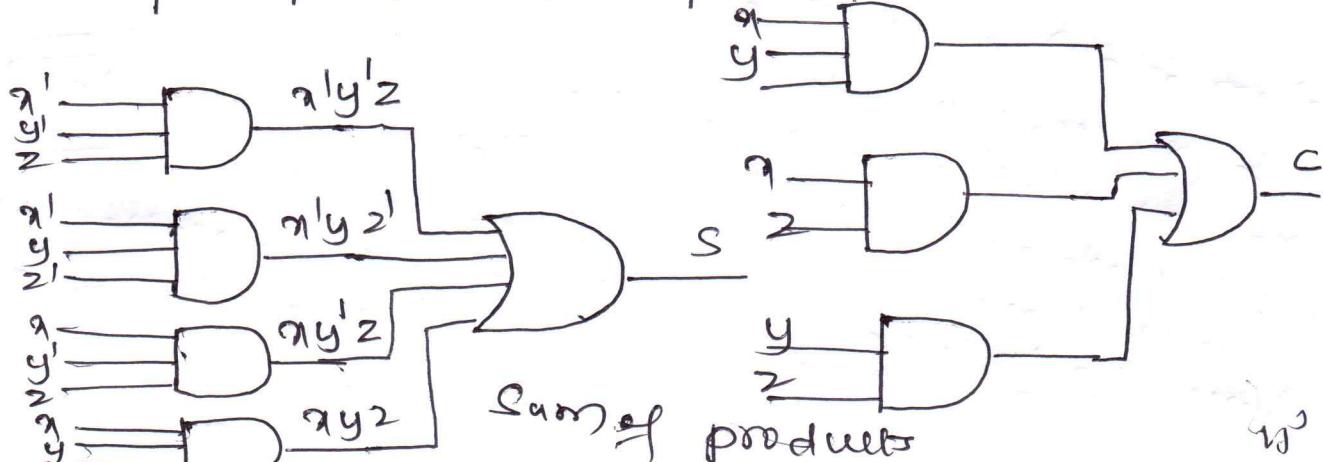

5b postulate 2 $\textcircled{a} x+0=x$ $\textcircled{b} x \cdot 1 = x^{17}$

Postulate 5 $\textcircled{a} x+x'=1$ $\textcircled{b} x \cdot x' = 0$

Theorem 1 $\textcircled{a} x+x=x$ $\textcircled{b} x \cdot x = x$

Theorem 2 $\textcircled{a} x+1=x$ $\textcircled{b} x \cdot 0=0$

Theorem 3 Inversion $(x')' = x$

Postulate 3 Commutative $\textcircled{a} x+y=y+x$ $\textcircled{b} xy=yx$

Theorem 4 Associative $\textcircled{a} x(y+z) = (x+y)z$ $\textcircled{b} xyz = (xy)z$

Postulate 4 Distributive $\textcircled{a} x(y+z) = xy + yz$ $\textcircled{b} (xy)z = x(yz)$
 $x+yz = (x+y)(yz)$

Theorem 5, De Morgan's $\textcircled{a} (x+y)' = x'y'$ $\textcircled{b} (xy)' = x'+y'$

Theorem 6. Absorption $\textcircled{a} (x+xy)=x$ $\textcircled{b} x(x+y)=x$

$\textcircled{1} x+x=x$

$x+x = (x+x)(1) = (x+x)(x+x') = x+x x' = x+0 = x.$

$\textcircled{2} x \cdot x = x \Rightarrow xx+0 = xx+x x' = x(x+x') = x.$

$\textcircled{3} x+1 = 1 \Rightarrow 1 \cdot (x+1) = (x+x')(x+1) = x+x \cdot 1 = x+x' = 1$

$\textcircled{4} x \cdot 0 = 0$

$\textcircled{5} (x')' = x$

Truth table

x	y	xy	$x+xy$	$(x+y)$	$(x+y)'$	x'	y'	xy'
0	0	0	0	0	1	1	1	1
0	1	0	0	1	0	1	0	0
1	0	0	1	1	0	0	1	0
1	1	1	1	1	0	0	0	0

Sc ① (r-1)'s complement $4456_{(10)} - 34234_{(10)}$

$$\begin{array}{r}
 + 04456 \\
 + 65765 - 9's \text{ complement} \\
 \hline
 70221 - \text{no carry} \quad \text{Ans} = -29778 \quad (9's \text{ complement} \\
 \text{of } 70221)
 \end{array}$$

⑪ Subtract using 2's Complement

$$\begin{array}{r}
 1010100_{(2)} - 1000100_{(2)} \\
 1010100_{(2)} \quad 1000100 - 0111011 \\
 + 0111100 - 2's \text{ complement} \quad + 1 \\
 \hline
 = 0010000 \quad \text{of } 1000100 \quad \overline{0111100} \\
 \therefore \text{Ans} = 0010000 = 10000
 \end{array}$$

6.9. Convert

$$\textcircled{1} \quad 3A6.C58D_{(16)} = (?)_8$$

$$\begin{array}{r}
 001110100110.1100010110001101_{(2)} \\
 1 \quad 6 \quad 4 \quad 6 \cdot 613064_{(8)}
 \end{array}$$

$$\therefore 3A6.C58D_{(16)} = 1646.613064_{(8)}$$

$$\textcircled{1} \quad 0.6875_{(10)} = (?)_9$$

$$\begin{array}{r}
 0.6875 \times 2 = 1.375 - 1 \\
 0.375 \times 2 = 0.750 - 0 \\
 0.750 \times 1 = 1.50 - 1 \\
 0.50 \times 1 = 1.000 - 1 \\
 \hline
 0.6875_{(10)} = 0.1011
 \end{array}$$

6 c q's Complement of 25.639.

$$10^2 - 10^3 - 25.639 = 99.999 - 25.639 \\ = 74.360$$

④ 1's complement $11101.0110_{(2)}$ □

$$2^5 - 1 - 11101 = 11111 - 1 - 11101 \\ = 11110 - 11101 \\ = 00010$$

1's Complement of $0.0110 \circ 1 - 2^4 = 0.0110$
 $= 0.1001$

$$\therefore 11101.0110 = 00010.1001$$

6b DeMorgan's theorem with truth table

$$\textcircled{I} (x+y)' = x'y' \quad \textcircled{II} (xy)' = x'+y'$$

$$\therefore x'y' \cdot (x+y)' = xy(x+y)' (x'+y')$$

0	0	1	0	1	1	1
0	1	1	0	0	1	1
1	0	0	1	0	0	1
1	1	0	0	1	0	0

6c minimize the following function

$$\begin{aligned} F(x,y,z) &= xy + x'z + yz \\ &= xy + x'z + yz(x+x') \\ &= xy + \underline{x'z} + \underline{yz} + \underline{x'yz} \\ &= xy + x'z(1+y) + xyz \\ &= xy + x'z. \end{aligned}$$

6 C ② $F_1(x, y, z) = \frac{\bar{x}yz' + x'y'z}{\bar{x}'yz' + x'y'z}$, complement

$$\begin{aligned} &= \frac{\bar{x}'y'z' + x'y'z}{\bar{x}'yz' + x'y'z} \\ &= (\bar{x}'y'z')(\bar{x}'y'z) \\ &= (\bar{x}' + \bar{y}' + \bar{z}')(\bar{x}' + \bar{y}' + \bar{z}) \\ &= (x + y' + z)(x + y + z') \end{aligned}$$

$F_2(x, y, z) = \frac{x(y'z' + yz')}{x(y'z' + yz')}$, complement

$$\begin{aligned} &= \overline{x + (y'z' + yz')} \\ &= \bar{x}' + (\bar{y}' + \bar{z}').(\bar{y} + \bar{z}) \\ &= \bar{x}' + (\bar{y}' \cdot \bar{z}').(y' + z) \\ &= \bar{x}' + (\bar{y}' \cdot z)(y' \cdot z) \\ &= \bar{x}' + (y + z)(y' + z') = P_2' \\ \Rightarrow & x + (y' + z')(y + z) \\ = & x' + (y + z)(y' + z') = F_2' \end{aligned}$$

7 a. Compare Embedded System and General Computing System.

General purpose Computing system
A system which is combination of general hardware & general operating system for variety of application

Embedded system
A system which is a combination of special purpose hardware and embedded as for executing a specific set of application

Contains general purpose operating system (GPOS)

Applications are alterable by user

Performance is key deciding factor in the selection of system Faster is Better

less/reduced operating power requirements

Response requirements are not time critical

Need not deterministic in execution behaviour

APPLICATIONS of Embedded systems

- ① Consumer electronics : camera, CamCards
- ② Household applications : Washing machine, DVD
- ③ Home automation & Security systems : AC, sprinkler, Alarm
- ④ Automotive industry : Antilock braking system (ABS)
- 5 Telecom
- 6 Computer peripherals
- 7 Health care
- 8 Measurement & Instrumentation
- 9 Banking and Retail
- 10 Card Readers.

may or may not contain operating system for functioning

If is pre-programmed & non alterable

Application specific documents are the key deciding factors

Highly tailored of power saving modes & operating system

Response time requirement is highly critical

Execution behaviour is deterministic
Hard Real time Systems

7.1 Core of Embedded System with Block diagram

Embedded Systems are domain and application specific and are built around a central core. The core of the embedded systems fall into any one category.

1. General purpose and domain specific processors


- 1. microprocessor
- 2. microcontroller
- ③ Digital signal processor

2. Application specific integrated circuits (ASICs)

3. programmable logic devices.

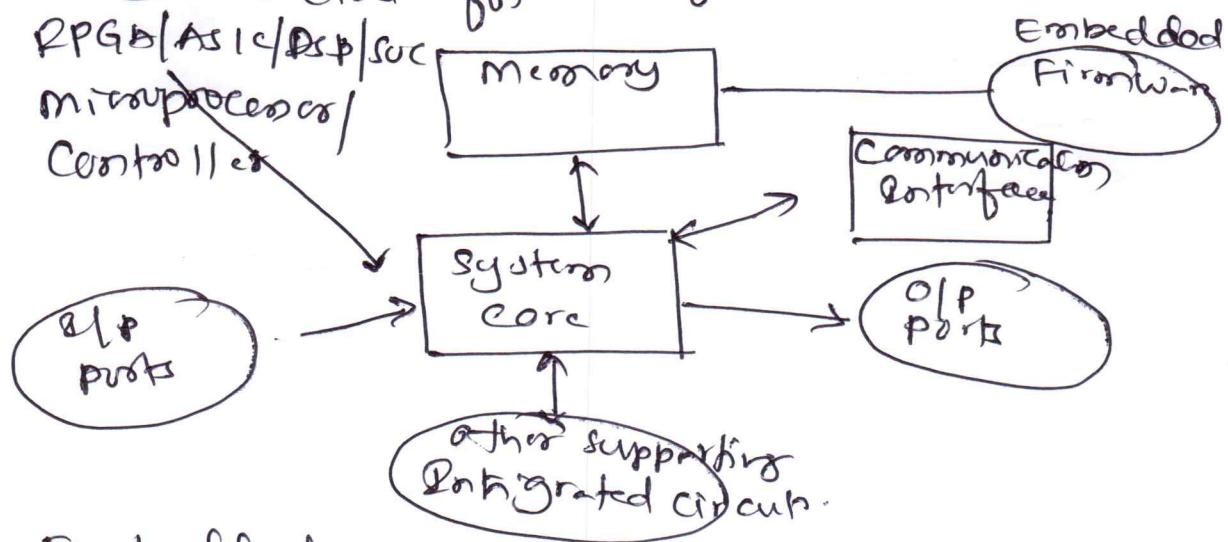4. commercial off the shelf components (COTS)

RPGD/ASIC/DSP/SOC
microprocessor/
Controller



Embedded System contains single chip controller which acts as master of the system

microprocessor (Intel 8085), microcontroller (Atmel AT89S51)

RPGA, (Field programmable gate array) Xilinx

Application specific integrated circuit (ASIC).

Embedded System can be viewed as reactive system. The control is achieved by processing information coming from the sensor and user interfaces and controlling some actuators, that

regulate the physical variable
 keyboards, switch buttons - user interface I/O devices, LED, LCD, Piezoelectric buzzers, user interface output devices. Embedded systems are designed for handheld application.

Memory of the system is responsible for holding control algorithms and other important configuration details. For most of the embedded systems there is no provision for changing the algorithms or configuration data is of fixed type which is a kind of Read only memory (ROM) and not available for end user for modification. Random access memory (RAM) is used for most of the systems as the working memory. The size of RAM varies from few bytes to kilobytes or megabytes, depending on the application.

T C Transducers are devices that convert the energy in the form of sound, light, heat into its equivalent electrical signal or vice versa.

Loudspeaker - low frequency electrical current into audible sounds, microphone transducer performs non-electrical to electrical conversion

Transducer Convecting Sound, pressure variation into voltage or current, microphone is an input transducer, Loudspeaker is an output transducer.


Sensors: Sensors define specific kind of transducer that generates electrical signal measurement, instrumentation or control system. Signal produced by sensor is electrical analog. Choice of sensor is governed by a number of factors accuracy, resolution cost and physical size.

Sensor is Active or passive.
Active sensor generates current or voltage output, passive sensor requires source of current; or voltage and modifies this in some way.

Actuators: Actuator is a form of transducer device (mechanical or electrical) which converts signal to the corresponding physical action (motion). Actuator acts as an output device.

Ques 7 segment LED display is an output device for displaying alphanumeric characters. It contains 8 LED (light-emitting diodes). 7 are used for displaying the alpha numeric and one is used to represent decimal point


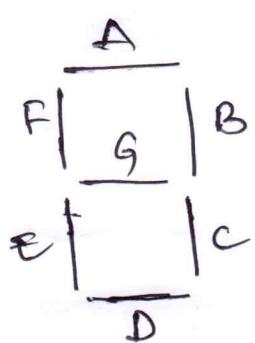
LED segments are named A to G and decimal point LED is named DP



For example displaying number 4, the segments F, G, C are lit. All other 6 LEDs are connected DP to one port of the processor.


The seven segment LED are available in two different configurations Common Anode &

Common Cathode

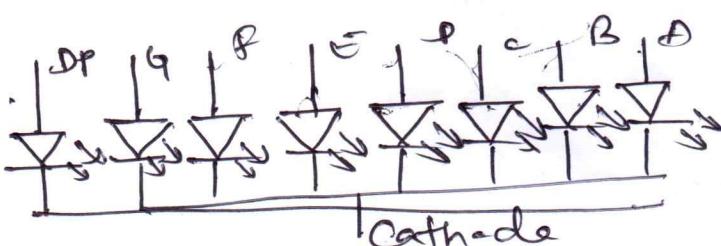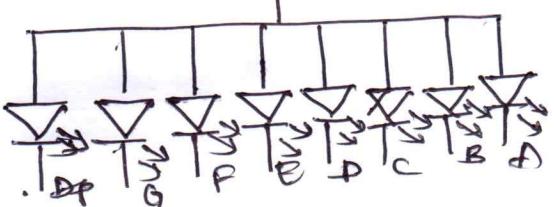

Based on the configuration of anode or cathode is connected to the port of the processor or controller. Segment A connects to least significant port pin, DP often most significant port pin is connected. The range of 20mA. Current can be limited by connecting the current limiter resistor to the anode or cathode of each segment.

LED - Light Emitting diode is important output device for visual in any embedded system. LED can be used as an indicator for the status of various signal. Indicating the presence of power Good, indicating the device ON, Battery low, charging etc. LED is p-n junction diode and it contains anode and cathode. For proper functioning of LED the anode should be connected to positive terminal of the supply voltage and cathode to negative terminal or ground. The current flowing through the LED must be limited to a value less than a maximum current that it can handle and LED to limit the current used to series between the power supply and the LED.

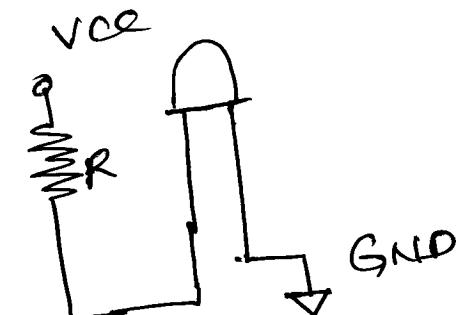


LED is interfaced to the processor port pin of the processor. Anode is directly connected to the port pin and Port pin drives the LED. Cathode of LED is connected to the port pin of the processor. And anode of LED is connected to the supply voltage through the current limiting resistor.

8b Embedded system is an electronic / ~~electro~~ 25 mechanical system to perform a specific function and is a combination of both Hardware & Firmware (Software)

Elements of Embedded system, It contains a single chip controller which act as a master brain of the system. The controller can be a microprocessor (Intel 8085), microcontroller (Atmel 89C51), Field Programmable Gate Array, Digital Signal processor (DSP) from Analog devices.

Embedded basically designed to regulate physical variable or manipulate the state of some device by sending some control signal to the actuator or device connected to the O/P port of the system. Embedded System can be reactive system. In embedded system the control is achieved by processing the information coming from the processor and user interface.

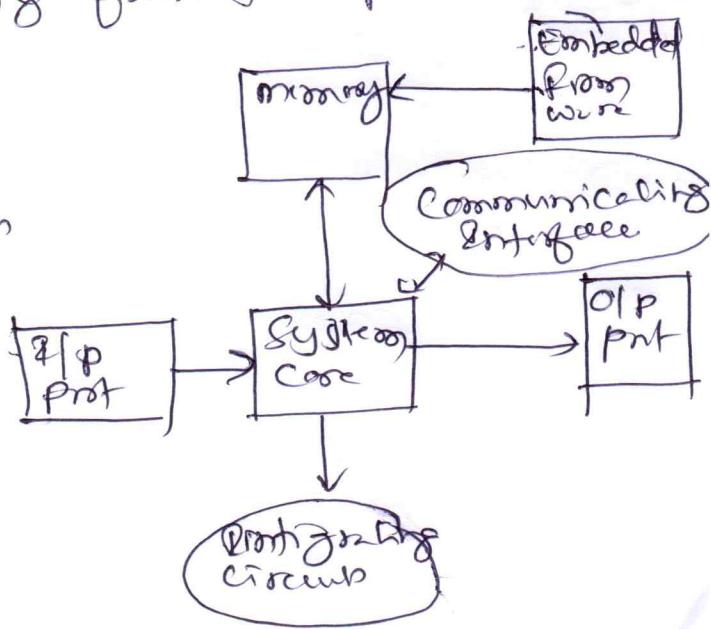- ① Key board, Actuators
- ② Communication interface
- ③ Integrated Circuits
- ④ I/O user interface.
- ⑤ memory
- ⑥ Embedded Processor
- ⑦ System Core (FPGA)
- A/D, D/A



Classification of embedded system

- ① Based on Generation
- ② Complexity of performance
- ③ Based on deterministic behaviour
- ④ Based on trigger
- ⑤ classification based on generation

1. First Generation - Embedded systems built around 8 bit microprocessor, 8085, Digital telephone keypads

2. Second Generation: Built around 16 bit microprocessors and microcontrollers, Instructions set more complex and powerful than first generation, It contains embedded operating system

3. Third Generation - powerful 32 bit processor & 16 bit microcontroller. Application and domain specific processor. The instruction set and processor are powerful and Concept of pipelining emerged (ASIC), Robotics, media, and Industrial control

4. Fourth generation: Advanced system on chip, reconfigurable processor and multi-core processor, high performance, tight integration and miniaturization in one embedded device market

2. classification based on complexity and performance


① Small scale embedded system → embedded system which are simple applications and not time critical. low performance and low cost, 8bit 16 bit microprocessor

② medium scaled embedded systems Slightly complex in hardware and firmware, Built around medium performance low cost 16 or 32 bit. This contain an embedded operating system

③ Large scale embedded systems which involves complex hardware and firmware. They built around high performance 32 bit RISC processor, Reconfigurable system on chip (FPGA) & multi-core processor and programmable logic devices. They contain multiple processor, Decoding / encoding of media, cryptographic function, compression etc.

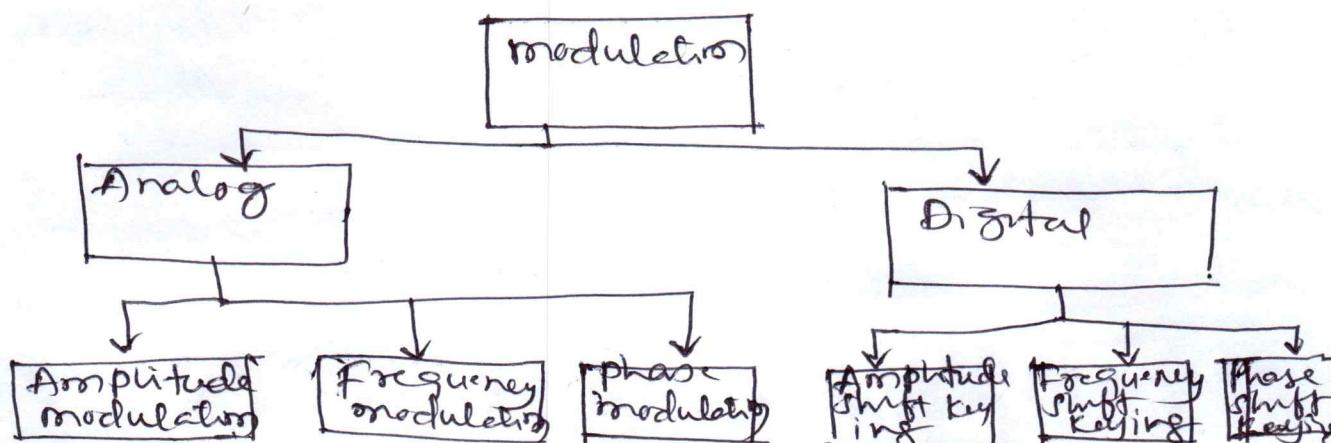9. a. Different types of modulation

Modulation is the process in which any of the parameter (amplitude, frequency or phase) of the high frequency carrier signal is varied according to the instantaneous value of low frequency message signal, keeping other parameters constant.



Analog modulation
FM, Radio, Short


Digital modulation
involves transmission of binary (0 and 1)

Amplitude modulation is the process in which the amplitude of carrier signal is


typically used for AM wave Broadcasting

involves transmission of

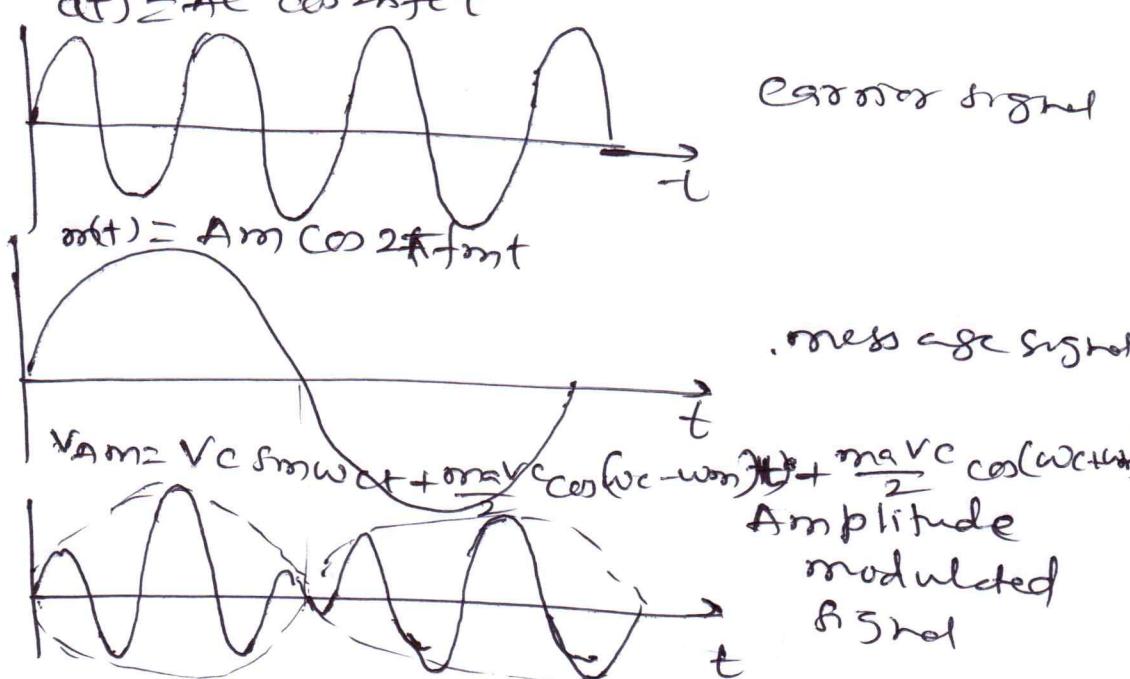according to the instantaneous value ³³ of the message signal, where the frequency and phase are kept constant



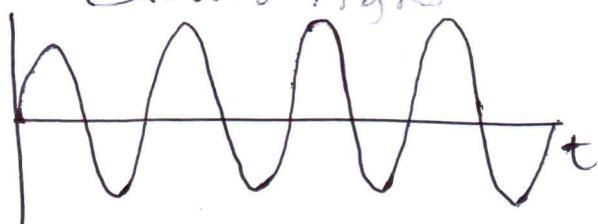
Frequency modulation is defined as a process in which the frequency of the carrier is varied in accordance with the instantaneous value of the message signal. Where as the amplitude and phase are kept constant.



9 b Modern Communication System

31

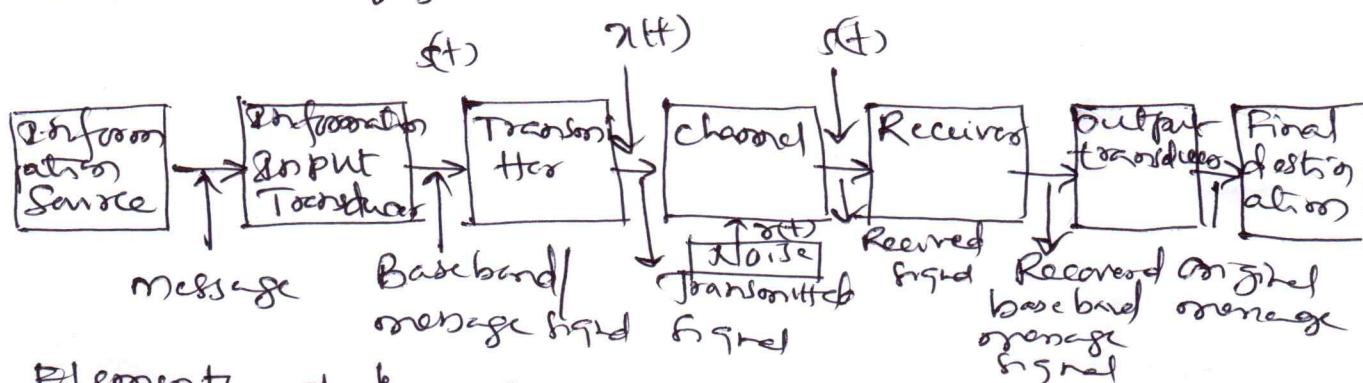General form of basic Communication System is shown in fig.



Elements of the Communication System

Information Source and Transducer - Non electrical signals are converting it into electrical signal

Transmitter - Base band signal (Electrical form) applied to the input transducer. The transmitter performs the operation filtering, amplification and modulation. The nature of processing depends on the type of the communication system.

Base band signal which uses in the low frequency spectrum and is translated to a high frequency spectrum - carrier communication system.

$x(t)$ → Base band signal, $s(t)$ → modulated signal

$s(t)$ is super imposed upon high frequency carrier. Finally signal is passed to the transmission medium or channel. Transmitted signal should have the adequate power to withstand the channel noise. The channel characteristics also impose constraints on the Band width.

Hardwired channel

Transmission line, co-axial cable, twisted pair cables, wave guides, optical fiber

Softwired (No physical link) Air or open space

Noise - Noise is defined as unwanted electrical signal which is not having information 29

Receiver - The receiver is to reproduce original message signal. The reproduction of original signal is accomplished by a process of demodulation or detection.

Demodulation is a reverse process of modulation. The received signal is $r(t)$. The received signal is weak signal. Voltage amplifier amplifies further processing, its voltage and power is amplified before send to the final destination block.

Destination : Destination is the final stage which is used to convert an electrical message signal into its original form, the destination is loudspeaker which works as transducer that converts electrical signal to original sound signal.

Q.C Advantages of Digital Communication over Analog Communication

Most of the signals are in analog in nature digital signals are obtained from analog domain by technique, Sampling, Quantization and encoding. digital signal have many advantages of digital communication over Analog communication

- Digital communication ~~of course~~²⁷ Internet and cyberspace could not exist without digital communication
- Digital communication is fast, easier and cheaper
- Digital communication is more immune to noise
- Digital Circuits are more reliable and consume less power
- Digital Circuit easy to design and cheaper than analog Circuits
- Hardware implementation is more flexible, easy to implement, less expensive, powerful microprocessor
- occurrence of cross talk is very rare
- Encryption in digital domain allows security of data
- compression allows data to reduce in lesser in size
- probability of error occurrence is reduced due to error detecting and error correcting codes.
- spread spectrum techniques is used to avoid signal jamming
- multiplexing is quite easy
- Better voice quality over a long distance
- Deliver more information with greater probability
- Simple to use digital devices with flexible features.


10a. Radio Waves propagation.

Radio waves exhibit the properties of light with the velocity 3×10^8 m/s. These EM wave consists of electric and magnetic field components traversed perpendicular to one another in nature.

EM waves exhibit properties such as reflection, diffraction, absorption, polarization and scattering.

① Ground or surface wave: Ground wave can be used for radio wave propagation. Ground wave transmission is very reliable irrespective of atmospheric conditions. Frequency range 30 kHz to 3 MHz, transmission distance 200-1000 km, Example AM radio broad cast.

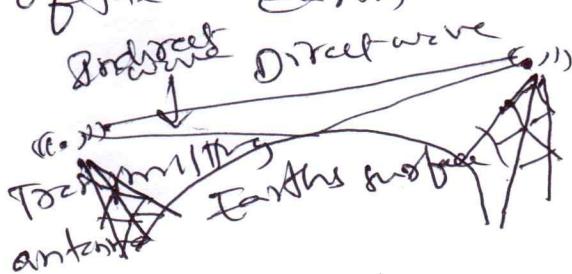② Space or tropospheric wave propagation: Radio waves moves in the earth's troposphere or within about 12 km over the surface of the earth.



Frequency range
3-MHz to 30MHz


TV Transmissions

Space wave made of two

Components ① Direct wave

② Radiated wave (Ground reflected wave)

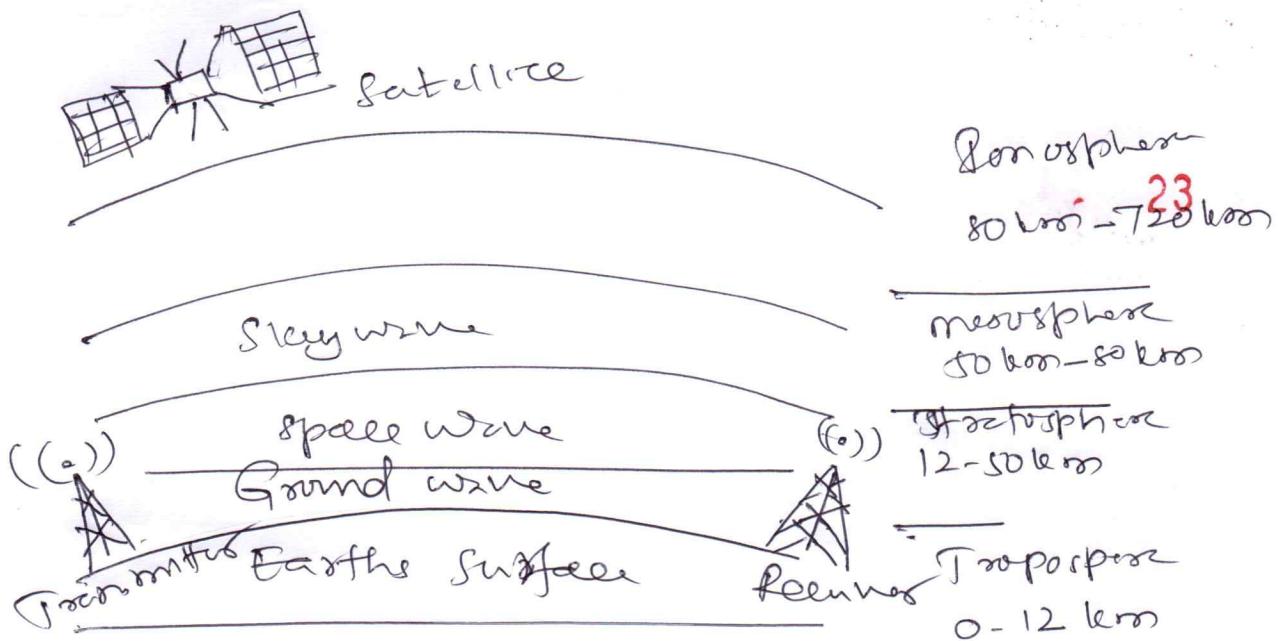③ Sky wave: Radio waves transmitted from the transmitting antenna to the receiving antenna after reflecting from ionosphere




Sky wave is responsible for short wave transmission around the globe via successive reflections after ionosphere and earth's surface.

10b modulation schemes: Digital modulation schemes are classified as



- ① Amplitude shift keying (ASK)
- ② Frequency shift keying (FSK)
- ③ Phase shift keying (PSK)

① ASK - represents digital data as a variation in the amplitude of a carrier wave. ASK signal can be generated when meaning binary data and sinusoidal carriers are applied to a product modulator. The binary data input digital signal is shown as a square wave. The carrier signal is shown as a sine wave. The output ASK signal is the product of the two signals, showing amplitude variations corresponding to the digital data.

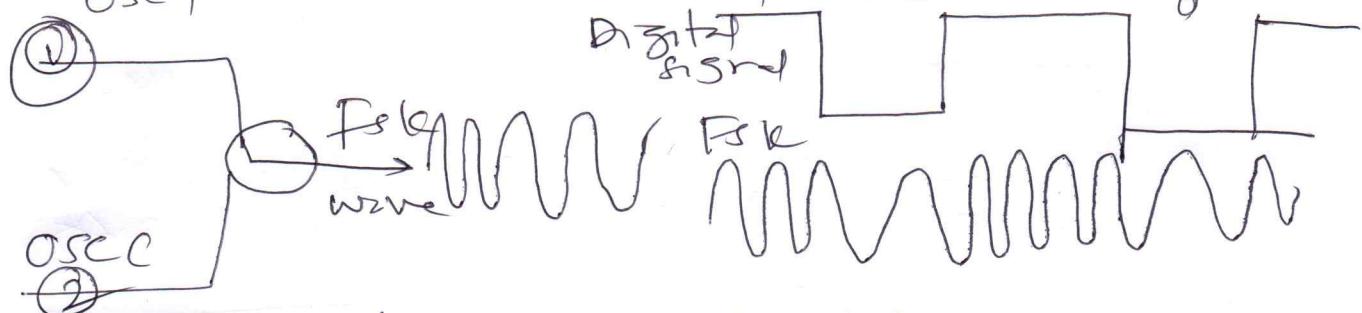⑩ FSK - Digital signal is transmitted by switching between low frequency and high frequency in order to represent 0's and 1's



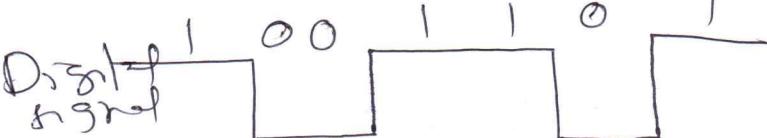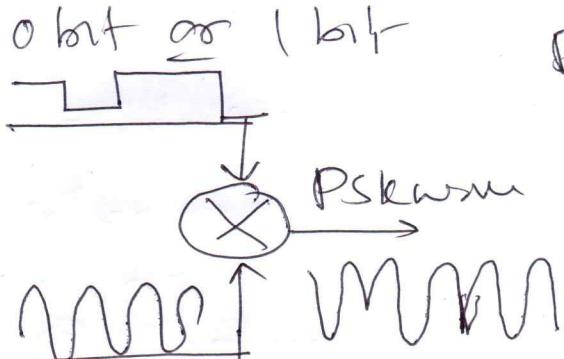⑪ Phase Shift Keying (PSK) - The carrier phase shifted between two different phases 0° and 180° depending on whether 0 bit or 1 bit




10c Radio signal transmission: wireless transmitter accepts a bit串-binary streams of bits 00 01 10 10 from the application software and is encoded as radio wave known as a carrier is adjusting its amplitude or phase



Transmitter operates in two stages which generates radio waves.

Quadrature Phase Shift Keying (QPSK) 37

Transmitted bits: 00 01 11 10

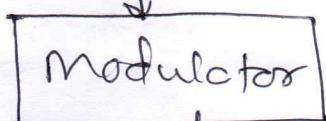

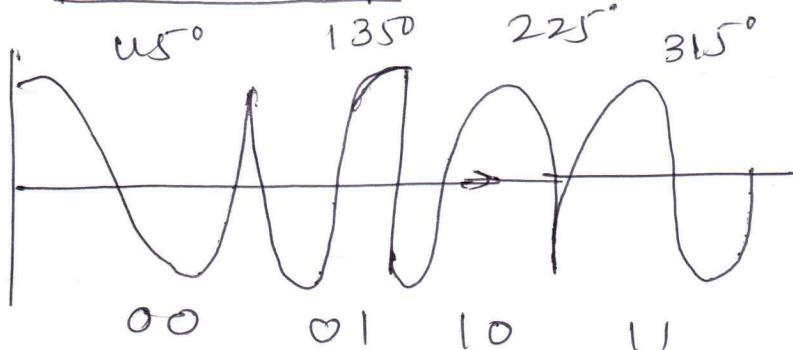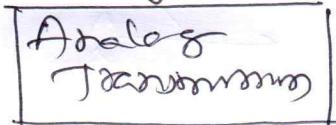
Transmitted symbol = $\cos \omega t, 135^\circ, 225^\circ, 315^\circ$, $I = a \cos \phi$ (real)



QPSK representation



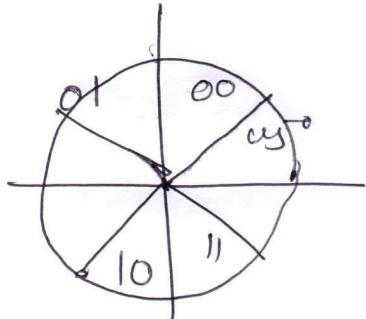$I + jQ = a \cos \phi$ (in magnitude part)




QPSK constellation diagram

multiple access techniques: provide communication to few multiple users over single channel: multiple mobile users share the allotted spectrum in the most effective manner

① FDMA \rightarrow Frequency division multiple access
Available band split into few small frequent channel and different channels are assigned to few different user

② TDMA \rightarrow Time division multiple access
various user can transmit at few same frequency band. Every user permitted to transmit specific time slot using common frequency band

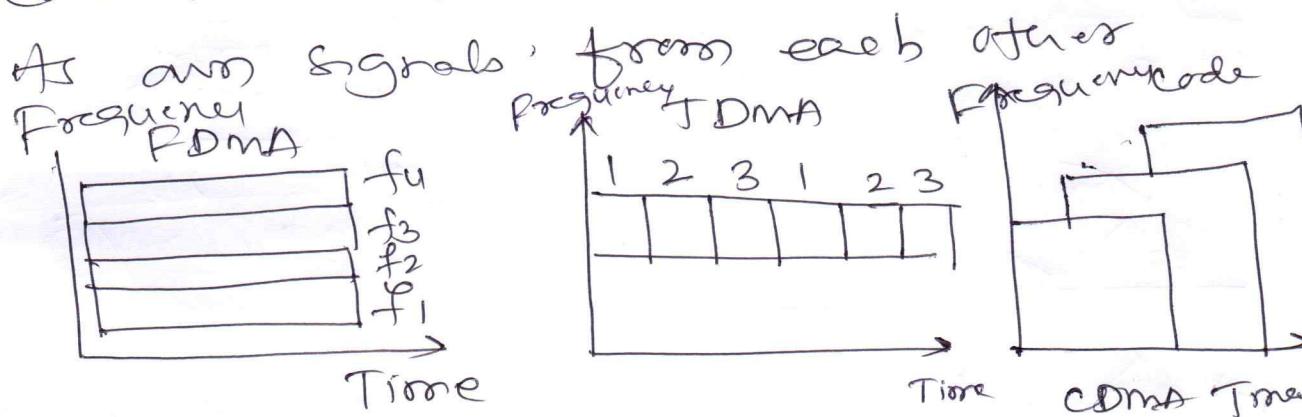③ Code division multiple access,
mobile receiver receives signals on the same
carrier frequency and at the same time
but the signals are labelled by using
codes, which allows mobiles to separate



(K.M. Wadephali)

Head of the Department
Dept. of Electronic & Communication Engg.
KLS V.D.I.T., HALIYAL (U.K.)

Dean, Academics
KLS VDIT, HALIYAL