

# **KLS Vishwanathrao Deshpande Institute of Technology**

(Accredited by NAAC with "A" Grade)

(Approved by AICTE, New Delhi, Affiliated to VTU, Belagavi)

(Recognized Under Section 2(f) by UGC, New Delhi)

Udyog Vidya Nagar, Haliyal - 581 329, Dist.: Uttara Kannada

Phone: 08284 - 220861, 220334, 221409, Fax: 08284 - 220813

[www.klsvdit.edu.in](http://www.klsvdit.edu.in) | [principal@klsvdit.edu.in](mailto:principal@klsvdit.edu.in) | [hodece@klsvdit.edu.in](mailto:hodece@klsvdit.edu.in)



## **DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

# **University / Model Question Paper** **Scheme & Solution**

Faculty Name	:	RANUL.C.M.
Course Name	:	Introduction to Electronic & Communication
Course Code	:	BESEK104C.
Year of Question Paper	:	2023-24 (Jan)
Date of Submission	:	12/04/2024

*Ranul.C.M.*

Faculty Member

*HOD*  
Head of the Department  
Dept. of Electronic & Communication Engg.

*VS*  
Dean (Acad.)

*KLS V.D.I.T., Haliyal (U.P.)*

# CBCS SCHEME

USN

BESCK104C/BESCKC104

## First Semester B.E./B.Tech. Degree Examination, Dec.2023/Jan.2024

### Introduction to Electronics and Communication

Time: 3 hrs.

Max. Marks: 100

**Note:** 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks , L: Bloom's level , C: Course outcomes.

<b>Module – 1</b>			<b>M</b>	<b>L</b>	<b>C</b>
<b>Q.1</b>	a.	What is Regulated power supply? With neat block diagram, explain the individual blocks.	8	L2	CO1
	b.	What is a rectifier? With neat circuit diagram and output waveforms, explain full wave bridge rectifier with capacitor filter.	8	L2	CO1
	c.	With circuit diagram brief out the operation of voltage doubler.	4	L2	CO1
<b>OR</b>					
<b>Q.2</b>	a.	Draw the circuit diagram of voltage regulator and explain the operation.	7	L2	CO1
	b.	Explain the concept of negative feedback amplifier with relevant equations and diagrams.	5	L2	CO1
	c.	Explain Frequency response of RC coupled amplifier.	8	L2	CO1
<b>Module – 2</b>					
<b>Q.3</b>	a.	Explain the Barkhausen criteria for oscillations. In wein bridge oscillator if $C_1 = C_2 = 200\text{nF}$ determine the frequency of oscillation when $R_1 = R_2 = 4\text{k}\Omega$ .	7	L3	CO2
	b.	With neat circuit diagram, explain the operation of ladder network oscillator.	7	L2	CO2
	c.	Explain the operation of single stage Astable multivibrator with its circuit diagram.	6	L2	CO2
<b>OR</b>					
<b>Q.4</b>	a.	List out the Ideal characteristics of an op-amp.	7	L2	CO2
	b.	Explain the following with respect to operational amplifier, i) Inverting amplifier ii) Integrator.	8	L2	CO2
	c.	An operational amplifier operating with negative feedback produces an output voltage of 2V when supplied with an input of $400\mu\text{V}$ . Determine the value of closed – loop voltage gain and express the answer in decibels.	5	L3	CO2
<b>Module – 3</b>					
<b>Q.5</b>	a.	Convert the following: i) $(\text{FACE})_{16} = (\quad)_{10}$ ii) $(65.45)_{10} = (\quad)_2$ iii) $(1111011011011.11011)_2 = (\quad)_8$ iv) $(2604.10546875)_{10} = (\quad)_{16}$	8	L3	CO3

	b.	Perform the following : i) $(1010100)_2 - (1000100)_2$ using 2's compliment. ii) $(4456)_{10} - (34324)_{10}$ using 10's compliment method.	6	L3	CO3
	c.	State and prove De – Morgan's theorems with its truth table.	6	L2	CO3

**OR**

Q.6	a.	Implement the Boolean functions using logic gates. i) $F_1 = x + y'z$ ii) $x'y'z + x'yz + xy'$	6	L3	CO3
	b.	Write the step by step procedure to design a combinational circuit.	6	L2	CO3
	c.	Implement full adder circuit with its truth table and draw the logic diagram of sum and carry.	8	L3	CO3

**Module – 4**

Q.7	a.	What is an embedded system? Compare embedded system and General computing systems.	7	L2	CO4
	b.	Explain classification of embedded systems.	7	L2	CO4
	c.	What is the difference between RISC and CISC processors?	6	L2	CO4

**OR**

Q.8	a.	Discuss major application areas of embedded systems with examples.	7	L2	CO4
	b.	Write short note on : i) Transducers ii) Sensors iii) Actuators.	6	L2	CO4
	c.	Write a short note on 7-segment LED display.	7	L2	CO4

**Module – 5**

Q.9	a.	With neat block diagram, explain modern communication system.	8	L2	CO5
	b.	Write a note on Hard wired channel and soft wired channel.	6	L2	CO5
	c.	Explain with a neat diagram, the concept of Radio wave propagation and its different types.	6	L2	CO5

**OR**

Q.10	a.	Explain Amplitude Modulation (AM) and Frequency Modulation (FM) with neat waveforms.	8	L2	CO5
	b.	List out the advantages of Digital communication over Analog communication.	6	L2	CO5
	c.	Explain different multiple Access Techniques.	6	L2	CO5


\*\*\*\*\*

## Module - 1

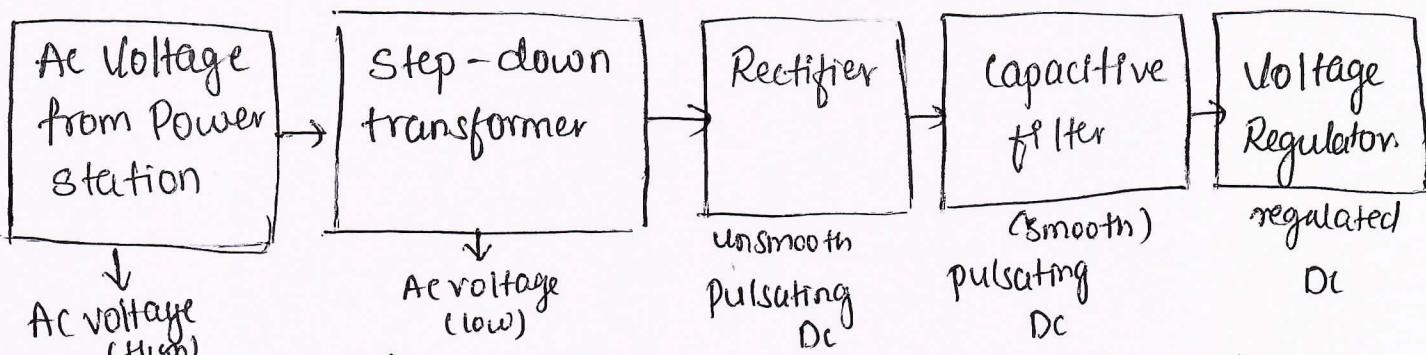- Q1 a. What is Regulated power Supply? with neat block diagram explain the individual blocks.

8M


→ Regulated power Supply: The basic diagram of DC power is Step-down transformer, Rectifier, reservoir/Smoothing filter, and a voltage regulator.



- \* Ac Voltage from power station is relatively high.
- \* Step down transformer is used to convert this to a low voltage
- \* Then the voltage from transformer is passed to rectifier using conventional silicon rectifier diodes which produces an unsmoothed DC or pulsating DC as output.
- \* This is then smoothed with the capacitive filter which gives smooth pulsating DC
- \* Then regulated by Voltage regulator. So that it remains relatively constant as size of variation into the both load current and incoming main voltage.

Rahil.c.m.

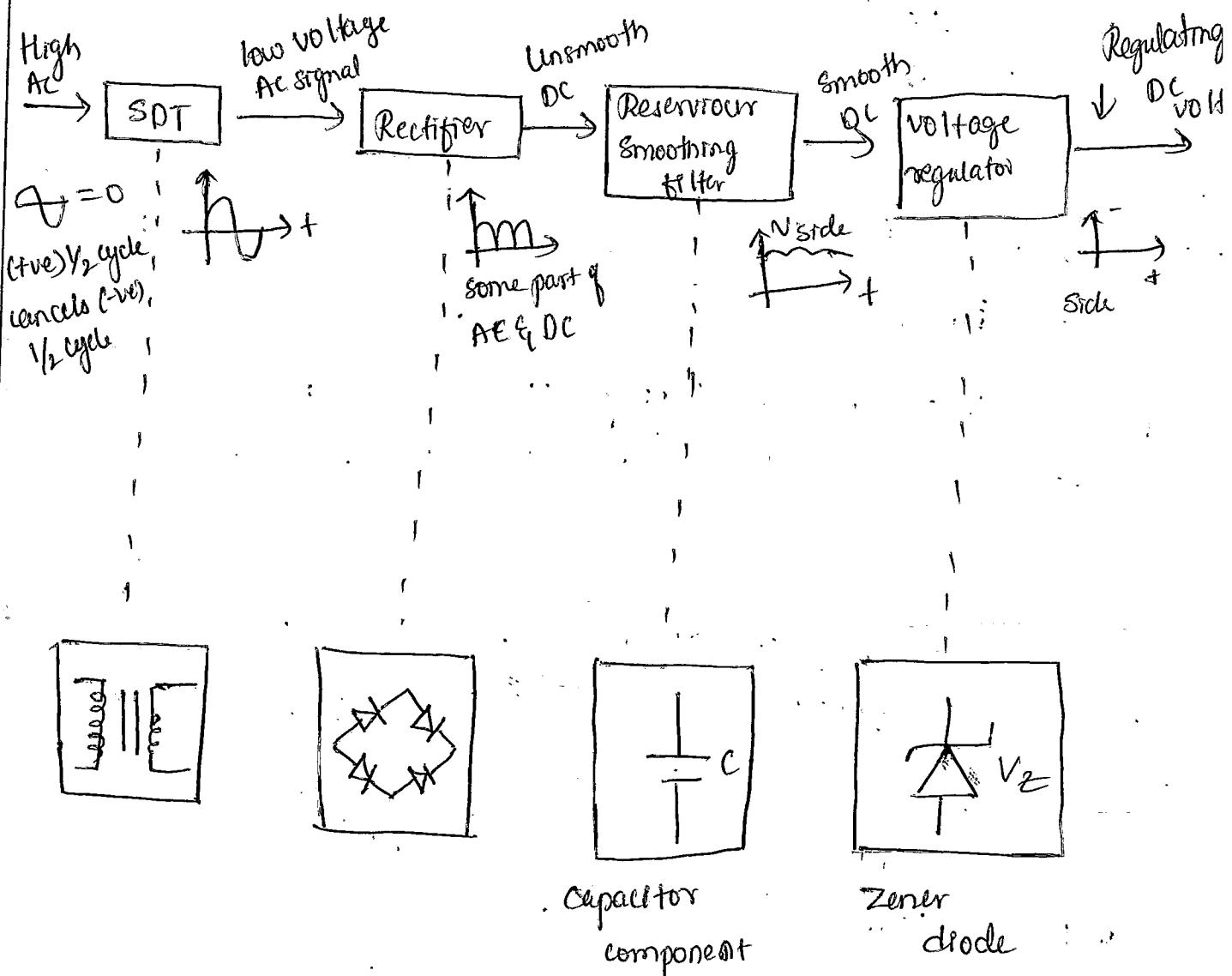~~MD~~  
Head of the Department  
Dept. of Electronic & Communication Engg.  
A.I.E.E.T.I.T. (Mumbai) (P.K.)



- \* The iron cored step down transformer feeds a rectifier arrangement.
- \* The output of the rectifier is then applied to high-value capacitor.
- \* This capacitor stores a considerable amount of charge and is being constantly discharged by rectifier arrangements.
- \* The capacitor also helps to a smooth out the voltage pulsating produced by the rectifier.
- \* Finally, a stabilising circuit provides a constant output voltage.


b. What is a rectifier? with neat circuit diagram and output waveforms, explain full wave bridge rectifier with capacitors or filter.

→ Rectifier: - Semiconductor diodes are commonly used to convert AC to pulsating direct current (DC) are referred to as rectifier.

or

8M

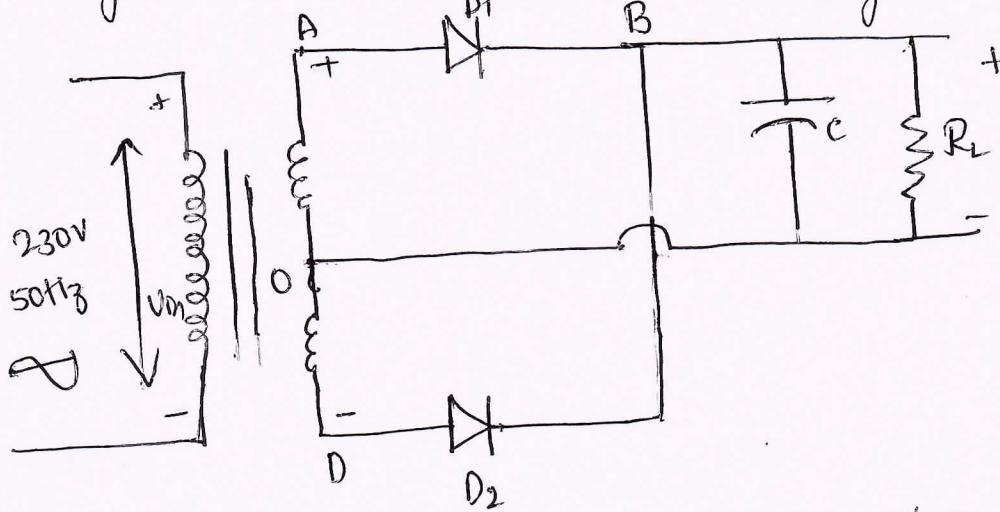Rectifier is the circuit which converts low voltage AC signal into unsmoothed DC signal voltage.




→ figure shows how a reservoir capacitor can be added to ensure that the output voltage remains at or near the peak voltage when where that diodes are not conducting.

→ This component operates in exactly the same way as for the half-wave circuit i.e. it charges to approximate 16.3V at the peak of the positive half wave.


→ In the circuit, the series resistance compresses the secondary forward voltage together with the resistance of the diode and connections.

Reell 1. m

- Hence C charges very rapidly as soon as either D<sub>1</sub> or D<sub>2</sub> starts to conduct.
- The time required for C to discharge is very much greater and discharge time constant is determined by the capacitive value and the load Resistance R<sub>L</sub>.
- In practice, R<sub>L</sub> is very much larger than the resistance of the secondary circuit and hence C takes an appropriate time to discharge.
- During this time, D<sub>1</sub> & D<sub>2</sub> will be reverse biased and held in a non-conducting state. As a consequence the only discharge path for C is through R<sub>L</sub>.

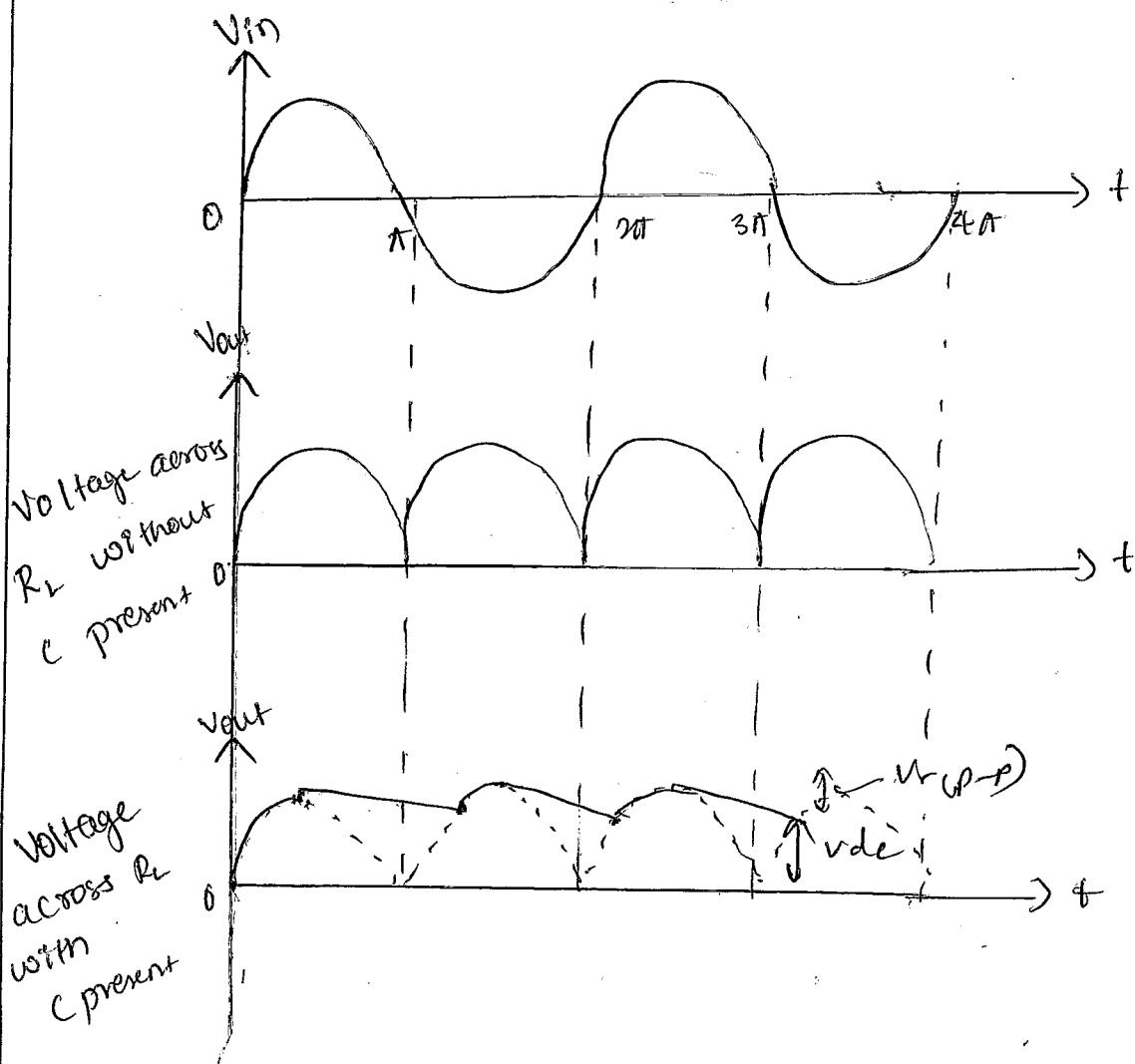

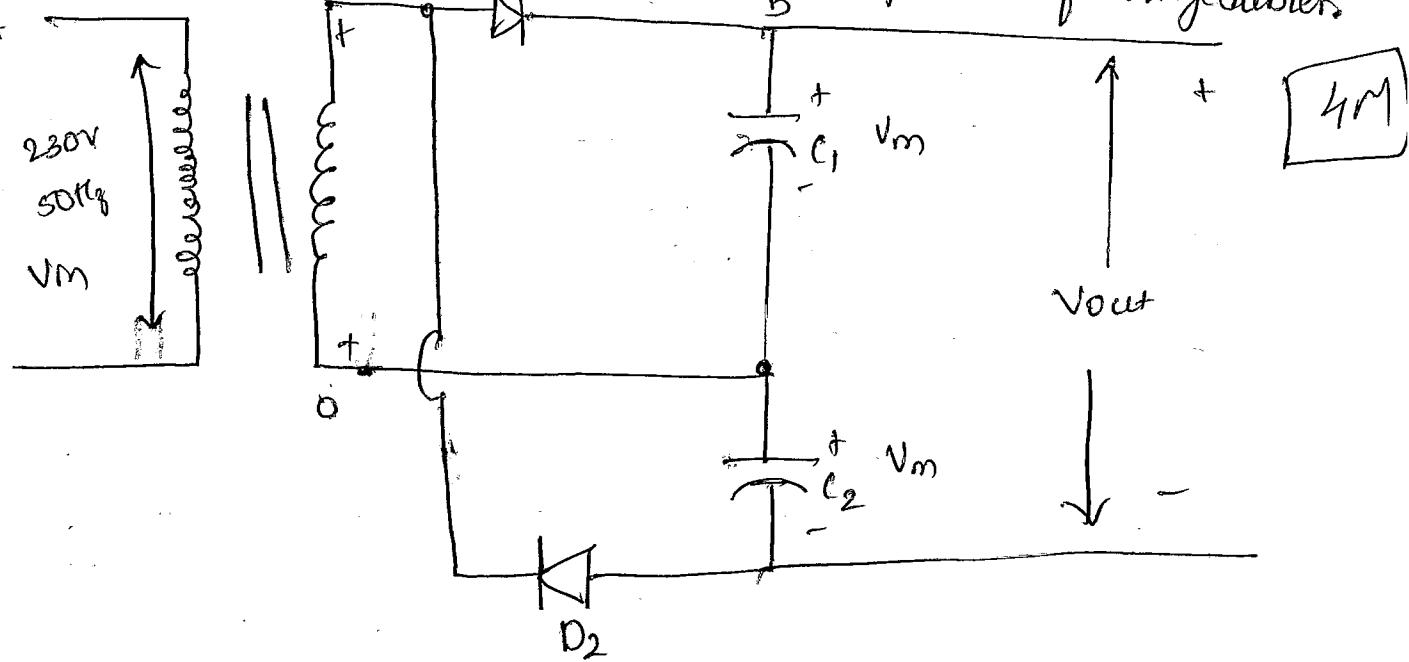C. With a circuit diagram brief out the operation of voltage doubler.



During the + half cycle diode D<sub>1</sub> is forward biased and D<sub>2</sub> is reversed biased

Apply KVL to Output Side

$$-V_{out_1} + V_{C_1} + V_{C_2} = 0$$

$$V_{out_1} = V_{C_1} + V_{C_2}$$

$$= V_m + 0$$

$$\boxed{V_{out_1} = V_m}$$

During negative half cycle diode D<sub>1</sub> is reversed biased diode D<sub>2</sub> is forward biased capacitor C<sub>2</sub> charges to the peak value of input voltage

Apply KVL to Output Side

$$-V_{out_2} + V_{C_1} + V_{C_2} = 0$$

$$V_{out_2} = V_{C_1} + V_{C_2}$$

$$= 0 + V_m$$

$$\boxed{V_{out_2} = V_m}$$

The output voltage thus is given by

Prob C.m

$$V_{out} = V_{out_1} + V_{out_2}$$


$$= V_m + V_m$$

$$= 2V_m$$

4M


(OR)

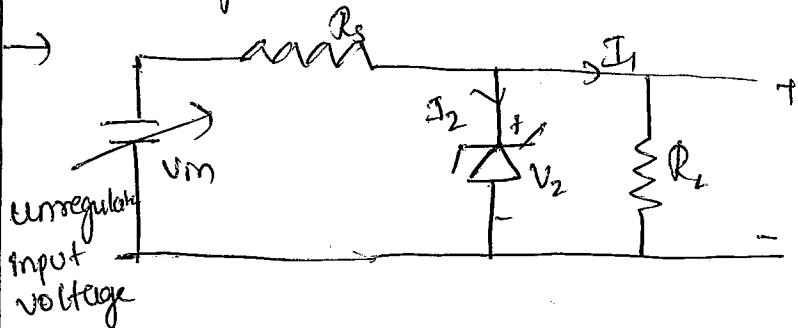- Q2. a. Draw the circuit diagram of voltage regulator and explain the operation.



7M

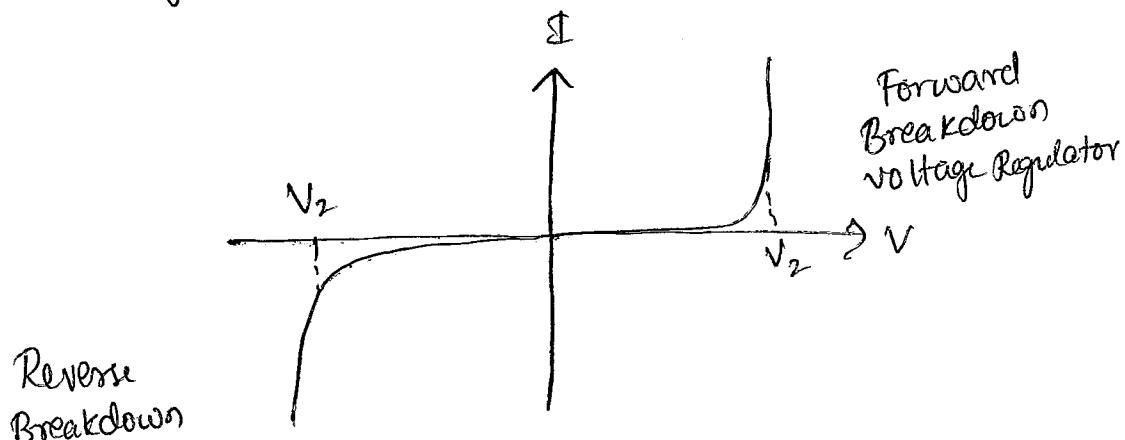Voltage Regulator is a circuit that maintains a constant dc output voltage irrespective of variation in the input line voltage or in the load.



$$V_o = \frac{V_{IN} \times R_L}{R_s + R_L}$$

\* If input voltage is less than regulating voltage then zener diode acts as off state the output voltage.

$$V_{out} = \frac{V_{IN} \times R_L}{R_s + R_L} \rightarrow ①$$


\* When input voltage exceeds the regulating voltage then zener diode is in the ON, state the output voltage [  $V_{out} = V_2$  ]  $\rightarrow ②$

The Max value of  $R_s$  can be determined from eqn

$$V_{out} = \frac{V_{IN} \times R_L}{R_s + R_L}, V_{out} = V_2$$

- b. Explain the concept of negative feedback amplifier with relevant equations and diagram.

5M

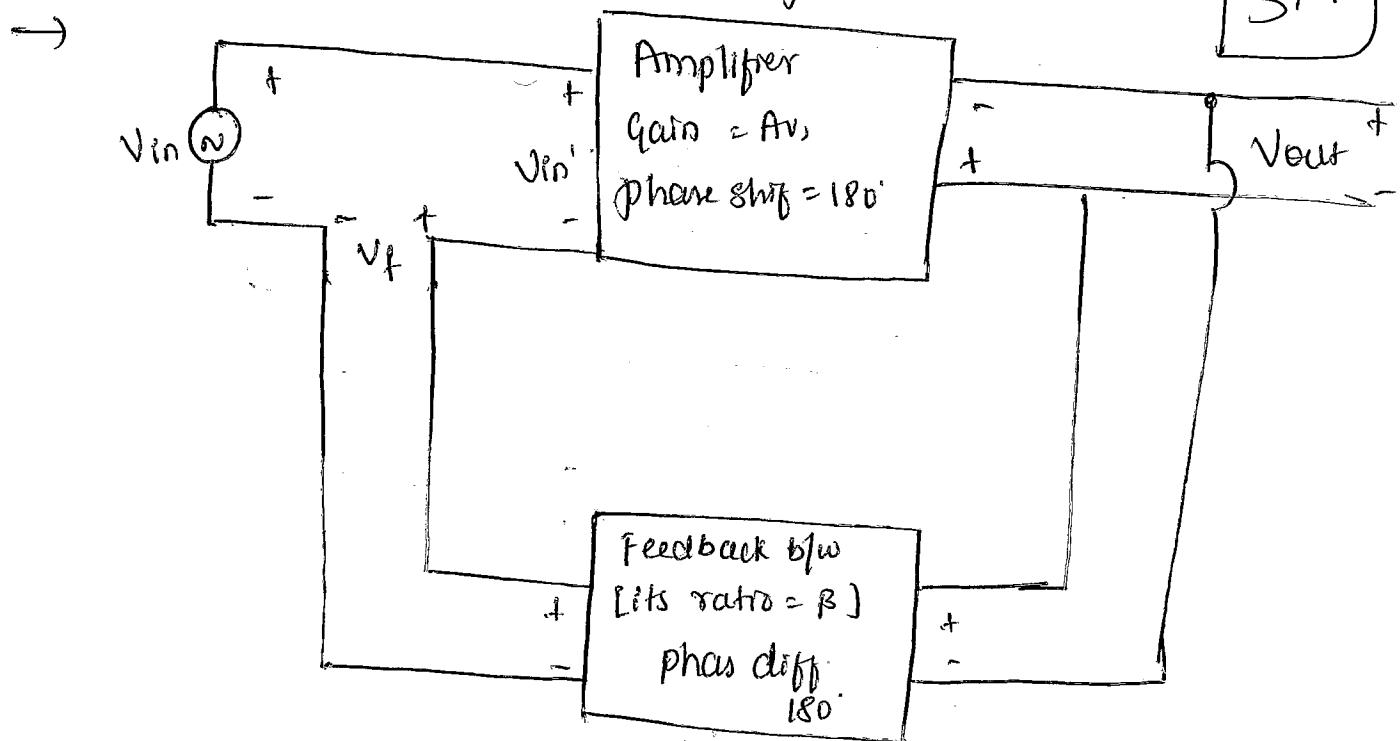

By applying KVL on input side  
we get,

$$-V_{in} + V_{in}' + \beta V_{out} = 0$$

$$V_{in}' = V_i - \beta V_{out}$$

$$V_{in} = V_{in}' + \beta V_{out}$$

$$V_{out} = A V_{in}'$$

$$V_{out} = A V \cdot V_{in}'$$

$$\because \beta V_{out} = V_f$$

$$\therefore A_V = \frac{V_o}{V_{in}}$$

$$V_o = V_{in}' A_V$$

overall gain of the amplifier :-

$$G = \frac{V_o}{V_i}$$

$$= \frac{A_V \cdot V_{in}'}{V_{in}' + \beta V_{out}}$$

$$= \frac{A_V \cdot V_{in}'}{V_{in}' + \beta \cdot A_V \cdot V_{in}}$$

$$= \frac{A_V \cdot V_{in}'}{V_{in}' [1 + A_V \cdot \beta]}$$

$$G_V = \frac{A_V}{1 + A_V \cdot \beta}$$

Rehd - C. M.

$$R_s + R_L = \frac{V_{IN} \times R_L}{V_{out}}$$

$$R_{S\max} = \frac{V_{IN} \times R_L - R_L}{V_{out}} \rightarrow ③$$

The min value of  $R_s$  can be

$$R_{S\min} = \frac{V_{IN} - V_2}{I_2} \rightarrow ④ \quad \therefore P_{Z\max} = I_2 V_2$$

$$= \frac{V_{IN} - V_2}{\left(\frac{P_{Z\max}}{V_2}\right)} = \frac{(V_{IN} - V_2) V_2}{P_{Z\max}}$$

$$R_{S\min} = \frac{V_{IN} V_2 - V_2^2}{P_{Z\max}}$$

Output resistance is the ratio of the change in output voltage to the output current.


$$R_{out} = \frac{\Delta V_{out}}{\Delta I_{out}}$$

Regulation is the ratio of change in output voltage to the change in the input voltage.

Regulation :  $\frac{\text{Change in Output Voltage}}{\text{Change in Input Voltage}} \times 100$

8M.

2.C.

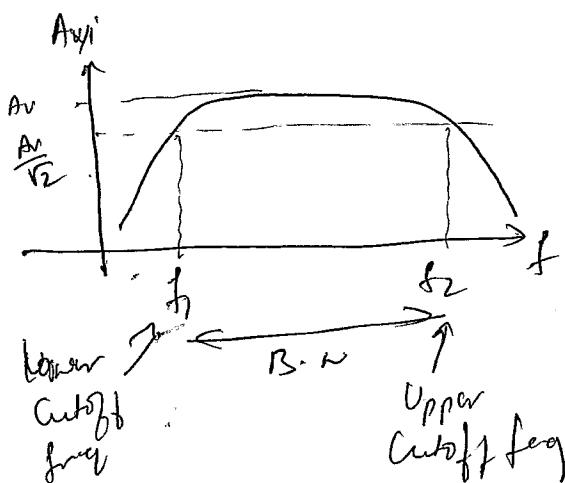

frequency Response indicates range of frequency over which gain drops 70.7% of its mid band value

- \* The graph shows frequency response of RC-Coupled Amplifier
- \* frequency below  $f_1$  and above  $f_2$  are blocked by the amplifier.

- Q3 a. Explain the Barkhausen criteria for oscillations. In wein bridge oscillator if  $C_1 = C_2 = 200\text{nF}$  determine the frequency of oscillation when  $R_1 = R_2 = 4\text{k}\Omega$
- Barkhausen criteria.


The overall loop gain of the circuit including Amplifier section & feedback section must be 1. The overall loop phase shift must be equal to  $0^\circ$  or  $360^\circ$ .

$$f = \frac{1}{2\pi \sqrt{C_1 C_2 R_1 R_2}} = \frac{1}{2\pi R C} = \frac{1}{2\pi \times 200\text{nF} \times 4\text{k}\Omega}$$

$$= 198.91\text{Hz}$$

- b. With neat circuit diagram, explain the operation of ladder network oscillator.

→

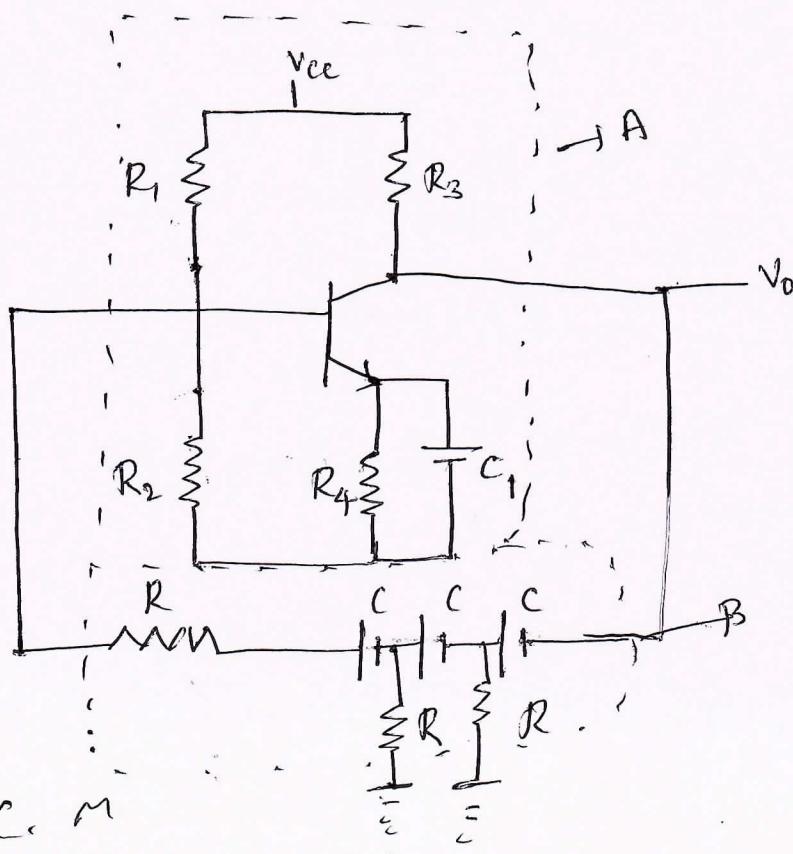


7M



- The above circuit shows, Laddar Network Oscillator. Here transistor Q<sub>1</sub>, along with R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub> & R<sub>4</sub> will acts as voltage divide biased circuit (Amplifier Section) providing phase shift of 180°.
- The feedback network three RC section where, each RC section with phase shift of 60° hence overall feedback section phase shift = 360°
- These overall with phase shift will become 360° or 0°
- The condition for Sustained oscillation is given by  
 $f = \frac{1}{2\pi R C \sqrt{2n}}$   
 $n = \text{no. of RC section}$
- we get  $f = \frac{1}{2\pi R C \sqrt{6}}$

- c. Explain the operation of single stage Astable multivibr with its circuit diagram.

16 M.

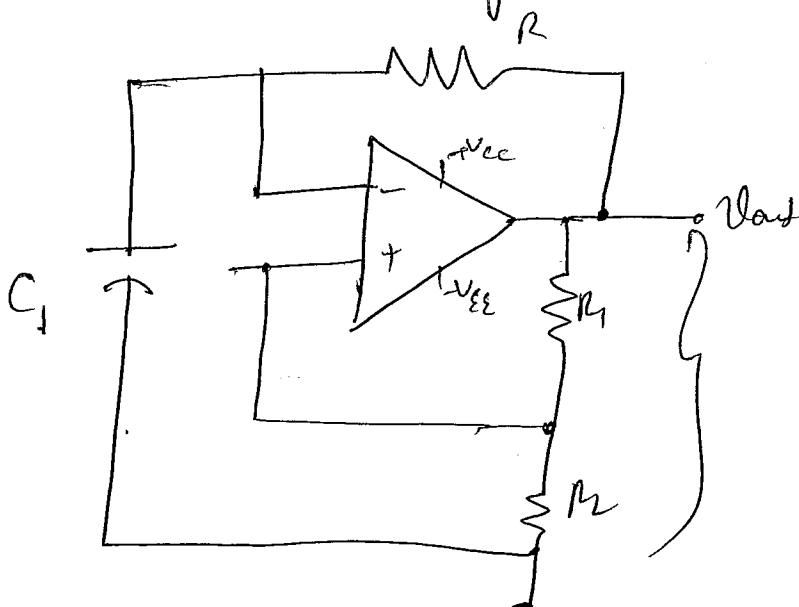

- Initially capacitor voltage,  $v = 0V$  Because of potential divider biased circuit  $R_1 \& R_2$  some + voltage is feed to Non Inverting amplifier terminal.
- Since NI Terminal is higher potential o/p OpAmp will be in positive now capacitor starts charging.
- When capacitor voltage exceeds the voltage at NET voltage, inverting terminal as at higher potential, o/p of opAmp will be negative saturation

(OR)

Q4.

- a. List Out the Ideal characteristics of op-amp.
- Ideal OpAmp:-
1. Open loop Voltage Gain should be very high (ideally  $\infty$ )
  2. The input resistance should be very high ( $\infty$ )
  3. o/p resistance should be very low.
  4. Full Power Bandwidth should be as wide as possible ( $\infty$ )
  5. Slew Rate should be as large as possible (ideally  $\infty$ )
  6. I/p offset should be as small as possible. (ideally 0)


Rehman C M

b. Explain the following with respect to operational amplifier.

i) Inverting amplifier

ii) Integrator.

8M

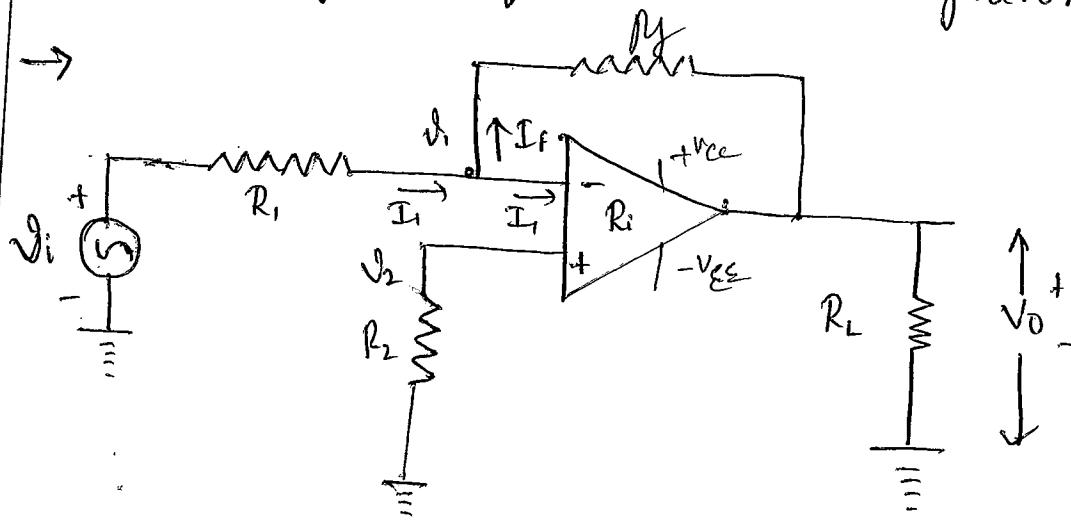

Applying KCL at  $V_1$

$$I_1 = I_r + I_f \rightarrow ①$$

Since,  $R_i = \infty$ ,  $I_r \approx 0$

$$\therefore I_1 = I_f \rightarrow ②$$

$$\frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_o}{R_f} \rightarrow ③$$

By concept of virtual ground

$$V_2 = V_1 = 0V \rightarrow ④$$

Substitute ④ in ③

$$\frac{V_{in}}{R_1} = -\frac{V_o}{R_f}$$

$A_v$  = open loop  
 $G_v$  = closed loop.


$$V_o = \left( -\frac{R_f}{R_1} \right) V_{in} \rightarrow ⑤$$

$\therefore A_v = -\frac{R_f}{R_1}$  The gain of inverting Amplifier is given by.

$$= \boxed{G_v = -\frac{R_f}{R_1}}$$


where (-) sign indicates  $180^\circ$  phase b/w input & o/p

$$[R_f = 10R_1]$$

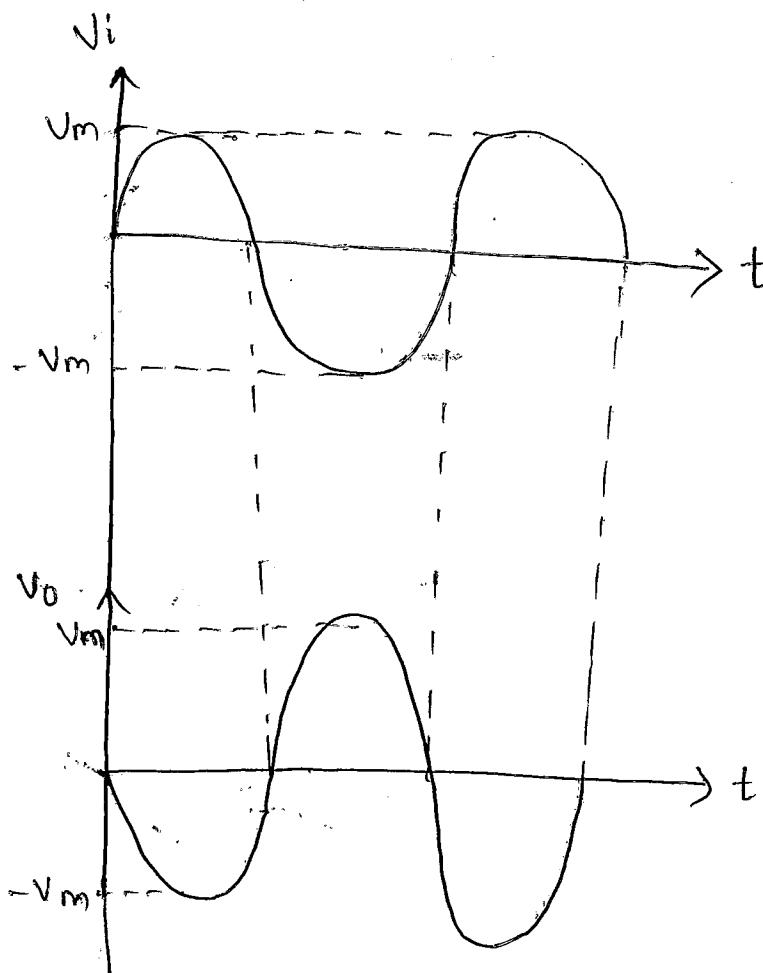


Here i/p signal is applied to I i/p terminal via  $R_1$ , Non I be ground via  $R_2$ .  $R_f$  is applied to connected b/w output & input side. Since i/p signal to inverting terminal is called Inverting Amplifier

#### ii) Integrator..:-

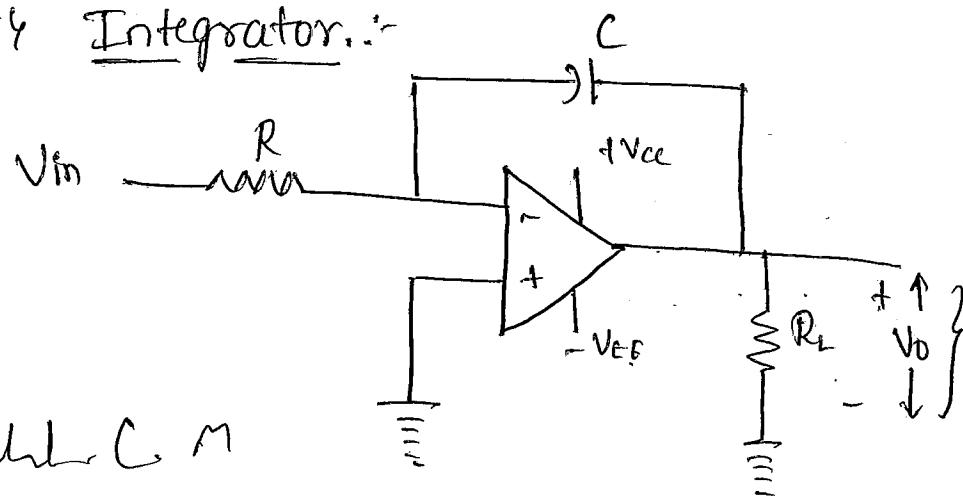

Dahl CM

Module - 2

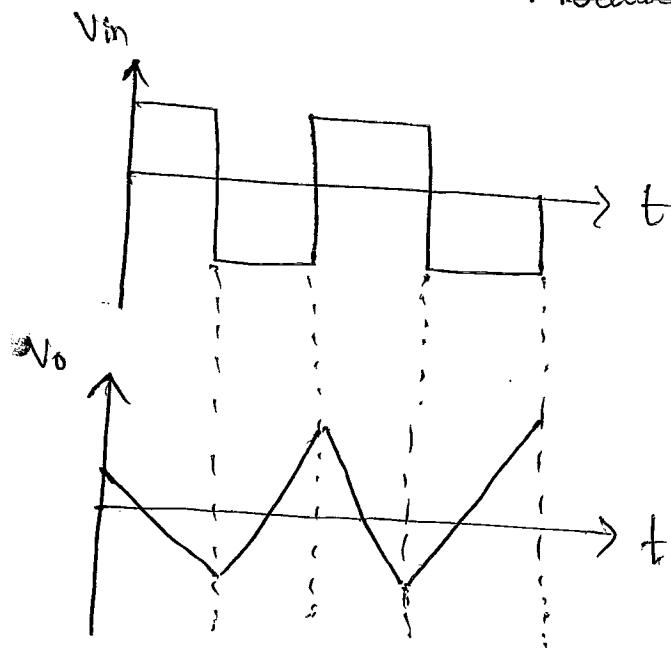

The circuit provides opposite function to that of difference here o/p is equivalent to area under the graph (input function).

If i/p v remain constant o/p voltage will ramp down depending on polarity of i/p.

C. An Operational Given,  $V_{in} = 400 \mu V$

5M

$$\text{Vout} = 2 \text{ V}$$

we have open loop voltage gain by.  $A_v = \frac{V_{out}}{V_{in}} = \frac{2 \text{ V}}{400 \times 10^{-6}}$

$$A_{v(2)} = 5000$$

$$A_{v(2)} = 20 \log 5000$$

$$A_{v(2)} = 73.98 \text{ dB}$$

$$A_{(2)} = 74 \text{ dB.}$$

## Module - 3

Q5

a. convert the following:-

$$\text{i) } (\text{FACE})_{16} = (?)_{10}$$

8 M

$$\rightarrow 15 \times 16^3 + 10 \times 16^2 + 12 \times 16^1 + 14 \times 16^0$$

$$= (64206)_{10}$$

$$\text{ii) } (65.45)_{10} = (?)_2$$

$$\begin{array}{r} \rightarrow 2 | 65 \\ 2 | 32 - 1 \\ 2 | 16 - 0 \\ 2 | 8 - 0 \\ 2 | 4 - 0 \\ 2 | 2 - 0 \\ 1 - 0 \end{array} \quad \begin{array}{l} 0.45 \times 2 = 0.9 \\ 0.9 \times 2 = 1.8 \\ 1.8 \times 2 = 3. \\ = (1000001.011)_2 \end{array}$$

$$\text{iii) } (1\underline{110}\underline{110}\underline{110}\underline{111}.\underline{110}\underline{11})_2 = (?)_8$$

$$\rightarrow 02131313(16)_8 \quad (17333.66)_8$$

$$\text{iv) } (2604, 10546875)_{10} = (?)_{16}$$

$$\begin{array}{r} \rightarrow 16 | 2604 \\ 16 | 162 - 12 \\ 16 | 10 - 2 \end{array} \quad \begin{array}{l} 0.10546875 \times 16 = 1.6875 \\ 0.6875 \times 16 = 11 \end{array}$$

$$= (A2C.B)_{16}$$

Rohit C. M

b. Perform the following :

6M.

if  $(1010100)_2 - (1000100)_2$ , using 2's complement.

$$\rightarrow M = 1010100 \quad N = 1000100$$

Step 1: Substituting r's complement for subtrahend

$$= r^n - N$$

$$= N = 1000100$$

$$n = 7$$

$$r = 2$$

$$= 2^7 - (1000100)_2$$

$$= (10000000)_2 - (1000100)_2$$

$$= (111100)_2$$

Step 2 : Add result to Relinear

$$\begin{array}{r} 1010100 \\ 0111100 \\ \hline 10010000 \\ \uparrow \\ \text{Ignore} \end{array} = \underline{\underline{(0010000)}_2}$$

ii)  $(4456)_{10} - (34324)_{10}$  Using 10's complement.

Step 1: Take r's complement of subtrahend

$$N = 34324$$

$$n = 5$$



$$r = 10$$

$$= r^n - N$$

$$= 10^5 - 34324$$

$$= 65676$$
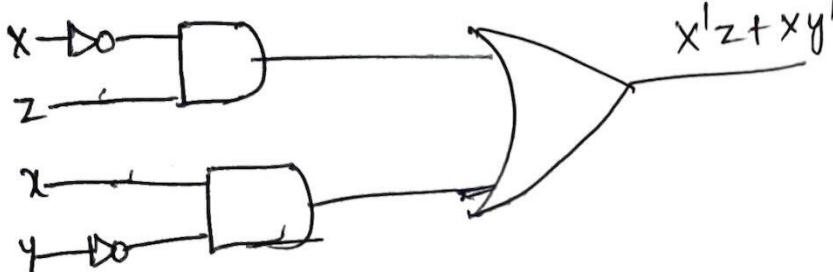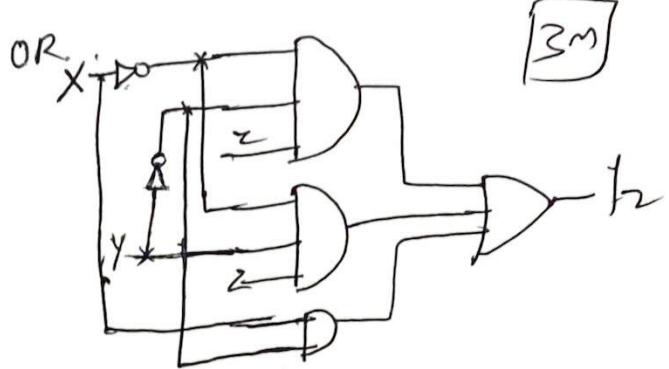
$$\begin{aligned}
 & \text{Simplify } \underline{x'y'z} + \underline{x'yz} + xy' \\
 &= x'z(\bar{y}+y) + xy' \\
 &= x'z \cdot 1 + xy' \\
 &= x'z + xy'
 \end{aligned}$$



b. write the step by step procedure to design a combinational circuit

6M

→ Step 1: Identifying the number of inputs to the circuits

Step 2: Identifying the number of output from the circuit

Step 3: Creating the truth-table i.e, we will create input column. and list all the possible combination

Step 4: Obtaining the Expression for output from the truth-table

Step 5: Simplifying the Expression for output boolean function and expression for each

Step 6: Implementing the circuit using Boolean function obtain by Step 5.

Step 2: Add result to minuend

$$\begin{array}{r} 04456 \\ 65676 \\ \hline 70132 \end{array}$$

Again r's complement for result

$$\begin{aligned} N &= 70132 & = r^n - N \\ n &= 5 & = 10^5 - 70132 \\ r &= 10 & = (-29868)_{10} \\ & & \equiv \end{aligned}$$


(OR)

Q6. a. Implement the Boolean functions using logic gates.

$$\text{if } F_1 = x + y'z$$

1. 6M

3m

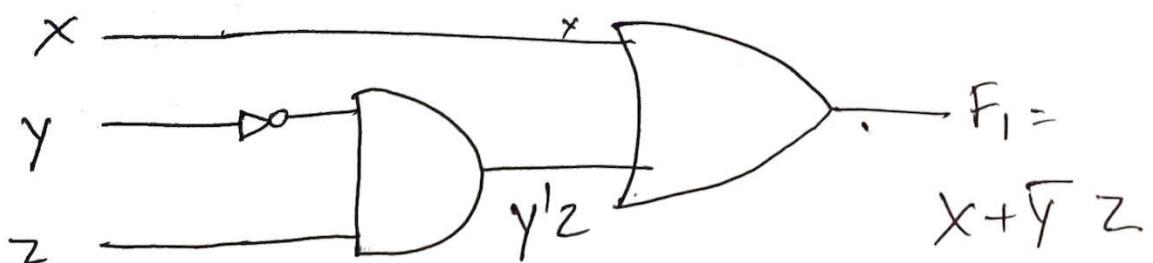

Sc.

Demorgan's Theorem

1. 6m

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

A	B	$A \cdot B$	$\overline{A \cdot B}$	$A + B$	$\overline{A+B}$	$\overline{A} \cdot \overline{B}$	$\overline{A} + \overline{B}$
0	0	0	1	0	1	1	1
0	1	0	1	1	0	0	1
1	0	0	1	1	0	0	0
1	1	1	0	1	0	0	0

c. Implement full adder circuit with its truth table and draw the logic diagram of sum and carry.

→ Full adder in a logical circuit that perform arithmetic sum of 3 input bit's

8M

ABC	Sum	Carry
000	0	0
001	1	0
101	1	0
011	0	1
100	1	0
101	0	1
110	0	1
111	1	1

The Expression of Sum is given by

$$S = A'B'C + A'BC' + A'BC + AB'C$$

$$S = C(A'B' + AB) + C'(A'B + AB')$$

$$\text{let } A'B + AB' = y \Rightarrow A \oplus B$$

$$A'B' + AB = y' \Rightarrow A \oplus B$$

$$(y') + C'y$$

$$C \oplus y$$

$$= C \oplus A \oplus B \quad [ \because y = A \oplus B ]$$

The Expression of Carry is given by

$$Cy = A'BC + AB'C + ABC' + ABC$$

$$= A'BC + AB'C + AB(C+C')$$

$$= A'BC + AB'C + A'B$$

$$= A'BC + AC(B'C+B)$$


$$= A'BC + AC(B+C)$$

$$= A'BC + AB + AC$$

$$= B(A'C + A) + AC$$

$$= B(A \oplus C) + AC$$

$$= AB + BC + AC$$

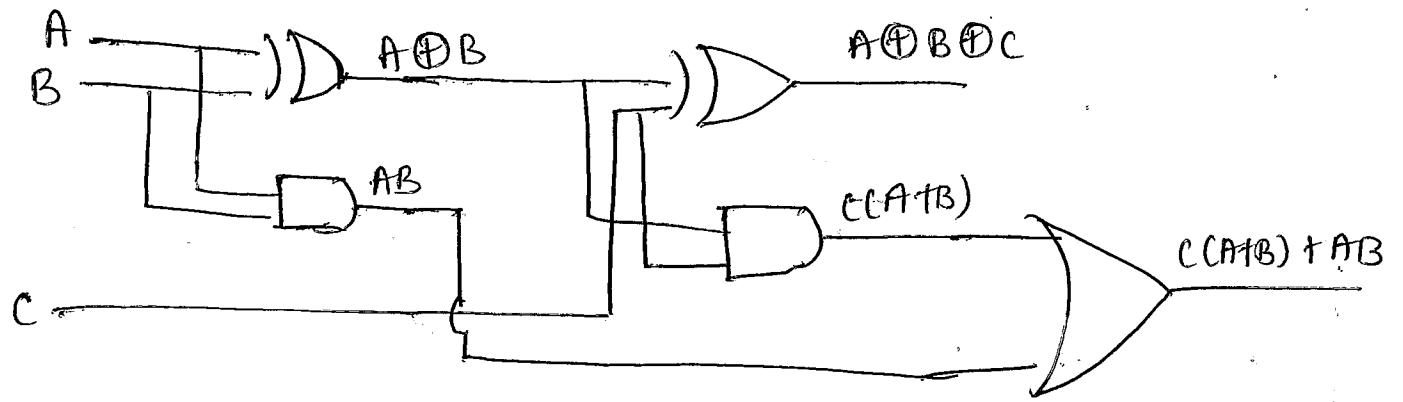

Q7. a. What is an embedded System? Compare embedded System and General computing Systems.

7M

→ An Embedded System is an electronic ~~specific~~ / ~~electro~~ function mechanical System designed to perform a specific function and it's combination of both hardware and firmware (software).

<u>General Purpose Computing System</u>	<u>Embedded System.</u>
<ul style="list-style-type: none"> <li>* It contains a General purpose operating System (GPOS)</li> <li>* Applications are alterable (programmable) by the user It is possible for the end user to reinstall the operating System</li> <li>* performance is the key deciding factor in the system</li> <li>* Less tailored towards reduced operating power requirements</li> <li>* Need not be deterministic in execution behaviour</li> <li>* A system which is a combination of generic hardware and a GPOS for executing various appln</li> </ul>	<ul style="list-style-type: none"> <li>* May or May not contain operating System for function</li> <li>* The software of ES is pre-programmed and it is non-alterable by the end user</li> <li>* Application Specific requirement are the key deciding factors Ex: performance, memory usage</li> <li>* Highly tailored to take advantage of power saving mode supported by hardware OS.</li> <li>* Execution behaviour is deterministic for certain type of ES</li> <li>* A system which is combination of special purpose hardware &amp; ES for executing specific set of appln</li> </ul>

Rohit C M

b. Explain classification of Embedded System.

17m

→ Based on Generation

- \* First Generation:- The early ES were built around 8 bit microprocessor & 4 bit microcontrollers
  - Ex: Digital telephone, Keypads

\* Second Generation:

These ES were built around 16 bit microprocessor & 8 or 16 bit microcontroller.

- \* The instruction set for second generation were much more complex & powerfull than the 1<sup>st</sup> generation.

\* Third Generation:

- \* These ES were built around 32 bit microprocessor & 16 bit microcontroller.

- \* A new concept of application & domain specific processor controller like Digital Signal. processor & Application Specific Integrated. Circuit [ASIC] come into picture

- \* The concept of instruction pipelining also evolved

- \* The instruction set for processor became more complex.

\* Fourth Generation.

- \* These generation Es are making use of high performance real time embedded operating system for their functioning

Ex: Small phone Device - Mobile Internal Device.

→ Based on Complexity & performance.

\* Small scale Es

- usually built around low performance & low cost 8 or 16 bit microprocessor / microcontroller.
- May or May not contain Os for its functioning.

\* Medium - Scale Es :

- usually built around medium performance & low cost 16 or 32 bit processor / controller.
- Usually contain Os for its functioning.

\* Large - Scale Es

- usually built around high performance & high cost 32 or 64 bit microprocessor / microcontrol & co-units / hardware

C. what is the difference between RISC and CISE processors?

RISC	CISE
* Lesser no. of instruction	* Greater no. of instruction.
* Instruction pipeling & increase execution speed	* No instruction pipelining feature
* Orthogonal instruction set	* Non-orthogonal Instruction set
* Operations are performed on register only	* Operations are performed on register or memories depending on the instruction
* A large no of registers available	* Limited no. of general purpose registers
* Signal fixed length instruction	* Variable length instruction
* with hardwired - Architecture	* Can be Harvard or Non-Newman Architecture.

Rohit C. M

(OR)

7 M

Q8 a. Discuss major application area of embedded System with example.

→ ① consumer Electronics : Camcorders, cameras etc.

② Household appliance : Television, DVD players, washing machine, fridge, microwave oven

③ Home automation & security System:

Air conditioners, sprinklers, intruder detection alarm, closed circuit, TV cameras.

④ Automotive industry : Anticlock breaking System (ABS) engine control, ignition System, automatic navigation system etc.

⑤ Telecom :- cellular telephones, telephone switches, handset multimedia appl' etc.

⑥ computer Networking System:- Network routers, switches hub, firewall etc.

⑦ Health Care: Different kinds of Scanners, EEG, ECG machines etc.

b. write short note on:

6 M

↳ Transducers: These are device that converts energy of form into equivalent electrical system vice-versa.

Ex: A loud speaker is a electrical current into auditable sound.

These may be used as both input & output device from the above mentioned example speaker is an output transducer - cer & microphones is an input transducer.

ii) Sensors: It is special kind of i/p transducer sensor is a device that converts a physical quantity into electrical signal. It can be categorised as active or passive.


- \* A active sensor generates current or voltage as output
- \* A passive require source of current or voltage as output for to convert physical quantity into electrical signal.

iii) Actuators:


It is an output transducer which converts an electrical quantity into physical quantity.

It is basically an output element.

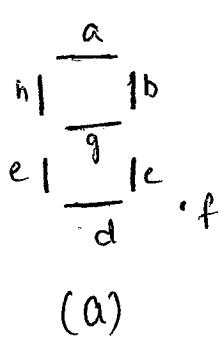
c. write a short note on 7-segment LED display? 7M



(a)

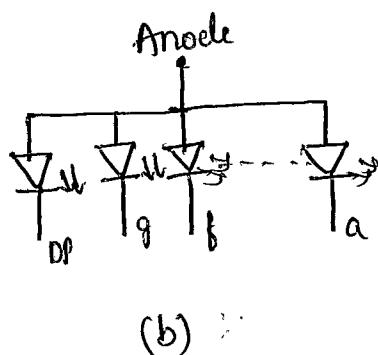

(b)

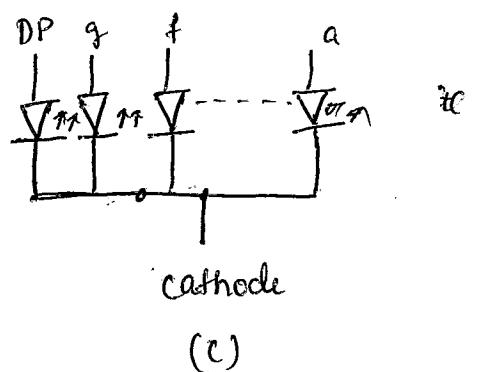

(c)

a) 7-segment LED display

b) common Anode LED display

c) common cathode LED display.

6

Rohit C. M

- \* It is an o/p device for displaying numeric value.
- \* It contains 8 LED segment arranged in special form
- \* Out of 8 LED's 7 LED's are used for displaying numeric character & 1 LED for displaying decimal pt.

7 Segment LED's are available in 2 configuration


at common anode

by common cathode.


In common anode configuration Anode of 8 LED's are connected together (to supply) hence in order to turn on LED should go low.

\* In common cathode configuration cathode of 8 LED's are connected together (to ground) hence in order to turn on LED the corresponding anode of the LED should go high.

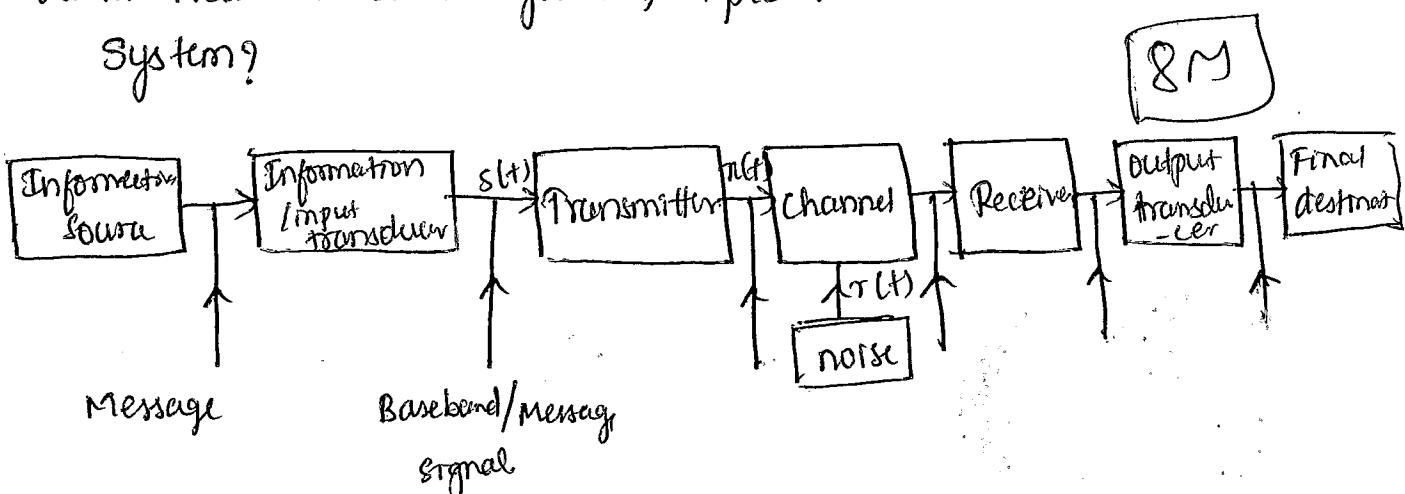Qq. a. With neat block diagram , explain modern communication System?



Generic Communication System

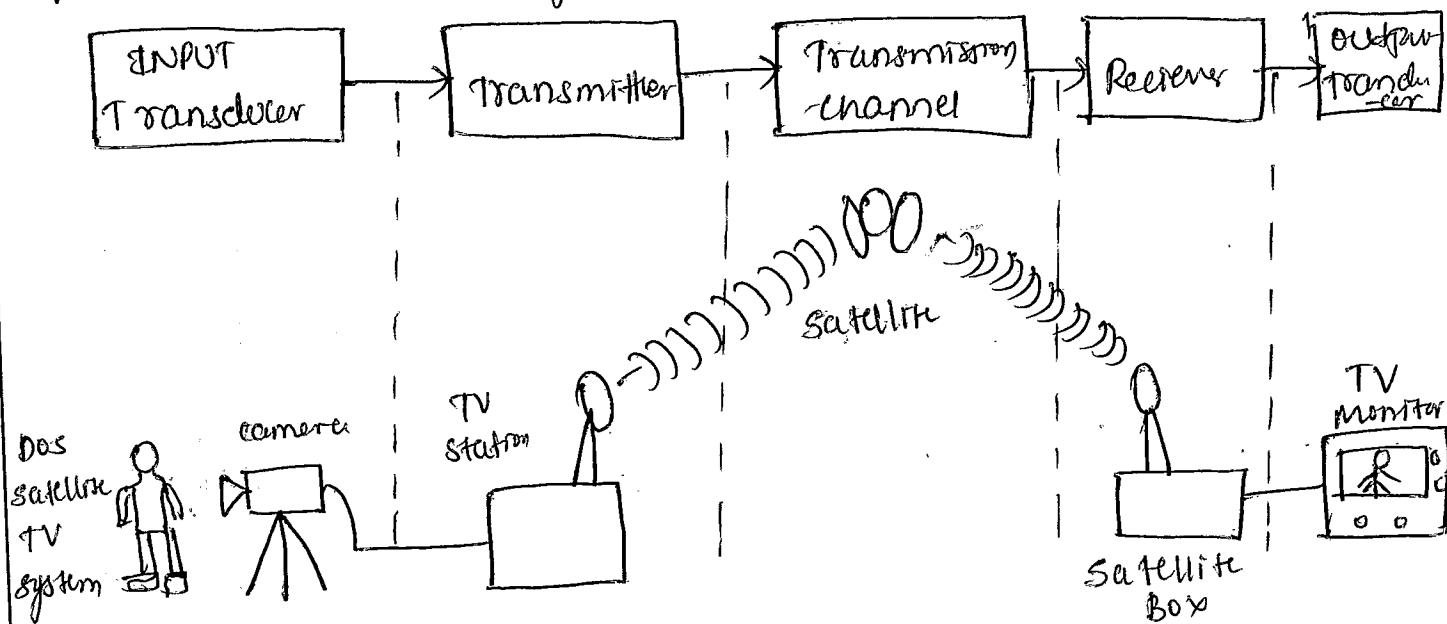

i) Information Source and Transducer.

Message or information originates in the information source may be in the form of sound picture, words .However, out of these messages only the desired message is selected and communicated.

Feb 1 CM

ii) Transmitter: The base band signal, output from the input transducer is applied to the input of the transmitter. The transmitter performs three operations: filtering, amplification and modulation.

iii) Channel or medium:

The term channel means the medium through which the message travel from the transmitter to the receiver.

iv) Receiver:

The main function of the receiver is to reproduce the original message signal.

v) Destination: Destination is the final stage which is used to convert an electrical message signal into its original form.

b. Write a note on Hard wired channel and soft wired channel.

a) Hardwired channel:-

Transmission lines: It is a conductive medium consisting of two or more conductors through which electrical signal are transmitted from transmitting point to receiver pt.

Ex: Twisted pair cables used in telephony, in which two conductors are twisted together for the purpose of improving electromagnetic compatibility.

6 M

waveguide: consisting of a hollow, metal tube of uniform cross high-frequency electrical signals with low losses.

wave guide: consisting of a hollow, metal tube of uniform cross-section used for transmitting electromagnetic waves.

optical fibre: consist of very thin hollow glass fibre through which signal is transmitted in the form of light energy.

by soft-wired channel

Natural resources which can be used as the transmission medium for signals.

Ex: Air or open space and sea water.

c. Explain with a neat diagram the concept of Radio wave propagation and its different types. 16m

→ Radio wave exhibit the properties of light with the velocity  $3 \times 10^8$  m/s. These are electromagnetic (EM) wave that consist of electric and magnetic field components, traversed perpendicular to one another in nature.

if Ground or surface wave.

Ground waves can be used for radio communication. Ground wave transmission is very affected irrespective of the atmospheric conditions.

Rec. C.m



Frequency range : 30 kHz to 3 MHz

Transmission distance : 100 to 1000 km


Example : AM radio.

ii) Space or tropo-spheric wave.

In space wave, radio wave move in the earth's troposphere within about 12 km over the surface of the earth.

Frequency range: 3 MHz to 30 MHz

Example : TV, transmission.

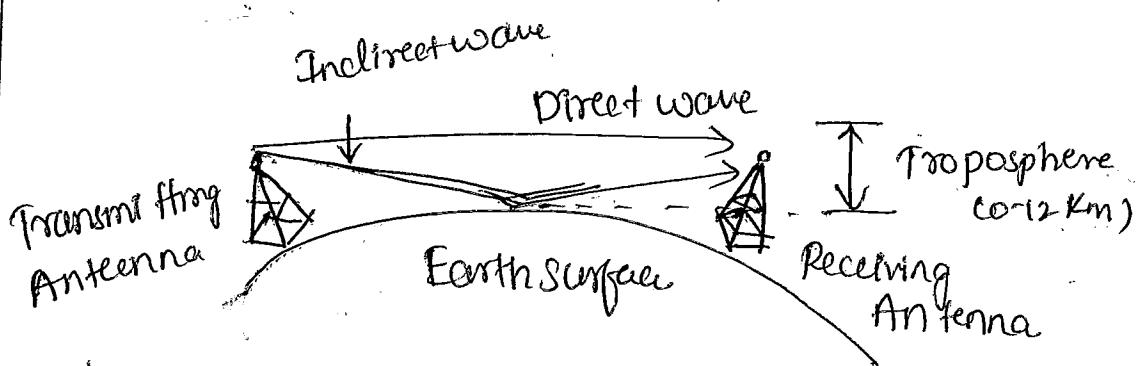


The space wave is made up of two components:  
at a direct or line-of-sight wave from the transmitting antenna to the receiving antenna and

## Sky Wave:

Radio wave transmitted from the transmitting antenna to the receiving antenna after reflection from the ionosphere

as shown.

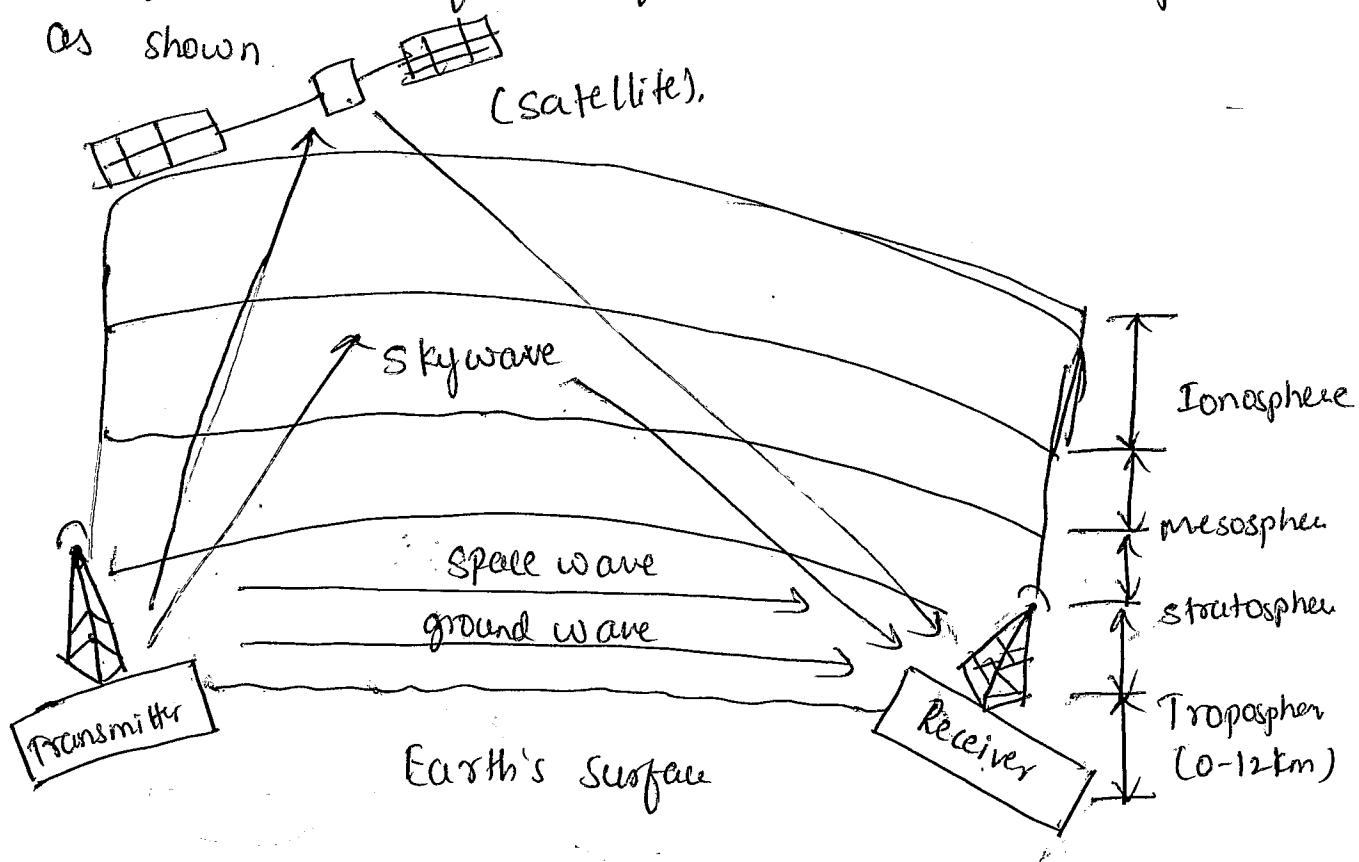

Sky wave is responsible for short wave transmission around the globe via successive reflections at the ionosphere and the earth's surface.

Advantages of sky wave propagation.

1. It supports large distance propagation
2. The frequency range of operation is considerably high.
3. Attenuation due to atmospheric conditions.

Disadvantage of sky wave

- \* long-distance propagation requires large-sized antenna


Rehl C M

(OR)

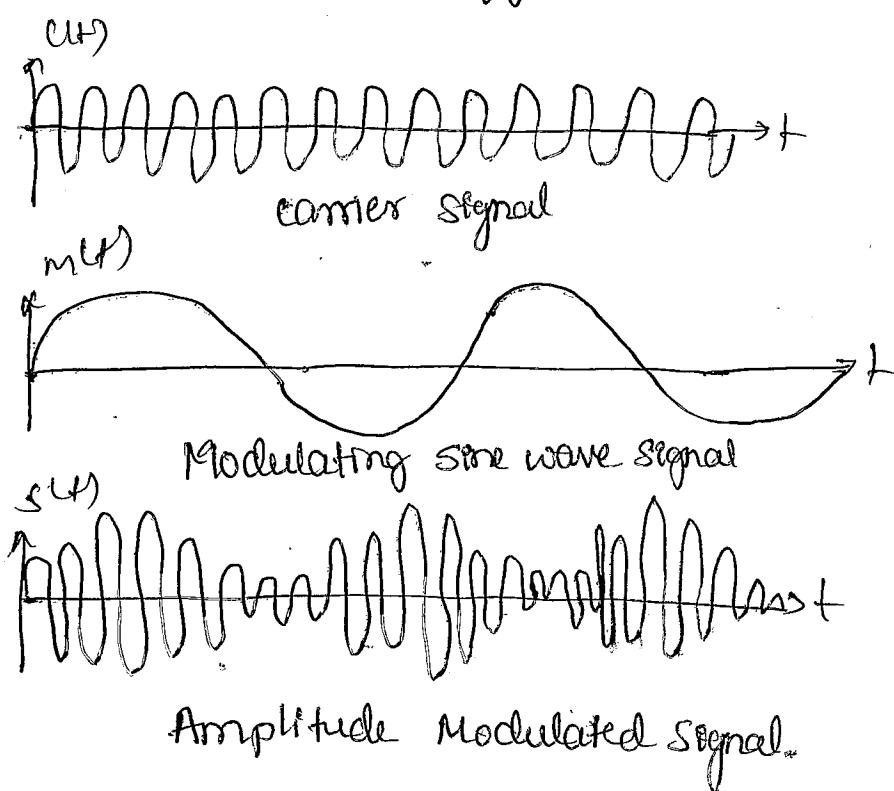10. a. Explain Amplitude Modulation (AM) and Frequency Modulation (FM) with neat waveforms.

8M

→ Amplitude Modulation (AM) : is the process in which the amplitude of the carrier signal is varied according to the instantaneous value of the message signal, whereas the frequency and phase are kept constant. It is as shown in the below figure



The first figure is the carrier wave, which is a high frequency signal and contains no information. Denoted as

$$c(t) = A_c \cos(2\pi f_c t)$$


The next one is the modulating wave, which is the message signal, contains information. Denoted as

$$m(t) = A_m \cos(2\pi f_m t).$$

The last one is the resultant amplitude modulated wave.  
 Mathematically, AM is denoted as

$$V_{AM} = V_c \sin \omega_c t + \frac{m_a V_c}{2} \cos(\omega_c - \omega_m)t - \frac{m_a V_c}{2} \cos(\omega_c + \omega_m)t$$

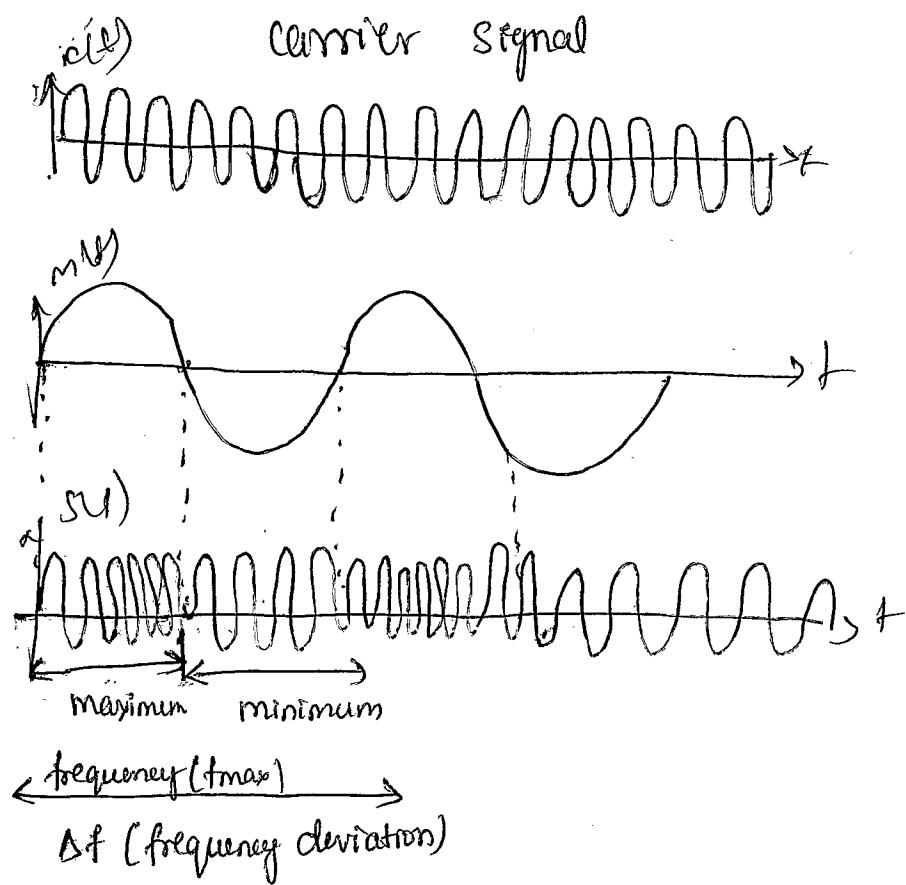Frequency Modulation: is defined as a process in which the frequency of the carrier is varied in accordance with the instantaneous value of the message signal, whereas the amplitude and phase are kept constant.



Mathematically, FM wave is denoted as

$$s(t) = A \sin [2\pi f_c t + m_f \sin(2\pi f_m t)]$$


$$\text{Modulation index } m_f = \frac{\Delta f}{f_m}$$

Rahul C. M


b. List out the advantages of Digital communication over Analog communication.

6m

### Analog Signals

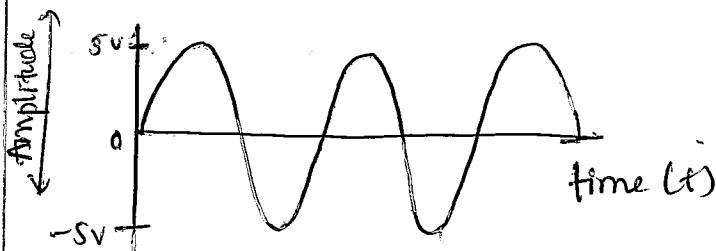

### Digital Signals

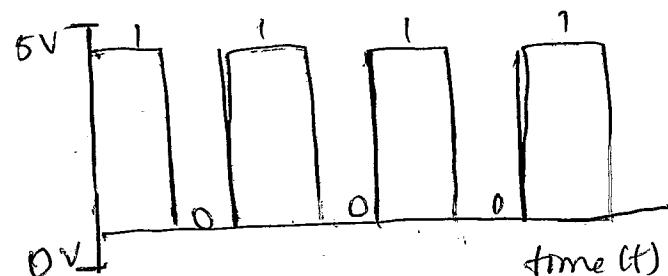

- \* Analog Signal is continuous and time varying
  - \* Trouble shooting is difficult
  - \* Easily affected by the noise
  - \* Analog signals use continuous value to represent the date usually in the form of sine wave
  - \* Analog Signal may be corrupted during data transmission
  - \* Analog Signals use more power
- Ex: Temperature, Pressure

- \* Digital signal have two or more states
  - \* Trouble shooting is easy
  - \* These are stable and less prone to noise
  - \* Digital signal use discrete value to represent date
  - \* Accuracy is immune from the noise
  - \* Digital signal are not corrupted during data transmission
  - \* Digital signal use less power
- Ex: Motor start, trip.

Q. Explain different multiple Access Techniques.

16 M

→ Multiple access is a technique to provide communication service to multiple users over a signal channel. It allows multiple mobile user share the allotted spectrum in the most effective manner.


### Frequency Division Multiple Access (FDMA).

Available frequency band is split into smaller frequency channels, and different channels are assigned to different user.


### Time Division Multiple Access (TDMA).

Various user can transmit at the same frequency band at different times. Every user is permitted to transmit only in specific time slot using a common frequency band.

FDMA

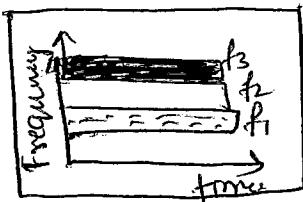

TDMA

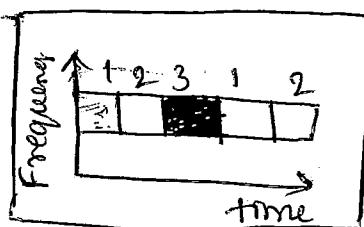

### Code Division Multiple Access (CDMA).

Mobile receive signals on the same carrier frequency and at the same time. But the signals are labelled by the use of codes.

Rahul. C M

## COMA

