

# CBCS SCHEME

USN

BEE303

## Third Semester B.E./B.Tech. Degree Examination, Dec.2023/Jan.2024

### Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.  
 2. M : Marks , L: Bloom's level , C: Course outcomes.

Module - 1			M	L	C
<b>Q.1</b>	a. With circuit diagram and waveform, explain Full Wave Bridge rectifier		6	L2	CO1
	b. Explain the analysis of Double end clipper circuit which clips both the peaks of an sinusoidal AC signal		7	L4	CO1
	c. For the circuit shown in Fig. Q1 (c) analyze and plot the waveform for $V_o$ for the input indicated.		7	L4	CO1

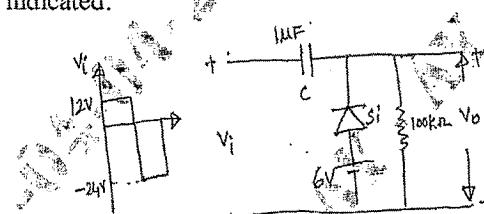


Fig. Q1 (c)

**OR**

<b>Q.2</b>	a. What are the factors affect the stability of operating point in a transistor?	5	L1	CO1
	b. Discuss the exact analysis of voltage divider bias to find $I_B$ , $I_{CQ}$ , $V_{CEO}$ and $I_{CSat}$ .	7	L4	CO1
	c. Design the values of $R_B$ , $R_E$ and $R_C$ for the emitter bias circuit shown in Fig. Q2 (c). Assume silicon transistor with $\beta = 100$ .	8	L3	CO1

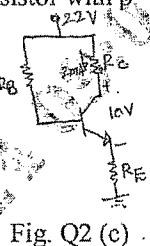


Fig. Q2 (c)

**Module - 2**

<b>Q.3</b>	a. Mention the advantages of h-parameters for transistor analysis.	5	L1	CO2
	b. Discuss the analysis of single stage amplifier, frequency response.	7	L4	CO2
	c. A transistor with $h_{ie} = 1.1 \text{ K}\Omega$ , $h_{fe} = 50$ , $h_{re} = 205 \times 10^{-4}$ , $h_{oe} = 25 \mu\text{A/V}$ is connected in CE configuration given in Fig. Q3 (c). Calculate $A_i$ , $A_{is}$ , $A_v$ , $A_{vs}$ , $R_i$ and $R_o$ .	8	L3	CO2

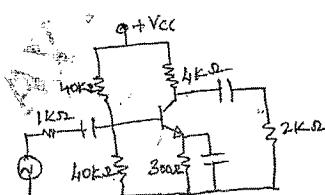


Fig. Q3 (c)

**OR**

<b>Q.4</b>	a.	Obtain the expression for Miller effect capacitance.	6	L2	CO2
	b.	Explain the high frequency analysis of BJT amplifier.	7	L2	CO2
	c.	Determine the lower cut-off frequency for the emitter follower using BJT amplifier with $C_S = 0.1 \mu F$ , $R_S = 1 K\Omega$ , $R_1 = 12 K\Omega$ , $R_2 = 4 K\Omega$ , $R_E = 1.5 K\Omega$ , $C = 0.1 \mu F$ , $\beta = 100$ , $V_{CC} = 15 V$ , $V_{BE} = 0.7 V$ , $f_0 = \infty$ and $h_{ie} = 1.04 K\Omega$ .	7	L3	CO2

**Module - 3**

<b>Q.5</b>	a.	With two stage cascaded amplifier explain the need of cascading.	6	L2	CO3
	b.	Write a note on cascade connection.	6	L1	CO3
	c.	Explain the DC analysis of Darlington emitter follower.	8	L2	CO3

**OR**

<b>Q.6</b>	a.	What are the characteristics of negative feedback amplifiers?	6	L1	CO3
	b.	An amplifier has mid-band voltage gain of 1000 with $f_L = 50 Hz$ and $f_H = 50 kHz$ , if 5% negative feedback is applied then calculate gain, $f_L$ and $f_H$ with feedback.	6	L3	CO3
	c.	Obtain expression for input and output resistance of voltage series amplifier.	8	L2	CO3

**Module - 4**

<b>Q.7</b>	a.	With waveforms, explain classification of power amplifiers.	6	L2	CO3
	b.	Derive an expression for second harmonic distortion using 2 point method for power amplifier.	6	L3	CO3
	c.	With circuit diagram and waveform, explain working of class B push pull amplifier. Also show that conversion efficiency is 78.5%.	8	L2	CO3

**OR**

<b>Q.8</b>	a.	With block diagram, explain the principle of working of an oscillator.	6	L2	CO3
	b.	Explain the principle of tuned oscillators. Also obtain expression for frequency of oscillations of Hartley oscillator.	6	L3	CO3
	c.	A quartz crystal has the following constants, $L = 50 mH$ , $C_1 = 0.02 pF$ , $R = 500 \Omega$ and $C_2 = 12 pF$ . Determine the values of $f_S$ and $f_p$ . If the external capacitance across the crystal changes from 5 pF to 6 pF, find the change in frequency of oscillations.	8	L3	CO3

**Module - 5**

<b>Q.9</b>	a.	Give the comparison between BJT and MOSFET.	6	L2	CO3
	b.	Explain the construction and working of n-channel JFET.	7	L2	CO3
	c.	Obtain the expression for $A_v$ , $Z_i$ and $Z_o$ for fixed bias common source amplifier using JFET.	7	L3	CO3

**OR**

<b>Q.10</b>	a.	Explain the characteristics of n-channel E-MOSFET. Also describe its working.	10	L2	CO3
-------------	----	---	----	----	-----

		b.	Design the fixed bias-FET common source amplifier shown in Fig. Q10 (b) to meet the following requirements. $A_v = 12$ , $Z_i = 10 \text{ M}\Omega$ , $V_{DD} = 40 \text{ V}$ .	10	L3	CO3
			<p>Fig. Q10 (b)</p> <p><math>I_{DSR} = 10 \text{ mA}</math></p> <p><math>V_P = -5 \text{ V}</math></p> <p><math>\tau_{OS} = 2.5 \mu\text{s}</math></p>			

Dec 2023 - Jan 2024



## Analog Electronic Circuits

Sub Code: BEE303.

Semester: 3<sup>rd</sup>

Prepared By: Prof. Ravindra Motekar.

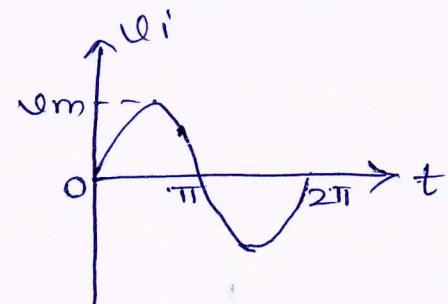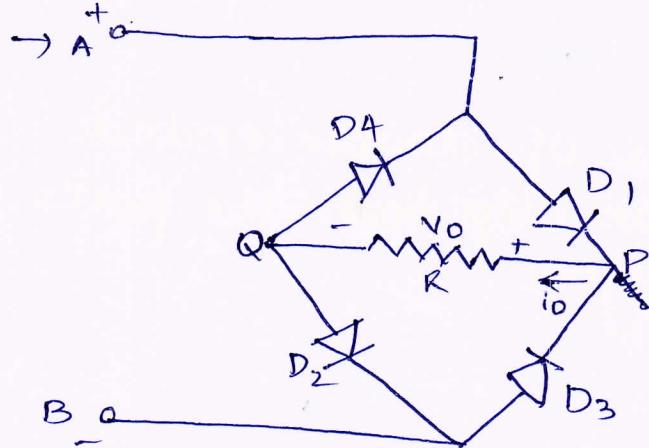1 a) With circuit diagram & waveform, explain Full wave Bridge rectifier.



Applying KVL we get

$$Vi - VK - V_0 - VK = 0$$

$$V_0 = Vi - 2VK$$


When  $Vi$  is at its peak value  $V_m$ , the peak level of  $V_0$  is.


$$V_{0m} = V_m - 2VK$$

$\therefore$  O/P Current is  $i_o = \frac{V_m - 2VK}{R} \sin \omega t$

$$\text{or } i_o = I_o \sin \omega t$$

$\therefore$  O/P Voltage  $V_0$

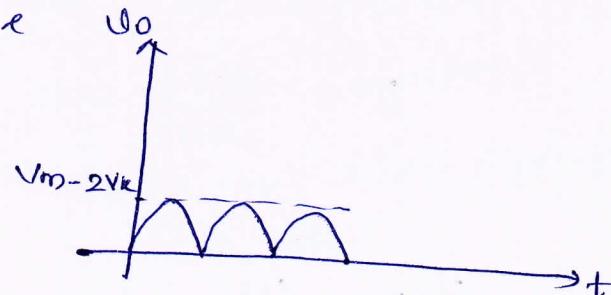

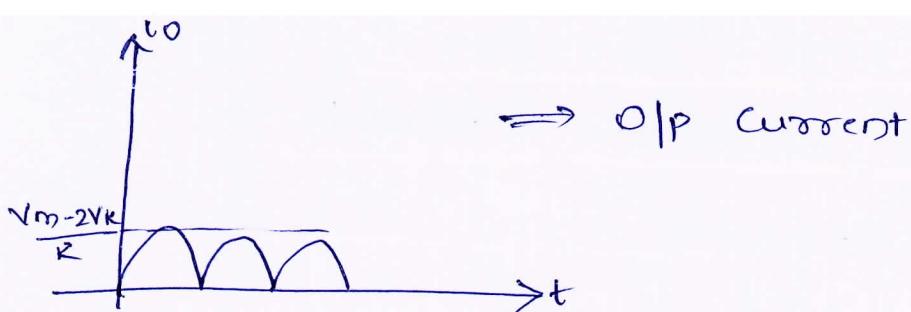

$$\text{W.E.T } V_{dc} = 0.636 V_m.$$



$$\therefore I_{dc} = \frac{V_{dc}}{R}$$

$$I_{dc} = 0.636 \left( \frac{V_m - 2V_K}{R} \right)$$

$$P.I.V = V_m - V_K$$

$$\text{for } V_m \gg V_K \quad P.I.V = V_m.$$

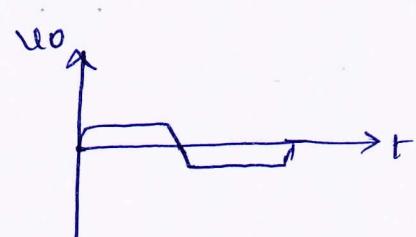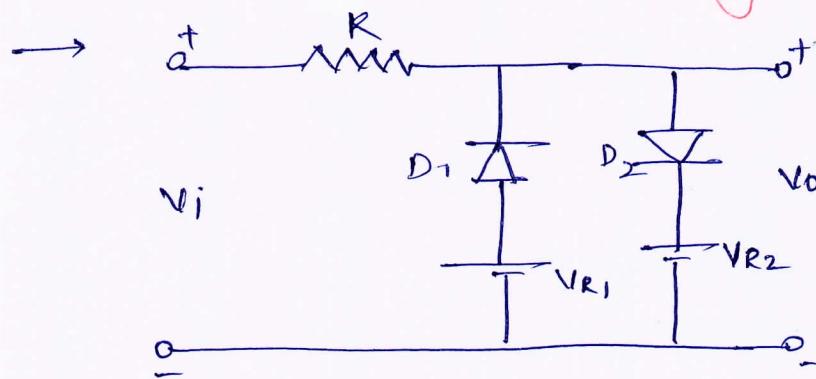b) Explain the analysis of double ended clipper ckt which can clip both the peaks of a sinusoidal AC signal.



Note that  $D_1$  conducts for  $v_i \leq V_{R1} - V_K$ .

$$\therefore v_o = V_{R1} - V_K \quad \text{for } v_i \leq V_{R1} - V_K$$

$$\text{slope} = \frac{\Delta v_o}{\Delta v_i} = 0$$

$D_2$  conducts for  $v_i \geq V_{R2} + V_K$ .

$$v_o = V_{R2} + V_K \quad \text{for } v_i \geq V_{R2} + V_K$$


$$\text{slope} = \frac{\Delta v_o}{\Delta v_i} = 0$$

for  $(V_{R1} - V_K) < v_i < (V_{R2} + V_K)$  neither  $D_1$  or  $D_2$  conducts

$$\therefore v_o = v_i$$

$$\text{slope} = \frac{\Delta v_o}{\Delta v_i} = 1$$

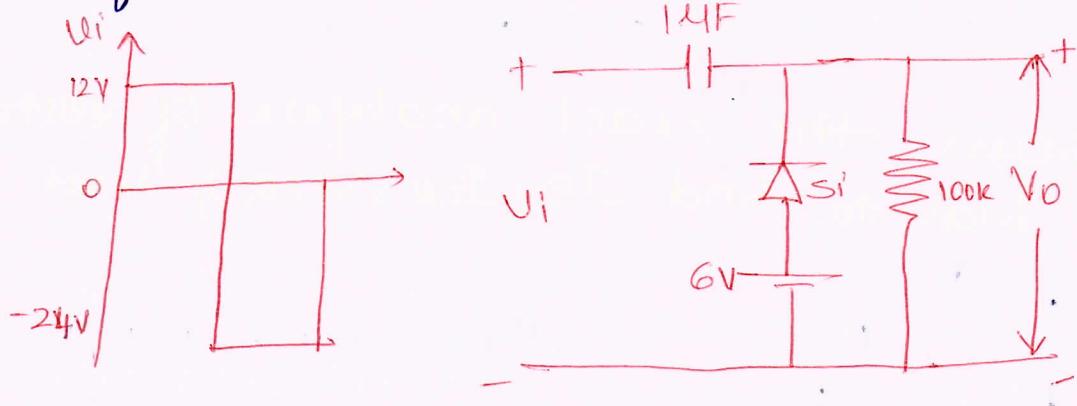1c) For the CKT shown analyse & plot the waveform for  $V_O$  for  $i_{IP}$  indicated.



$$\rightarrow V_I + V_C + 0.7 - 6 = 0$$

$$V_C = -V_I + 5.3$$

When  $V_I = -24V$ :

$$V_C = -(-24) + 5.3 = 29.3V$$


Now, when  $V_I = 12V$ ,

$$V_I + 29.3 - V_O = 0$$

$$V_O = V_I + 29.3$$

$\therefore$  when  $V_I = 12V$ ,  $V_O = 12 + 29.3 = 41.3V$

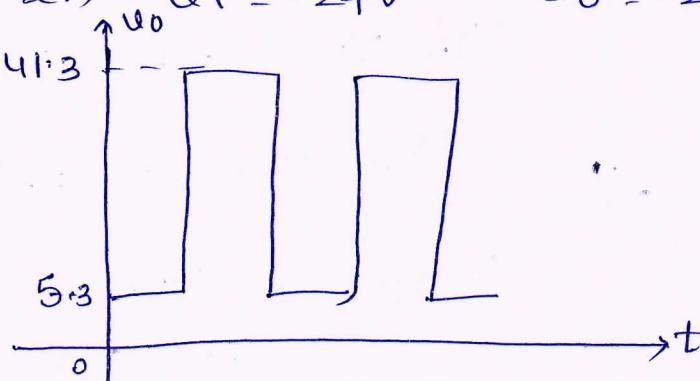when  $V_I = -24V$   $V_O = -24 + 29.3 = 5.3V$ .




2a) What are the factors that affect the stability of operating point in a transistor?

- $\rightarrow$  i) Variation of Reverse saturation current or leakage current. It increases (or doubles) by ~~by~~ for every  $10^\circ C$  rise in temperature
- $\rightarrow$  ii) Variation of  $V_{BE}$ : The Base to emitter

Voltage decreases by  $2.5\text{mV}$  for every  $1^\circ\text{C}$  rise in temperature.

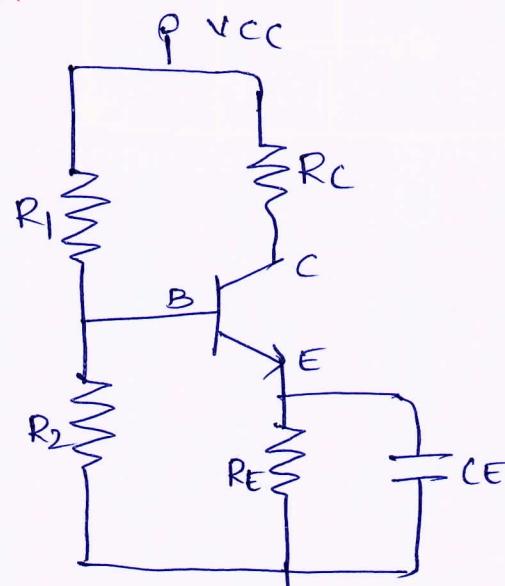iii)  $\beta$  varies w.r.t. temperature.

2b) Discuss the exact analysis of voltage divider bias to find  $I_B$ ,  $I_C$ ,  $V_{CEQ}$  &  $I_{CSAT}$ .



→ first we find  $R_{TH}$

$$R_{TH} = R_1 \parallel R_2$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

To, find  $V_{TH}$ ,

$$V_{TH} = V_{BE} I_R$$

$$V_{TH} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

$$\therefore V_{TH} - V_{BE} - I_B R_{TH} - I_E R_E = 0$$

$$V_{TH} - V_{BE} - I_B R_{TH} - (I_B + I_C) R_E = 0,$$

$$V_{TH} - V_{BE} - I_B R_{TH} - I_B (1 + \beta) R_E = 0,$$

$$\therefore I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E}$$

$$I_C = \beta I_B = \beta \left[ \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E} \right]$$


KVL for CE loop

$$V_{CE} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= V_{CC} - I_C R_C - (I_B + I_C) R_E$$

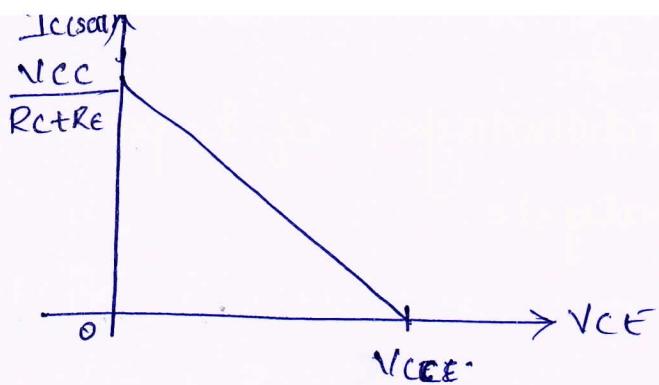
$$\boxed{V_{CE} = V_{CC} - I_C (R_C + R_E)}$$



$$\frac{V_{CE(sat)}}{I_C = 0} = V_{CC}$$

$$\frac{I_{C(sat)}}{V_{CE=0}} = \frac{V_{CC}}{R_C + R_E}$$

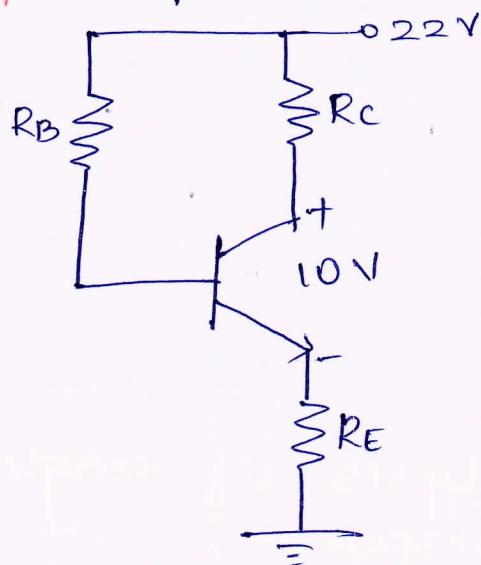20) Design values of  $R_B$ ,  $R_E$  &  $R_C$  for emitter bias ckt shown in fig. Assume Si transistor with  $\beta = 100$



$$R_C = \frac{V_{CC} - V_C}{I_C}$$

$$= \frac{12V - 7.6V}{2mA}$$

$$= 2.2k\Omega$$

$$I_E \approx I_C = 2mA$$

$$R_E = \frac{V_E}{I_E} = \frac{2.4V}{2mA} = 1.2k\Omega$$

$$I_B = \frac{I_C}{\beta} = \frac{2mA}{100} = 0.02mA$$

$$\therefore R_B = \frac{8.9V}{I_B} = \frac{8.9}{0.02mA}$$

$$= 445k\Omega$$


## Module 2

3a. Mention the advantages of h-parameters for transistor analysis.

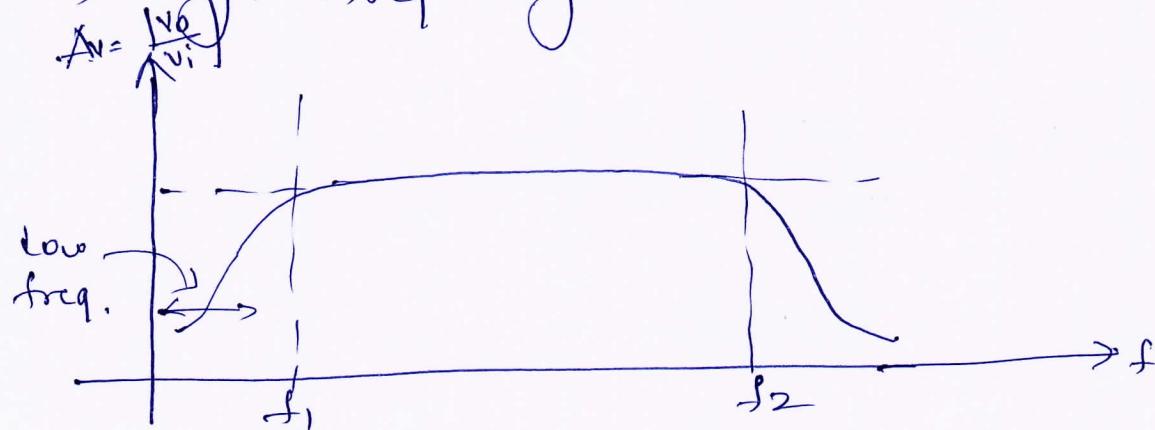- 1) h-parameters are useful in analysis & design of circuits using transistors.
- 2) At audio frequencies, h-parameters are real nos which makes calculations easy.
- 3) These parameters can be easily determined using transistor characteristic.
- 4) The models developed are independent of if transistor is n type or p type.
- 5) h-parameters are graphically obtained for one config<sup>n</sup>, other config<sup>n</sup> can also be obtained easily.

3b. Discuss Analysis of single stage Amplifier freq response.


- The freq range is divided into 3 regions.
  - 1) low freq region.
  - 2) mid freq region.
  - 3) High freq region.



The drop in gain at low freq is due to the coupling capacitors ( $C_s$  &  $C_{s2}$ ) &  $C_E$


At high freq, drop in gain is due to internal wiring capacitance & stray capacitance

2)

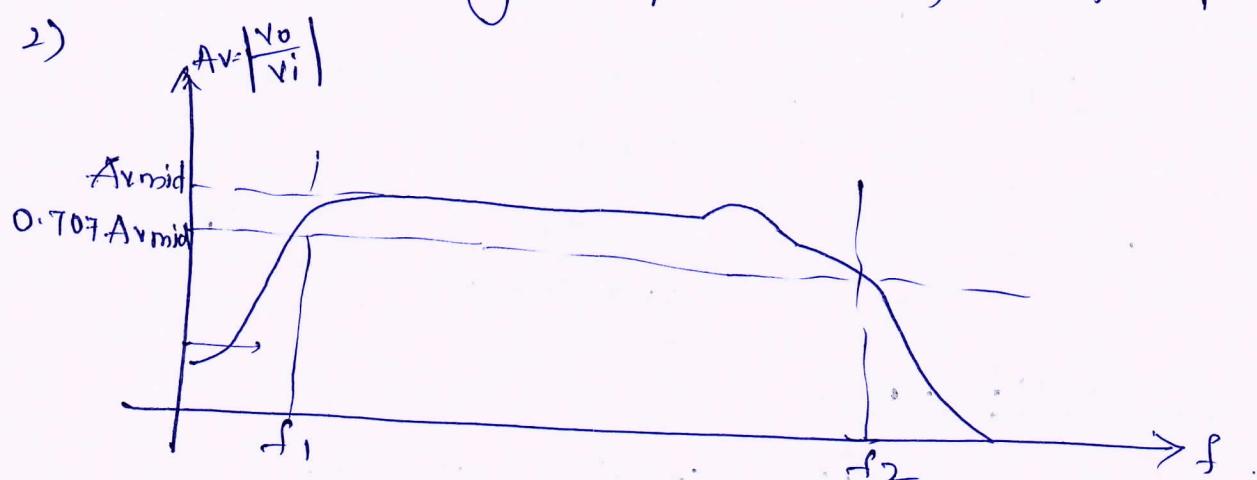

The magnetizing inductive reactance of the core is  $X_L = 2\pi f L$  & at low freq, the gain drops due to small value of  $X_L$ . At  $f=0$ , there is no change in flux in the core.

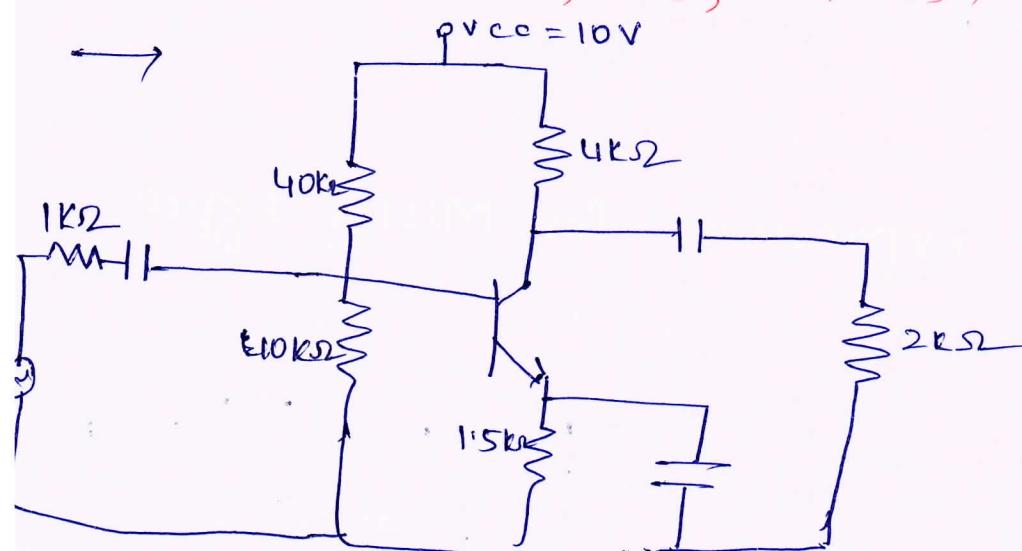3(c) A transistor with  $\beta_{ie} = 1.1K\Omega$ ,  $\beta_{fe} = 50$ ,  $h_{re} = 205 \times 10^4$ ,  $h_{oe} = 25.4A/V$  is in CE config. Calculate  $A_i$ ,  $A_{is}$ ,  $A_v$ ,  $A_{vs}$ ,  $R_i$  &  $R_o$ .



$$\beta R_E \geq 10R_2$$

$$10R_2 = 10(10k) = 100k\Omega$$

$\therefore$  we can use approximate analysis.

$$V_B = \frac{V_{CC}R_2}{R_1 + R_2} = \frac{(10V)(10k)}{39k + 10k} = 2.04V$$

$$V_E = V_B - V_{BE}$$

$$= 2.04 - 0.7$$

$$= 1.34 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{1.34 \text{ V}}{1.5 \text{ k}\Omega} = 0.893 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{0.893 \times 10^3} = 29.1 \Omega$$

$$\rightarrow R_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$= 39 \text{ k} \parallel 10 \text{ k} \parallel (100) (29.1) = 2.13 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_i} = -R_o \parallel R_L$$


$$R_o = R_C \parallel r_o = 4 \text{ k}\Omega \parallel 20 \text{ k}\Omega = 3.33 \text{ k}\Omega$$

$$A_v = -\frac{2149 \text{ k}}{29.1 \Omega} = -85.56$$

$$A_{vS} = A_v \left( \frac{R_i}{R_i + R_S} \right) = -(85.56) \times 0.68 \\ = -58.18$$

$$R_{SD} =$$

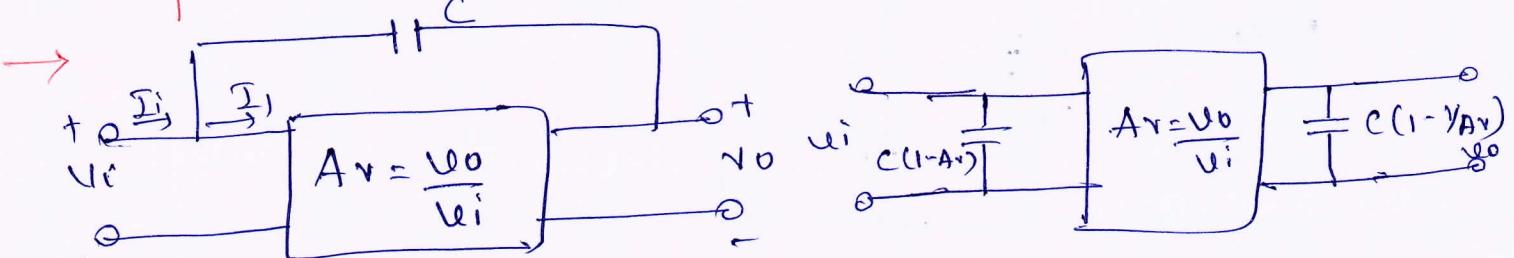4a) Obtain the expression for Miller Effect Capacitance.



$$\text{let } I_i = I_1 + I_2$$

$$I_i = \frac{V_i}{Z_i} \quad \& \quad I_1 = \frac{V_i}{R_i}$$

$$\therefore I_i = \frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{(1-A_v)V_i}{X_C}$$

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{(1-A_v)}{X_C}$$

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{CM}}$$

$$\frac{1}{2\pi f C_M} = \frac{1}{(1-A_v)2\pi f C}$$

$$\therefore \frac{1}{C_M} = \frac{1}{(1-A_v)C}$$

or  $C_M = (1-A_v)C$

Applying KCL we have

$$I_o = I_1 + I_2$$

$$I_1 = \frac{V_o}{R_o} \quad \& \quad I_2 = \frac{V_o - V_i}{X_C}$$

$$\therefore I_o = \frac{V_o - V_o/A_v}{X_C} = \frac{V_o (1 - Y_{A_v})}{X_C}$$


$$\& \frac{I_o}{V_o} = \frac{1 - Y_{A_v}}{X_C}$$

$$\therefore X_{CMo} = \frac{X_C}{1 - Y_{A_v}}$$

$\therefore C_{MO} = C(1 - Y_{A_v})$

Hb) Explain the high frequency analysis of BJT amplifier

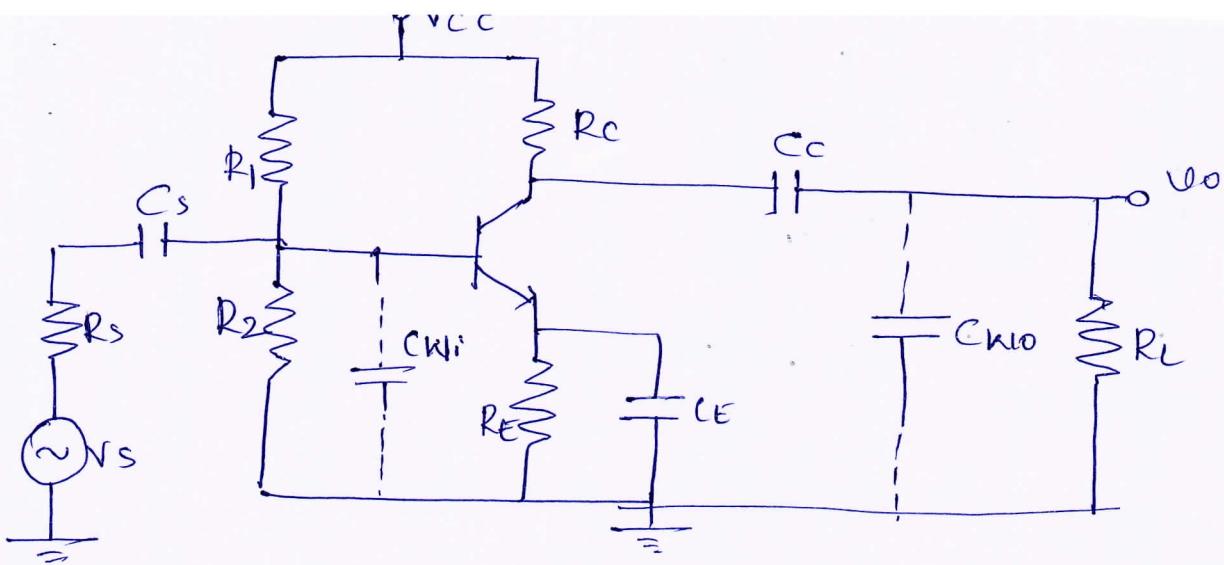- At high freq, there are 2 parameters that define -3dB cut off freq.
- 1) N/w capacitance.
- 2) Freq dependent of beta ( $\beta$ )



The capacitances  $C_{bc}$ ,  $C_{be}$  &  $C_{ce}$  are parasitic  
Capacitances & Capacitances  $C_{wi}$  &  $C_{wo}$  are wiring  
Capacitance.

$$f_{HI} = \frac{1}{2\pi R T_{HI} C_i}$$

$$f_{HO} = \frac{1}{2\pi R T_{HO} C_o}$$

$$\text{where } C_i = C_{wi} + C_{be} + C_{mi} = C_{wi} + C_{be} + (1 - A_v) C_{bc}$$

$$C_o = C_{wo} + C_{ce} + C_{mo}$$

4c) Determine lower cut off freq for emitter follower using BJT amplifier with  $C_s = 0.1 \mu F$

$$R_s = 1k\Omega, R_1 = 12k\Omega, R_2 = 4k\Omega, R_E = 1.5k\Omega, C = 0.1 \mu F$$

$$\beta = 100, V_{CC} = 15V, V_{BE} = 0.7V, \infty = \infty \text{ & } h_{ie} = 1.04k\Omega$$

$$V_B = V_{CC} \cdot \frac{R_2}{R_1 + R_2}$$

$$= 15 \times \frac{4k}{12k + 4k} = 3.75V$$

$$V_E = V_B - V_{BE} = 3.75 - 0.7V \\ = 3.05V$$

$$I_E = \frac{V_E}{R_E} = \frac{3.05}{1.5k} = 2.03mA$$

$$I_C \approx I_E = 2.03mA$$


$$\begin{aligned}
 Z_{in} &= h_{ie} + (1+\beta) R_E \\
 &= 1.04 \times 10^3 + (1+100) 1.5 \times 10^3 \\
 &\approx 152.5 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 Z_{total} &= R_s + Z_{in} \\
 &= 1 \text{ k}\Omega + 152.5 \text{ k}\Omega \\
 &= 153.54 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 f_L &= \frac{1}{2\pi R_s C_S} = \frac{1}{2\pi \times 153.54 \text{ k}\Omega \times 0.14} \\
 &\approx 10.36 \text{ Hz}
 \end{aligned}$$
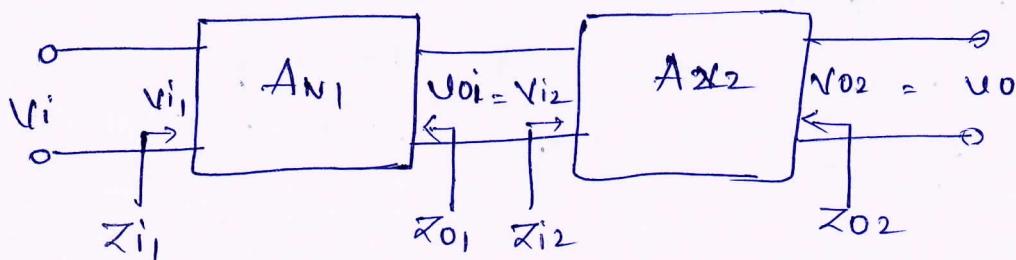
### Module 3

5a) With two stage cascaded amplifier, explain the need of Cascading.



When amplification from a single stage is not sufficient, then 2 or more amplifier stages need to be connected in series. Such an arrangement is called Cascade Amplifier.

WKT  $V_{01} = V_{i2}$  &  $V_{02} = V_o$

$$A_{v1} = \frac{V_{01}}{V_{i1}} \quad A_{v2} = \frac{V_{02}}{V_{i2}}$$


$$\begin{aligned}
 \therefore A_v &= \frac{V_{01}}{V_{i1}} \cdot \frac{V_o}{V_{01}} \\
 &= \frac{V_o}{V_i} = A_{v1} \cdot A_{v2}.
 \end{aligned}$$

5b) Write a note on Cascade Connection.

→ Question repeated as previous.

5c) Explain DC Analysis of Darlington Emitter Follower.

→

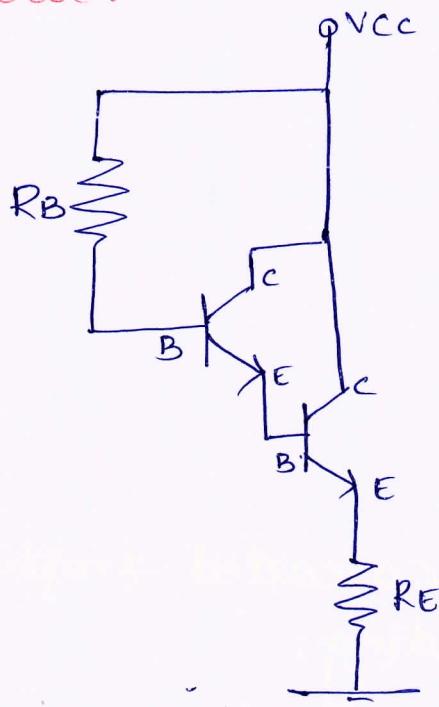

Applying KVL to i/p Ckt

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - (I_B + \beta I_B) R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - (1 + \beta) I_B R_E = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) R_E}$$

Applying KVL to CE loop.

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Here,  $\beta = \beta_D$  &  $V_{BE} = 1.6V$  to  $1.8V$ .

6a) What are the characteristics of Negative feedback Amplifier.

→ 1) Stability of Transfer Gain:-  
Stability of Transfer Gain with feedback is less as compared to without feedback. Hence stability is maintained.

2) Reduction in Noise

3) Reduction in freq distortion.

4) Improves Overall Bandwidth.

5) Negative fb improves freq response of Amplifier.

6b. An amplifier has mid-band voltage gain of 1000 with  $f_L = 50\text{Hz}$  &  $f_H = 50\text{kHz}$ . If 5% negative feedback is applied then calculate gain,  $f_L$  &  $f_H$  with feedback.

→

$$A_f = \frac{A}{1 + A\beta}$$

$$\beta = 5\%$$

$$= 0.05$$

$$= \frac{1000}{1 + 1000 \times 0.05} = 19.61$$

$$f_{L(f)} = f_L \times (1 + A\beta)$$

$$f_{H(f)} = f_H \times (1 + A\beta)$$

$$f_{L(f)} = 50 \times (1 + 0.05 \times 1000) = 2550\text{ Hz}$$


$$f_{H(f)} = 50 \times 10^3 \times (1 + 0.05 \times 1000)$$

$$= 50\text{ kHz} \times 5.1$$

$$= 2.55\text{ MHz}$$

6c) Obtain expression for  $i_{op}$  &  $O/P$  resistance of Voltage Series Amplifier.

→

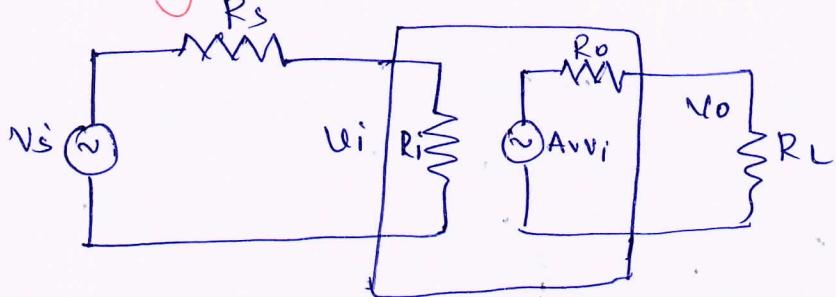

By Vltg Div rule at i<sub>op</sub> side

$$V_{oi} = \frac{V_s \cdot R_i}{R_i + R_s}$$

$$V_i = V_s \frac{R_i + R_s}{R_i}$$

$$V_i = \frac{V_s}{1 + \frac{R_s}{R_i}}$$

if  $R_s/R_i \ll 1$  or  $R_s \ll R_i$

or  $R_i \gg R_s$  then  $V_i = V_s$ .

Ideally  $[R_i = \infty]$

iii) By vltg Div Rule at O/P side.

$$V_o = A_v \frac{V_i \cdot R_L}{R_o + R_L}$$

$$\therefore V_o = \frac{A_v V_i}{\frac{R_o + R_L}{R_L}}$$

$$V_o = \frac{A_v V_i}{\frac{R_o}{R_L} + 1}$$

$\therefore R_o/R_L \ll 1$  or  $R_o \ll R_L$


i.e., Ideally  $[R_o = 0]$ .

## Module 4

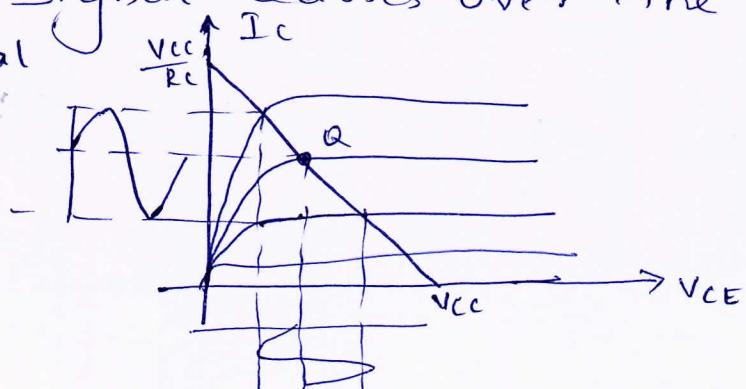7. a) With waveforms explain the classification of a power amplifier.


→ Class A Power Amplifier :-

→ Q pt is located at the centre of load line.  
So the O/P signal varies over the full cycle of the I/P signal.



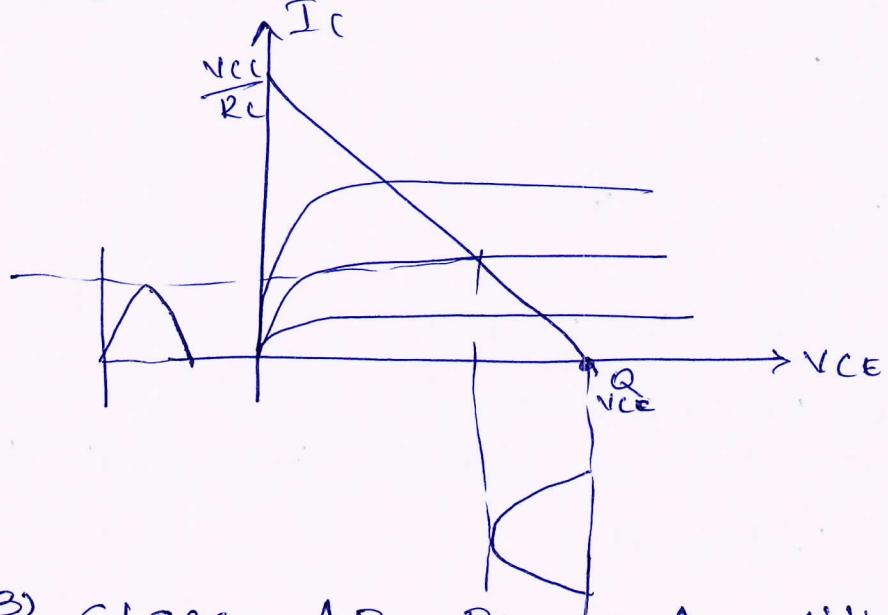
## 2) Class B Power Amplifier:-

→ Q-pt is located at the cut off region of the load line as shown in fig. so O/P signal varies for one half cycle of i/p signal.  $I_c$  flows for  $180^\circ$ .


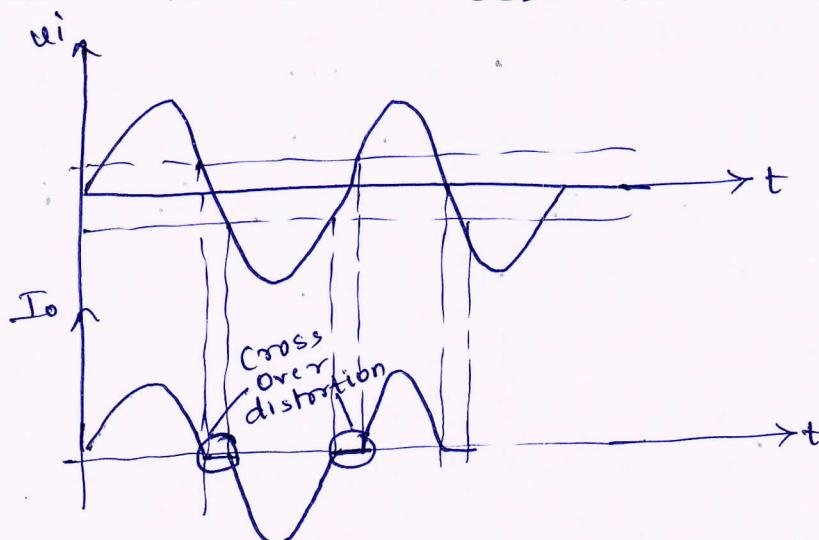
## 3) Class AB Power Amplifier.

Q-pt & i/p signal are selected such that O/P signal obtained is more than  $180^\circ$  but less than  $360^\circ$ . i.e.,  $\eta$  of class AB is more than Class A but less than Class B.




## 4) Class C power Amplifier:-

Here, the transistor is biased below the cut off region.

Q-pt remains active for less than half a cycle.

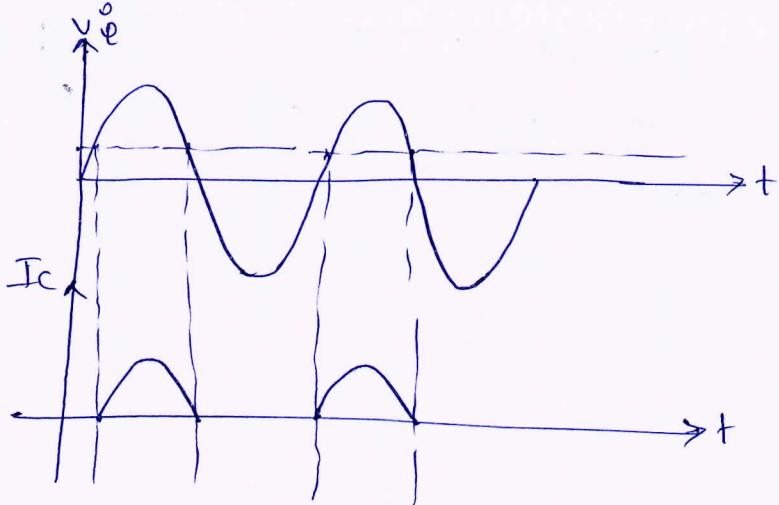
$\therefore$  for remaining, transistor is in cutoff region.  
So,  $I_C$  flows for less than  $180^\circ$



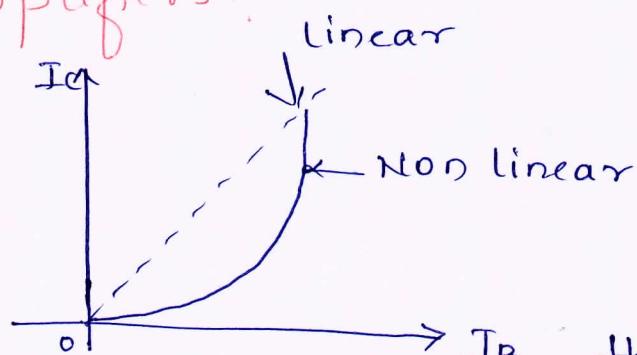5) Class D power Amplifier  $\rightarrow$

Designed to operate as pulse signal which are ON for a short interval & OFF for a longer interval.

7b) Derive an expression for second harmonic distortion using 2 point method for power amplifiers?



$$\therefore i_b = I_{Bm} \cos \omega t$$

Due to this  $I_C$  swings about its Q value but non linear as shown in fig.

Mathematically  $i_c = G_1 i_b + G_2 i_b^2$

$$= G_1 I_{Bm} \cos \omega t + G_2 I_{Bm}^2 \cos^2 \omega t \quad \text{--- (1)}$$


But,  $\cos^2 \omega t = \frac{1 + \cos 2\omega t}{2}$

$$\therefore i_c = G_1 I_{Bm} \cos \omega t + G_2 I_{Bm} \left( \frac{1 + \cos 2\omega t}{2} \right)$$

$$i_c = G_1 I_{Bm} \cos \omega t + \frac{1}{2} G_2 I_{Bm}^2 + \frac{G_2 I_{Bm}^2 \cos 2\omega t}{2}$$

$$\therefore i_c = B_0 + B_1 \cos \omega t + B_2 \cos 2\omega t$$
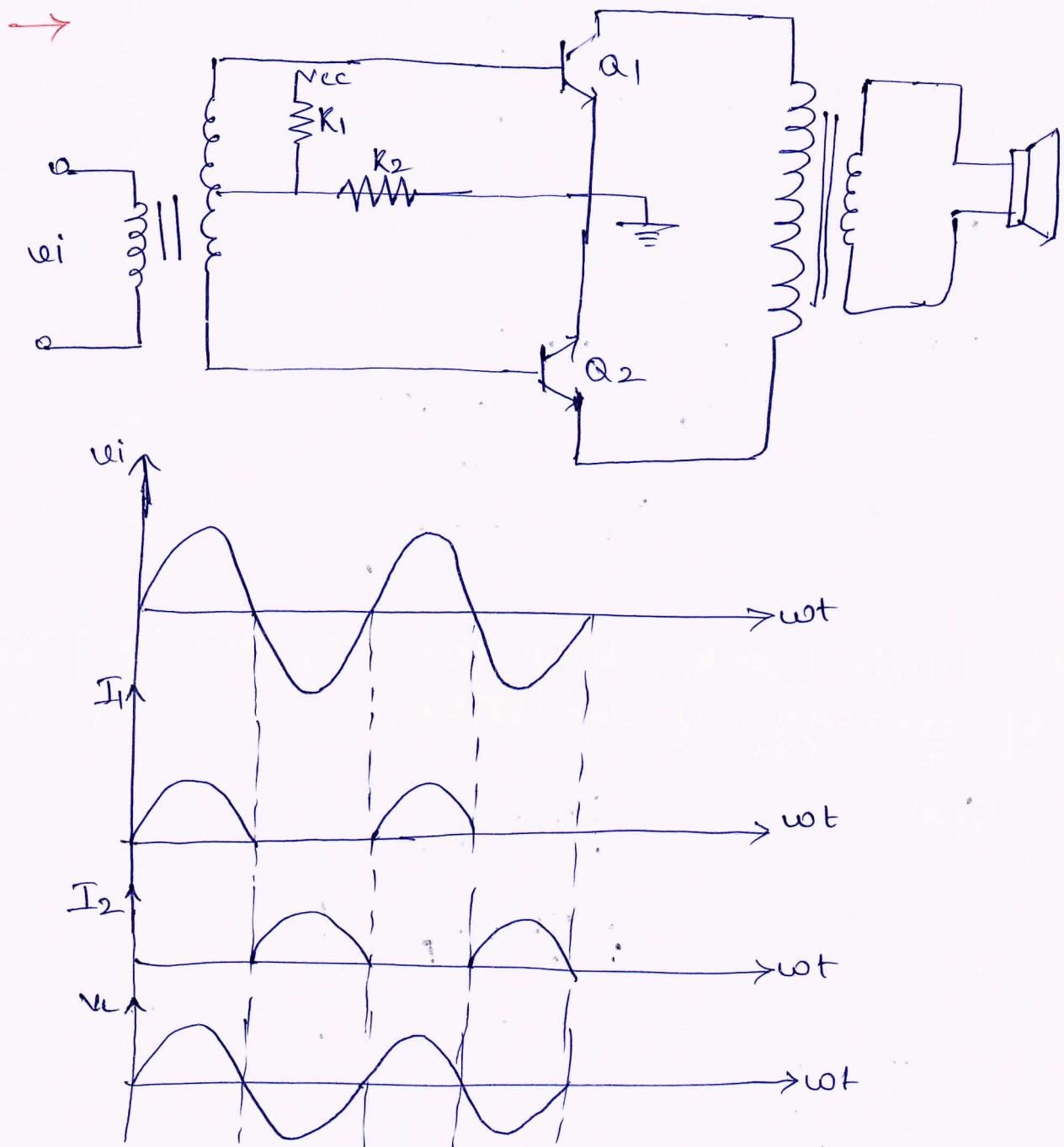
#C) With CKT diagram & waveform, explain working of class B push pull amplifier. Also show that conversion  $\eta$  is 78.5%.



The CKT consist of

- 1) Two centre tapped tfr ( $T_1 \& T_2$ )
- 2) Two identical tfr ( $Q_1 \& Q_2$ )

During the half cycle,  $Q_1$  is +ve &  $Q_2$  is -ve  
& as a result  $Q_1$  conducts &  $Q_2$  is off.  
When i/p signal goes -ve,  $Q_1$  turns off &  
 $Q_2$  is ON. Each transistor handles one half of  
signal at each instant.

$$I_{dc} = \frac{2Im}{\pi}$$

$$P_i(dc) = V_{cc} I_{dc}$$

$$= V_{cc} \cdot \left( \frac{2Im}{\pi} \right)$$

$$\boxed{P_i(dc) = \frac{2V_{cc} \cdot Im}{\pi}}$$


$$P_o = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{4V_{cc}}$$

$$V_{max} = V_{cc} \text{ and } V_{min} = 0$$

$$\therefore \eta_{max} = \frac{V_{cc} \cdot \pi}{4V_{cc}} \times 100$$

$$\boxed{\eta = 78.5\%}$$

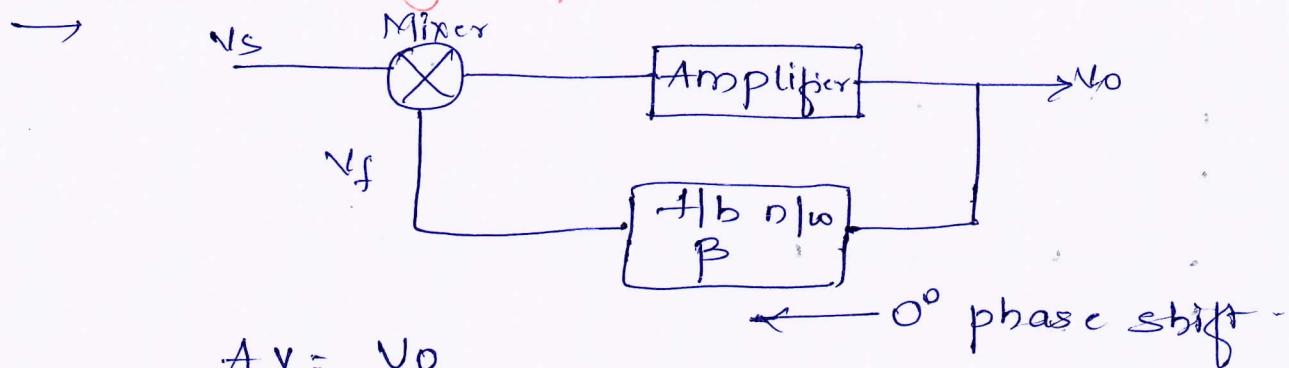8 a) With block diagram. explain the principle of working of oscillator.



$$Av = \frac{V_o}{V_i}$$

$$\& Av = \frac{V_o}{V_s}$$

$\therefore$  feedback is +ve,  $V_{ltg} V_f$  is added to  $V_s$  to generate i/p of amplifier

$$\& V_i = V_s + V_f$$

$$\therefore A_f = \frac{V_o}{V_i - \beta V_o}$$

Dividing Nr & Dr by  $V_i$  we get

$$A_f = \frac{V_o/V_i}{V_i/V_i - \beta V_o/V_i}$$

$$\therefore \boxed{A_f = \frac{A_v}{1 - A_v \beta}}$$


$$\therefore V_f = B V_o$$

$$\therefore V_f = B A v_i$$

Now if  $|A_v \beta| = 1$  then  $V_f = V_i$ .

so total phase shift should be  $0^\circ$  or  $360^\circ$ .  
if they are in same phase, hence satisfies  
Barkhausen Criteria.

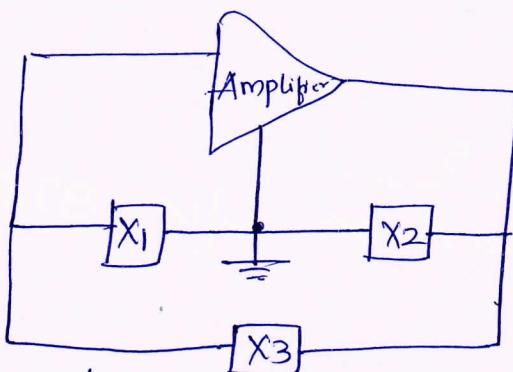8b. Explain the principle of tuned oscillator.  
Also obtain expression for freq of Hartley oscillator.



\* LC oscillators employ  $\pi$  type LC ckt to generate oscillations.  
\*  $\pi$  type LC ckt is also

Called tuned ckt or resonant ckt.

These oscillators exhibits high Q than RC oscillators resulting in good freq & stability.

Here  $X_1$  &  $X_2$  may be both L or both C

&  $X_3$  may be either L if both  $X_1$  &  $X_2$  are C  
& must be C if both  $X_1$  &  $X_2$  are L

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

$$L_{eq} = L_1 + L_2$$

$$\& L_{eq} = L_1 + L_2 + 2M$$

$$h_{fe} \geq \frac{L_1 + M}{L_2 + M}$$

$$\& h_{fe} \geq L_1/L_2$$

8c) A Quartz crystal has  $L = 50 \text{ mH}$ ,  $C_1 = 0.02 \text{ pF}$ ,  $R = 500 \Omega$ ,  $C_2 = 12 \text{ pF}$ . Determine  $f_s$  &  $f_p$ . If ext capacitance across crystal changes from  $5 \text{ pF}$  to  $6 \text{ pF}$ . find the change in freq of oscillation.

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{50 \times 10^{-3} \times 5 \times 10^{-12}}}$$

$$= \frac{1}{2\pi\sqrt{250 \times 10^{-15}}}$$

$$= 318.3 \text{ kHz.}$$

$$f_p = \frac{1}{2\pi\sqrt{LC_p}}$$




$$C_p = \frac{C_1 C_2}{C_1 + C_2} = 0.0199 \times 10^{-12}$$

### Module 5

9a. Give the comparison b/w BJT & MOSFET.

BJT	FET
1) Bipolar	1) Unipolar
2) Current controlled device	2) Vtg controlled device.
3) 3 terminals B, E & C	3) 3 terminals G, D & S
4) Conduction by both charge carriers	4) Only majority charge carriers.
5) sensitive to temp	5) Any ambient temp

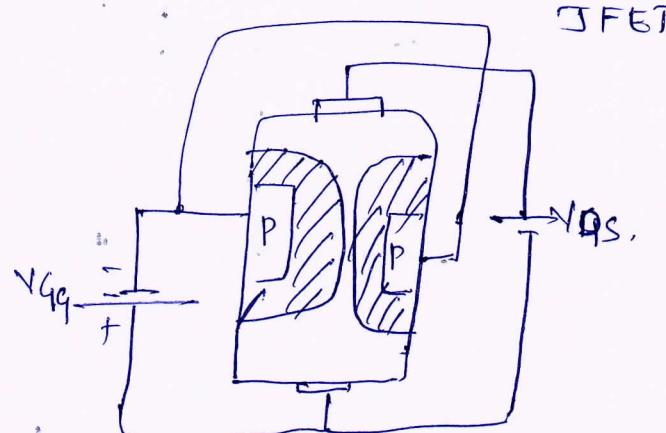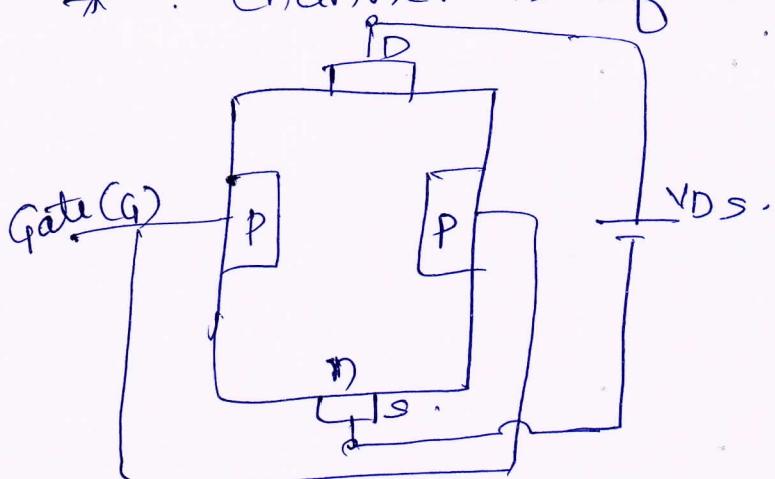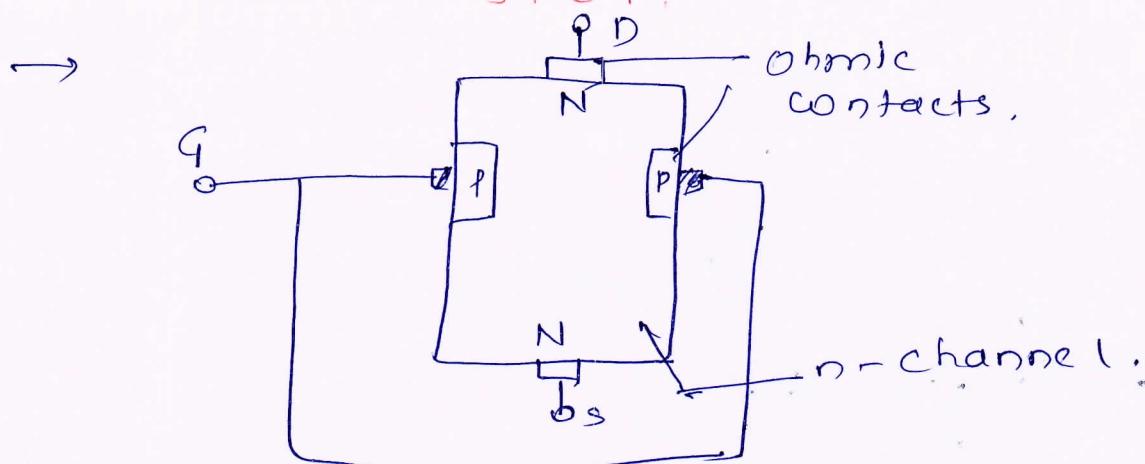ab. Explain Construction & working of n channel JFET.



When Gate is not connected,


$V_{DS}$  is applied +ve at drain & -ve at source.  
 $I_D$  starts flowing.

Now when, Gate is biased -ve w.r.t source  
PN junctions are reverse biased & depletion regions are formed.



As Channel is light doped, depletion region penetrates deeply & result is  $I_D$  decreases

Now, when  $V_{GS}$  is applied  $I_{DS}$  starts to increase

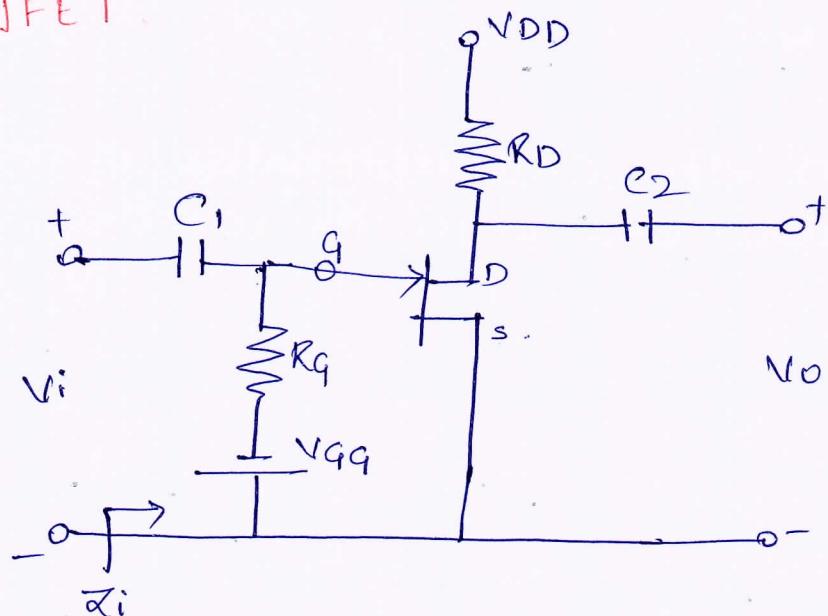Qc. Obtain expression for  $A_v$ ,  $Z_i$  &  $Z_o$  for fixed bias Common Source amplifier Using JFET.



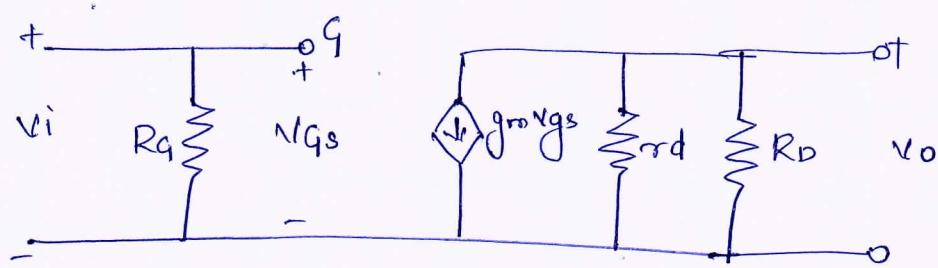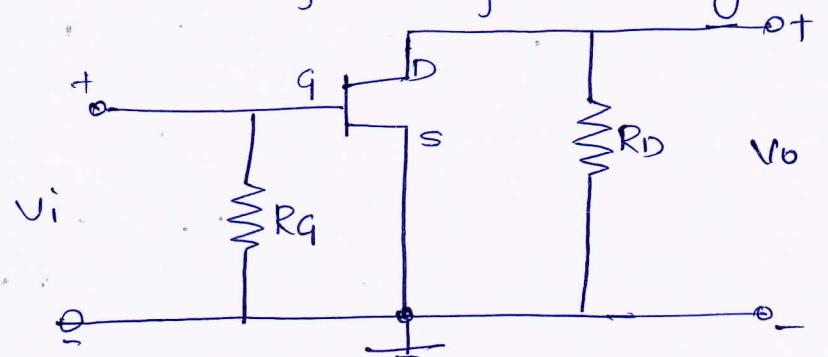A c equivalent circuit is obtained by setting the capacitors  $C_1$  &  $C_2$  & reducing  $V_{DD}$  &  $V_{GG}$  to zero.



from fig, i)  $Z_i = R_g$ .

$$\text{ii}) Z_o = r_d \parallel R_D$$

iii) Applying KCL  $g_m V_{GS} + I_1 + I_2 = 0$

$$I_1 = \frac{V_o}{r_d} \quad \text{&} \quad I_2 = \frac{V_o}{R_D}$$

$$g_m V_{GS} + \frac{V_o}{r_d} + \frac{V_o}{R_D} = 0$$

$$g_m V_{GS} = -V_o \left[ \frac{1}{r_d} + \frac{1}{R_D} \right]$$

$$g_m V_{GS} = -V_o \left( \frac{\tau_d + R_D}{\tau_d R_D} \right)$$

$$\therefore \frac{V_o}{V_i} = -g_m (\tau_d || R_D)$$

10 a) Explain the characteristics of n-channel MOSFET & also describe its working.

→ E-MOSFET is fabricated to operate only in enhancement mode.

- \* Hence,  $V_{GSQ}$  can only be positive for n channel & negative for p-channel device.

$$\therefore I_D = k [V_{GS} - V_{GS(TH)}]^2$$




$V_{GS(TH)}$  → Threshold voltage.

It is important to note that Drain current is zero for  $V_{GS} > V_{GS(TH)}$  & it significantly increases for  $V_{GS} \geq V_{GS(TH)}$ .


$k$  → constant

$$\therefore g_m = 2k [V_{GS(Q)} - V_{GS(TH)}]$$

\* Small signal AC Model of MOSFET.

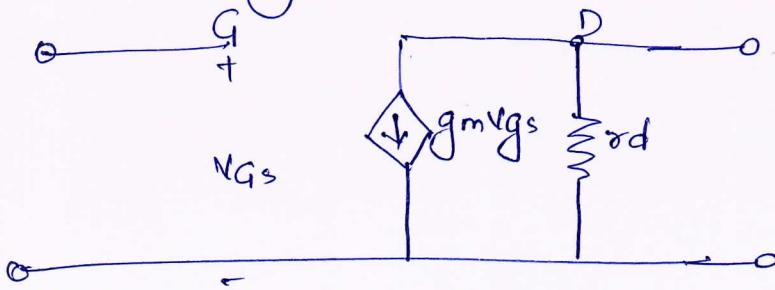

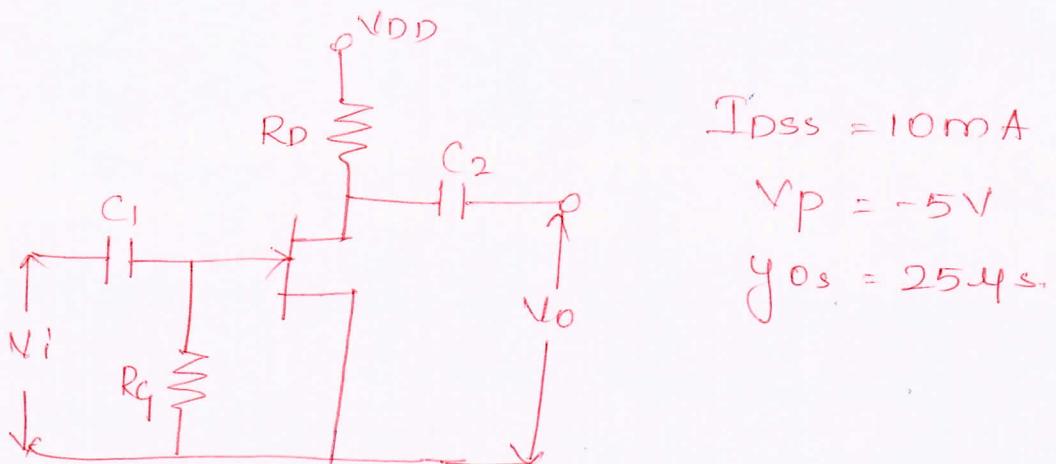10b) Design the fixed bias FET common source amplifier shown in fig to meet the following requirements  $A_v = 12$ ,  $Z_i = 10M\Omega$ ,  $V_{DD} = 40V$



$$\rightarrow g_m = \frac{2I_{DSS}}{|V_P|} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

$$= \frac{2 \times 10mA}{5} \left[ 1 - \frac{0}{-5} \right]$$

$$g_m = 4ms.$$

$$r_d = y_{os} = \frac{1}{25\mu s} = 40k\Omega$$

$$Z_i = R_G = 10M\Omega$$

$$Z_o = r_d || R_D$$

$$A_v = -g_m [r_d || R_D]$$

$$12 = -4 \times 10^{-3} \left[ \frac{40k \times R_D}{40k + R_D} \right]$$

$$-3 \times 10^{-3} = \frac{R_D}{40k + R_D}$$

$$\therefore Z_o = 40k || 3k$$

$$= 2.79k\Omega$$

$$R_D = (-75 \times 10^{-9}) 40k + R_D$$

$$= (-3 \times 10^{-3}) + (75 \times 10^{-9} R_D)$$

$$1R_D = 3 \times 10^{-3}$$

$R_D = 3k\Omega$

~~Ans~~