

CBCS SCHEME

ESS _____

BECC304

BECC304

Third Semester B.E./B.Tech. Degree Examination, Dec 2023/Jan 2024
Network Analysis

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. M: Marks, L: Bloom's level, C: Course outcomes.

		Module - 1		
Q.1	a. Explain the classification of electrical networks.	M	L	C
	b. For the network shown in Fig. Q1(b), find the current through load resistor 'R' using loop analysis.	8	L2	CO1
		6	L3	CO1
	Fig. Q1(b)			
	c. For the network shown in Fig. Q1(c), find the equivalent resistance between the terminals A - B using Star - Delta transformation.	6	L3	CO1
	Fig. Q1(c)			
		OR		
Q2	a. Derive an expression for the equivalent impedances between the terminals for Delta - Star transformation.	6	L2	CO1
	b. Use nodal analysis to find the value of voltage V_x in the circuit shown in Fig. Q2(b), such that the current through $(2 + j3)\Omega$ impedance is zero.	7	L3	CO1
	Fig. Q2(b)			
	c. Determine the current through 1Ω resistor shown in Fig. Q2(c), using Source Shifting / Transformation method.	7	L3	CO1
	Fig. Q2(c)			

1 of 5

D. S. S. S.

Head of the Department
Dept. of Electronic & Communication Engg.
KLS VJIT, HALYAL (U.K.)

		Module - 2		
Q3	a. Using Superposition theorem, obtain the current 'I' for the network shown in Fig. Q3(a).	10	L2	CO1
	Fig. Q3(a)			
	b. Using Millman's theorem, calculate the current through the load in the circuit shown in Fig. Q3(b).	10	L3	CO2
	Fig. Q3(b)			
		OR		
Q4	a. State and explain Norton's theorem.	6	L2	CO2
	b. For the network shown in Fig. Q4(b), find the current through 16Ω resistor using Thevenin's theorem.	7	L3	CO2
	Fig. Q4(b)			
	c. For the network shown in Fig. Q4(c), find the value of Z_L for which maximum power transfer occurs. Also find the maximum power.	7	L3	CO2
	Fig. Q4(c)			
		Module - 3		
Q5	a. Explain the initial and final conditions in basic elements.	6	L2	CO3

2 of 5

b. For the circuit shown in Fig. Q5(b), the switch 'K' is changing the position from 1 to 2 at $t = 0$. Steady state condition has been reached at position 1. Find the value of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$.

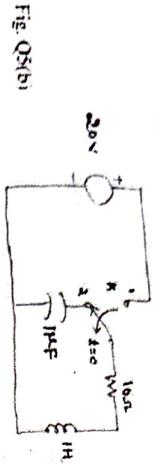


Fig. Q5(b)

c. Obtain an expression for transient response $i(t)$ of a series R - L circuit when excited by DC supply.

OR

Q.6 a. In the circuit shown in Fig. Q6(a), $v_1(t) = e^{-t}$ for $t \geq 0$ and zero for all $t < 0$. If the capacitor is initially uncharged, determine the value of $v_2(t)$, $\frac{dv_2(t)}{dt}$, $\frac{d^2v_2(t)}{dt^2}$ and $\frac{d^3v_2(t)}{dt^3}$ at $t = 0^+$.

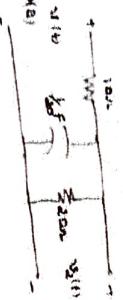


Fig. Q6(a)

b. For the circuit shown in Fig. Q6(b), the switch is closed at $t = 0$. Determine i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$.

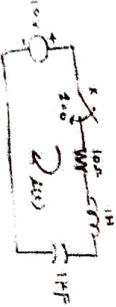


Fig. Q6(b)

Q.7 a. State and prove Initial Value Theorem.

Module - 4

b. Find the Laplace transform of the periodic waveform shown in Fig. Q7(b).



Fig. Q7(b)

c. Using Laplace transform, determine the current $i(t)$ in the circuit shown in Fig. Q7(c), when the switch 'S' is closed at $t = 0$. Assume zero initial conditions.

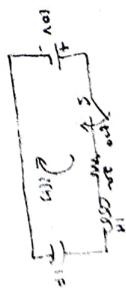


Fig. Q7(c)

Q.8 a. State and prove differentiate by 'S' domain property.

OR

b. In the circuit shown in Fig. Q8(b), the switch is closed at $t = 0$. Obtain the expression for the current.



Fig. Q8(b)

c. Obtain the Laplace Transform of the square wave shown in Fig. Q8(c).

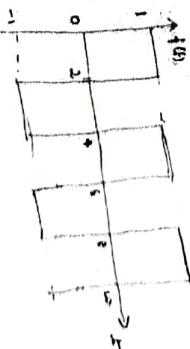


Fig. Q8(c)

Q.9 a. What are Impedance and Hybrid parameters? Derive the expression for the same.

Module - 5

b. Derive an expression for Transmission parameters in terms of Z parameters.

c. For the circuit shown in Fig. Q9(c) find Y - parameters.



Fig. Q9(c)

OR

Q.10 a. Derive an expression for bandwidth of a series Resonant circuit.

<p>b. A series R L C circuit consists of a resistance of 1 kΩ and an inductance of 100mH in series with capacitance of 10pF connected across 100V supply. Determine i) Resonant frequency ii) Quality factor iii) Maximum current in the circuit iv) Bandwidth v) Half power frequencies v) Selectivity factor</p>	7	13	C05
<p>c. For the circuit shown in Fig. Q10(c), find i) Resonant frequency ii) Quality factor iii) Bandwidth iv) Impedance at resonance v) Current at resonance.</p>	6	13	C05

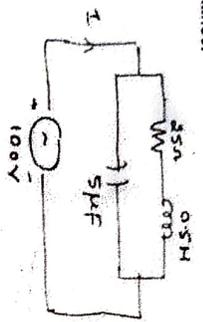


Fig. Q10(c)



Network Analysis - Dec. 2023/Jan. 2024.


Q1.a. Explain the classification of Electrical Network.

Ans: classification of Electrical Network.

- (i) Linear network.
- (ii) Non-Linear network
- (iii) Active network
- (iv) Passive network
- (v) Unilateral network
- (vi) Bilateral network
- (vii) Lumped network.
- (viii) Distributed network.

8x1 = 8M.

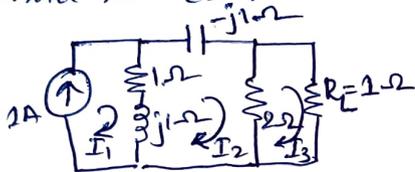Q1.b. Find the current through load resistor 'RL' using loop analysis.



From fig. $I_1 = 1A$.

Loop 2 \Rightarrow KVL Eqn is $-3I_2 + 2I_3 = -(1+j) \rightarrow \textcircled{1}$

Loop 3 \Rightarrow KVL Eqn is $2I_2 - 3I_3 = 0 \rightarrow \textcircled{2}$

Solving Eqn $\textcircled{1}$ & $\textcircled{2}$.

$$\begin{bmatrix} -3 & 2 \\ 2 & -3 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -(1+j) \\ 0 \end{bmatrix}$$

$I_3 = \frac{\Delta_3}{\Delta}$ where $\Delta = \begin{vmatrix} -3 & 2 \\ 2 & -3 \end{vmatrix} = 5$

$\Delta_3 = \begin{vmatrix} -3 & -(1+j) \\ 2 & 0 \end{vmatrix} = 2(1+j)$

$I_3 = \frac{2(1+j)}{5} = \boxed{0.567 \angle 45^\circ A}$

1M

1M



1M

2M

1M.

Q1.c. Find the Equivalent resistance between the terminal A-B using Star-Delta transformation.

Step 1 - Convert upper delta-Star.

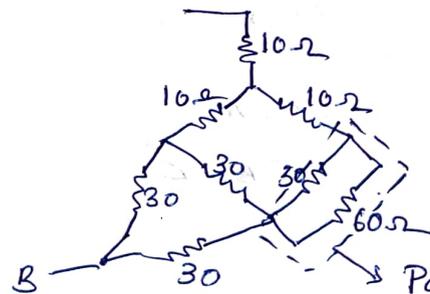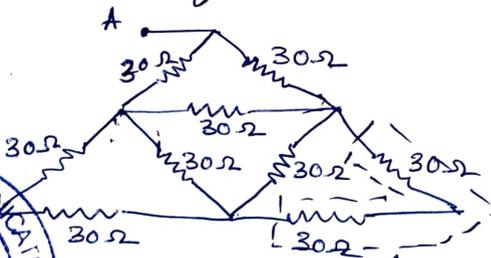

$R_1 = \frac{30 \times 30}{30 + 30 + 30}$

$R_1 = 10\Omega$


$R_1 = R_2 = R_3 = 10\Omega$

Series $30 + 30 = 60\Omega$.

$R = \frac{30 \times 60}{30 + 60} = 20\Omega$

2M




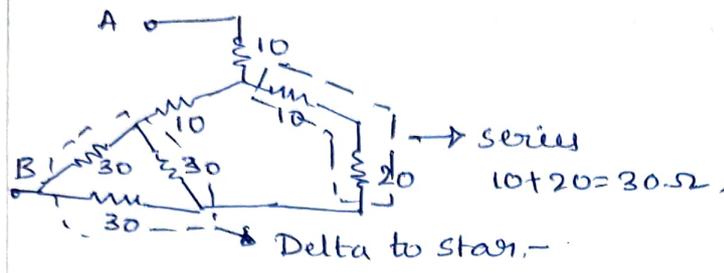


$$R_1 = \frac{30 \times 30}{30 + 30 + 30} = 10$$

$$R_1 = R_2 = R_3 = 10 \Omega$$

2M

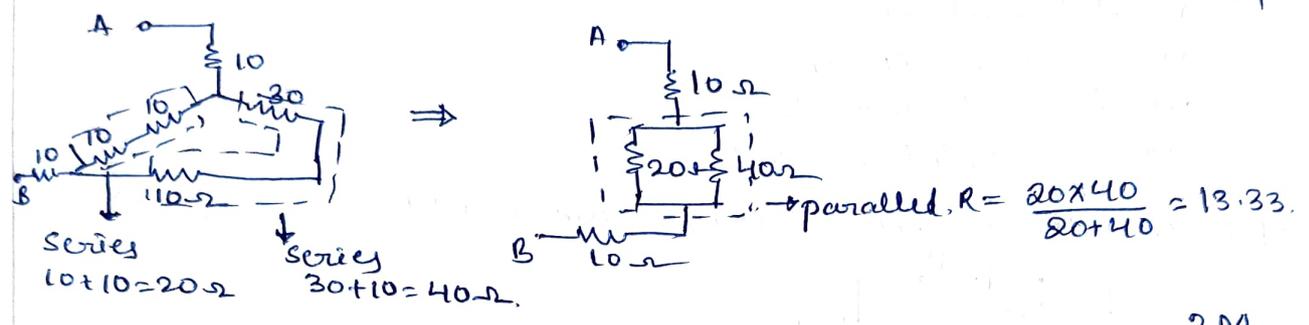


2M

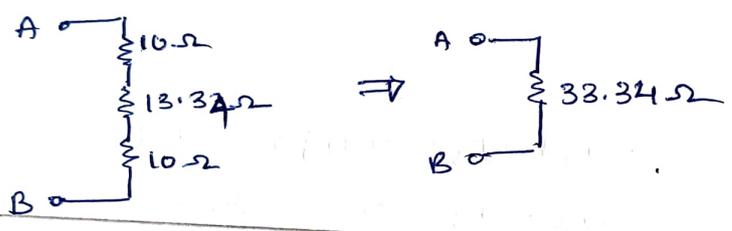

Q2.a. Derive an expression for equivalent impedance between the terminals for Delta to star transformation.

Ans

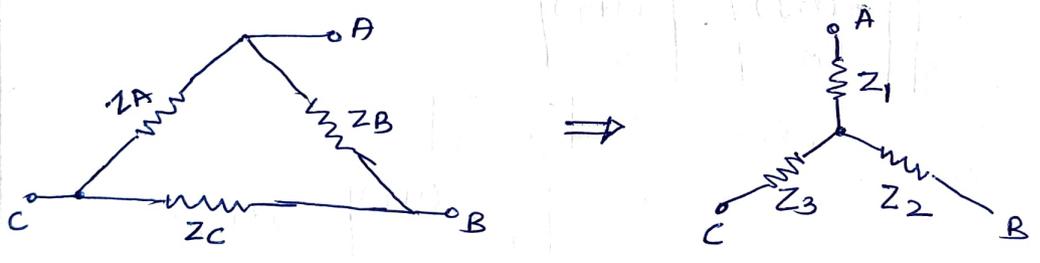

$$Z_1 = \frac{Z_A Z_B}{Z_A + Z_B + Z_C}$$

$$Z_2 = \frac{Z_B Z_C}{Z_A + Z_B + Z_C}$$


$$Z_3 = \frac{Z_C Z_A}{Z_A + Z_B + Z_C}$$



Head of the Department
of Electronic & Communication Engg.
KLS VJIT, HALIYAL (U.K.)

(06M)

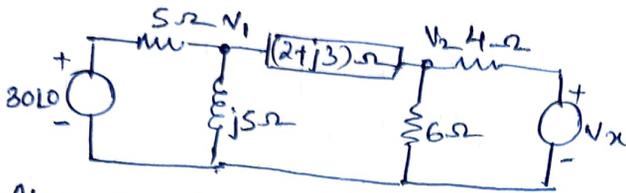Q2 b. Use nodal analysis to find value of voltage "Vx" in the circuit shown, such that current through (2+j3)Ω impedance is zero.



At node 1. \Rightarrow KCL Eqn is.
$$-\frac{(V_1 - 30\angle 0)}{5} - \frac{V_1}{j5} = 0 \quad \text{--- 02M.}$$

$$V_1 = 21.21 \angle 45^\circ \text{ V} \quad \text{--- 01M.}$$

At node 2 \Rightarrow KCL Eqn is
$$0 - \frac{V_2}{6} - \frac{V_2 - V_x}{4} = 0.$$


$$\Rightarrow 0.416V_2 - 0.25V_x = 0 \quad \text{--- 02M.}$$

Since $I_3 = 0$. $V_1 = V_2$
$$V_2 = V_1 = 21.21 \angle 45^\circ \quad \text{--- 01M.}$$

$$V_x = 1.667 (21.21 \angle 45^\circ)$$



$$\Rightarrow \boxed{V_x = 35.33 \angle 45^\circ \text{ V.}}$$

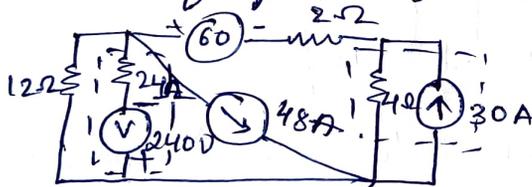Q2 c. Determine the current through 12Ω resistor shown, using source shifting / Transformation method.




Step 1 converting voltage source to current source, & 30A current source to voltage source.
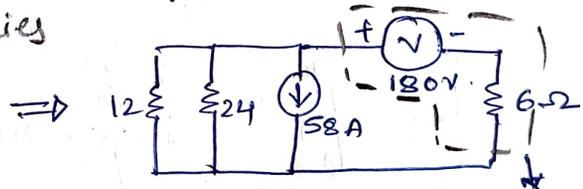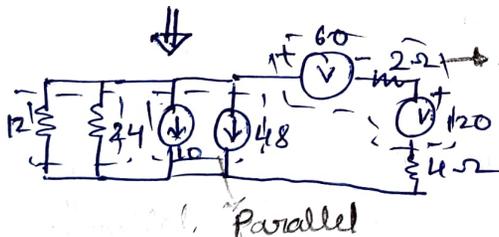
$$I = \frac{240}{24} = 10\text{A.} \quad V = 30 \times 4 = 120\text{V.} \quad \text{--- 02M}$$



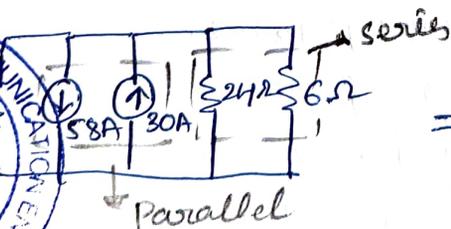Step 2 convert 120V voltage source to current source.
$$I = \frac{180}{6} = 30\text{A.} \quad \text{--- 02M}$$




$$I_{12\Omega} = \frac{28 \times (4.8\Omega)}{4.8\Omega + 12\Omega}$$


$$\boxed{I_{12} = 8\text{A}} \quad \text{--- 01M}$$



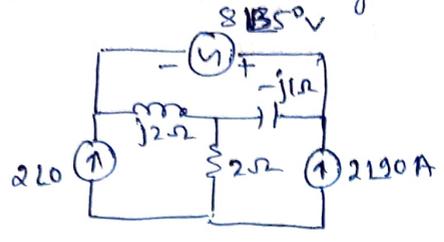Q3 a. find current "I" using superposition Theorem.



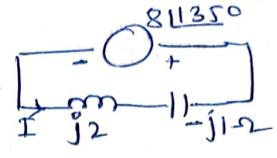
step ① - consider 2135° , open circuit $210A$ & $2190A$.



$$I' = \frac{-2135^\circ}{j1} = 8 \angle 225^\circ A$$


$$\boxed{I' = -5.65 - j5.65 A}$$

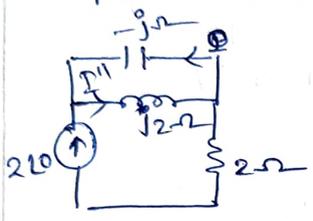Step ② considers $210A$, s.c. 2135° & o.c. $2190A$.



$$I'' = \frac{210(-j1)}{2j-j1} \Rightarrow \boxed{I'' = -2A}$$

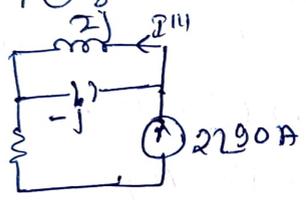Step ③ considers $2190A$, s.c. 2135° & o.c. $210A$.




$$I''' = \frac{2190(-j)}{2j-j} = -2jA \Rightarrow \boxed{I''' = -2jA}$$

$$I = I' + I'' + I''' \Rightarrow -5.65 - j5.65 - 2A - 2jA$$

$$I = -7.65 - j7.65$$

$$\boxed{I = 10.82 \angle -135^\circ A}$$

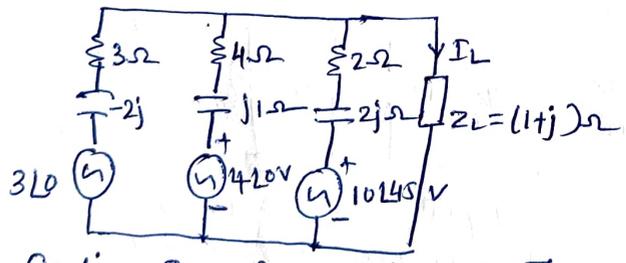Q3 b. Using Millman's theorem, calculate current through the load in the circuit.



Find I_L using millman's Theorem,

$$Z_1 = 3 - j2 \Rightarrow \gamma_1 = 0.297 \angle 33.69^\circ = 0.2304 + j0.1536$$

$$Z_2 = 4 + j1 \Rightarrow \gamma_2 = 0.2425 \angle -14.03^\circ = 0.235 - j0.0587$$

$$Z_3 = 2 - j2 \Rightarrow \gamma_3 = 0.353 \angle -45^\circ = 0.25 - j0.25$$

$$\gamma = \gamma_1 + \gamma_2 + \gamma_3 = 0.7156 - j0.155 = 0.732 \angle -12.33^\circ$$



02M

$$Z_m = \frac{1}{Y_m} = \frac{1}{0.732 \angle -12.23} = 1.365 \angle 12.23 \quad 01M$$

$$V_1 Y_1 = 0.6914 + j0.4609$$

$$V_2 Y_2 = 0.941 + j0.235$$

$$V_3 Y_3 = 8.536 + j0 \quad 03M$$

$$V_m = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3} = \frac{5.173 \angle 2.5}{0.732 \angle -12.23} \quad 02M$$

$$I = \frac{V_m}{Z_m + 2L} = \frac{7.065 \angle 14.73}{1.365 \angle 12.23 + (1+j)}$$

$V_m = 7.065 \angle 14.73 \text{ V}$

$Z_m = 1.365 \angle 12.23$

$I_L = 2.649 \angle -14.17 \text{ A}$

$01M$

$02M$

$01M$

$02M$

Q4a.

State and Explain Norton's theorem.

Ans


Statement of Norton's theorem -

Norton's theorem state that a linear two terminal circuit can be replaced by equivalent circuit consisting of a current source I_n in parallel with a resistor R_n where I_n is the short circuit current through the terminals and R_n is the input or equivalent resistance at the terminals when the independent source are turn-off.


Explanation

02M,
04M

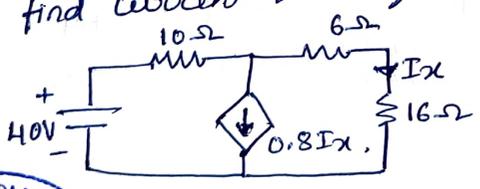
Q4. b. find current through 16Ω resistor using Thevenin's theorem.



Step 1, open circuit 16Ω resistor.

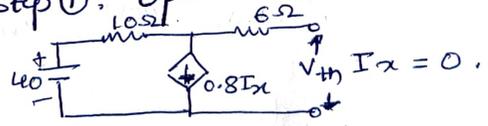

Can be redrawn as,

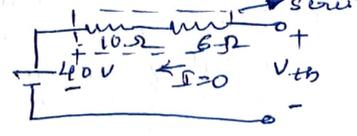


$$R_{eq} = 10 + 6 = 16\Omega$$

$$V_{th} = 40V$$

-02M



Step 2 Short circuit 16Ω Resistor.

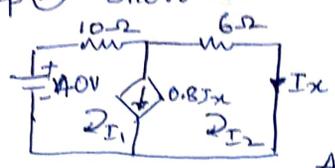

$$I_1 - I_2 = 0.8 I_x$$

Since $I_x = I_2$

$$I_1 - 1.8 I_2 = 0 \rightarrow (1)$$

Apply KVL to outer loop.
 $-10I_1 - 6I_2 + 40 = 0 \rightarrow (2)$

Solving Eq 1 & 2 $I_1 = 3A$ & $I_2 = 1.67A$


$I_x = 1.67A$

02M

$$R_{eq} = \frac{V_{TH}}{I_{sc}} = \frac{40V}{1.67A} = 24\Omega$$

01M

Step 3 Thevenin's Equivalent circuit

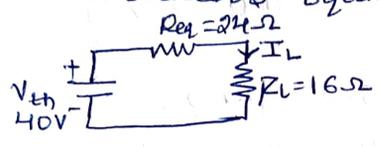


$$I_L = \frac{V_{TH}}{R_{eq} + R_L} = \frac{40}{24 + 16} = \frac{40}{40} = 1A$$

$I_L = 1A$

02M

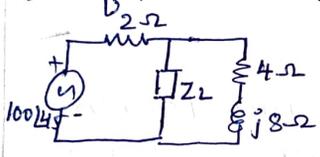Q4 c. for the given network, find the value of Z_L for which maximum power transfer occurs. also find the maximum power.



for P_{max} $Z_L = Z_{eq}^*$

to find Z_{eq}



$$Z_{eq} = 2 \parallel (4 + j8)$$

$$= \frac{2(4 + j8)}{2 + 4 + j8}$$


$$Z_{eq} = (1.76 + j0.32)$$

02M

$$Z_L = Z_{eq}^* = 1.76 - j0.32$$

01M

Find the P_{max} , find V_{TH} .

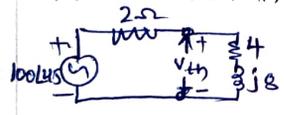

Applying KVL to the loop.

$$-2I - 4I - j8I + 100 \angle 45^\circ = 0$$

$$I = 10 \angle -8.13^\circ A$$

02M

$$V_{TH} = I(4 + j8) = 10 \angle -8.13^\circ (4 + j8)$$

$$|V_{TH}| = 89.44 \angle 5.3^\circ V$$

01M

$$P_{max} = \frac{V_{TH}^2}{4R_L} = \frac{(89.44)^2}{4(1.76)} = 1136.29W \rightarrow 01M$$

Q5 a. Explain the initial & final condition of Element.



(i) Resistor $\rightarrow t=0$ & $t=\infty$ both are same.

(ii) Capacitor $\rightarrow t=0$ open circuit $t=0$ zero voltage
 $t=\infty$ to close $t=\infty$ peak value.


(iii) Inductor $\rightarrow t=0$ open circuit $t=0$ zero current
 $t=\infty$ to close $t=\infty$ peak.

$t=0$ same continuity? close circuit to open
 $t=\infty$ same continuity? close to open
 $t=0$ \rightarrow conducting? close to open
 $t=\infty$ - continuity? open


06M

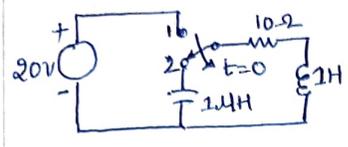Q5 b.

For the circuit shown, the switch 'K' is changing the position from 1 to 2 at $t=0$. Steady State condition has been reached at position 1. Find the value of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$




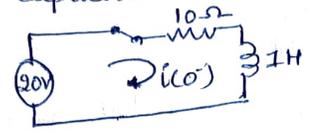Switch Position at 1
Inductor act as short circuit.
Capacitor act as open circuit.



$i(0^-) = \frac{20}{10} = 2A$ 02M
 $i(0^+) = i(0^-) = 2A$ 02M
 $V_C(0^-) = V_C(0^+) = 0V$ 02M

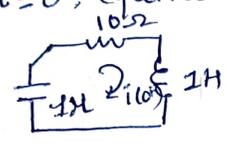When switch position at 2, for $t \geq 0$, equivalent circuit



Apply KVL to the loop.
 $Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = 0 \rightarrow \text{①}$ 02M

At $t=0^+$
 $\frac{di(0^+)}{dt} = -20A/sec$ 02M


differentiate Eq ① with t .

$R \frac{di(t)}{dt} + L \frac{d^2i(t)}{dt^2} + \frac{i(t)}{C} = 0$ 02M

at $t=0^+$ $\frac{d^2i(t)}{dt^2} = 2 \times 10^6 A/sec$ 02M

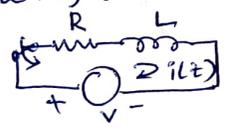Q5 c.

Obtain an expression for transient response $i(t)$ of a series R-L circuit when excited by DC supply.



At $t=0^-$
 $i(0^-) = i(0^+) \Rightarrow I_0 = 0A$
 At $t=0^+$, when switch is closed.


$-Ri(t) - L \frac{di(t)}{dt} + V = 0$

$V = Ri(t) + L \frac{di(t)}{dt}$

on solving Eq 2 $i(t) = \frac{V}{R} - \frac{V}{R} e^{-R/L t}$ 06M

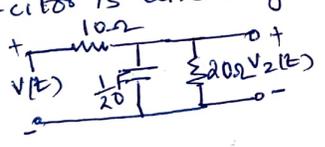Q6 a.

In the circuit shown, $v_1(t) = e^{-t}$ for $t \geq 0$ and zero for all $t < 0$. if the capacitor is uncharged, determine the value of $v_2(t)$, $\frac{dv_2(t)}{dt}$, $\frac{d^2v_2(t)}{dt^2}$ & $\frac{d^3v_2(t)}{dt^3}$ at $t=0^+$



Since capacitor is initially uncharged,
 $v_2(0^+) = 0$

Applying KCL at node V_2 ,

$\frac{v_2(t) - v_1(t)}{10} + C \frac{dv_2(t)}{dt} + \frac{v_2(t)}{20} = 0 \Rightarrow 0.15v_2(t) + 0.05 \frac{dv_2(t)}{dt} = 0.12 e^{-t} \rightarrow \text{①}$ 03M

At $t=0^+$ $0.15v_2(0^+) + 0.05 \frac{dv_2(0^+)}{dt} = 0$

$\frac{dv_2(0^+)}{dt} = 2V/sec$

differentiate Eq ① w.r.t. t $0.15 \frac{dv_2(t)}{dt} + 0.05 \frac{d^2v_2(t)}{dt^2} = -0.12 e^{-t}$ 02M


At $t=0^+$ $\frac{d^2v_2(t)}{dt^2} = 8V/sec^2$ 02M

At $t=0^+$ $\frac{d^3v_2(t)}{dt^3} = 26V/sec^3$ 02M



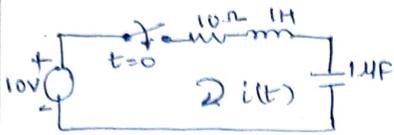Q6 b.

for the circuit shown, the switch is closed at $t=0$, Determine $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t=0^+$.
 The switch 'K' is open. at $t=0^-$ & closed at $t=0^+$.



Since there is no current through inductor $i(0^+) = 0A$

At $t=0^+$ apply KVL $-Ri(t) - L \frac{di(t)}{dt} - \frac{1}{C} \int_0^t i(t) dt = 10$

$-Ri(t) + L \frac{d(i(t))}{dt} + V_C(t) = 10$

at $t=0^+$ $2i(0^+) + \frac{di(0^+)}{dt} + V_C(0^+) = 10 \rightarrow \textcircled{1}$

$\frac{di(0^+)}{dt} = 10 \text{ n/sec.}$

Differentiating Eq 2, $R \frac{di(t)}{dt} + L \frac{d^2i(t)}{dt^2} + \frac{1}{C} i(t) = 0$
 at $t=0^+$ $\frac{R di}{dt} + \frac{1}{C} i = 0 \Rightarrow t=0^+, .$

Q7 a.

State and Prove Initial value theorem.

Statement: $\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(s) = f(0^+)$
 where $F(s)$ is Laplace transform of $f(t)$.


Proof: w.k.t.

$L[f'(t)] = sL[f(t)] - f(0) = sF(s) - f(0)$
 $\therefore sF(s) = L[f'(t)] + f(0)$


$= \int_0^{\infty} e^{-st} f'(t) dt + f(0)$
 Taking limit as $s \rightarrow \infty$ on both sides. we have
 $\lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} [\int_0^{\infty} e^{-st} f'(t) dt + f(0)]$
 $= \int_0^{\infty} \lim [e^{-st} f'(t) dt + f(0)]$
 $= 0 + f(0)$
 $= f(0) // \text{proved.}$

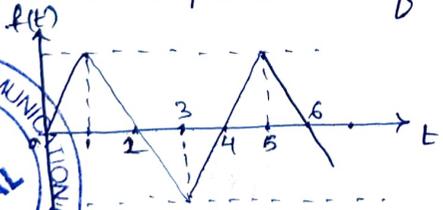Q7 b.

Find the Laplace transform of the periodic waveform shown




Consider the first cycle of the waveform

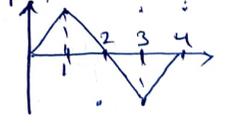


$T=4\text{sec}$


(iv)

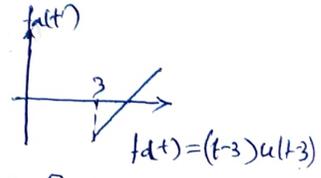

(ii)

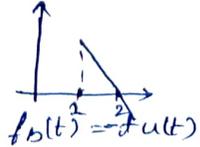

(iii)


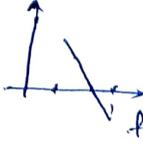


$f_a(t) = t u(t)$

$f_b(t) = -t u(t)$

$f_c(t) = -(t-1)u(t-1)$

$f_d(t) = (t-3)u(t-3)$

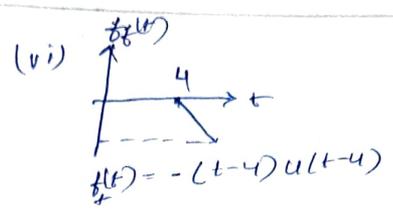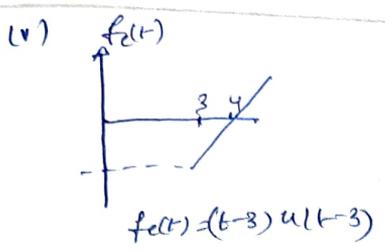

$$f(t) = f_a(t) + f_b(t) + f_c(t) + f_d(t) + f_e(t) + f_f(t)$$

$$= \delta u(t) - (t-1)u(t-1) - (t-1)u(t-1) + (t-3)u(t-3) + (t-3)u(t-3) - (t-4)u(t-4)$$

$$F(s) = \frac{1}{s^2} [1 - 2e^{-s} + 2e^{-3s} - e^{-4s}]$$

$$f(s) = \frac{1}{1-e^{-4s}} F(s)$$

$$= \frac{1}{1-e^{-4s}} \left[\frac{1-2e^{-s}+2e^{-3s}-e^{-4s}}{s^2} \right]$$

Q 7c. using Laplace transform, determine the current $i(t)$ in the circuit, where the switch 's' is closed at $t=0$. Assume zero initial condition.



Apply KVL to the loop.

$$-2i(t) - (1) \frac{di(t)}{dt} - \frac{1}{1} \int i(t) dt + 100 = 0 \quad -02M$$

$$\Rightarrow 2i(t) + \frac{di(t)}{dt} + \int i(t) dt = 100$$

taking Laplace Transform

$$2I(s) + sI(s) + \frac{I(s)}{s} = \frac{100}{s}$$

$$I(s) \left(2 + s + \frac{1}{s} \right) = \frac{100}{s}$$

$$I(s) = \frac{100s}{(s+1)^2}$$

$$i(t) = 100t e^{-t} \quad 03M$$

03M

01M.

Q 8a. state and prove differentiate by 's' domain property.

State ment: The differentiation in frequency domain or s-domain property of Laplace transform states that the multiplication of the function by t^n in time domain results in the differentiation in the s-domain. Therefore if

$$x(t) \xrightarrow{LT} X(s)$$

$$\text{then } t x(t) \xrightarrow{LT} \frac{d}{ds} X(s)$$

Proof: $L[x(t)] = X(s) = \int_0^{\infty} x(t) e^{-st} dt$

$$\frac{d}{ds} X(s) = \frac{d}{ds} \left[\int_0^{\infty} x(t) e^{-st} dt \right]$$

$$= \int_0^{\infty} -t x(t) e^{-st} dt = L[-t x(t)]$$


$$\therefore L[t x(t)] = -\frac{d}{ds} X(s) \quad //$$



MKS

Head of the Department
Dept. of Electronic & Communication Engg.
KLS VJIT, HALIYAL (U.K.)

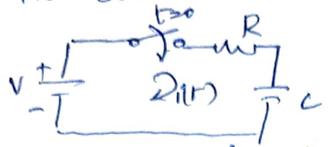Q8b. In the circuit shown, the switch is closed at $t=0$, obtain the expression for the current.



Before closing the switch, there was no charges in the capacitor; $V_C(0^-) = 0V$

After closing the switch, Apply KVL to the loop.

$$Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt = V$$

$$\Rightarrow Ri(t) + \frac{1}{C} \int_{0^-}^t i(t) dt + \frac{1}{C} \int_{0^+}^t i(t) dt = V$$



taking Laplace Transform.

$$I(s)R + \frac{1}{sC} I(s) + \frac{V(0^-)}{s} = \frac{V}{s}$$

$$I(s) = \frac{(V/R)}{s + 1/RC}$$

$$i(t) = \left(\frac{V}{R}\right) e^{-t/RC}$$

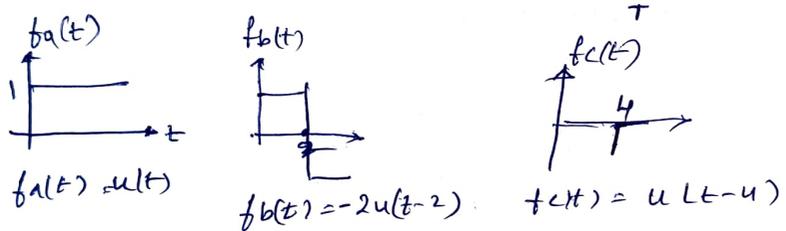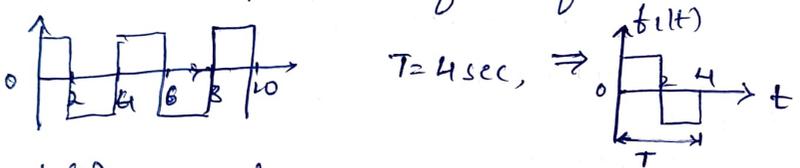Q8c. Obtain the Laplace transform of the square wave shown in the fig.



$$f(t) = f_a(t) + f_b(t) + f_c(t)$$

$$= u(t) + (-2)u(t-2) + u(t-4)$$

$$F(s) = \frac{1}{s} + \frac{-2e^{-2s}}{s} + \frac{1}{s} e^{-4s}$$

$$F(s) = \frac{1}{1 - e^{-Ts}} f_1(s)$$

$$F(s) = \frac{1}{1 - e^{-4s}} \left[\frac{1 - 2e^{-2s} + e^{-4s}}{s} \right]$$

03M

01M

01M

02M

Q9a. What are Impedance & Hybrid Parameters? Derive the expression for the same.

Ans. Impedance \rightarrow or z-parameters represents relation between voltage & current at each port of the network.

$$Z_{11} = \frac{V_1}{I_1}, Z_{12} = \frac{V_1}{I_2}, Z_{21} = \frac{V_2}{I_1}, Z_{22} = \frac{V_2}{I_2}$$

03M

Hybrid parameter \rightarrow h-parameters, the combinations of spacing and amplitude parameter, voltage and current ratios.

$$h_{11} = \frac{V_1}{I_1}, h_{12} = \frac{V_1}{V_2}, h_{21} = \frac{I_2}{I_1}, h_{22} = \frac{I_2}{V_2}$$

03M





Derive expression for Transmission parameters in terms of Z-parameters.

$[T] = \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} AV_2 + B(-I_2) \\ CV_2 + D(-I_2) \end{bmatrix}$
 $[Z] = \begin{bmatrix} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{21}I_1 + Z_{22}I_2 \end{bmatrix}$


$[T] \text{ in terms of } [Z] = \begin{bmatrix} Z_{11}/Z_{21} & \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}} \\ 1/Z_{21} & Z_{22}/Z_{21} \end{bmatrix}$

OSM

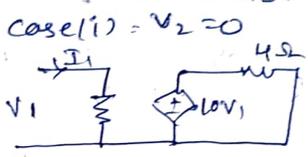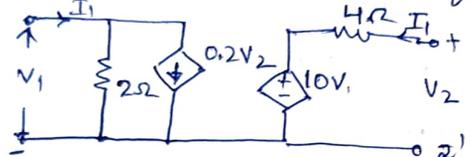
Q9 c. For the circuit shown, find Y-Parameters.



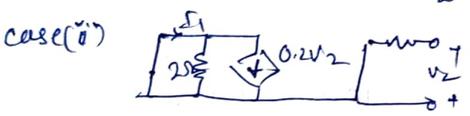$V_1 = 2I_1$
 $Y_{11} = \frac{I_1}{V_1} = \frac{1}{2} = 0.5 \text{ S}$



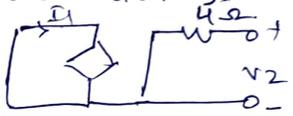where 2Ω is Redundant, hence circuit will be rewritten as.



$I_1 = 0.2V_2$
 $Y_{12} = \frac{I_1}{V_2} = 0.2 \text{ S}$
 $\& V_2 = \Delta I_2$
 $Y_{22} = \frac{I_2}{V_2} = \frac{1}{4} = 0.25 \text{ S}$

Apply KVL to loop 2


$-4I_2 - 10V_1 = 0$
 $Y_{21} = \frac{I_2}{V_1} = \frac{-10}{4} = -2.5 \text{ S}$

$[Y] = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.5 & 0.2 \\ -2.5 & 0.25 \end{bmatrix}$

OSM.

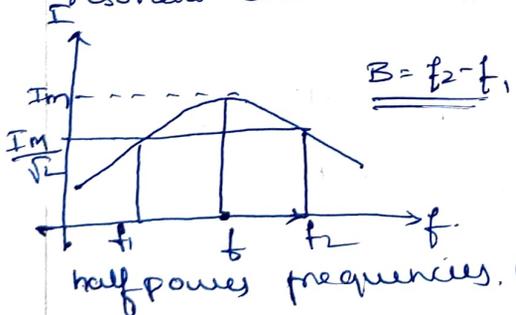Q10 a. Derive an expression for Bandwidth of a series Resonant circuit.

Band width: The range of frequencies between these two cut-off frequencies i.e. $(f_2 - f_1)$ is called as Bandwidth of the resonant circuit.



Inductive reactance = Capacitive reactance

$X_L = X_C$
 $\omega L = \frac{1}{\omega C}$

$2\pi f L = \frac{1}{2\pi f C}$

$f^2 = \frac{1}{4\pi^2 LC}$

$f = \sqrt{\frac{1}{4\pi^2 LC}}$

$f_1 = \frac{1}{2\pi\sqrt{LC}}$

$\approx f_0 = \sqrt{f_1 f_2}$

$\frac{1}{\sqrt{2}} \cdot \frac{V}{R} = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$

$(\omega L - \frac{1}{\omega C})^2 = R^2$

$\omega L - \frac{1}{\omega C} = \pm R$

$(f_2 - f_1) = \frac{R}{2\pi L}$



Q10 b. A series RLC circuit of a resistance of $1k\Omega$ and an inductance of $100mH$. in series with capacitance of $10pF$ connected across $100V$ supply.

Determine: i) Resonant frequency ii) Quality factor iii) Maximum current in the circuit iv) Bandwidth v) Halfpower frequencies v) selectivity factor.

i) Resonant frequency $\Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} = 159.23\text{kHz}$

ii) Quality factor $\Rightarrow Q_0 = \frac{1}{R}\sqrt{L/C} = 100$

iii) Bandwidth $\Rightarrow (f_2 - f_1) = \frac{R}{2\pi L} = 1.592\text{kHz}$


iv) Maximum current $I_0 = \frac{V}{R} = 0.1A$

v) Halfpower frequencies $f_1 = f_0 - \Delta f = 158.43\text{kHz}$

$f_2 = f_0 + \Delta f = 160.02\text{kHz}$

07M.

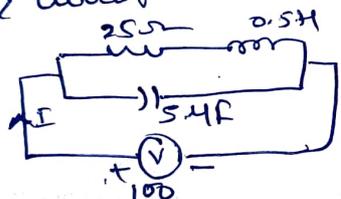Q10 c. For the circuit shown, find i) Resonant frequency. ii) Quality factor. iii) Bandwidth iv) Impedance at Resonance v) current at resonance.



i) Resonance frequency $= f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = 100.39\text{Hz}$

ii) Quality factor $Q_0 = \frac{\omega_r L}{R} = 12.60$

iii) Bandwidth $\approx \frac{f_r}{Q_0} = 7.96\text{Hz}$

iv) Impedance at Resonance $Z_{or} = \frac{L}{CR} = 4000\Omega$

v) current at Resonance $I_0 = \frac{V}{Z_{or}} = 0.025A$

06M



Handwritten signature and stamp: Head of the Department, Dept. of Electronic & Communication Engg., KLS VJIT, HALYAL (K.A.)