

Third Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025 Analog Electronic Circuits


Time: 3 hrs.

Max. Marks: 100


Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks , L: Bloom's level , C: Course outcomes.

Module - I		M	L	C		
Q.1	a.	Explain the operation of positive shunt clipper.		8	L2	CO1
	b.	Derive an expression for the stability factor $S_{(V_{BE})}$ and $S_{(I_{CO})}$ for fixed bias circuit.		6	L3	CO1
	c.	For the circuit shown in Fig Q1(c), sketch the output voltage waveform.		6	L3	CO1
		<p style="text-align: center;">Fig Q1 (c)</p>				
OR						
Q.2	a.	With circuit diagram, explain voltage divider biasing circuit. Also derive the I_B and V_{CE} .		8	L2,3	CO1
	b.	Draw and explain the working of negatives peak clamper.		6	L1,2	CO1
	c.	Determine the following for the fixed bias configuration shown in Fig Q2(c). i) I_{BQ} and I_{CQ} ii) V_{CEQ} iii) V_B and V_C iv) V_{BC}		6	L3	CO1
		<p style="text-align: center;">Fig Q2(c)</p>				

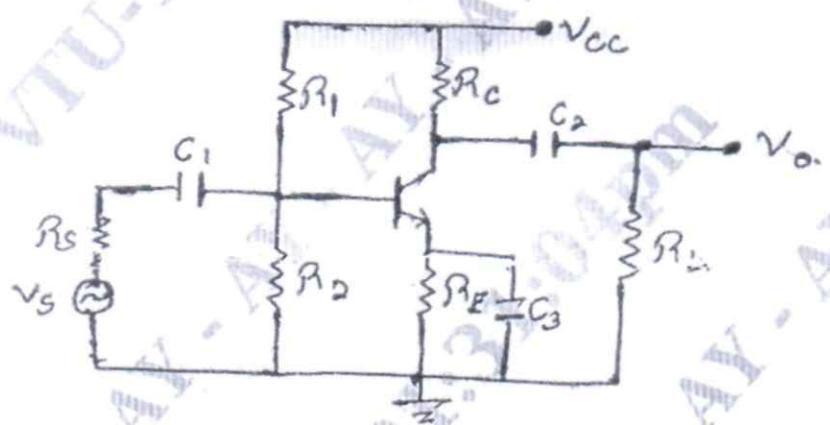Module - 2					
Q.3	a.	State and prove dual of miller's theorem	6	L1,4	CO2
	b.	Define h-parameters. Draw the h-parameter model of a transistor in CE mode.	6	L1,2	CO2
	c.	Obtain midband analysis of BJT single stage amplifier. Derive expression for current gain and input impedance.	8	L3,4	CO2
OR					
Q.4	a.	Mention various capacitors effects on frequency response. Derive equations for miller input capacitors and miller output capacitance.	10	L1,3	CO2
	b.	Consider a single stage CE amplifier with $R_s = 1K$, $R_1 = 50K$, $R_2 = 2K$, $R_c = 2K$, $R_L = 2K$, $h_{fe} = 50$, $h_{ie} = 1.1K$, $h_{oe} = 25 \mu A/V$ and $h_{re} = 2.5 \times 10^{-4}$ as shown in Fig Q4(b). Find A_i , R_i , R_o , A_v .	10	L3	CO2
 <p style="text-align: center;">Fig Q4(b)</p>					
Module - 3					
Q.5	a.	Explain the need of a cascading amplifier. Draw and explain to block diagram of two stage cascade amplifier.	8	L2	CO3
	b.	For voltage series feedback amplifier, derive an expression for input impedance and output impedance.	8	L3	CO3
	c.	A feedback amplifier has a gain of 1000 without feedback. Find the gain with feedback for a negative feedback of 10% (gain in dB).	4	L3	CO3
OR					
Q.6	a.	Draw a feedback amplifier in block diagram form. Identify each block and explain its function.	10	L1,2	CO3


	<p>b. For the Darlington emitter – follower shown in Fig Q6(b), calculate</p> <ol style="list-style-type: none"> The DC bias voltage V_B, V_E, V_C and current I_B and I_C The input and output impedances The voltage and current gains The ac output voltage for $V_i = 120\text{mV}$. 	10	L3	CO3
--	--	----	----	-----

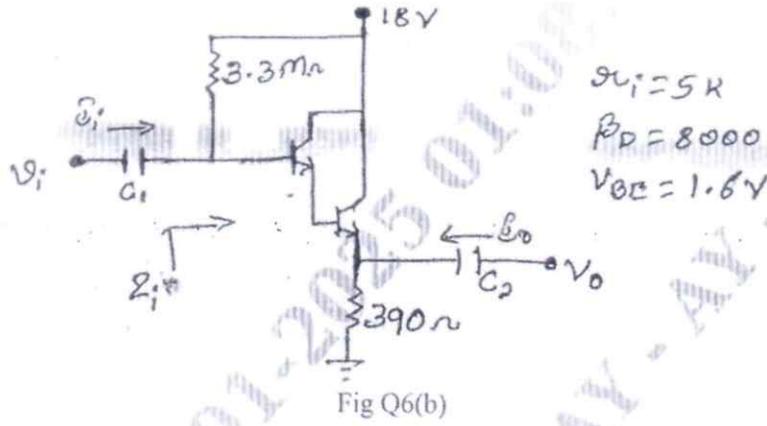

Module – 4

Q.7	<p>a. Analyze the working of series fed directly coupled class A power amplifier with respect to efficiency.</p>	8	L4	CO4
-----	--	---	----	-----

	<p>b. Design the component values of wein bridge oscillator of Fig Q7(b) for a frequency of oscillations of 4 KHz.</p>	4	L4	CO4
--	--	---	----	-----

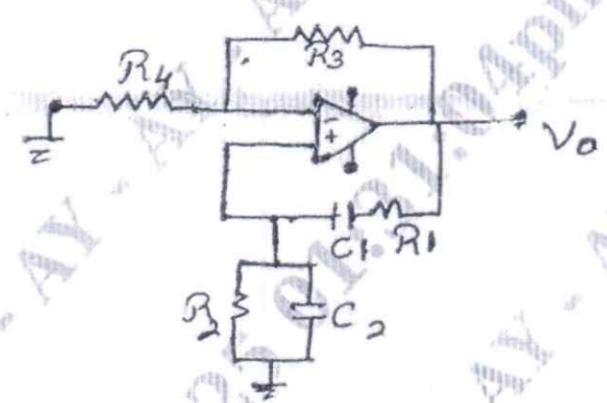

	<p>c. Explain the characteristics of crystal with neat diagram, explain the crystal oscillation in series resonances circuit.</p>	8	L2	CO4
--	---	---	----	-----

OR

Q.8	<p>a. Examine the basic principle of oscillators.</p>	6	L4	CO4
-----	---	---	----	-----

	<p>b. An ideal class B push pull power amplifier with input is output transformers has $V_{cc} = 20\text{V}$, $N_2 = 2N_1$ and $R_L = 20\Omega$. The transistors has $h_{FE} = 20$. Let the input be sinusoidal. For maximum output signal at $V_{CE(P)} = V_{CC}$. Determine :</p> <ol style="list-style-type: none"> The output signal power The collector dissipation in each transistor Conversion efficiency 	6	L3	CO4
--	---	---	----	-----

	c.	Discuss the different types of power amplifiers.	8	L4	CO4
Module - 5					
Q.9	a.	Explain the basic operation and characteristics of n-channel depletion type MOSFET.	10	L2	CO4
	b.	Derive expression for z_i , z_o , A_v for voltage divider bias circuit using FET.	10	L3	CO4
OR					
Q.10	a.	With neat diagram, explain the construction of n channel JFET.	10	L2	CO5
	b.	Data sheet for a JFET indicates that $I_{DSS} = 10\text{mA}$ and $V_{GS(off)} = -4\text{V}$. Determine the drain current for $V_{GS} = 0\text{V}$, -1V and -4V .	6	L3	CO5
	c.	Discuss the difference between JFET and MOSFET.	4	L4	CO5

Analog Electronic Circuits (BEE303)


Subject Code : BEE303.

Semester : 3rd

Prepared By : Prof. Ravindra Motekar.

Module 1

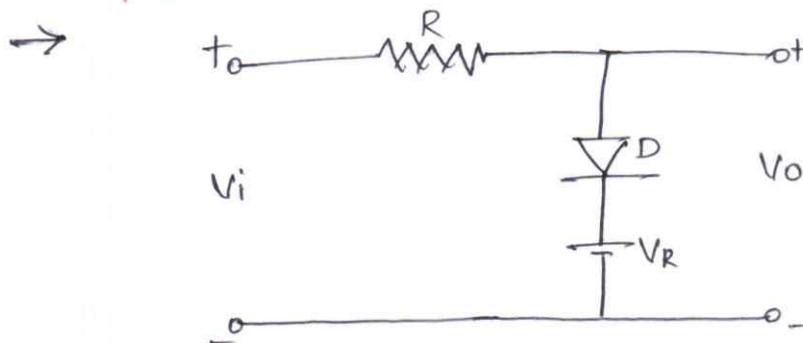1a) Explain the operation of Positive shunt clipper — 8M.



In 11c1 clipper, diode appears in the parallel branch or shunt with the applied input signal



$$V_i \geq V_R + V_K$$

from the equivalent ckt, we find that

$$V_o = V_R + V_K \quad \text{for } V_i \geq V_R + V_K$$

$$V_i - iR - V_o = 0$$
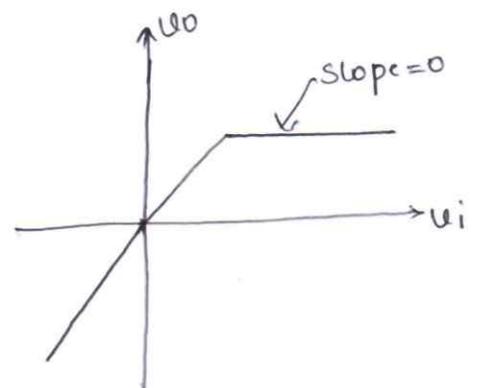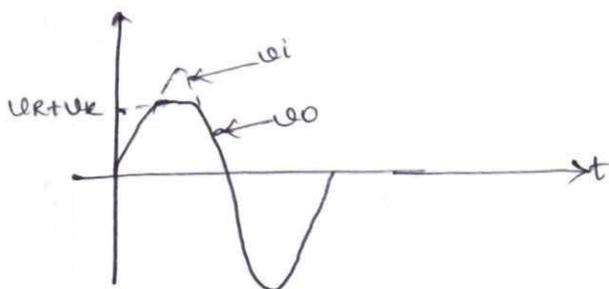
$$\text{or } V_o = V_i, \quad \text{for } V_i < V_R + V_K$$



1b) Derive an expression for stability factor $S(V_{BE})$ & $S(I_{CO})$ for fixed bias circuit - 6M

$$\rightarrow S(I_{CO}) = \frac{\partial I_C}{\partial I_{CO}}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

But $V_{CC} \gg V_{BE}$

$$I_B \approx \frac{V_{CC}}{R_B}$$

$$\frac{\partial I_B}{\partial I_C} = 0$$

$$\therefore S(I_{CO}) = 1 + \beta$$

$$S(V_{BE}) = \frac{\partial I_C}{\partial V_{BE}}$$

$$V_{CC} = I_B R_B + V_{BE}$$

$$\therefore V_{BE} = V_{CC} - I_B R_B$$

$$\text{But } I_B \approx \frac{I_C}{\beta}$$



$$\therefore V_{BE} = V_{CC} - \frac{I_C}{\beta} R_B$$

Differentiating w.r.t V_{BE} , keeping β constant, we get

$$1 = 0 - \frac{R_B}{\beta} \frac{\partial I_C}{\partial V_{BE}}$$

$$\therefore S(V_{BE}) = -\beta / R_B$$

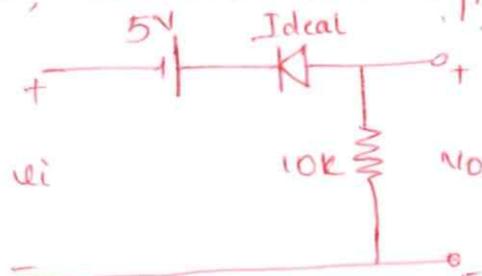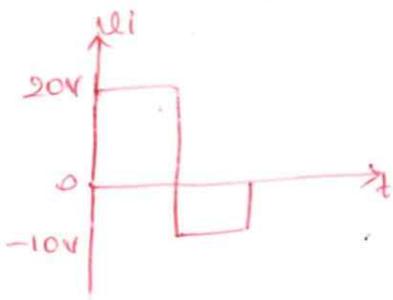
1c) for the ckt shown, sketch the o/p vltg waveform $\rightarrow 6M$



$$V_i + 5 - V_o = 0$$

$$V_o = V_i + 5 \text{ for } V_i \geq 4.3V$$


when $V_i = 20V$
 $V_o = 20 + 5 = 25V.$

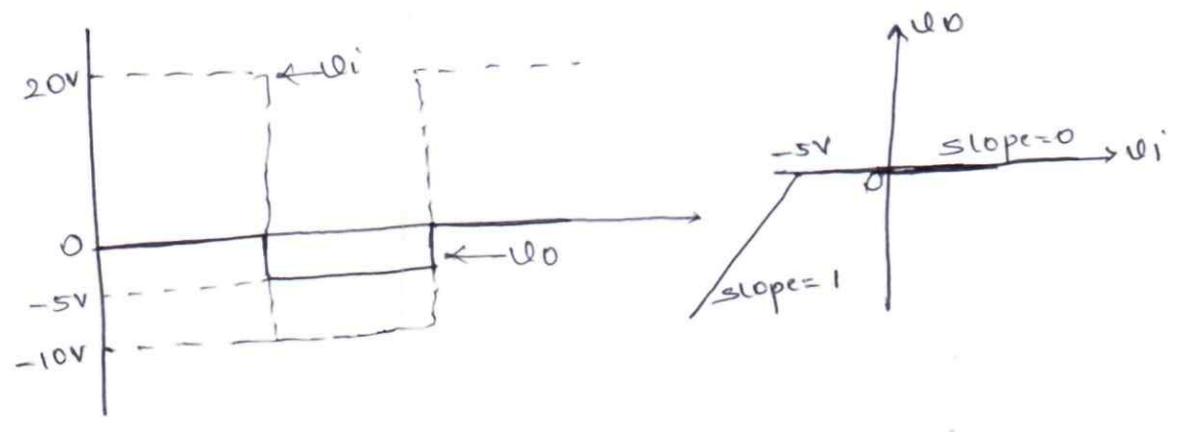

OR

2(a) With neat ckt diagram, explain voltage divider biasing ckt. Also derive I_B & V_{CE} . (8M)


→

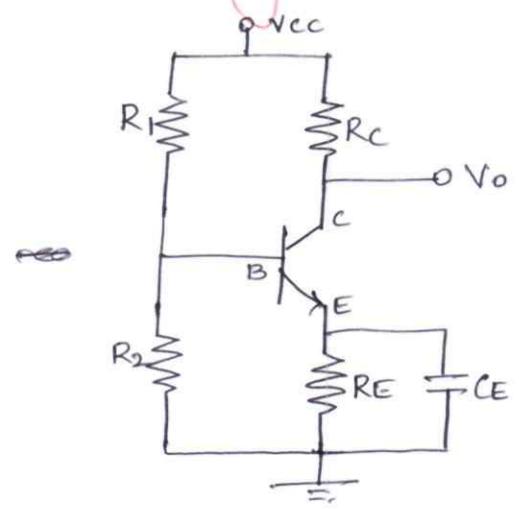

To find V_{TH} & R_{TH} . Using Thevenin's theorem.

$$V_{TH} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

$$R_{TH} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

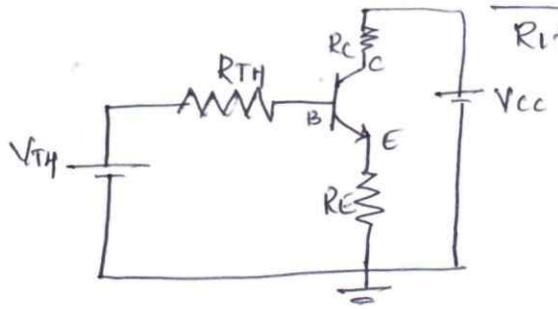

Applying KVL to i/p ckt we get

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$



$$\therefore I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E}$$

$$\& V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

2(b) Draw & explain the working of Negative peak clamper (6M)

→

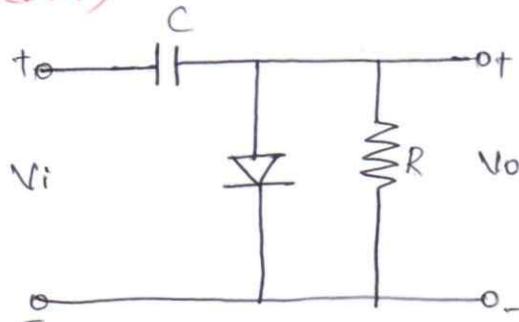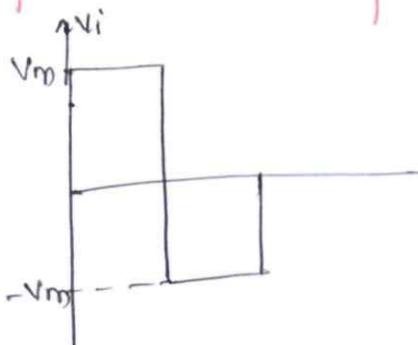

By KVL equⁿ $V_i - V_C - V_K = 0$

$$V_C = V_i - V_K$$

$$V_i = V_m$$

$$V_C = V_m - V_K$$

& Writing KVL equⁿ again,


$$V_i - V_C - V_O = 0$$

$$V_O = V_i - V_C$$

$$V_C = V_m - V_K$$

$$\therefore V_O = V_i - [V_m - V_K]$$

o/p waveform is.

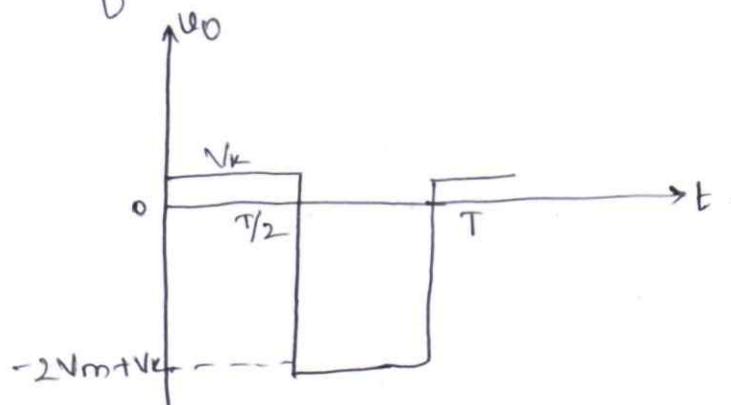


2(c) Determine the toll for the fixed bias configuration shown in fig. (6M)

(i) I_{BQ} & I_{CQ}

(ii) V_{CEQ}

(iii) V_B & V_C

(iv) V_{BC} .

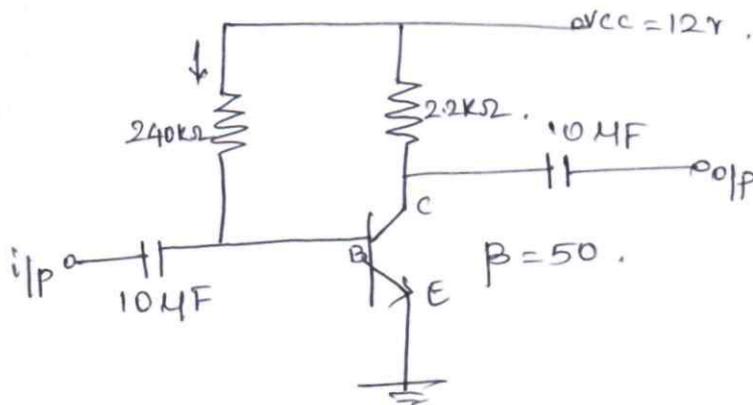

$$(i) \quad I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.7}{240 \times 10^3} = 47.08 \mu\text{A}.$$

$$I_C = \beta I_B = 50 \times 47.08 \mu\text{A} = 2.35 \text{mA}.$$

$$(ii) \quad V_{CE} = V_{CC} - I_C R_C \\ = 12 - (2.35 \text{mA})(2.2 \times 10^3) \\ = 6.83 \text{V}.$$


$$(iii) \quad V_{BE} = V_B - V_E \\ \therefore V_B = 0.7 \text{V}$$

$$V_{CE} = V_C - V_E \\ \therefore V_C = 6.83 \text{V}.$$

$$(iv) \quad V_{BC} = V_B - V_C \\ = 0.7 - 6.83 \\ = -6.13 \text{V}.$$

Module 2

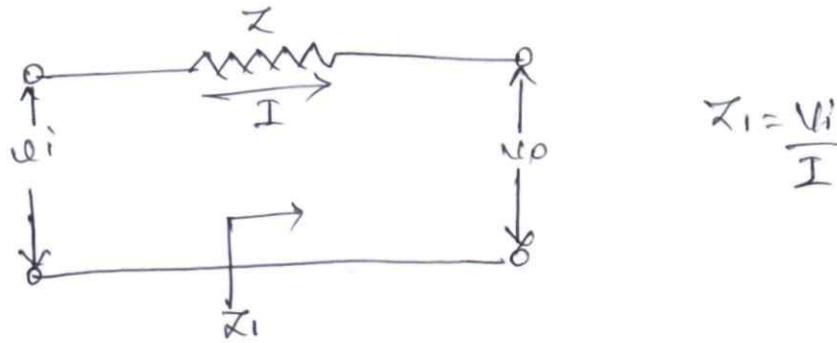3(a) state & prove dual of Miller's theorem. (6M)




$$Z_1 = \frac{V_i}{I}$$

where, $I = \frac{V_i - V_o}{Z} = \frac{V_i \left[1 - \frac{V_o}{V_i} \right]}{Z}$

$$\therefore Z_1 = \frac{Z}{1 - A_v} = \frac{Z}{1 - k}$$

Miller's theorem states that effect of resist Z on the o/p ckt is ratio of V_o to current I which flows from o/p to i/p.

$$\therefore Z_2 = \frac{V_o}{I}$$

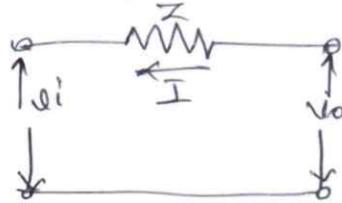

where, $I = \frac{V_o - V_i}{Z} = \frac{V_o \left[1 - \frac{V_i}{V_o} \right]}{Z}$

$$= \frac{V_o \left[1 - \frac{1}{A_v} \right]}{Z}$$

$$= \frac{V_o \left[\frac{A_v - 1}{A_v} \right]}{Z}$$

$$\therefore Z_2 = \frac{Z k}{k - 1}$$

$\therefore Z_2 = \frac{V_o}{I} \quad \therefore \frac{V_o}{V_i} = A_v = k$

3(b) Define h parameters. Draw the h-parameter model of a transistor in CE mode. (6M)

$$\rightarrow h_{11} = \frac{V_i}{I_i} \Big|_{V_o = 0}$$

$$h_{12} = \frac{V_i}{V_o} \Big|_{I_i = 0}$$

$$h_{21} = \frac{I_o}{I_i} \Big|_{V_o = 0}$$

$$h_{22} = \frac{I_o}{V_o} \Big|_{I_i = 0}$$

from the above discussion we say that all 4 parameters are not the same. They are different & all have different units. Hence called as hybrid parameters.


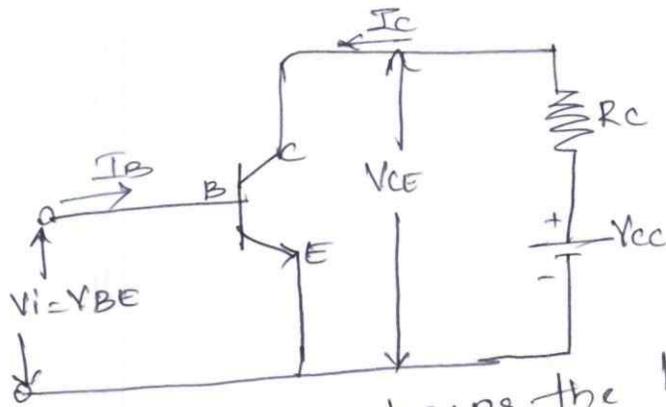


fig below shows the h-parameter equivalent model

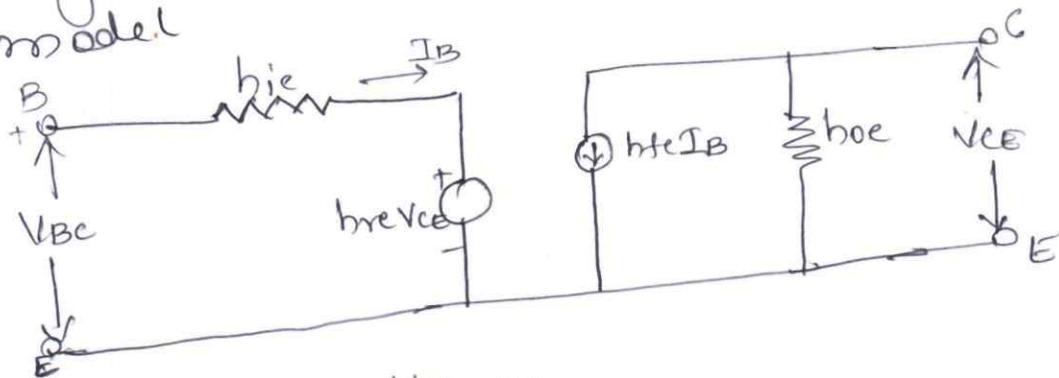

we can write as,

$$V_{be} = h_{ie} I_B + h_{re} V_{CE}$$

$$I_C = h_{fe} I_B + h_{oe} V_{CE}$$


$$h_{ie} = \frac{\Delta V_{be}}{\Delta I_B} \Big|_{V_{CE} \text{ constant}}$$

$$h_{re} = \frac{\Delta V_{BE}}{\Delta V_{CE}} \Big|_{I_B \text{ constant}}$$

$$h_{fe} = \frac{\Delta I_C}{\Delta I_B} \Big|_{V_{CE} \text{ constant}}$$

$$\} h_{oe} = \frac{\Delta I_C}{\Delta V_{CE}} \Big|_{I_B \text{ constant}}$$

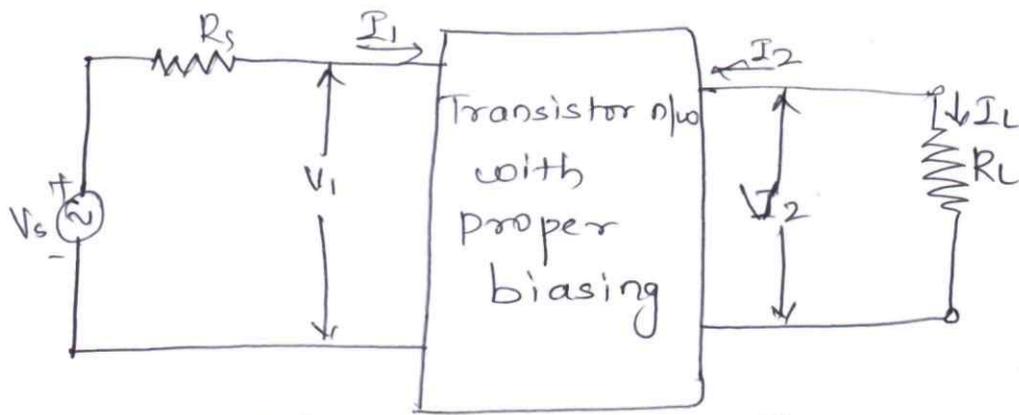(3c) Obtain midband analysis of BJT single stage amplifier. Derive expression for A_I & Z_i (8M)



* Current Gain: - $A_I = \frac{I_L}{I_1} = \frac{-I_2}{I_1}$

from ckt, $I_2 = h_f I_1 + h_o V_2$

$\therefore I_2 + h_o I_2 R_L = h_f I_1$

$\therefore (1 + h_o R_L) I_2 = h_f I_1$

$\therefore \frac{I_2}{I_1} = \frac{h_f}{1 + h_o R_L}$

$\therefore A_I = \frac{-I_2}{I_1} = \frac{-h_f}{1 + h_o R_L}$

* Input Impedance (Z_i)

$R_i = \frac{V_1}{I_1}$

\therefore from i/p ckt we have,

$V_1 = h_i I_1 + h_r V_2$

$\therefore Z_i = \frac{V_1}{I_1} = \frac{h_i I_1 + h_r V_2}{I_1}$

$\therefore Z_i = \frac{h_i - h_r h_f R_L}{1 + h_o R_L}$

OR



4a) Mention various Capacitors effects on freq response. Derive expression for miller's i/p & o/p Capacitance (10m)

→ 1) effect of Coupling Capacitors:-

$$X_c = \frac{1}{2\pi f C}$$

2) effect of Bypass Capacitors.

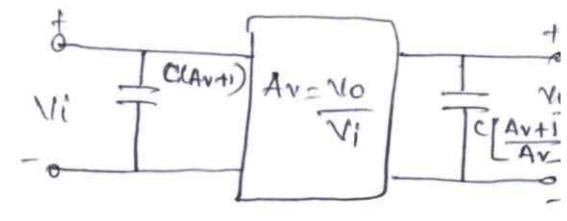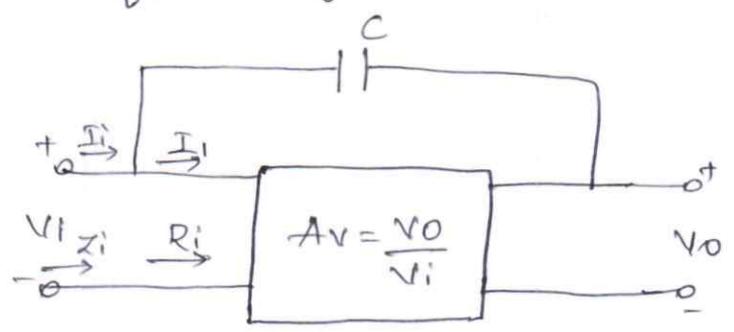3) effect of Internal transistor capacitances



let $I_i = I_1 + I_2$

$$I_i = \frac{V_i}{Z_i} \quad \& \quad I_1 = \frac{V_i}{R_i}$$

$$\& \quad I_2 = \frac{V_i - V_o}{X_c} = \frac{V_i - A_v V_i}{X_c} = \frac{(1 - A_v) V_i}{X_c}$$

$$\therefore I_i = \frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{(1 - A_v) V_i}{X_c}$$

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{CM}}$$

$$\frac{1}{2\pi f C_M} = \frac{1}{(1 - A_v)(2\pi f C)}$$

$$\therefore \frac{1}{C_M} = \frac{1}{C(1 - A_v)}$$

$$\therefore \boxed{C_M = (1 - A_v) C}$$

Applying KCL we have

$$I_o = I_1 + I_2$$

where $I_1 = V_o/R_o$ & $I_2 = \frac{V_o - V_i}{X_c}$

$$I_0 \approx \frac{V_0 - V_i}{X_C}$$

$$\therefore I_0 = \frac{V_0 - V_0/A_v}{X_C} = \frac{V_0(1 - 1/A_v)}{X_C}$$

$$\& \frac{I_0}{V_0} = \frac{1 - 1/A_v}{X_C}$$


$$\text{or } \frac{V_0}{I_0} = \frac{X_C}{1 - 1/A_v} = X_{CMO}$$

$$\therefore X_{CMO} = \frac{X_C}{1 - 1/A_v}$$

$$\frac{1}{2\pi f C_{MO}} = \frac{1}{2\pi f C (1 - 1/A_v)}$$

$$\therefore \boxed{C_{MO} = C(1 - 1/A_v)}$$

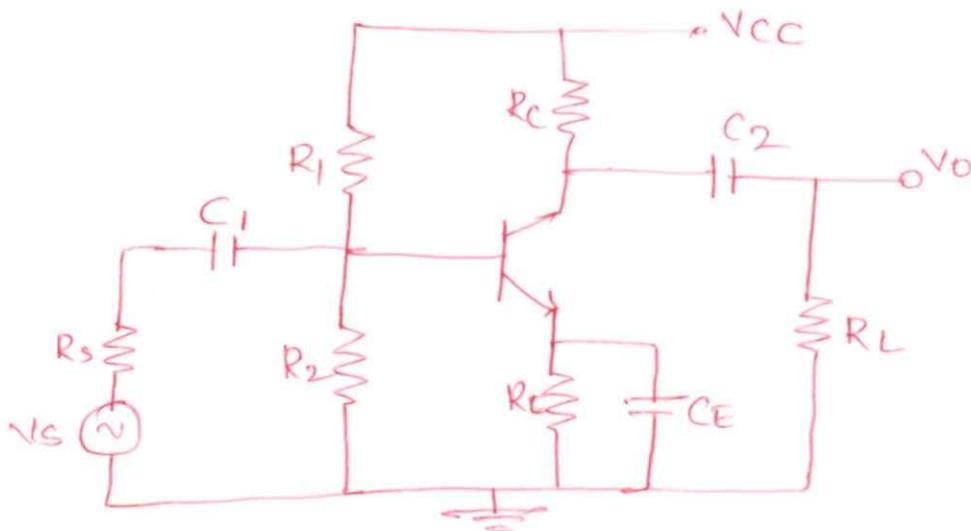4(b) Consider a single stage amplifier with, $R_s = 1K\Omega$, $R_1 = 50K$, $R_2 = 2K$, $R_c = 2K$, $R_L = 20$, $h_{fc} = 50$, $h_{ie} = 1.1K$, $h_{oe} = 25 \mu A/V$ & $h_{re} = 2.5 \times 10^{-4}$ as shown in fig. find A_i , R_i , R_o , A (10M)



$$\text{Sol}^n \rightarrow R_i = R_1 \parallel R_2 \parallel h_{ie}$$

$$= \left(\frac{1}{50K} + \frac{1}{2K} + \frac{1}{1.1K} \right)^{-1}$$

$$\approx 700 \Omega$$

(2) Voltage Gain (A_v)

$$A_v = \frac{-h_{fe} (R_c \parallel R_L)}{h_{ie}}$$

$$R_c \parallel R_L = 2k \parallel 2k = 1k\Omega$$

$$A_v = \frac{-50 \cdot 1k}{1.1k} \approx -45.45$$

(3) O/P Resistance (R_o)

$$R_o = R_c \parallel \left(\frac{1}{h_{oe}}\right)$$

$$= 2k \parallel \left(\frac{1}{25 \times 10^{-6}}\right)$$

$$= 2k \parallel 40k$$

$$= 1.905k\Omega$$

(4) Current Gain (A_i)

$$A_i = \frac{I_L}{I_s} = A_v \cdot \frac{R_i}{R_L}$$

$$A_i = -45.45 \times \frac{700}{2000}$$

$$\approx -15.9$$


Module - 3

5(a)

explain the need of a cascading amplifier
Draw & explain block diagram of 2 stage
Cascade Amplifier (8M)

→ When the amplification from a single stage amplifier is not sufficient for a particular purpose, or when the i/p or o/p impedance is not of suitable magnitude, then two or more amplifier stages are connected in

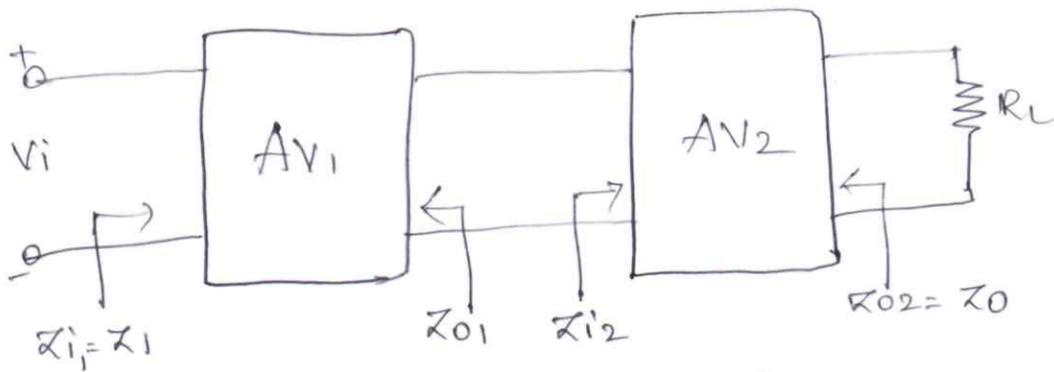Cascade. The cascade of CE & CB stages is called cascade amplifier.



$$Z_i = Z_{i1} \quad \& \quad Z_o = Z_{o3}$$

$$A_{VT} = \frac{V_o}{V_i}$$


$$A_{VT} = \frac{V_o}{V_{i2}} \cdot \frac{V_{i2}}{V_i}$$

$$A_{VT} = \frac{V_o}{V_i}$$

$$A_{VT} = A_{V1} \cdot A_{V2}$$

$$A_{IT} = -A_{VT} \cdot \frac{Z_i}{R_L}$$

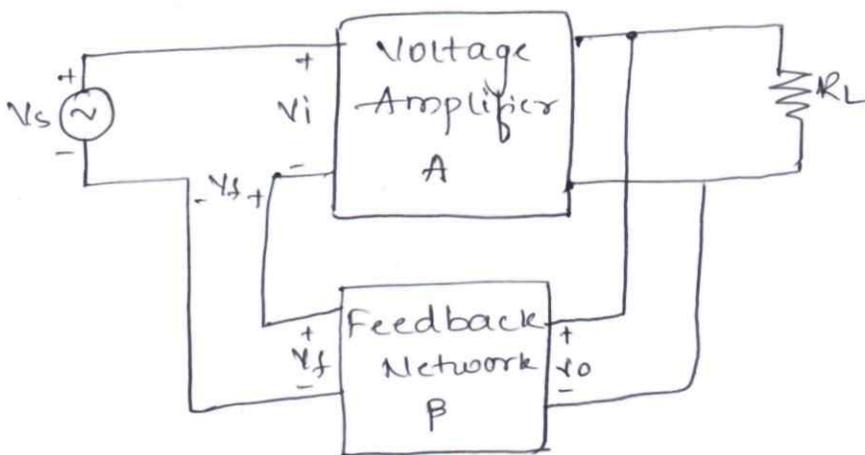5b) For voltage series feedback Amplifier.
derive an expression for i/p & o/p impd (SM)



Transfer gain without f/b

$$A = \frac{V_o}{V_i}$$

Transfer gain with f/b $A_f = \frac{V_o}{V_i}$

$$A = A_v \quad \& \quad A_f = A_v f$$

$$\therefore \beta = \frac{V_f}{V_o}$$

$$\text{or } \boxed{V_f = \beta V_o}$$

5(c) A f/b amplifier has a gain of 1000 without f/b. Find the gain with f/b for a negative f/b of 10%. (gain in dB). (4M)

$$\rightarrow A = 1000$$


$$\beta = 10\% = 0.1$$

$$A_f = \frac{A}{1 + A\beta}$$

$$A_f = \frac{1000}{1 + 1000(0.1)} \approx 9.90$$


$$\begin{aligned} \text{Gain (dB)} &= 20 \log_{10}(A_f) \\ &= 20 \log_{10}(9.90) \\ &= 19.91 \text{ dB} \end{aligned}$$

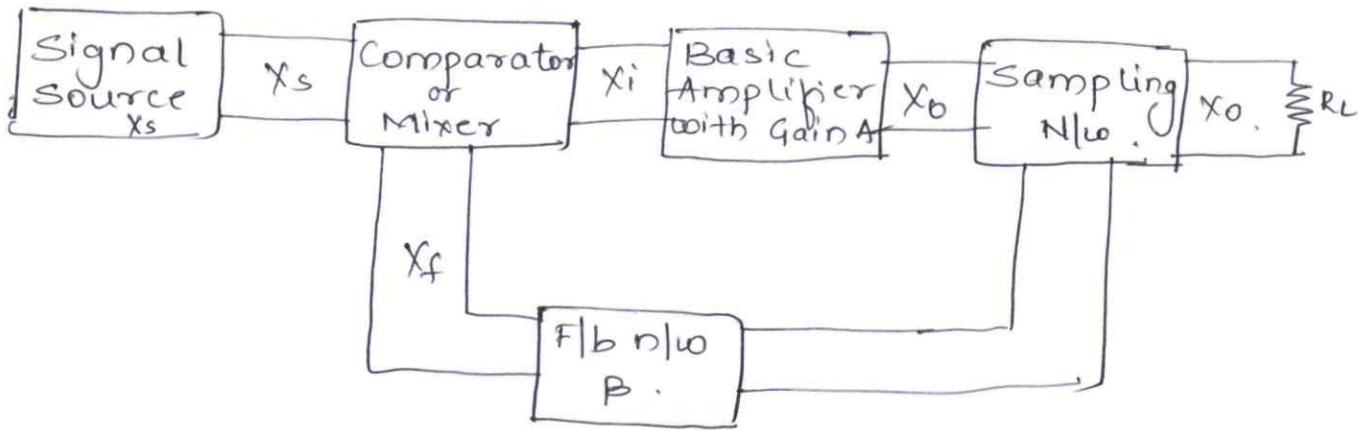6a) Draw a f/b amplifier in block diagram form. Identify each block & explain its functions (10M)




* Signal Source :-

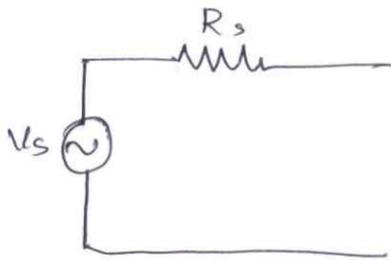It may be either a vltg source or a current source. vltg source is represented by Thevinin's Representation & current source by Norton's form.




← Thevinin's form.

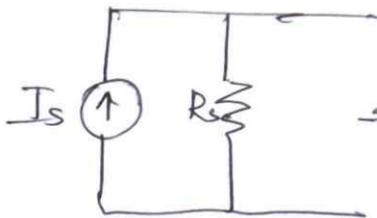


← Norton's form

* Comparator or Mixer :-

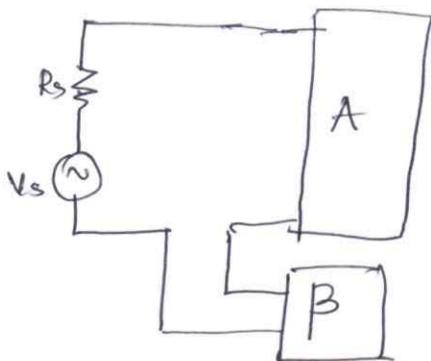There are of 2 types of mixing possible, either series mixing or shunt mixing.



series mixing


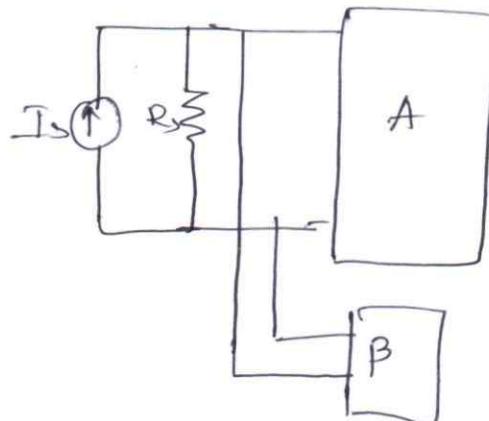


shunt mixing

* Amplifier :- $A_v = \frac{V_o}{V_i}$ $A_I = \frac{I_o}{I_i}$
 $A_{V_s} = \frac{V_o}{V_s}$ $A_{I_s} = \frac{I_o}{I_s}$

* Sampling N/w:

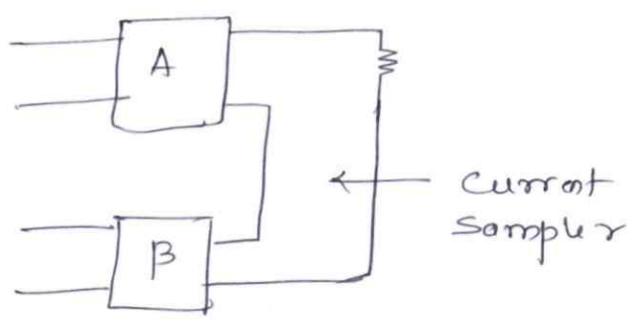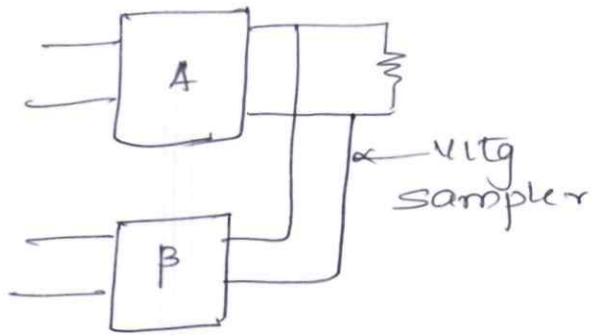
Depending upon the o/p, it may be either voltage or current sampling.



* feedback n/w β , consists of all passive elements. In many cases 'R' only is used.

(b) For the Darlington Emitter follower shown in fig, calculate.

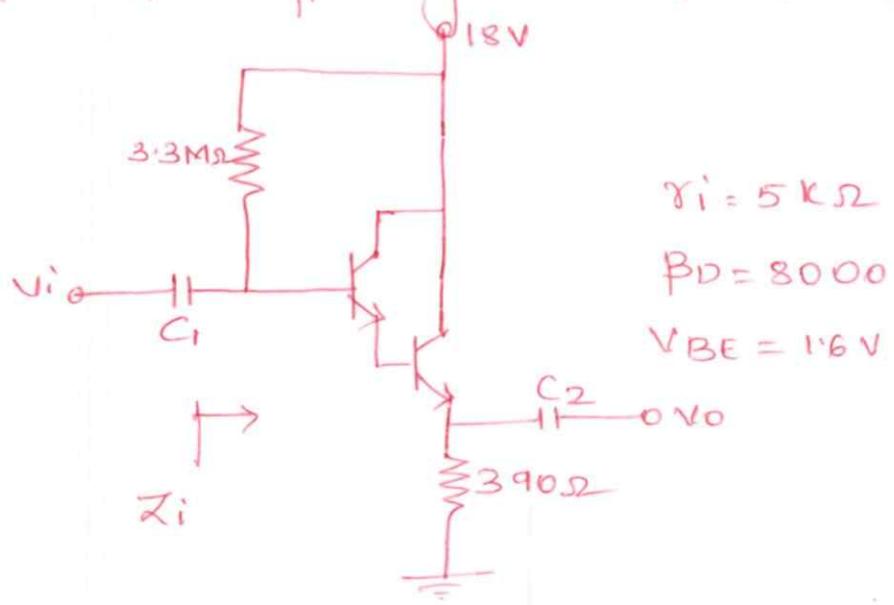- (i) DC bias V_{tg} , V_B , V_C & V_E & current I_B & I_C
- (ii) I_P & o/p impedances
- (iii) V_{tg} & current gains.
- (iv) AC o/p x_{tg} for $V_i = 120mV$ (10M)



$r_i = 5k\Omega$
 $\beta_D = 8000$
 $V_{BE} = 1.6V$

(i)

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta_D R_E}$$

$$= \frac{18 - 1.6}{3.3M + (8000)(390)} = 2.55 \mu A$$

$$I_E = I_{E2} \approx I_{C2} = \beta_D I_B$$

$$= (8000)(2.55 \mu A) = 20.4 mA$$

$$V_E = I_E R_E = (20.4 mA)(390) = 7.96 V$$

$$V_B = V_{BE} + V_E = 1.6 + 7.96 = 9.56 V$$

$$\therefore V_C = V_{CC} = 18 V$$

ii)

$$Z_b = r_i + (1 + \beta_D) R_E$$

$$= 5k + (8001)(390)$$

$$= 3.13 M\Omega$$

$$r_i = R_B || Z_b = 3.3 M\Omega || 3.13 M\Omega$$

$$= 1.6 M\Omega$$

$$Z_o = r_i || R_E || \frac{r_i'}{\beta_D}$$

$$= 5k || 390 || \frac{5k}{8000} = 0.625 \Omega$$

(3)

$$A_v = \frac{R_E (1 + \beta_D)}{r_i + R_E (1 + \beta_D)}$$

$$= \frac{390 (8001)}{5k + 390 (8001)}$$

$$= \frac{390 (8001)}{5k + 390 (8001)}$$

$$= 0.998$$

$$= 0.998$$

(4)

$$A_I = \frac{\beta_D R_B}{R_B + \beta_D R_E}$$

$$= \frac{8000 (3.3M)}{3.3M + (8000)(390)}$$

$$= \frac{8000 (3.3M)}{3.3M + (8000)(390)} = 4 || 2.15$$

(5)


$$V_o = A_v V_i = (0.998)(120 mV)$$

$$= 119.76 mV$$

(a) Analyze the working of series fed directly coupled class A power amplifier with efficiency (8m)

→ The simple fixed bias ckt can be used to discuss class A series fed amplifier.

* DC Analysis.

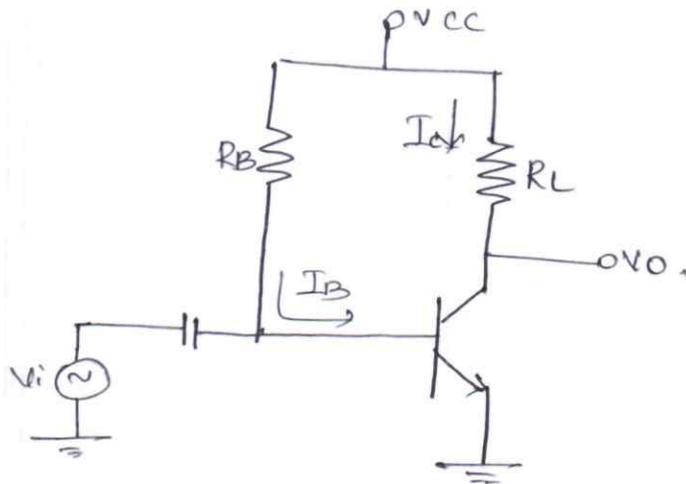

Applying KVL to base loop, we get.

$$V_{CC} - I_B R_B - V_{BE} = 0.$$

$$\boxed{I_B = \frac{V_{CC} - V_{BE}}{R_B}} \quad \text{--- (1)}$$

$$I_C = \beta I_B. \quad \text{--- (2)}$$

Applying KVL to CE loop.

$$V_{CC} - I_C R_L - V_{CE} = 0.$$

$$\boxed{I_C = \frac{V_{CC} - V_{CE}}{R_L}} \quad \text{--- (3)}$$

∴ Equⁿ (3) can be written as.

$$I_C = \left(-\frac{1}{R_L}\right) V_{CE} + \frac{V_{CC}}{R_L}$$

where slope of line is $(-1/R_L)$.

* AC Analysis

$$P_{o(ac)} = \frac{V_{CE(p-p)} \cdot I_{C(p-p)}}{8}$$

$$\therefore \% \eta = \frac{P_{o(ac)}}{P_{i(dc)}} \times 100.$$

$$V_{max} = V_{cc} \quad , \quad V_{min} = 0.$$


$$I_{max} = 2I_c \quad , \quad I_{min} = 0.$$

$$\therefore \% \eta = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8V_{cc} \cdot I_c} \times 100$$

$$= \frac{(V_{cc} - 0)(2I_c - 0)}{8V_{cc} I_c} \times 100$$

$$\boxed{\% \eta = 25\%}$$

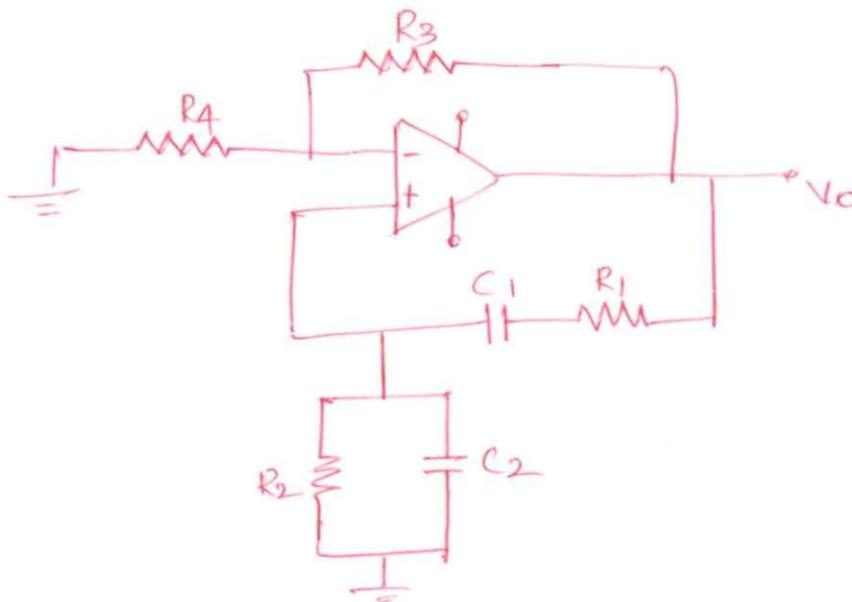7b) Design the component values of Wein bridge oscillator for freq of oscillations of 4KHz. (4m)



Solⁿ:

$$\text{Let } R_1 = R_2 = R \quad \& \quad C_1 = C_2 = C.$$

$$f = \frac{1}{2\pi RC}$$

$$\text{let } C = 0.01\mu F$$

$$R = \frac{1}{2\pi f C} = \frac{1}{2\pi (4\text{KHz})(0.01\mu F)} = 3.97\text{K}\Omega.$$

$$\text{for sustained oscillations } \frac{R_3}{R_4} > 2$$



$$R_3 \geq 2R_4$$

let $R_4 = 10k\Omega$



then, $R_3 \geq 20k\Omega$

∴ select $R_3 = 30k\Omega$

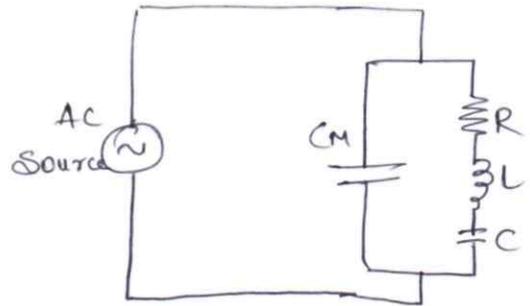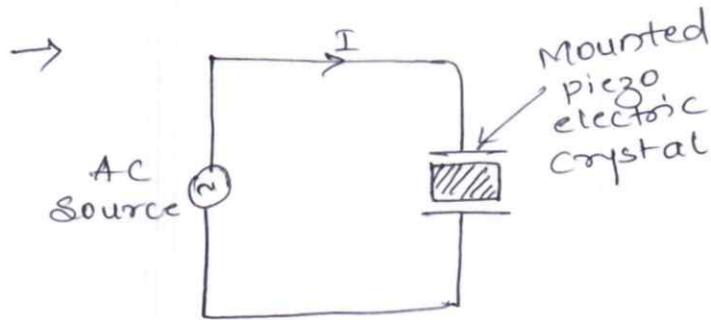7(c) Explain the characteristics of crystal with neat diagram, explain crystal oscillations in series resonance ckt. (8m)



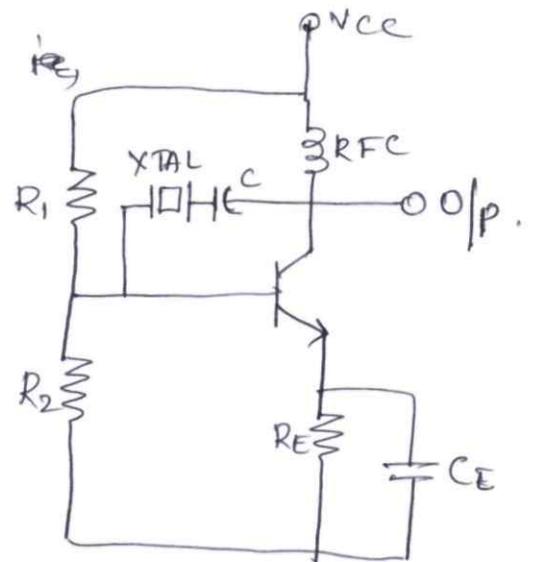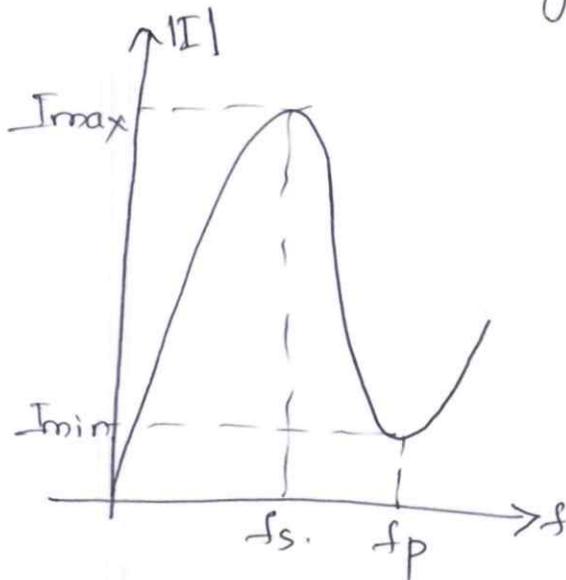Here, $L =$ elect. equivalent inductance of crystal
 $C =$ " " capacitance " "
 $R =$ " " resistance " "
 $C_M =$ Mounting capacitance.



$$\text{i.e., } \omega L = \frac{1}{\omega C}$$


$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$f = f_s = \frac{1}{2\pi\sqrt{LC}}$$

8(a) Explain the basic principle of Oscillator (6m)

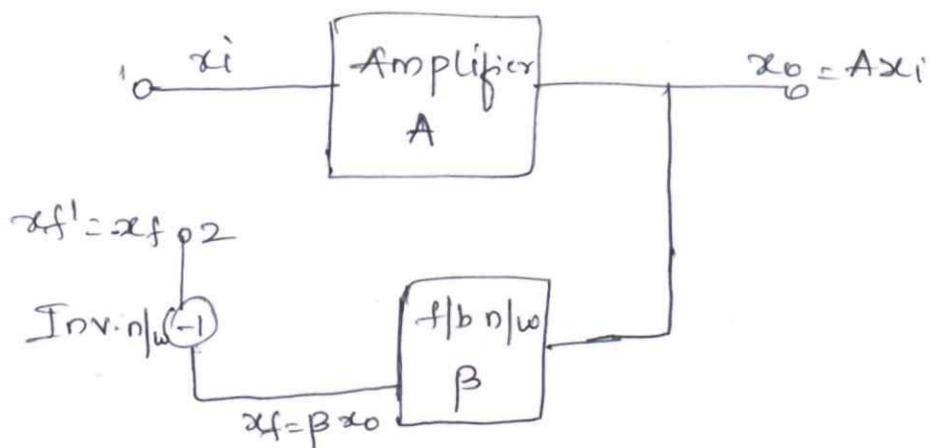→ An Oscillator is a ckt, designed to provide periodic o/p with no i/p signal. It requires only DC power. It is basically an amplifier with positive feedback.



$$x_f = \beta x_o = A\beta x_i$$

& o/p in r n/w is $x_f' = -x_f = -A\beta x_i$.

$$\text{Now, Loop gain} = \frac{x_f'}{x_i} = \frac{-A\beta x_i}{x_i} = -A\beta$$

$$\text{Loop gain} = -A\beta = 1$$

$$-A\beta = 1 + j0$$

$$-A\beta = 1 \angle 0 \text{ or } 360.$$

$$-A\beta = |-A\beta| \angle 0.$$

$$\angle 0 = \angle -A\beta = 0^\circ \text{ or } 360^\circ.$$

8(b) An ideal class B push pull amplifier with i/p is o/p transformer has $V_{CC} = 20V$, $N_2 = 2N_1$ & $R_L = 20\Omega$. The transistor has $h_{fe} = 20$. Let i/p be sinusoidal. for max. o/p signal at $V_{CE(p)} = V_{CC}$

Determine (i) o/p signal power.

(ii) collector dissipation in each transistor.

(iii) conversion η

(6m)

→ Given : $V_{CC} = 20V$

$$R_L = 20\Omega$$

$$N_2 = 2N_1$$

or $\frac{N_1}{N_2} = 0.5$

$$V_{CE(p)} = V_{CC} = 20V$$

(i) $P_{O(ac)} = \frac{V_{CE}^2(p)}{2R_L'}$

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 R_L = 0.5^2 \times 20 = 5\Omega.$$

$$\therefore P_{O(ac)} = \frac{20^2}{(2)(5)} = 40W.$$

(ii) $P_{2(Q)} = P_i(dc) - P_{O(ac)}$

$$P_i(dc) = \frac{2}{\pi} V_{CC} I_{C(p)}$$

$$\therefore I_{C(p)} = \frac{V_{CE(p)}}{R_L'} = \frac{V_{CC}}{R_L'}$$

we get $P_i(dc) = \frac{2}{\pi} \frac{V_{CC}^2}{R_L'} = \frac{2(20V)^2}{\pi \cdot 5} = 50.93W.$

~~miss~~ $P_{2(Q)} = 50.93 - 40 = 10.93W.$

$$P_Q = \frac{P_{2(Q)}}{2} = \frac{10.93}{2} = 5.46W.$$


(iii) $\% \eta = \frac{P_{O(ac)}}{P_i(dc)} \times 100.$

$$= \frac{40}{50.93} \times 100 = 78.4\%.$$

8(c) Discuss the different types of power Amplifiers - - (8m)


- 1) Class A power Amplifier
- 2) Class B power Amplifier
- 3) class C power Amplifier
- 4) Class AB power Amplifier
- 5) class D power Amplifier

1) Class A power Amplifier

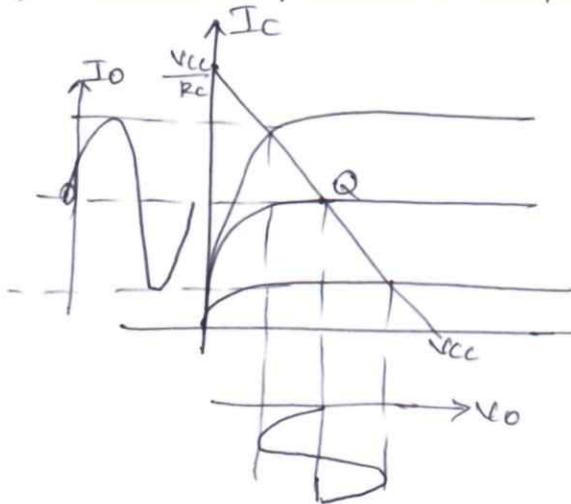

In, Class A power amp Q. pt is located at centre of load line. So o/p varies for 360° cycle of i/p signal

2) Class B power Amplifier

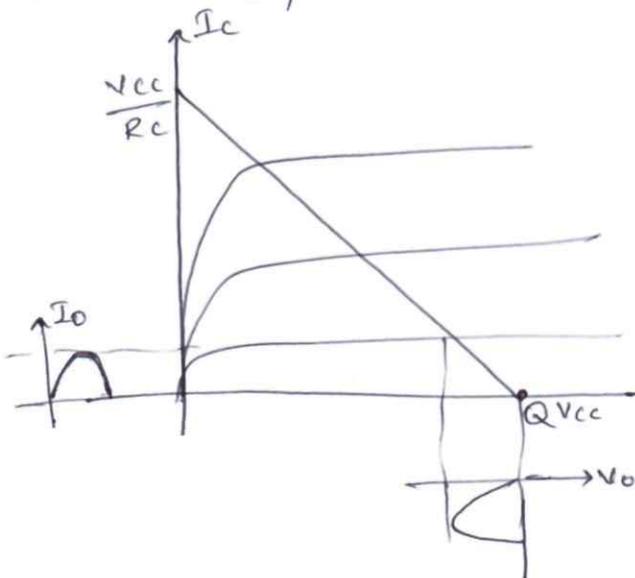

In class B, power amplifier, Q. pt is located at the cutoff region of load.

So, o/p varies for 180° of the i/p signal

3) Class AB: In class AB power amp, Q pt is selected such that o/p signal obtained is more than 180° but less than 360° of the i/p signal.

4) Class C: In class C, amplifier Q pt is located below the cutoff region. So o/p signal varies for less than a half cycle i/p.

5) Class D: In class D power amplifier, o/p is designed to operate with digital signals ON/OFF.

9a) Explain the basic operation & characteristics of n-channel depletion type MOSFET? (10M)

→ WKT, $I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$ — (1)

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right] \text{ — (2)}$$

where $g_{m0} = \frac{2I_{DSS}}{|V_P|}$ — (3)

Note! 1) In JFET, V_{GS} can be negative for n-channel devices & positive for p-channel.

Hence, g_m is always less than g_{m0} .
But for DMOSFET, V_{GS} can be of either polarity.


(2) for ex: if V_{GS} is -ve for an n-channel device, the device operates in depletion mode

ie, $g_m < g_{m0}$ & $I_D < I_{DSS}$ from (1) & (2)

(3) On other hand, if V_{GS} is +ve, the device operates in enhancement mode.

In this mode, $g_m > g_{m0}$ & $I_D > I_{DSS}$.



* small signal model & symbol of DMOSFET

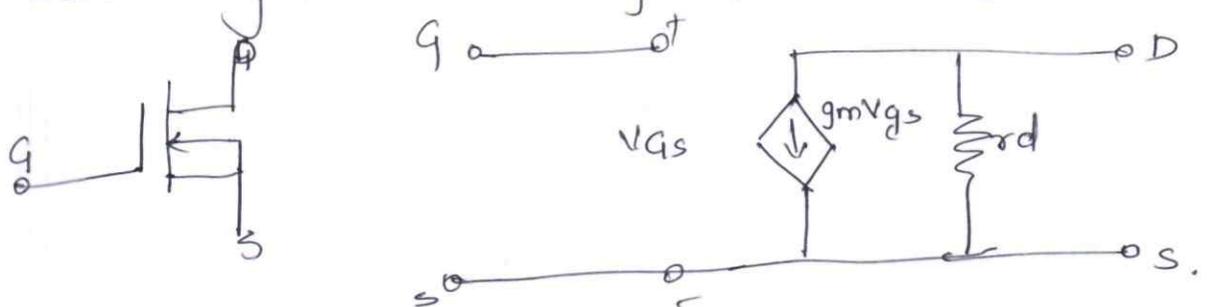


i) It is exactly same as JFET

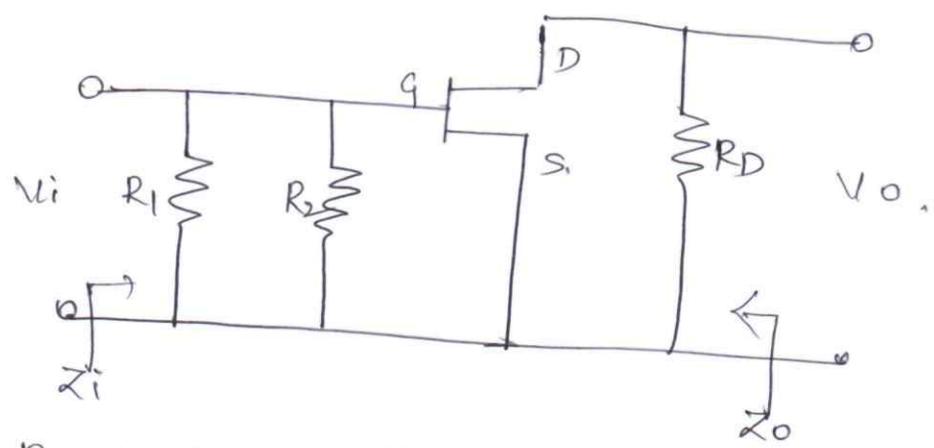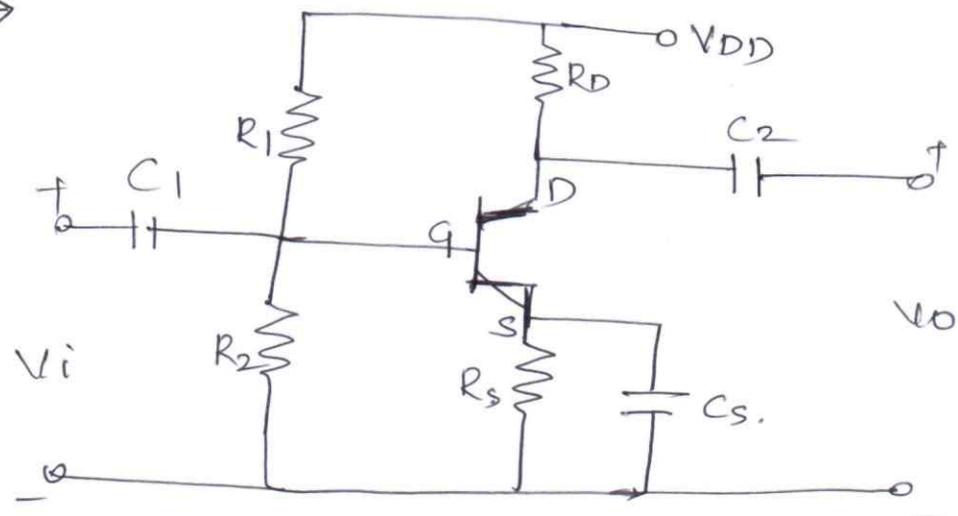ii) only difference is value of g_m .

9b) Derive expression for Z_i , Z_o & A_v for Vtg divider Biasing ckt using JFET --- (10m).



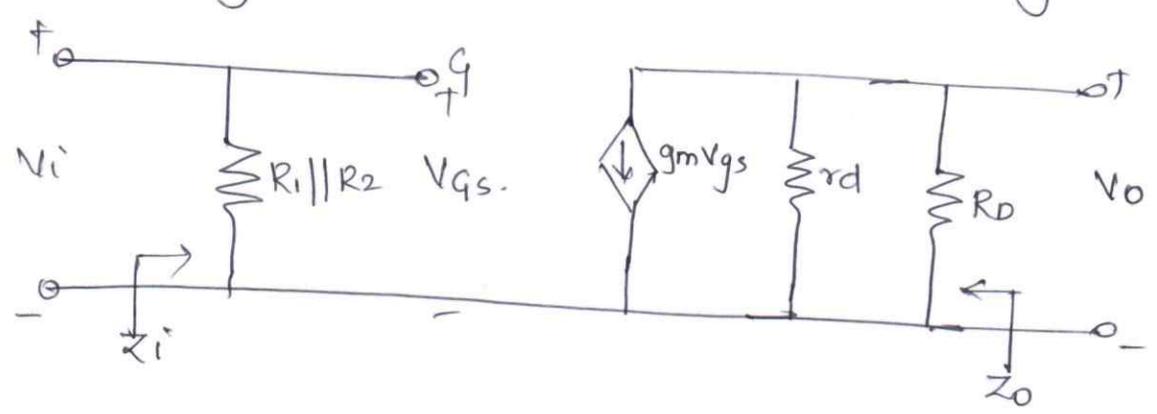Replacing JFET with small signal ac model



$$\therefore Z_i = R_1 \parallel R_2$$

$$Z_o = r_d \parallel R_D$$

$$\& A_v = -g_m (r_d \parallel R_D)$$


for $r_d \gg 10R_D$.

$$Z_i = R_1 \parallel R_2$$

$$Z_o = R_D$$

$$A_v \approx -g_m R_D$$

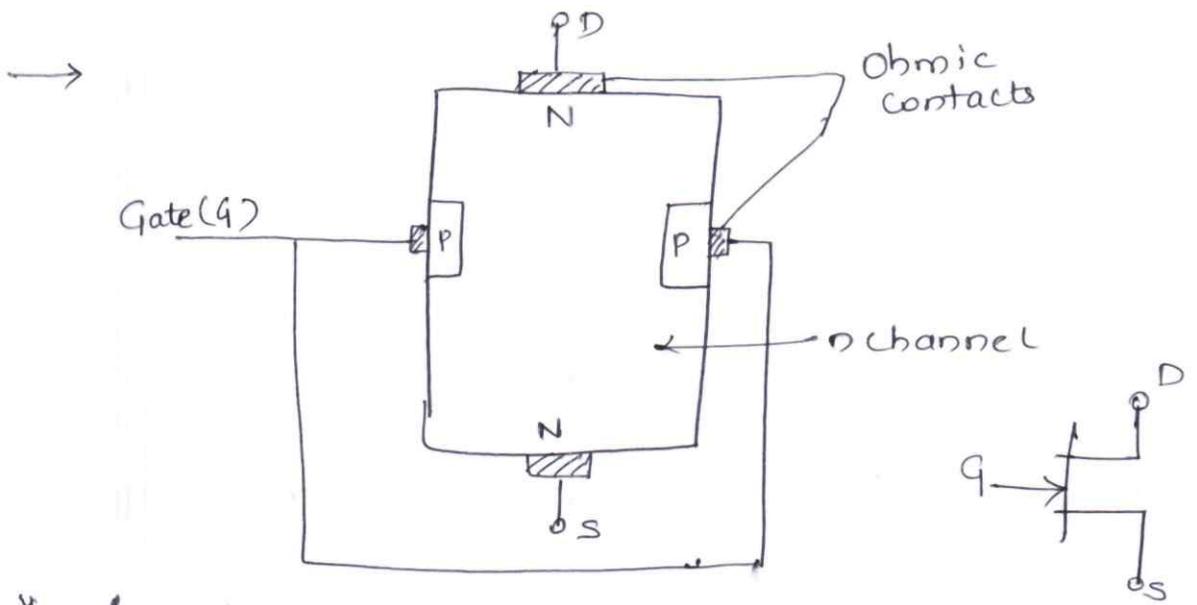10(a) With neat diagram explain construction of n channel JFET. — (10M)



- * A piece of n type material is referred to as channel.
- * It has 2 smaller pieces of p-type material forming a pn junction.
- * The channel ends are designated as Drain & source.
- * The 2 pieces of p-type material are connected together & their terminal is called as Gate.
- * Since the channel is of n-type it is called as n channel JFET.

10(b). Data sheet for a JFET indicates that $I_{DSS} = 10\text{mA}$ & $V_{GS(off)} = -4\text{V}$. Determine the drain current for $V_{GS} = 0\text{V}, -1\text{V}$ & -4V (6M)

$$\rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

$$I_{DSS} = 10\text{mA}$$

$$V_{GS(off)} = -4\text{V}$$

Case 1: $\rightarrow V_{GS} = 0\text{V}$

$$I_D = 10 \left(1 - \frac{0}{-4} \right)^2 = 10 \times 1^2 = 10\text{mA}$$

Case 2: $V_{GS} = -1V$

$$\begin{aligned} I_D &= 10 \left(1 - \frac{-1}{-4} \right)^2 = 10 (1 - 0.25)^2 \\ &= 10 \times 0.75^2 \\ &= 10 \times 0.5625 \\ &= 5.625 \text{ mA} \end{aligned}$$

Case 3: $V_{GS} = -4V$

$$\begin{aligned} I_D &= 10 \left(1 - \frac{-4}{-4} \right)^2 = 10 (1 - 1)^2 \\ &= 0 \text{ mA} \end{aligned}$$

10c) Discuss the difference b/w JFET & MOSFET.

→ JFET	MOSFET. (AM)
1) Junction Field Effect Transistor.	1) Metal Oxide Semiconductor field effect transistor.
2) PN junction b/w gate & channel	2) Gate insulated by SiO_2 layer
3) High i/p impedance	3) Very high.
4) Operates in Depletion mode	4) Both Depletion & Enhancement mode
5) Slow speed	5) Faster switching speed.

Borke

Prof
6/6/25

G. V. S.

HEAD
Dept. of Electrical & Electronics Engg
KLS's V. D. Institute of Technology
HALIYAL-581 328