

# KLS Vishwanathrao Deshpande Institute of Technology

(Accredited by NAAC with "A" Grade)

(Approved by AICTE, New Delhi, Affiliated to VTU, Belagavi)

(Recognized Under Section 2(f) by UGC, New Delhi)

Udyog Vidya Nagar, Haliyal - 581 329, Dist.: Uttara Kannada


www.klsvdit.edu.in | principal@klsvdit.edu.in | hodece@klsvdit.edu.in




**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

## University / Model Question Paper Scheme & Solution

Faculty Name	:	Dr. Nagaraj Bhat
Course Name	:	Network Analysis
Course Code	:	BEC304
Year of Question Paper	:	Dec 2024- Jan 2025
Date of Submission	:	

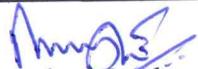  
Faculty Member

  
Head of the Department  
Dept. of Electronic & Communication Engg.  
KLS V.D.N.T. HALIYAL (U.K.)

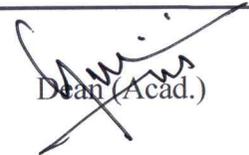  
Dean (Acad.)

# CBCGS SCHEME

USN

BEC304





## Third Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025 Network Analysis

Time: 3 hrs.





Max. Marks: 100



*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.  
2. M : Marks , L: Bloom's level , C: Course outcomes.*

Module – 1			M	L	C
Q.1	a.	Three impedances are connected in Delta. Obtain the star equivalent of the network.	7	L3	CO1
	b.	For the circuit shown in Fig. Q1(b). Find the voltage 'V' at node by using nodal analysis.  Fig. Q1(b) <div style="text-align: center;"> </div>	6	L3	CO1
	c.	Determine the current in 12Ω resistor shown in Fig. Q1(c) using source transformation method.  Fig. Q1(c) <div style="text-align: center;"> </div>	7	L3	CO1
<b>OR</b>					
Q.2	a.	Find the loop currents $I_1$ , $I_2$ , and $I_3$ in the circuit shown in Fig. Q2(a).  Fig. Q2(a) <div style="text-align: center;"> </div>	7	L3	CO1

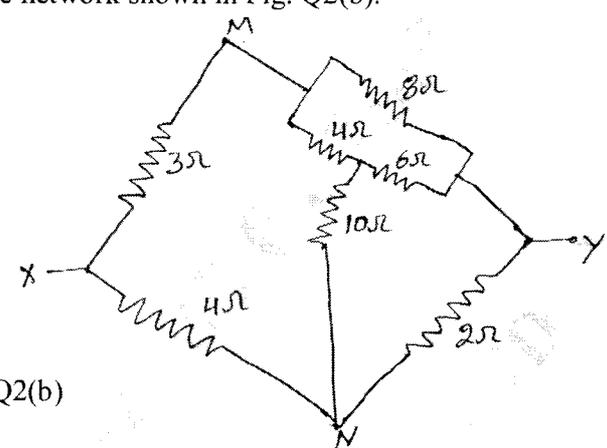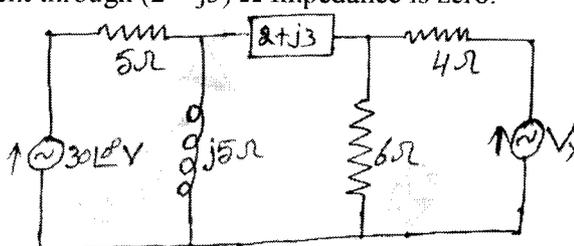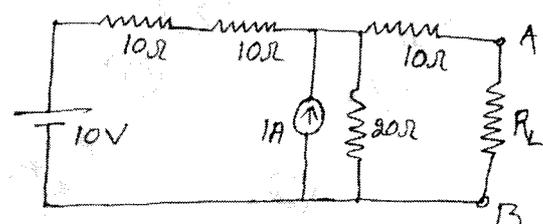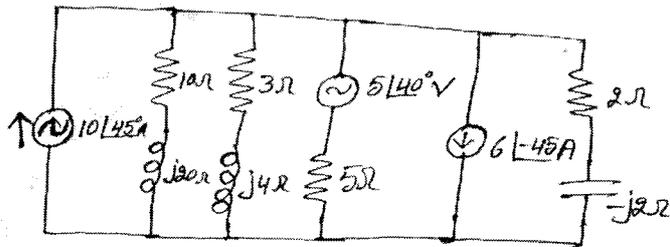
	<p><b>b.</b> Determine the resistance between the terminals X, Y using star delta transformation in the network shown in Fig. Q2(b).</p>  <p>Fig. Q2(b)</p>	6	L3	CO1
	<p><b>c.</b> Use the nodal analysis to find the value of <math>V_x</math> and the circuit shown in Fig. Q2(c). Such that the current through <math>(2 + j3) \Omega</math> Impedance is zero.</p>  <p>Fig. Q2(c)</p>	7	L3	CO1
<b>Module – 2</b>				
<b>Q.3</b>	<p><b>a.</b> State and prove Superposition theorem.</p>	7	L2	CO2
	<p><b>b.</b> For the circuit shown in Fig. Q3(b), obtain the Thevenin's equivalent circuit.</p>  <p>Fig. Q3(b)</p>	7	L3	CO2
	<p><b>c.</b> Using Millman's theorem, find current flowing through <math>(3 + j4) \Omega</math> impedance for the circuit shown in Fig. Q3(c).</p>  <p>Fig. Q3(c)</p>	6	L3	CO2

OR

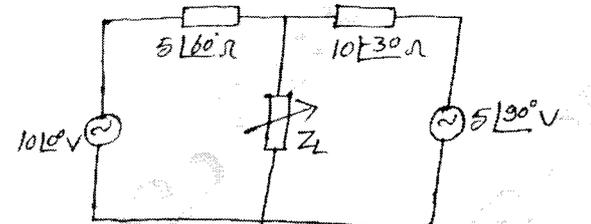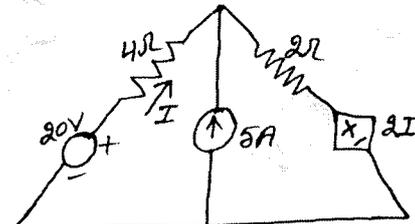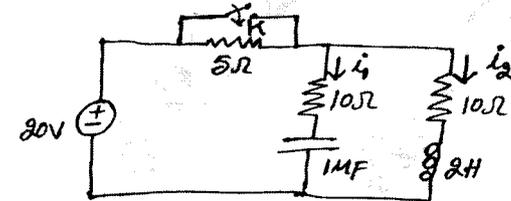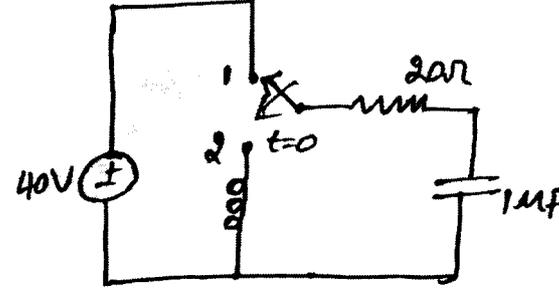
Q.4	<p>a. State and prove Norton's theorem.</p>	7	L2	CO2
	<p>b. Find the value of <math>Z_L</math> for Maximum Power transfer and the value of Maximum power for the circuit shown in Fig. Q4(b).</p> <div style="text-align: center;">  </div> <p>Fig. Q4(b)</p>	6	L3	CO2
	<p>c. Find current 'I' using Super position theorem for the circuit shown in Fig. Q4(c).</p> <div style="text-align: center;">  </div> <p>Fig. Q4(c)</p>	7	L3	CO2
<b>Module – 3</b>				
Q.5	<p>a. Use the concepts of initial condition to illustrate the voltage behavior in inductor circuit for DC supply.</p>	6	L3	CO3
	<p>b. In the circuit steady state is reached with switch 'K' open. The switch is closed at <math>t = 0</math>. Compute <math>i</math>, <math>di/dt</math> and <math>d^2i/dt^2</math> at <math>t = 0^+</math>.</p> <div style="text-align: center;">  </div> <p>Fig. Q5(b)</p>	7	L3	CO3
	<p>c. The switch is moved from position (1) to position (2) at <math>t = 0</math>. The steady state has been reached before switching. Computer <math>i</math>, <math>di/dt</math> and <math>d^2i/dt^2</math> at <math>t = 0^+</math> for Fig. Q5(c).</p> <div style="text-align: center;">  </div> <p>Fig. Q5(c)</p>	7	L4	CO3
OR				

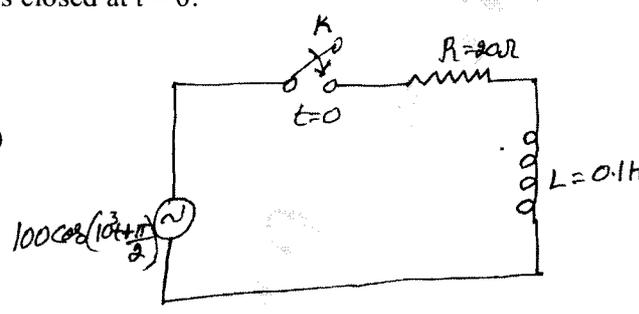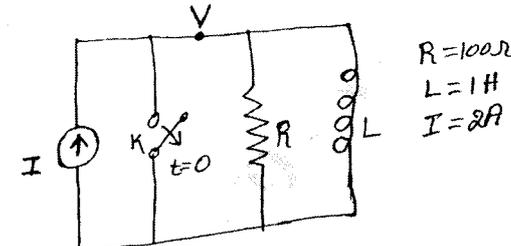
<p><b>Q.6</b></p>	<p><b>a.</b> In the circuit shown in Fig. Q6(a), determine complete solution for current when switch 'K' is closed at <math>t = 0</math>.</p>	<p><b>10</b></p>	<p><b>L3</b></p>	<p><b>CO3</b></p>
<p style="text-align: center;">Fig. Q6(a)</p> 				
	<p><b>b.</b> Compute <math>v</math>, <math>dv/dt</math>, <math>d^2v/dt^2</math> at <math>t = 0^+</math> for the circuit shown in below Fig. Q6(b), when the switch K is opened at <math>t = 0</math>.</p>	<p><b>10</b></p>	<p><b>L4</b></p>	<p><b>CO3</b></p>
<p style="text-align: center;">Fig. Q6(b)</p> 				

**Module - 4**

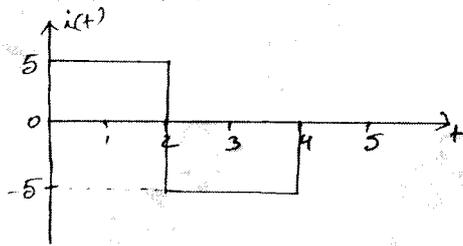
<p><b>Q.7</b></p>	<p><b>a.</b> Using waveform synthesis method to express the voltage pulse in terms of unit step. Find i) <math>L\{i(t)\}</math> ii) <math>L\{\int i(t).dt\}</math>.</p>	<p><b>8</b></p>	<p><b>L3</b></p>	<p><b>CO4</b></p>
<p style="text-align: center;">Fig. Q7(a)</p> 				
	<p><b>b.</b> State and prove initial value and final value theorem for Laplace transform.</p>	<p><b>6</b></p>	<p><b>L2</b></p>	<p><b>CO4</b></p>
	<p><b>c.</b> Obtain the Laplace transform of step and ramp function with relevant expressions.</p>	<p><b>6</b></p>	<p><b>L3</b></p>	<p><b>CO4</b></p>

**OR**


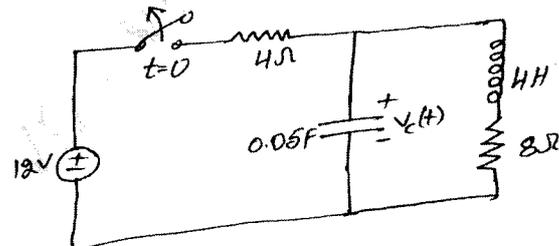
<p><b>Q.8</b></p>	<p><b>a.</b> Determine <math>i_L(t)</math> for <math>t \geq 0</math> using Laplace transform for circuit shown in Fig. Q8(a).</p>	<p><b>10</b></p>	<p><b>L3</b></p>	<p><b>CO4</b></p>
<p style="text-align: center;">Fig. Q8(a)</p> 				

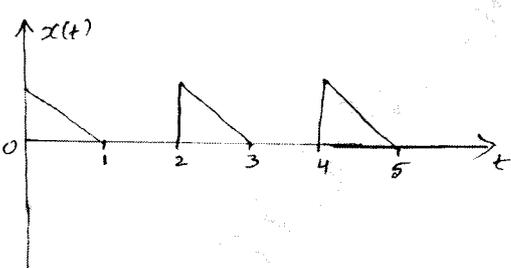	<p><b>b.</b> Find the Laplace transform of the periodic signal <math>x(t)</math> as shown in Fig. Q8(b).</p>  <p>Fig. Q8(b)</p>	10	L3	CO4
--	---	----	----	-----

**Module – 5**

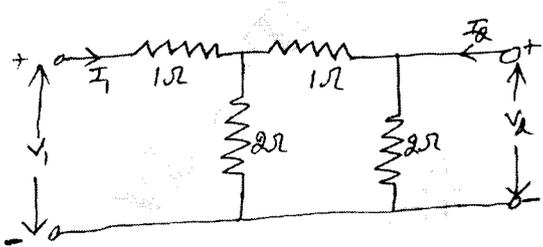
<b>Q.9</b>	<p><b>a.</b> Define Z – parameters. Determine Y parameters in terms of Z – parameters.</p>	6	L3	CO5
	<p><b>b.</b> Show that resonant frequency is geometric mean of cut off frequency in series R – L – C circuit.</p>	7	L3	CO5
	<p><b>c.</b> Apply the two – port network analysis technique to determine ABCD – parameters of the network shown in Fig. Q9(c).</p>  <p>Fig. Q9(c)</p>	7	L3	CO5

**OR**
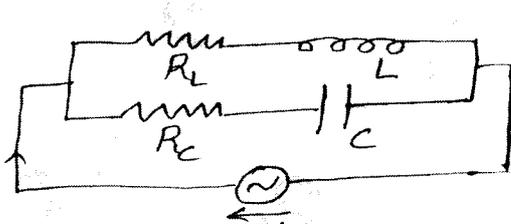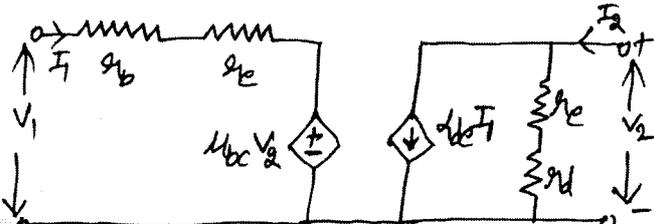
<b>Q.10</b>	<p><b>a.</b> Derive the expression for the resonant frequency of the circuit shown in Fig. Q10(a). Also show that the circuit resonates at all frequency if <math>R_L = R_C = \sqrt{\frac{L}{C}}</math>.</p>  <p>Fig. Q10(a)</p>	10	L3	CO5
	<p><b>b.</b> The model of a transistor in the CE mode is shown in Fig. Q10(b). Determine the h – parameters.</p>  <p>Fig. Q10(b)</p>	10	L3	CO5

\*\*\*\*\*

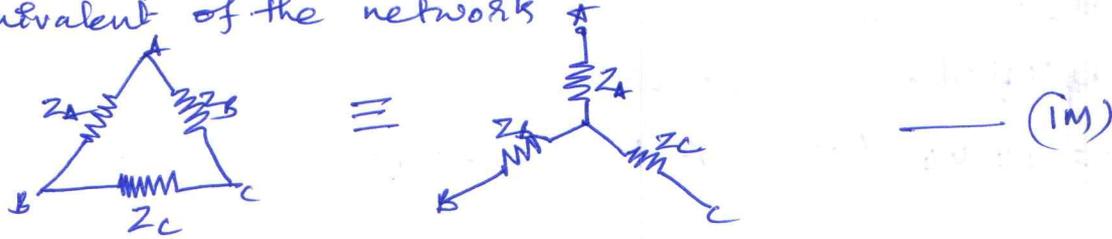1 a) Three impedances are connected in Delta. obtain the star equivalent of the network



Impedances Between A & B with C open in  $\Delta$  & Y is

$$Z_A + Z_B = \frac{Z_{AB} (Z_{BC} + Z_{CA})}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (1)}$$

Similarly  $Z_B + Z_C = \frac{Z_{BC} (Z_{AB} + Z_{CA})}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (2)}$  } 3M

Similarly  $Z_C + Z_A = \frac{Z_{CA} (Z_{AB} + Z_{BC})}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (3)}$


Solving Equations (1) - (2) + (3)

we get  $Z_A = \frac{Z_{AB} Z_{CA}}{\sum Z_{AB}} \quad \text{--- (4)}$  } 4M

Similarly  $Z_B = \frac{Z_{AB} Z_{BC}}{\sum Z_{AB}} \quad \text{--- (5)}$

Similarly  $Z_C = \frac{Z_{BC} Z_{CA}}{\sum Z_{AB}} \quad \text{--- (6)}$

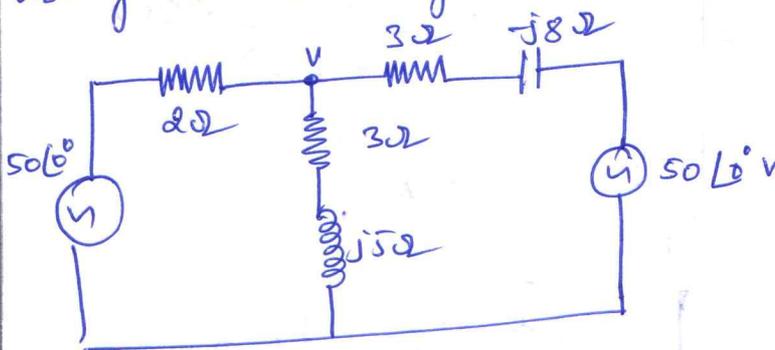1b) For the circuit shown find the voltage 'V' at node by using nodal analysis



Applying Nodal Analysis to the above circuit we get

$$\frac{V_1 - 50\angle 0^\circ}{2} + \frac{V_1 - 50\angle 0^\circ}{(3 - j8)} + \frac{V_1}{3 + j5} = 0 \quad \text{--- 2M}$$





Head of the Department  
Dept. of Electronic & Communication Engg.  
KLS VJIT, HALASJI (K.L.)

$$\frac{V_1}{2} + \frac{V_1}{3-j8} + \frac{V_1}{3+j5} - \frac{50\angle 0^\circ}{2} + \frac{50\angle 0^\circ}{(3-j8)} = 0 \quad \text{--- (2M)}$$

on simplification of above

$$V_1 = 44.44 \angle 13.03 \text{ Volts} \quad \text{--- (2M)}$$

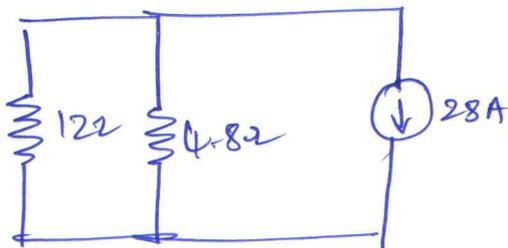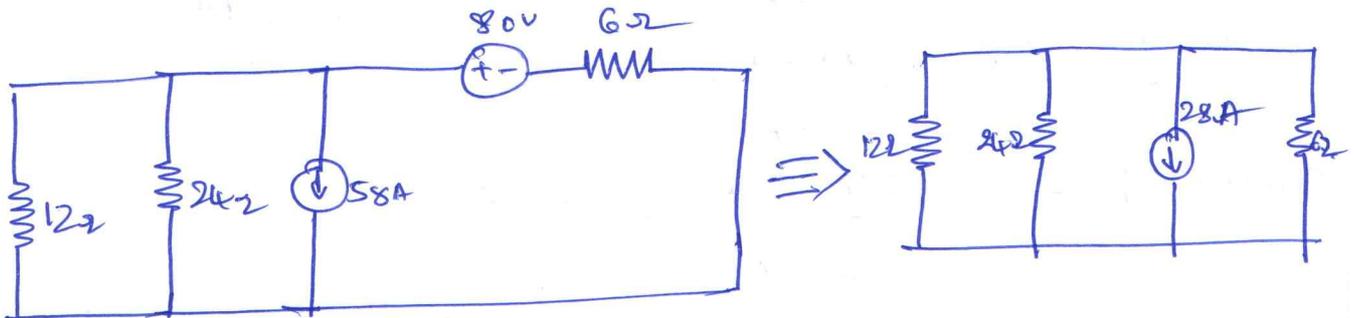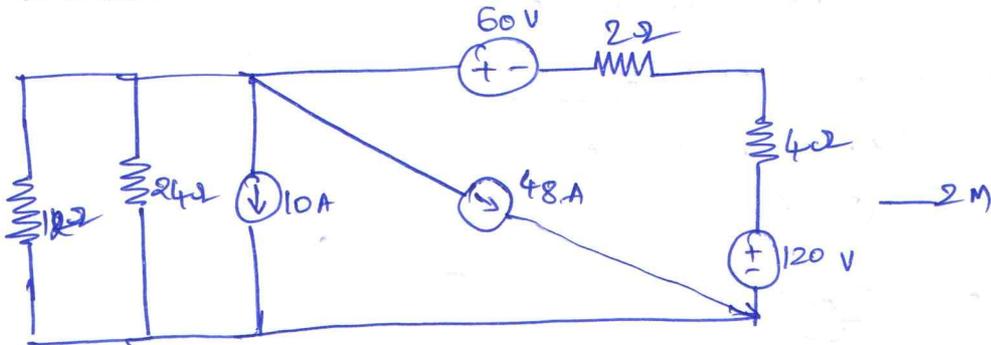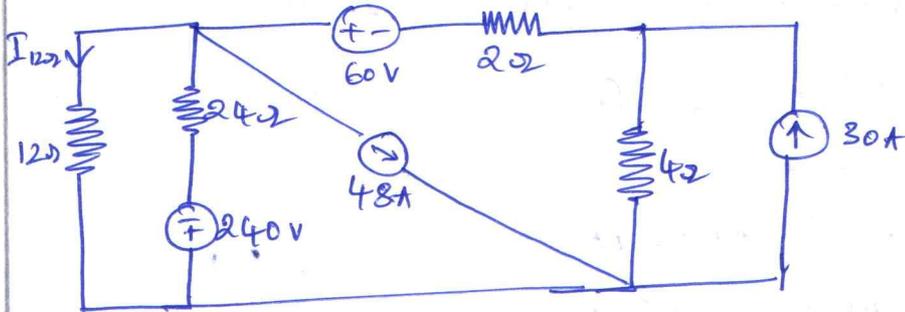
1 c) Determine the current in 12Ω resistor using source Transformation



$$\Rightarrow I_{12\Omega} = \frac{4.8}{(4.8 + 12)} \times 28 \text{ A}$$

$$\boxed{I_{12\Omega} = 8 \text{ A}}$$

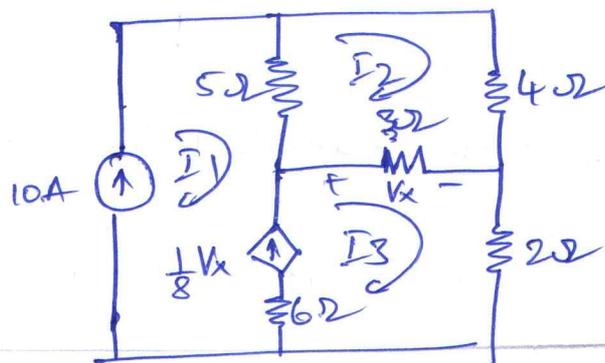2 a) Find the loop currents  $I_1, I_2$  &  $I_3$  in the circuit shown



2 a) From the circuit it can be seen that  $I_1 = 10A$  — 1M. (1)

Applying KVL to loop 2

$$5(I_2 - I_1) + 4I_2 + 3(I_2 - I_3) = 0 \quad \text{--- (2) --- 2M}$$

From the circuit, across loop 3




$$\frac{1}{8} V_x = (I_3 - I_1) = \frac{1}{8} (3I_3 - 3I_2)$$

$$\Rightarrow 3I_2 + 5I_3 = 80 \quad \text{--- (3) --- 1M}$$

on solving Equations (1), (2) & (3)


$$\boxed{I_1 = 10A}, \quad \boxed{I_2 = 7.10A}, \quad \boxed{I_3 = 11.73A} \quad \text{--- 3M}$$

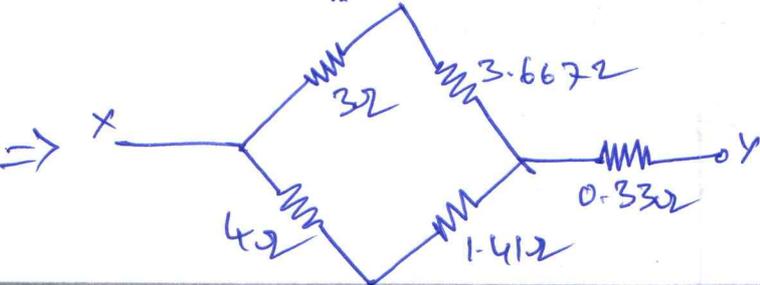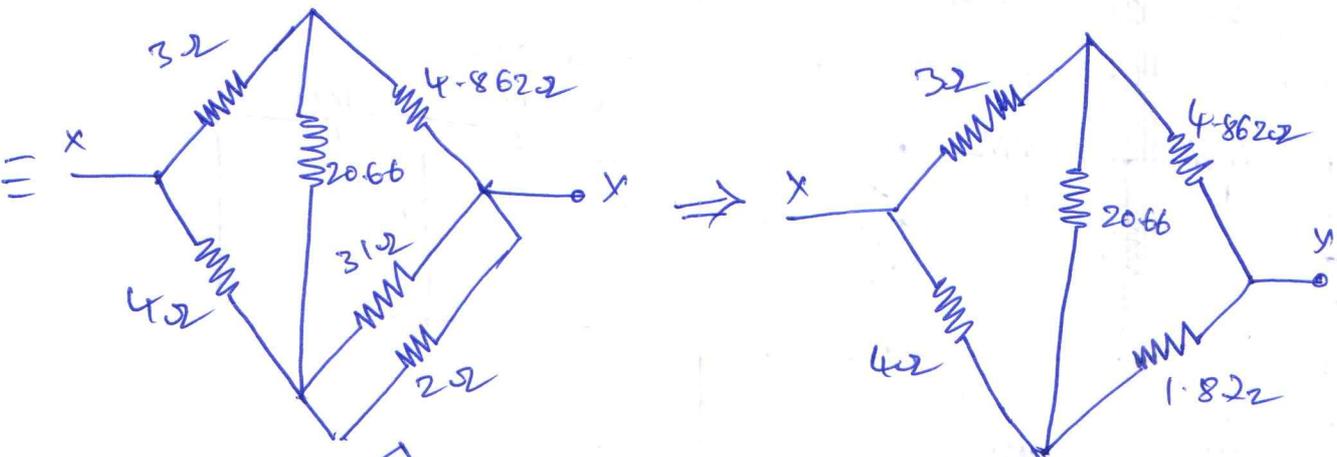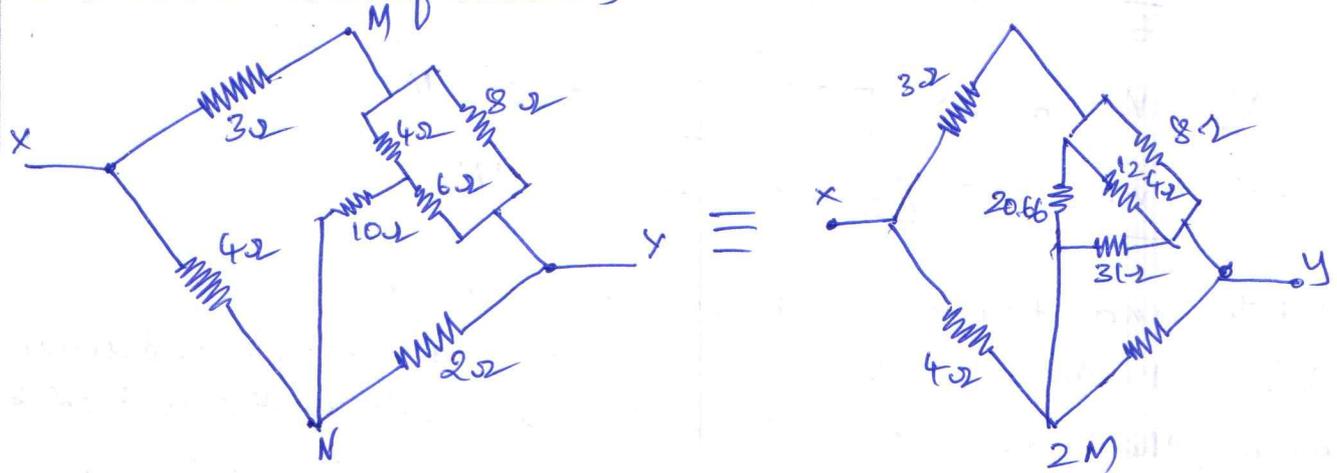2 b) Determine the resistance between the terminals x, y using Star Delta Transformation



$$\boxed{R_{xy} = 3.31\Omega}$$

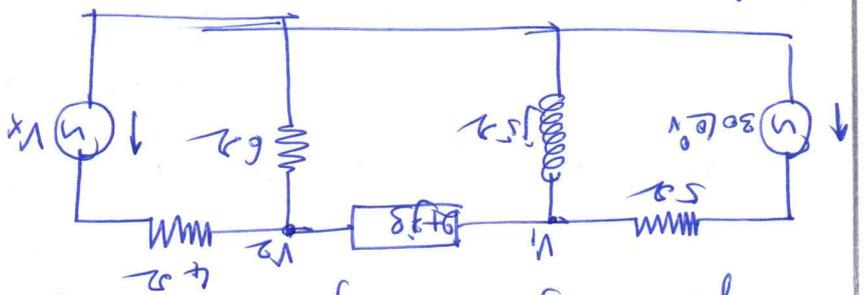2c Use Nodal Analysis to find the value of  $V_x$  and the current through  $(2 + j3)\Omega$  impedance is zero



Applying KCL at Node  $V_1$

$$I_1 - I_2 - I_3 = 0 \Rightarrow \frac{V_1 - 30}{5} + \frac{V_1}{j5} + 0 = 0 \quad \therefore (2 + j3)V_1 = 0 \text{ [given]}$$

$$\Rightarrow V_1 = 21.21 \angle 45^\circ \text{ volts} \quad \text{--- } 4 \text{ M.}$$


Applying KCL at Node  $V_2$

$$0 + \frac{V_2}{6} + \frac{V_2 - V_x}{4} = 0$$

$$V_2 - V_1 = 0 \Rightarrow V_2 = V_1$$

$$\therefore V_x = 35.33 \angle 45^\circ \text{ V} \quad \text{--- } 1 \text{ M.}$$

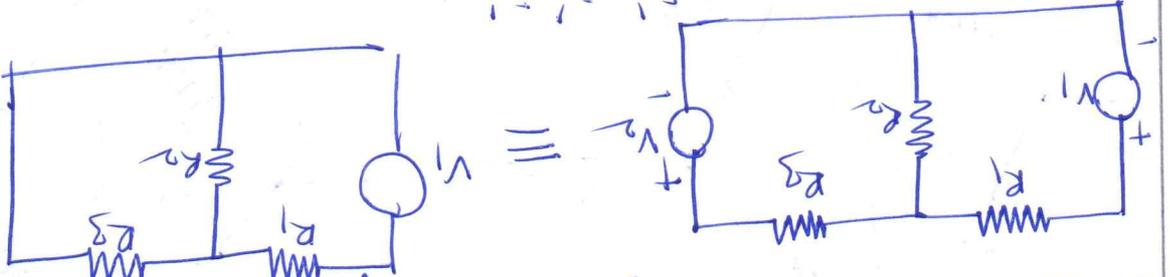3a) State and Prove Superposition Theorem.  
 Statement: In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as algebraic sum of individual contributions of each source acting alone.





Calculate currents  $I_1, I_2, I_3$

$$I_3 = I_3' + I_3''$$

$$I_2 = I_2' + I_2''$$

$$I_1 = I_1' + I_1''$$

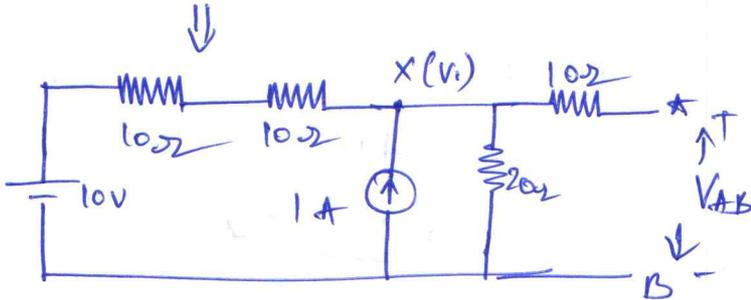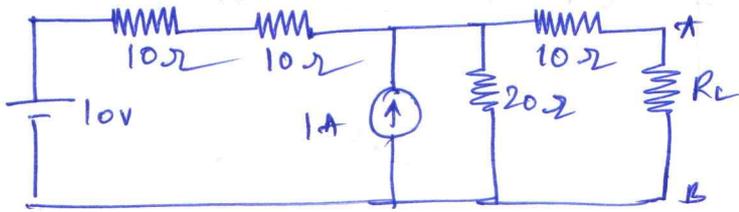3b) Obtain the Thevenin's Equivalent circuit




Applying KCL at Node x

$$\frac{V_1 - 10}{20} - 1 + \frac{V_1}{20} = 0$$

$$\Rightarrow V_1 = 15 \text{ V} = V_{AB} = V_{TH}$$


— 3M

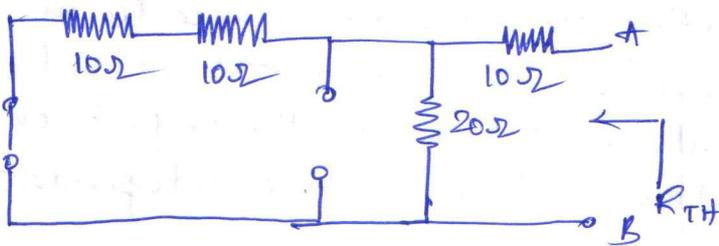


$$R_{TH} = (20 \parallel 20) \Omega + 10 \Omega$$

$$\Rightarrow R_{TH} = 20 \Omega \text{ — 2M}$$


Thevenin's Equivalent circuit

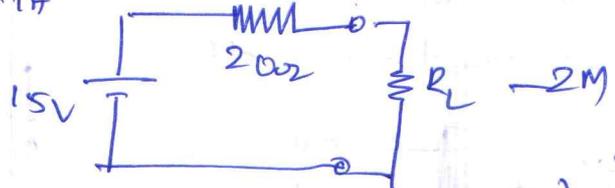

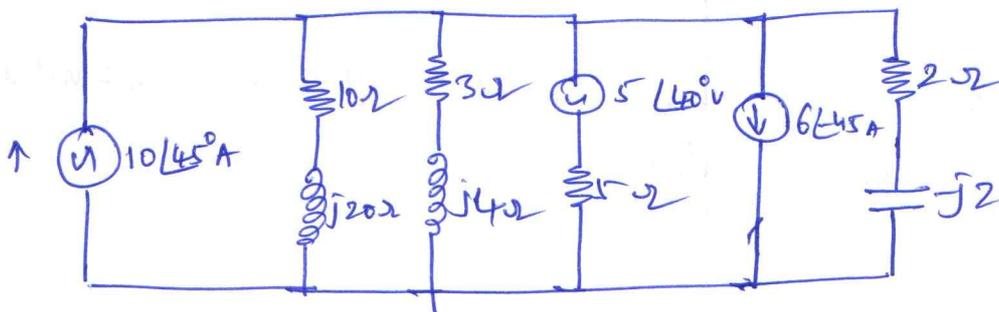
3c) Using Millman's Theorem find the current through  $(3 + j4) \Omega$  impedance for the circuit shown.



Applying Millman's Theorem

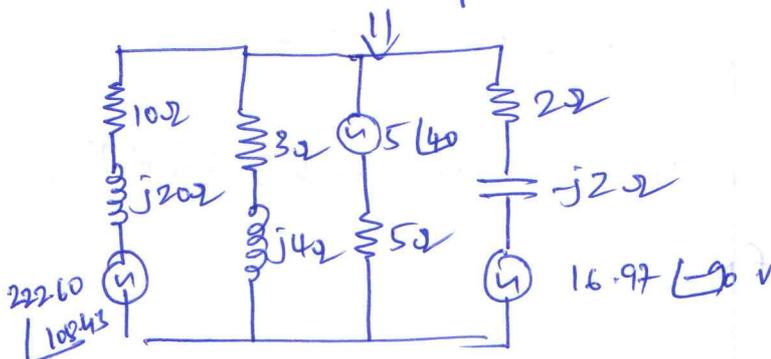


→  $R_T = V_{oc} = \frac{1}{N_{oc}} = R_N$   
 → connect 1 A current source to terminals a-b & find  $V_{oc}$   
 → Note that  $I_N = 0$   
 2) If the nio contains resistors, dependent sources  
 →  $R_N = \frac{V_{oc}}{I_N}$   
 → find open-circuit voltage  $V_{oc}$   
 → determine short circuit current  $I_N$  with all sources activated  
 If the nio contains resistors, independent sources & dependent sources are turned off.

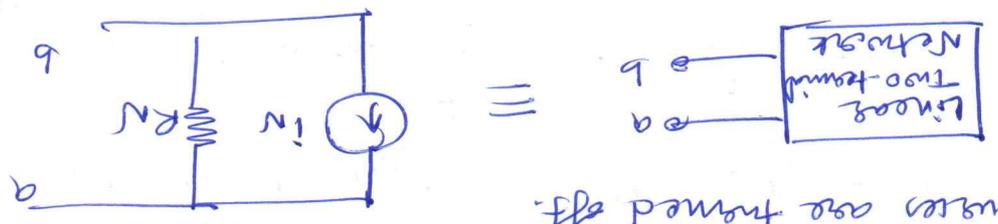


A linear two-terminal network can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with resistor  $R_N$ , where  $I_N$  is the short circuit current through the terminals and  $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.

4a) State and prove Norton's Theorem.

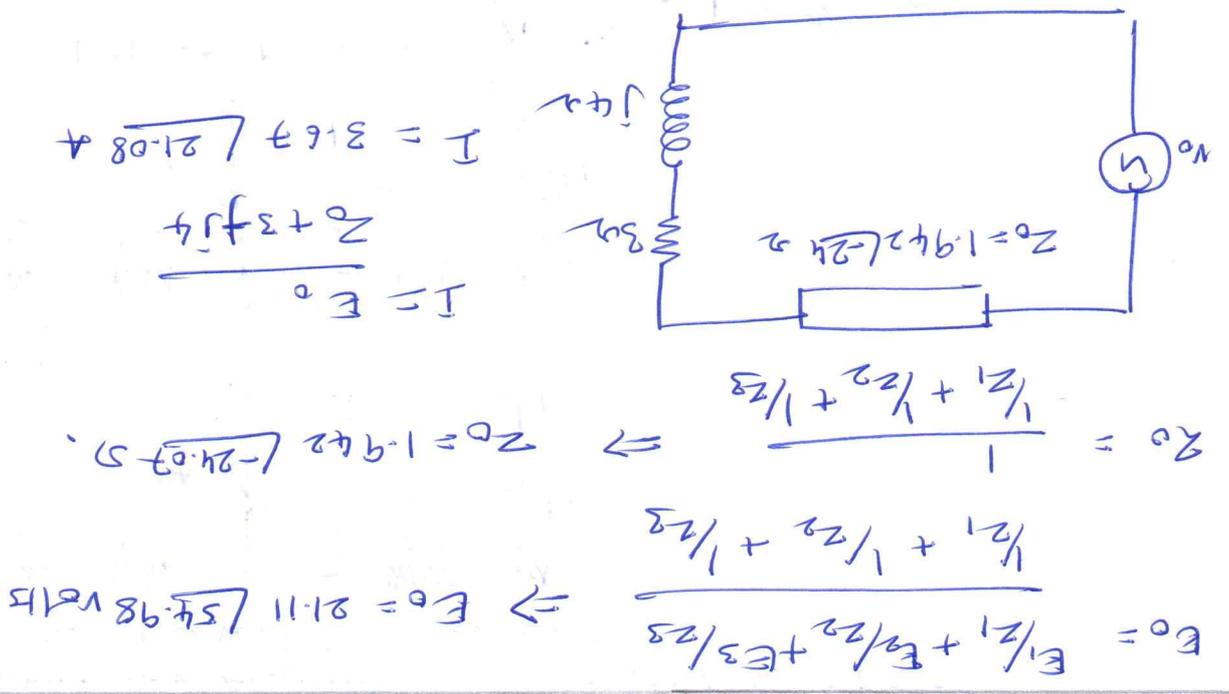

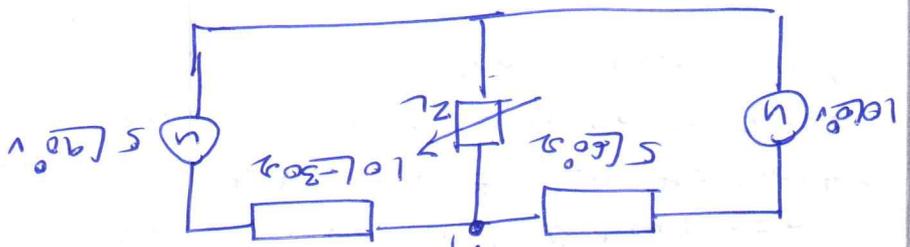4b) Find the value of  $Z_L$  for Maximum Power Transfer and the Value of Maximum power for the circuit.



Applying KCL at node

$$V_1 - 10\angle 0^\circ + 0 + V_1 - 5\angle 90^\circ = 0$$

$$\frac{5\angle 60^\circ}{10\angle 30^\circ} = 0$$

$$\Rightarrow V_1 = 6.708 \angle 26.5^\circ \text{ --- } 2M$$

$$\Rightarrow V_0 = 6.708 \angle 26.5^\circ$$



$$\Rightarrow Z_0 = \frac{(5\angle 60^\circ)(10\angle 30^\circ)}{(5\angle 60^\circ + 10\angle 30^\circ)} = (3.732 + j2.464)\Omega - 2M$$

The condition for Maximum Power  $Z_L = Z_0^*$  (3.732 - j2.464)

$$\therefore I_L = \frac{V_0}{Z_0 + Z_0} = \frac{6.708 \angle 26.5^\circ}{2 \times 3.732} = 0.898 \angle -26.5^\circ \text{ --- } 2M$$

$$P_{max} = I_L^2 \times R_L = (0.898)^2 \times 3.732 = 3.0142 \text{ W. --- } 2M$$

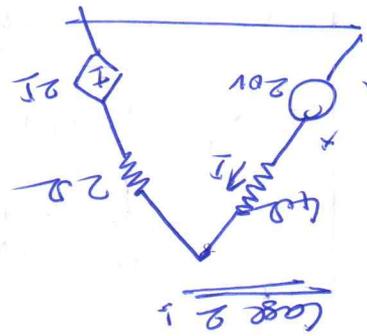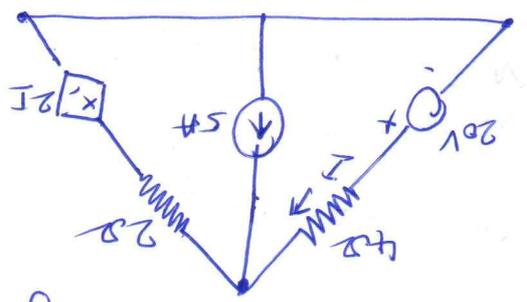4c) Find current  $I$  using superposition theorem.



$$I' = 2.5 \text{ A --- } 2M$$

$$-20 + 4I' + 2I' + 2I' = 0$$

WKT from case 2  $V_1 = -4I$

$$5 - 4 \times 2.5$$


$$I'' = -1.25 \text{ A --- } 1M$$

On Applying superposition theorem  $I = I' + I''$

$$= 2.5 - 1.25 = 1.25 \text{ A --- } 2M$$

$$V_1 - 0 - 5 + V_1 - 2I = 0$$
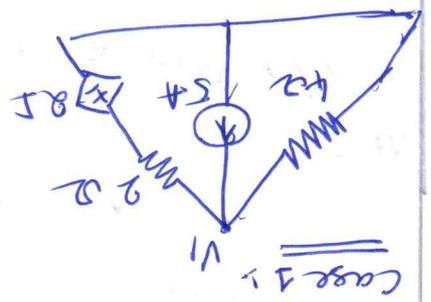
$$\frac{4}{4} V_1 = -4I \text{ --- } 2M$$




5a) Use the concept of initial condition to illustrate the voltage

behaviors in inductor circuit for DC supply

\* The switch is closed at  $t=0$ . Hence  $t=0$

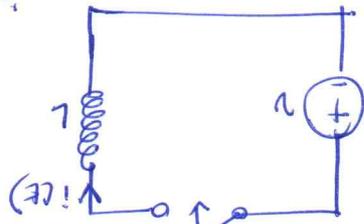corresponds to the instant when the switch is just open and  $t=0^+$  corresponds to the instant when the switch is just closed.





$$\therefore i = \frac{1}{L} \int_0^{\infty} v \cdot dt + \frac{1}{L} \int_0^{\infty} v \cdot dt$$

$$\Rightarrow i(t) = i(0^-) + \frac{1}{L} \int_0^t v \cdot dt$$


Putting  $t=0^+$  on the both sides.
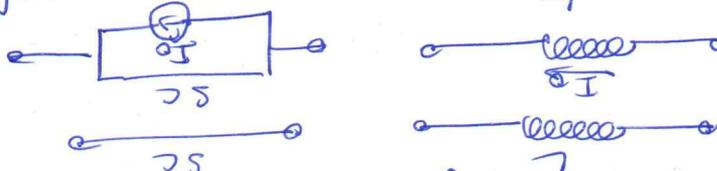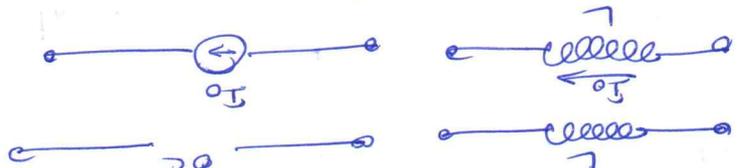
$$i(0^+) = i(0^-) + \frac{1}{L} \int_0^0 v \cdot dt \Rightarrow i(0^+) = i(0^-)$$



Under steady condition

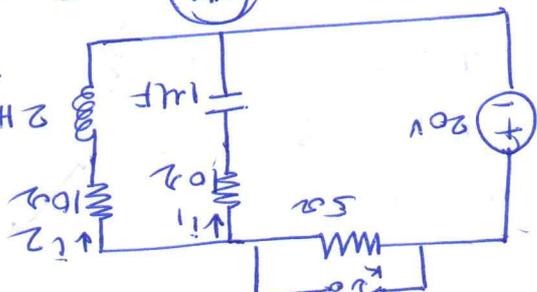5b) In the circuit the steady state is achieved with 'k' open. The switch is closed at  $t=0$ . compute  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t=0^+$



At  $t=0^-$ ,  $i_2(0^-) = \frac{20}{15} = 1.33A = i_1(0^-)$   
 $V_C(0^-) = 10 \cdot i_2(0^-) = 10 \times 1.33 = 13.3V = V_C(0^+)$

At  $t=0^+$  the circuit produces


$$20 = 10 i_1(0^+) + \frac{1}{C} \int_0^+ i_1(t) \cdot dt \quad \text{--- (1)}$$

$$i_1(0^+) = 20 - 13.3 = 0.67A$$

Differentiating Equation (1)  
 $\frac{d}{dt} i_1(0^+) = -0.67 = -0.67 \times 10^5 A/sec$   
 $2M$

Applying KVL to loop 2  
 $20 = 10 i_2(0^+) + 2 \cdot \frac{di_2(0^+)}{dt} \Rightarrow \frac{d}{dt} i_2(0^+) = 3.35 A/sec - 2M$

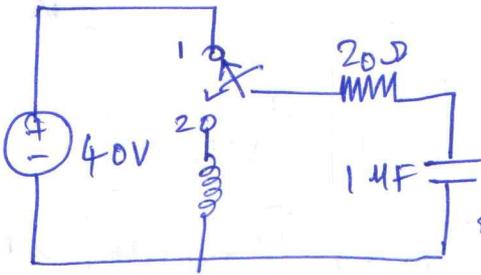
5c) The switch is moved from position (1) to position (2) at  $t=0$ . The steady state has been reached before switching. Compute  $i$ ,  $di/dt$  and  $d^2i/dt^2$  at  $t=0^+$



At  $t=0^-$  the switch is in position 1

$$\begin{aligned} \therefore V_C(0^-) &= V_C(0^+) = 40V \\ \therefore i(0^-) &= 0A = i(0^+) \end{aligned} \quad ] \quad 2M.$$

At  $t=0^+$  the switch is in position 2

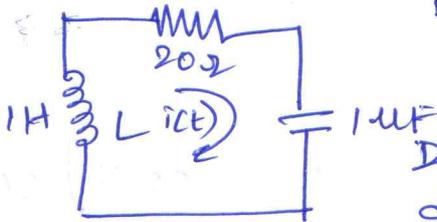

By KVL

$$R i(t) + \frac{1}{C} \int i(t) dt + L \frac{di(t)}{dt} = 0 \quad \text{--- 1M}$$

Differentiating Equation (1)


$$\frac{di(0^+)}{dt} = -40 A/sec \quad \text{--- 2M}$$

Differentiating Eqn

$$R \frac{di(t)}{dt} + \frac{1}{C} i(t) + L \frac{d^2i(t)}{dt^2} = 0 \Rightarrow \frac{d^2i(t)}{dt^2} = 8000 A/sec^2$$

3M

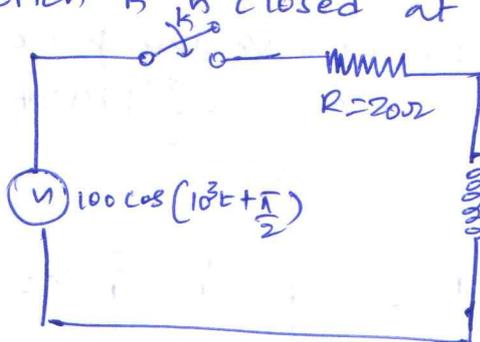6a) In the circuit determine the complete solution for current when switch 'k' is closed at  $t=0$



$$20i + 0.1 \frac{di}{dt} = 100 \cos(10^3 t + \pi/2)$$

$$\therefore \frac{di}{dt} + 200i = 1000 \cos(10^3 t + \pi/2) \quad \text{--- 2M}$$

$$i_c = k \cdot e^{-t/(L/R)} = k \cdot e^{-200t}$$

$$i_p = \frac{V}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t + \phi + \tan^{-1}(\frac{\omega L}{R}))$$

$$i_p = 100$$

$$\frac{100}{\sqrt{(20)^2 + (1000 \times 0.1)^2}} \cos \left[ 1000t + \frac{\pi}{2} - \tan^{-1} \left( \frac{1000 \times 0.1}{20} \right) \right] \quad \text{--- 2M}$$

$$i_p = 0.9805 \cos(1000t + \frac{\pi}{2} - 78.69^\circ) \quad \text{--- 1M}$$

$$i = i_p + i_c = k \cdot e^{-200t} + 0.98 \cos(1000t + \frac{\pi}{2} - 78.6^\circ) \quad \text{--- 2M}$$


Now to find  $k$ , At  $t=0$

$$0 = k + 0.98 \cos(0 + \pi/2 - 78.6^\circ) \Rightarrow k = -0.98 \cos(\pi/2 - 78.6^\circ)$$

$\therefore$  The complete solution is

$$i = \left[ -0.98 \cos(\pi/2 - 78.6^\circ) e^{-200t} + 0.98 \cos(1000t + \pi/2 - 78.6^\circ) \right] \quad \text{--- 3M}$$

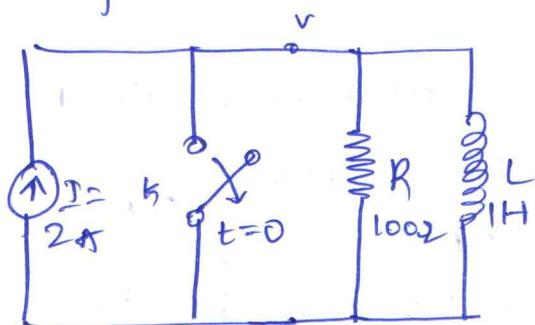6b) Compute  $v$ ,  $dv/dt$ ,  $d^2v/dt^2$  at  $t=0^+$  for the circuit when switch  $K$  is opened at  $t=0$  10



At  $t=0^-$ , switch is closed

$$i(0^-) = 0 = i(0^+) \quad 2M$$

$$I = I_R + I_L$$

$$2 = \frac{v(t)}{100} + \left[ \frac{1}{1} \int_{-\infty}^t v(t) dt \right]$$

$$2 = \frac{v(t)}{100} \left[ \int_{-\infty}^0 v(t) dt + \int_0^t v(t) dt \right] \quad 2M$$







$$\int_0^t v(t) dt + \frac{v(t)}{100} = 2$$

$$\text{At } t=0^+ \Rightarrow \int_0^{0^+} v(t) dt + \frac{v(0^+)}{100} = 2 \Rightarrow \boxed{v(0^+) = 200 \text{ V}} \quad 3M$$

$$v(t) \neq \frac{1}{100} \frac{dv(t)}{dt} = 0 \Rightarrow \frac{dv}{dt}(0^+) = -200 \text{ V/sec.}$$

$$\frac{dv}{dt} + \frac{1}{100} \frac{d^2v(t)}{dt^2}(0^+) = 0 \Rightarrow \frac{d^2v(t)}{dt^2}(0^+) = 2 \times 10^5 \text{ V/sec}^2 \quad 3M$$

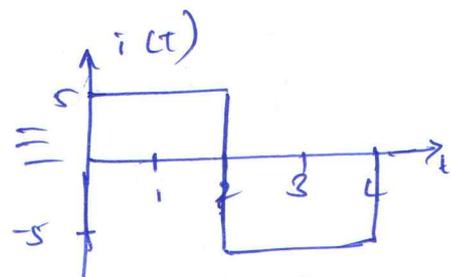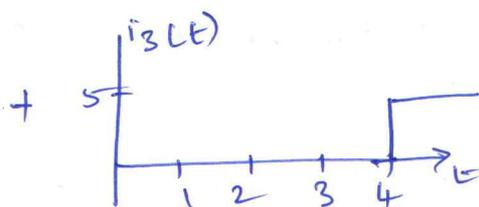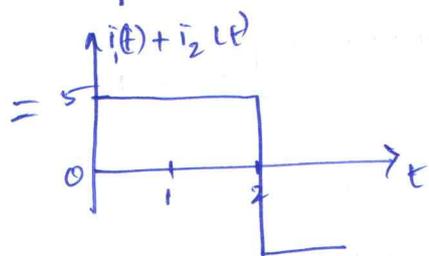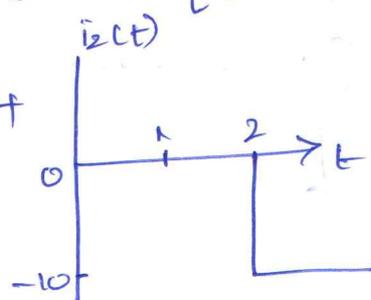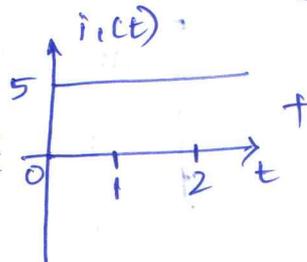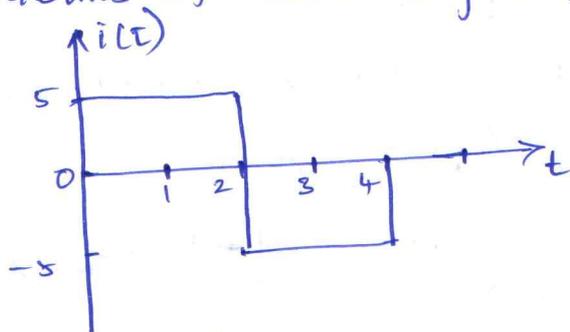7a) Using waveform synthesis method express the voltage pulse in terms of unit step & find i)  $\mathcal{L}\{i(t)\}$  ii)  $\mathcal{L}\{\int i(t) dt\}$



$$i(t) = i_1(t) + i_2(t) + i_3(t) = 5u(t) - 10u(t-2) + 5u(t-4)$$

Taking LT of above Eq<sup>n</sup>

$$I(s) = \frac{5}{s} - \frac{10}{s} e^{-2s} + \frac{5}{s} e^{-4s} = \frac{5}{s} [1 - e^{-2s} + e^{-4s}] = \frac{5}{s} [1 - e^{-2s}]^2$$

$$f(t) = \int i(t) dt = \int [5u(t) - 10u(t-2) + 5u(t-4)] dt = 5r(t) - 10r(t-2) + 5r(t-4)$$

7b) State and Prove Initial value and final value theorem for Laplace transform.

6

Initial Value Theorem: This allows to find initial value  $x(0)$  directly from its Laplace Transform.

If  $x(t)$  is a causal signal then  $x(0) = \lim_{s \rightarrow \infty} s \cdot X(s)$ .

$$L \left\{ \frac{dx(t)}{dt} \right\} = s \cdot X(s) - x(0) = \int_0^{\infty} \frac{dx}{dt} e^{-st} dt$$

If we let  $s \rightarrow \infty$ , then integral on RHS vanishes due to damping

$$\lim_{s \rightarrow \infty} [s \cdot X(s) - x(0)] = 0 \Rightarrow x(0) = \lim_{s \rightarrow \infty} s \cdot X(s) \quad -3M$$

Final Value Theorem: This allows to find final value  $x(\infty)$  directly from its Laplace Transform.

If  $x(t)$  is a causal signal then  $\lim_{t \rightarrow \infty} x(t) = \lim_{s \rightarrow 0} s \cdot X(s)$

$$L \left\{ \frac{dx(t)}{dt} \right\} = s \cdot X(s) - x(0) = \int_0^{\infty} \frac{dx}{dt} e^{-st} dt = s \cdot X(s) - x(0)$$

if  $s \rightarrow 0$  then

$$\begin{aligned} \lim_{s \rightarrow 0} [s \cdot X(s) - x(0)] &= \lim_{s \rightarrow 0} \int_0^{\infty} \frac{dx}{dt} e^{-st} dt = \int_0^{\infty} \frac{dx}{dt} \left( \lim_{s \rightarrow 0} e^{-st} \right) dt \\ &= \int_0^{\infty} \frac{dx}{dt} dt = x(t) \Big|_0^{\infty} = x(\infty) - x(0) \end{aligned}$$

$$\lim_{s \rightarrow 0} s \cdot X(s) - x(0) = x(\infty) - x(0) \quad \boxed{x(\infty) = \lim_{s \rightarrow 0} s \cdot X(s)}$$

7c) Obtain the Laplace Transform of step and Ramp functions with relevant expressions

6

$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

$$f(t) = r(t) = t \text{ for } t \geq 0$$

$$L \{ f(t) \} = \int_0^{\infty} f(t) \cdot e^{-st} dt$$

$$L \{ f(t) \} = \int_0^{\infty} f(t) \cdot e^{-st} dt$$

$$= \int_0^{\infty} u(t) \cdot e^{-st} dt$$

$$= \int_0^{\infty} t \cdot e^{-st} dt$$

$$= \int_0^{\infty} 1 \cdot e^{-st} dt$$



$$L \{ r(t) \} = \left[ \frac{t e^{-st}}{-s} \right]_0^{\infty} - \int_0^{\infty} \frac{e^{-st}}{-s} \cdot 1 \cdot dt$$

$$= \frac{e^{-st}}{-s} \Big|_0^{\infty} = -\frac{1}{s} [e^{-\infty} - e^0] = \frac{1}{s}$$

$$= 0 + \frac{1}{s} \int_0^{\infty} e^{-st} dt = \frac{1}{s} \left[ \frac{1}{s} \right]$$

$$= \frac{1}{s^2}$$

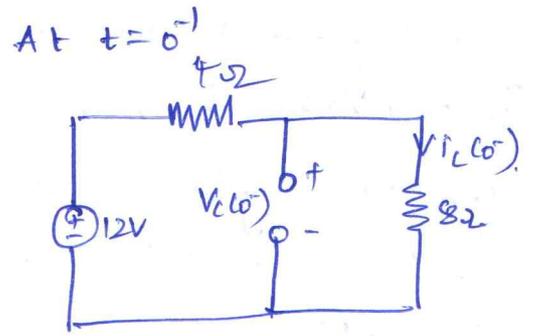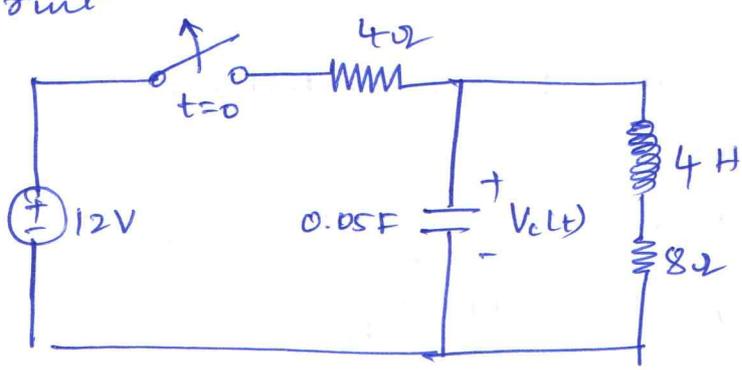
8a) Determine  $i_L(t)$  for  $t \geq 0$  using Laplace Transform for the circuit.



$i_L(0^-) = \frac{12}{12} = 1A = i_L(0^+) \therefore V_C(0^-) = 8 \times i_L(0^-) = 8V = V_C(0^+)$  (4M)

At  $t=0^+$

Apply KVL to loop (2)

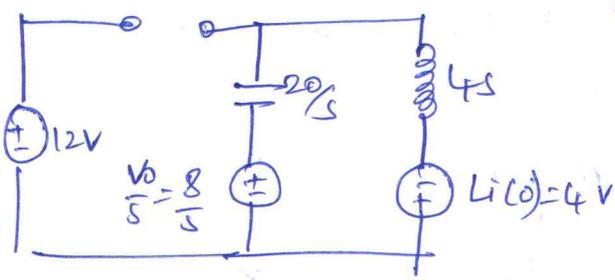


$\frac{8}{s} - \frac{20}{s} I_L(s) - 4s I_L(s) + 4 - 8 I_L(s) = 0$   
 $\therefore I_L(s) = \frac{8 + 4s}{20 + 4s^2 + 8s}$  (4M)

$I_L(s) = \frac{4(s+2)}{4(s^2 + 2s + 5)} = \frac{s+2}{s^2 + 2s + 5} = \frac{(s+1) + 1}{(s+1)^2 + 2^2}$   
 $= \frac{s+1}{(s+1)^2 + 2^2} + \frac{1}{2} \times \frac{2}{(s+1)^2 + 2^2}$

$i_L(t) = [e^{-t} \cos(2t) + \frac{1}{2} e^{-t} \sin(2t)] u(t)$  (2M)

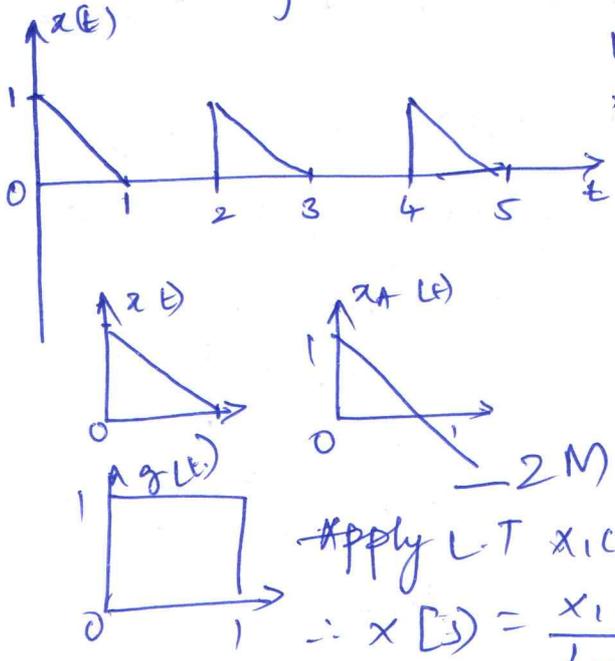8b) Find the Laplace Transform of the periodic signal



Laplace Transform of a periodic signal is given by  $L\{f(t)\} = \frac{1}{1-e^{-sT}} \int_0^T e^{-st} f(t) dt$  (1M)

$x_1(t) = x(t) \cdot g(t)$   
 $= [-t+1] [u(t) - u(t-1)]$   
 $= -t u(t) + t u(t-1) + u(t) - u(t-1)$   
 $= -t u(t) + (t-1) u(t-1) + u(t-1)$   
 $+ u(t) - u(t-1)$   
 $= u(t) - x(t) + x(t-1) - 1$  (4M)

Apply L.T  $x_1(s) = 1/s - 1/s^2 + e^{-s}/s^2 = \frac{s-1+e^{-s}}{s^2}$   
 $\therefore X(s) = \frac{x_1(s)}{1-e^{-sT}} = \frac{s-1+e^{-s}}{s^2(1-e^{-2s})}$  (3M)

9a Define Z-parameters. Determine Y parameters in terms of Z-parameters. 6

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}, \quad Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}, \quad Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$


$$\Delta = Z_{11}Z_{22} - Z_{12}Z_{21} = \Delta Z \quad \Delta_1 = Z_{22}V_1 - Z_{12}V_2 \quad \Delta_2 = Z_{11}V_2 - Z_{21}V_1$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{Z_{22}V_1 - Z_{12}V_2}{\Delta Z} \quad \text{--- 2M}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-Z_{21}V_1 + Z_{11}V_2}{\Delta Z} \quad \text{--- 2M}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Z_{22}/\Delta Z & -Z_{12}/\Delta Z \\ -Z_{21}/\Delta Z & Z_{11}/\Delta Z \end{bmatrix} \quad \text{--- 2M}$$

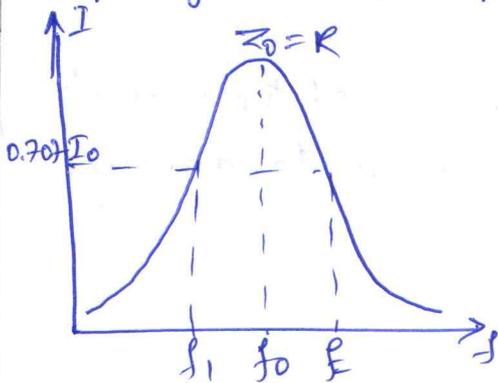9b Show that Resonant frequency is geometric mean of cut off frequency in series R-L-C circuit. 7



$$Z_1 = \sqrt{R^2 + (X_{C1} - X_{L1})^2}$$

$$Z_2 = \sqrt{R^2 + (X_{L2} - X_{C2})^2}$$

$$Z_1 = Z_2$$

$$R^2 + (X_{C1} - X_{L1})^2 = R^2 + (X_{L2} - X_{C2})^2$$

$$X_{C1} - X_{L1} = X_{L2} - X_{C2} \quad \text{--- 2M}$$

$$\frac{1}{\omega_1 C_1} - \omega_1 L = \omega_2 L - \frac{1}{\omega_2 C_2}$$



$$\omega_1 \omega_2 = \frac{1}{LC} \quad \text{--- 2M} \quad \text{--- 1} \quad \omega_0 = \frac{1}{2\pi \sqrt{LC}}$$

$$2\pi f_0 = \frac{1}{\sqrt{LC}} \Rightarrow \omega_0^2 = \frac{1}{LC} \quad \text{--- 2} \quad \text{--- 2M}$$

$$\text{From } \text{--- 1} \text{ \& } \text{--- 2} \quad f_0 = \sqrt{f_1 f_2} \quad \text{--- 2M}$$

9c Apply two-port network Analysis to determine ABCD parameters of the networks

7

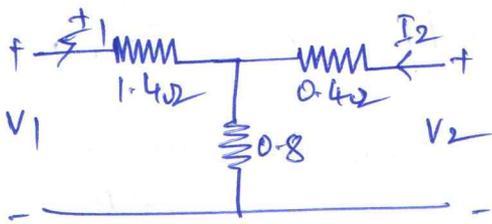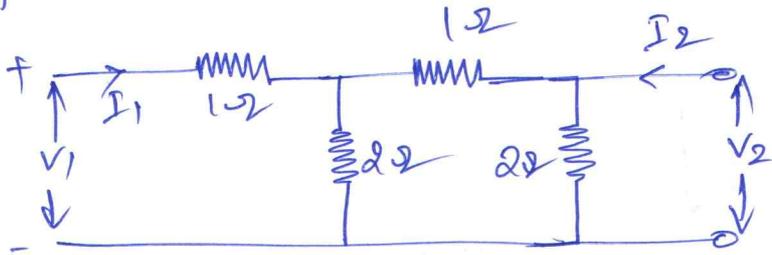

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

2 M

Apply KVL

$$V_1 = 2.2I_1 + 0.8I_2 \quad \text{--- (1)}$$

$$V_2 = 0.8I_1 + 1.2I_2 \quad \text{--- (2)}$$

2 M


$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 2.2 & 0.8 \\ 0.8 & 1.2 \end{bmatrix}$$

NBT

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} Z_{11}/Z_{21} & -\Delta Z/Z_{21} \\ 1/Z_{21} & Z_{22}/Z_{21} \end{bmatrix} = \begin{bmatrix} 2.75 & 2.5 \\ 1.25 & 1.5 \end{bmatrix} \quad \text{3 M}$$

10a) Derive Expression for Resonant frequency of the circuit  
 Also show that the circuit resonates at all frequency  
 if  $R_L = R_C = \sqrt{\frac{L}{C}}$

10

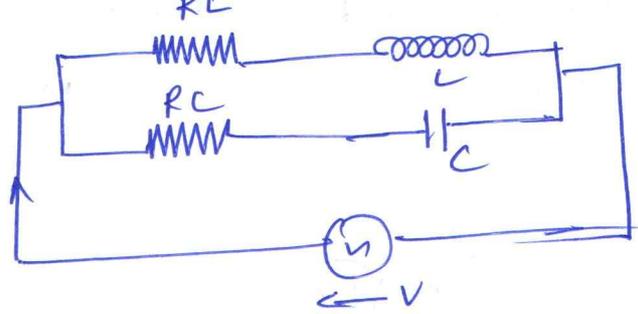

$$Y_L = \frac{1}{Z_L} = \frac{1}{R_L + jX_L} = \frac{R_L - jX_L}{R_L^2 + X_L^2}$$

$$Y_C = \frac{1}{Z_C} = \frac{1}{R_C - jX_C} = \frac{R_C + jX_C}{R_C^2 + X_C^2}$$

$$Y_T = \left[ \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} \right] + j \left[ \frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} \right]$$

$$\frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} = 0$$

$$R_C^2 + \omega^2 L^2 C = L \omega^2 C^2 R_C^2 + L$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{R_L^2 - L/C}{LC(R_C^2 - L/C)}}$$

$$Y = \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2}$$


Assuming  $R_L = R_C = R$

$$Y = \frac{R}{R^2} \left[ \frac{2R^2 + X_C^2 + X_L^2}{2R^2 + X_C^2 + X_L^2} \right]$$

$$Y = \frac{1}{R}$$

$$\therefore R_L = R_C = R = \sqrt{\frac{L}{C}}$$

10b) Determine h-Parameters

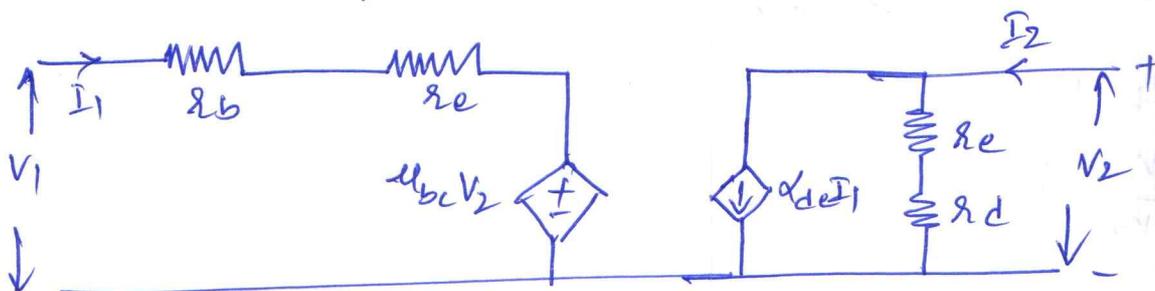

$$V_1 = h_{11} I_1 + h_{12} V_2$$


$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$\therefore h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad 2M$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

10

Case (1):  $V_2 = 0$

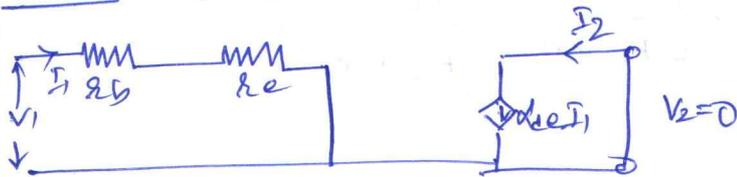


$$V_1 = I_1 (r_b + r_e)$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = r_b + r_e$$

$$I_2 = \alpha_{dc} I_1$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \alpha_{dc}$$

Case 2:  $I_1 = 0$

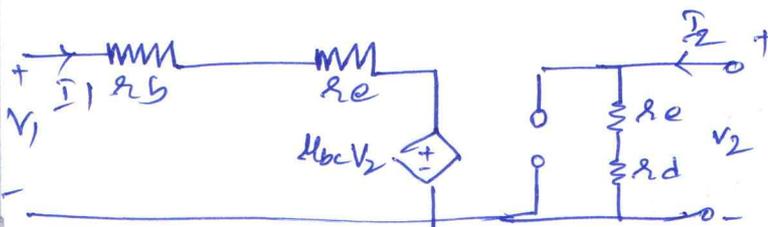

$$V_2 = I_2 (r_e + r_b)$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{r_e + r_b}$$

$$V_1 = \mu_{bc} V_2$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$= \mu_{bc}$$

MHA  
 Head of the Department  
 Dept. of Electronic & Communication Engg.  
 KLS V.D.I.T. HALIYAL (U.K.)